
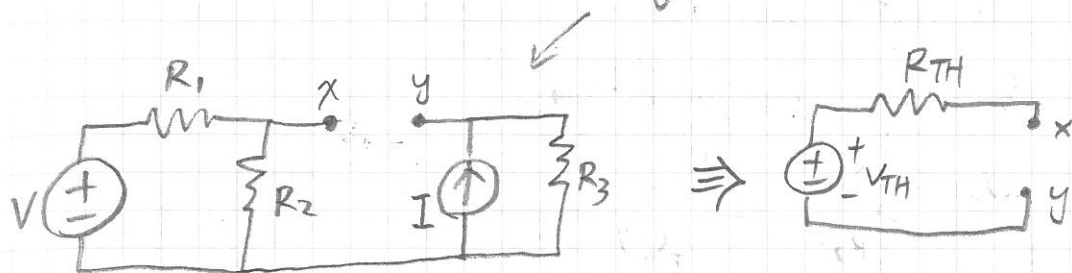


Exercise: create the Thévenin Equivalent Circuit for the following circuit:

P29

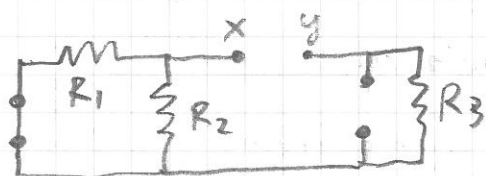


first of all, for R_{TH} :



$$\Rightarrow R_{TH} = (R_1 // R_2) + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3$$


then, for V_{TH} :

approach ①, using superposition


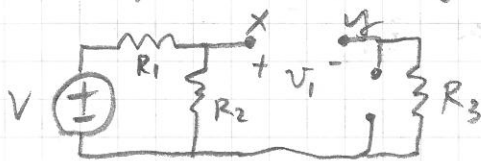


$$V_{TH} = V_1 + V_2$$


$$= \frac{R_1}{R_1 + R_2} V + (-IR_3)$$

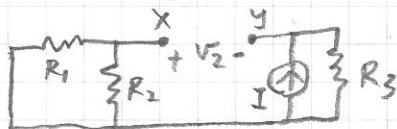

$$= \frac{R_1}{R_1 + R_2} V - IR_3$$

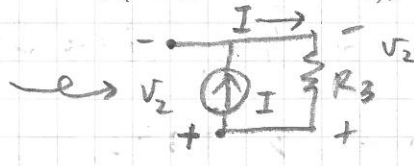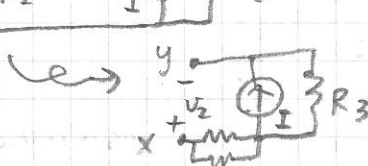

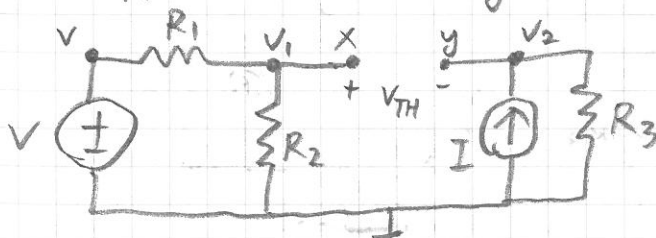
approach ②, using the node method (Page 21)



$$V_{TH} = V_1 - V_2 = \frac{R_2}{R_1 + R_2} V - IR_3$$


$$\text{KCL: } \begin{cases} \frac{V - V_1}{R_1} + \frac{0 - V_1}{R_2} = 0 \\ I + \frac{0 - V_2}{R_3} = 0 \end{cases} \Rightarrow \begin{cases} V_1 = \frac{R_2}{R_1 + R_2} V \\ V_2 = IR_3 \end{cases}$$

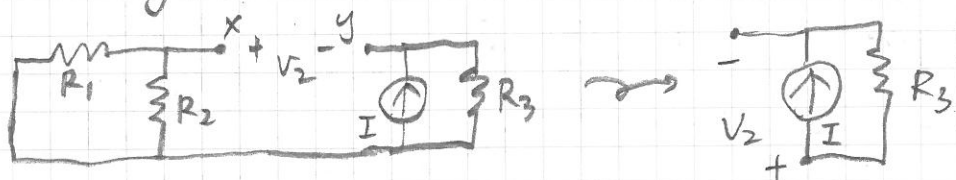P30 In the exercise on the previous page, you might wonder why we can do the following transformation:



Could it be possible that there are some current flowing through R_1 and/or R_2 ?

We can use KCL to figure it out:

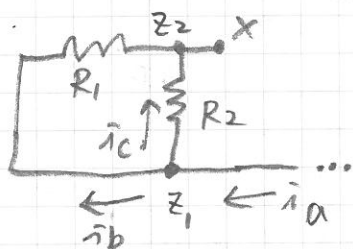

for node z_1 , we have

$$\hat{i}_a - \hat{i}_b - \hat{i}_c = 0$$


for node z_2 , we have

$$\hat{i}_b + \hat{i}_c = 0$$

← compare


Therefore, we see that $\hat{i}_a = 0$.

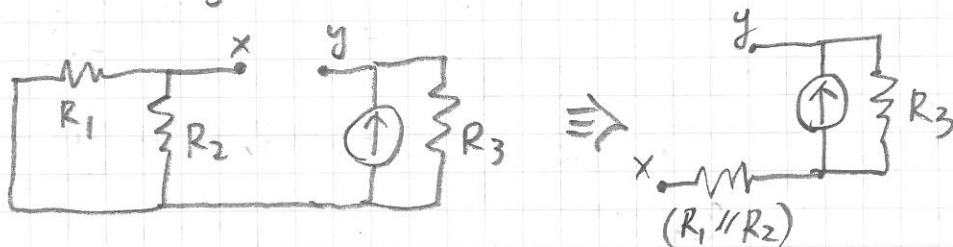In practice, it is often helpful to think in terms of equivalent resistance, which may make the situation much more obvious:




Exercise : In the following circuit, determine voltage V_0 :

P31

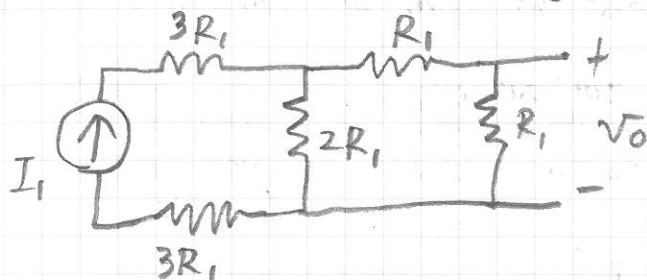


We may do the following transformation :

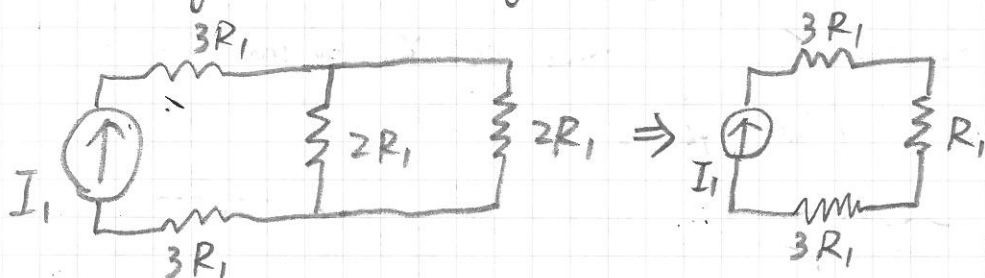

then we might conclude that $V_0 = I_1 \cdot R_1$, but it is wrong.

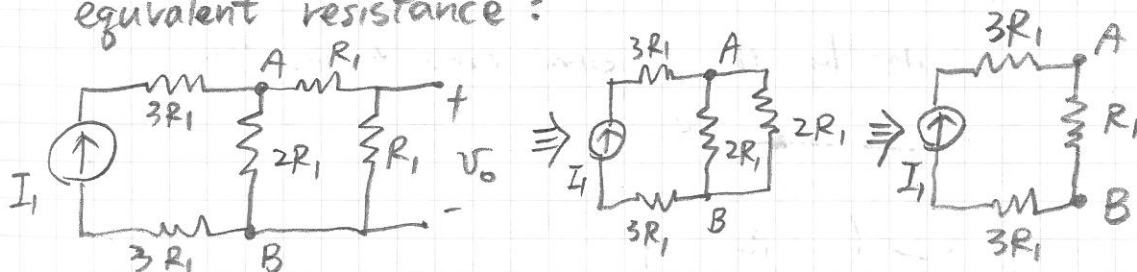To see this, it could be helpful to clearly label the nodes between which you calculate the equivalent resistance :






thus we see that V_0 is not the voltage across A, B, and $V_0 = (\text{voltage across A, B}) \times \frac{R_1}{R_1 + R_1}$

$$= (I_1 \cdot R_1) \times \frac{R_1}{R_1 + R_1} = \frac{1}{2} I_1 R_1 \text{ is the correct answer.}$$

✗

P32 ★ Norton's Theorem

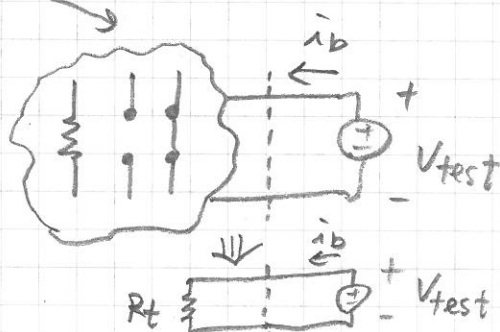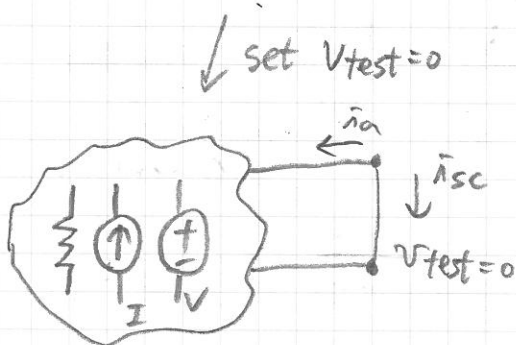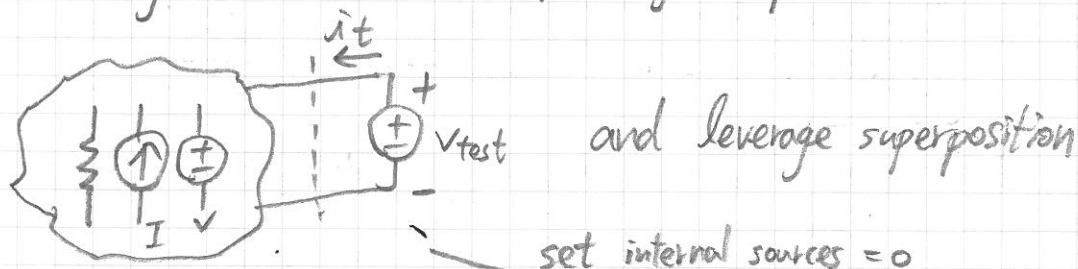
For the same goal as that of Thévenin's Theorem, here we choose to attach a testing independent voltage source to a possibly complex circuit:



$$\text{then } i_t = i_a + i_b = -i_{sc} + \frac{V_{test}}{R_t}$$

$$\Rightarrow i_t + i_{sc} - \frac{V_{test}}{R_t} = 0$$

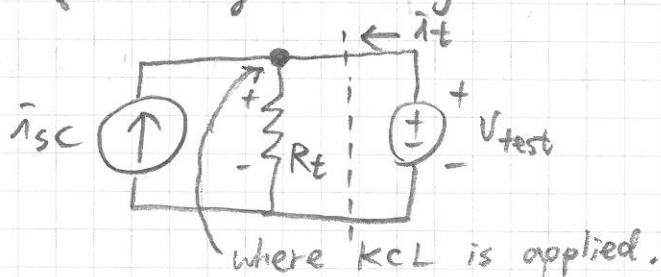Think of above in terms of KCL, then, equivalently the original circuit is like





And $R_t = R_{TH}$, since we applied same procedure of decomposition as we did in Thévenin's Theorem.

Relation between

Norton's Equivalent Circuit

and

Thévenin's Equivalent Circuit:

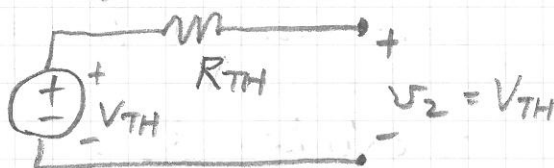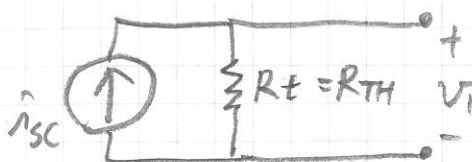

since $V_1 = V_2$, we have

$$i_{sc} \cdot R_t = V_2 = V_{TH}$$

$$\Rightarrow R_t = \frac{V_{TH}}{i_{sc}} = \frac{V_{oc}}{i_{sc}}$$

(recall that $V_{TH} = V_{oc}$ page 28)

in other word,

$$\text{等效电阻} = \frac{\text{開路電壓}}{\text{短路電流}}$$


Example: find $V = ?$




approach ①: voltage divider

$$V = 3 \times \frac{2}{1+2} = 2V$$

approach ②: Thévenin's Theorem

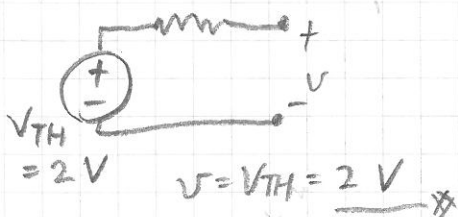


approach ③: Norton's Theorem

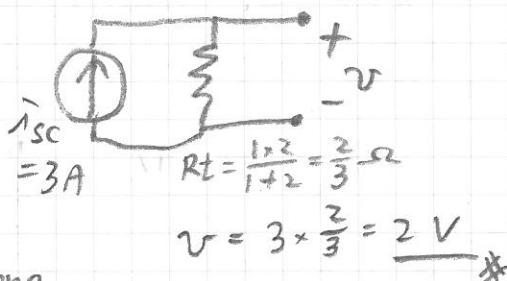


\Rightarrow these three agree in one.


P34 Example: find $v_{xy} = ?$

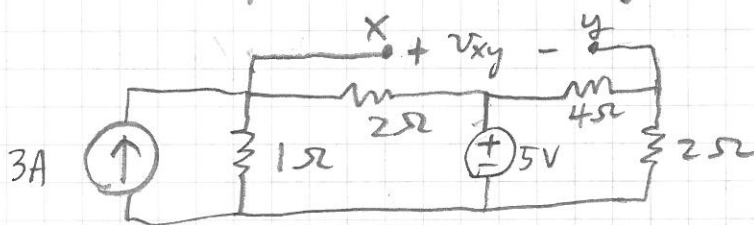

Using Norton's Theorem, we have

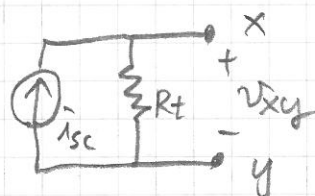


to calculate R_t :

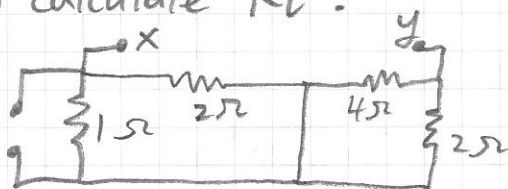

$$R_t = (1\Omega // 2\Omega) + (4\Omega // 2\Omega) = 2\Omega$$

to calculate i_{sc} :

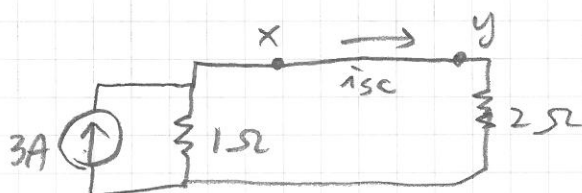


$$i_{sc} = 3 \times \frac{1}{1+2} = 1\text{ A}$$

(current divider)

Therefore $v_{xy} = i_{sc} \times R_t = 2\text{ V}_\#$

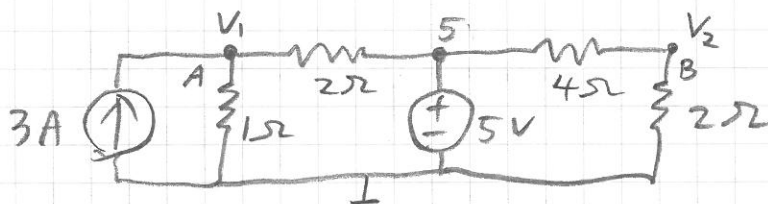Alternatively, we may use the node method:



KCL at node A: $3 + \frac{0 - V_1}{1} + \frac{5 - V_1}{2} = 0 \Rightarrow V_1 = \frac{11}{3}$


KCL at node B: $\frac{5 - V_2}{4} + \frac{0 - V_2}{2} = 0 \Rightarrow V_2 = \frac{5}{3}$

$$v_{xy} = V_1 - V_2 = \frac{11}{3} - \frac{5}{3} = 2\text{ V}_\#$$

★ Nonlinear Devices

P35

Silicon Diode

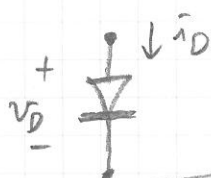

$$i_D = I_S (e^{v_D/V_{THER}} - 1)$$

I_S : saturation current $\approx 10^{-12} A$

V_{THER} : thermal voltage

$$V_{THER} = \frac{kT}{q}$$

T : temperature in Kelvins

$$^{\circ}K = ^{\circ}C + 273.15$$

k : Boltzmann's constant


$$= 1.38 \times 10^{-23} J/^{\circ}K$$

q : charge of an electron

$$= 1.602 \times 10^{-19} C$$

Example: CPU 溫度計, see example 16.1 in the textbook.


Hypothetical Nonlinear Device

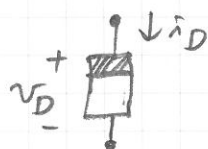

$$i_D = \begin{cases} 1K \cdot v_D^2 & \text{for } v_D > 0 \\ 0 & \text{otherwise} \end{cases}$$

where $1K$ is a positive constant

Example: find v_D and i_D :

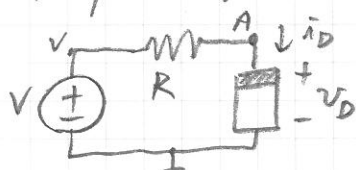

$$KCL \text{ at } A: \frac{V - v_D}{R} + (-i_D) = 0$$

Plug in the i - v relation, we have

$$\begin{cases} \frac{V - v_D}{R} - 1K v_D^2 = 0 & \text{for } v_D > 0 \\ \frac{V - v_D}{R} = 0 & \text{otherwise} \end{cases}$$

$$\Rightarrow v_D = \frac{-1 + \sqrt{1 + 4RKV}}{2RK}$$

$$\text{and } i_D = 1K \left(\frac{-1 + \sqrt{1 + 4RKV}}{2RK} \right)^2 \text{ for } v_D > 0$$

Exercise: find i_3 ?

(hint: Page 29 and the above example)



assuming $1K = 1$

You can do it!

$$\text{Ans: } i_3 = \left(\frac{\sqrt{7} - 1}{3} \right)^2 + 1$$