


ed:

# ★ Thévenin's Theorem



P27

Goal: Given an arbitrary linear circuit, we would like to know how it would respond to external excitation; in other word, we'd like to know its  $i$ - $v$  characteristic.

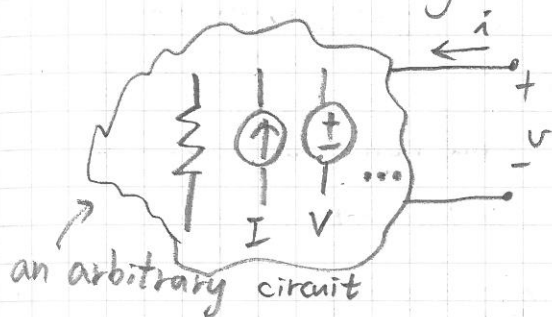Approach: leverage the concept of superposition!




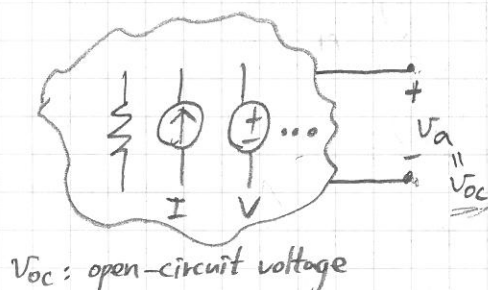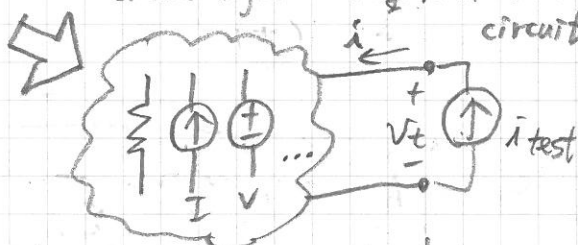We append a testing current source, with the original circuit together they form a new circuit.



$v_{oc}$ : open-circuit voltage

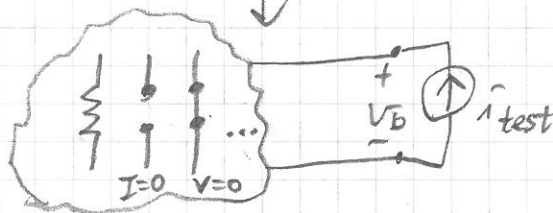set  $i_{test} = 0$       set internal sources = 0






By superposition,

$$v_t = v_a + v_b$$

$$\Rightarrow \boxed{v_t = v_{oc} + i_{test} R_{eq}}$$

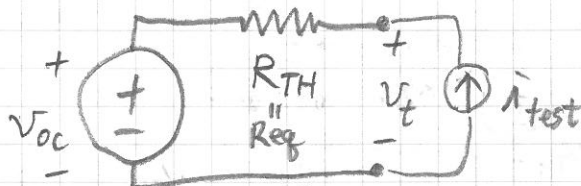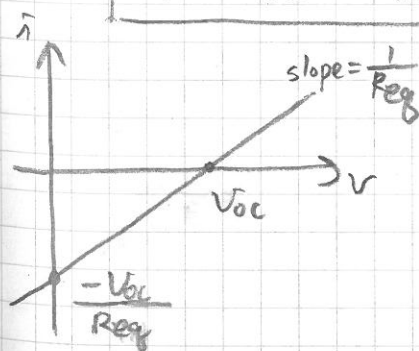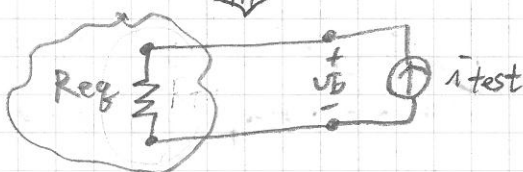
$\Rightarrow$  equivalently, this relation describes the following circuit:



We rename  $R_{eq}$  to  $R_{TH}$  to honor Thévenin

75

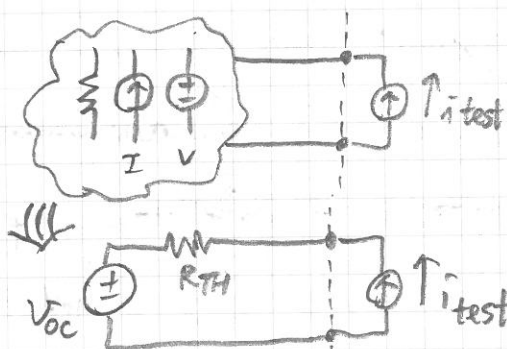P28 Therefore, we have the following equivalence:




In other word, we may reduce an arbitrary <sup>linear</sup> circuit to an equivalent circuit of the form:




We name  $V_{TH} = V_{OC}$   
in honor of Thévenin.

Example:

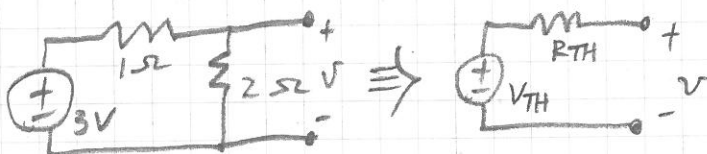

$$V_{TH} = V = 3 \times \frac{2}{1+2} = 2V, \quad R_{TH} = \frac{1 \cdot 2}{1+2} = \frac{2}{3} \Omega \quad \text{from} \quad \begin{array}{c} 1\Omega \\ \parallel \\ 2\Omega \end{array}$$

Another example: find  $I = ?$

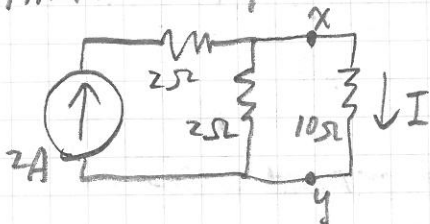


calculating  $V_{TH}$ :




$$V_{TH} = 2A \times 2\Omega = 4V$$

calculating  $R_{TH}$ :

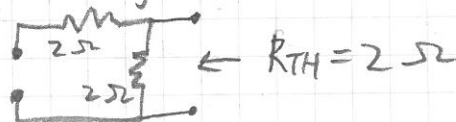

$$\Rightarrow I = \frac{4}{2+10} = \frac{1}{3} A$$

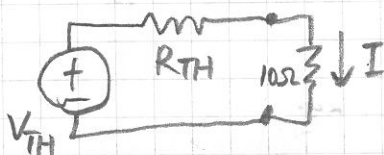
We may replace the left side of x-y by an equivalent circuit:




$$\text{Then } I = \frac{V_{TH}}{R_{TH} + 10\Omega}$$

Exercise: create the Thévenin Equivalent Circuit for the following circuit:

P29

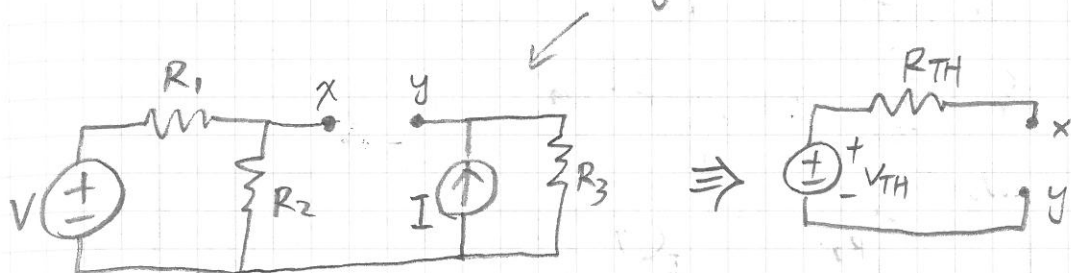


first of all, for  $R_{TH}$ :

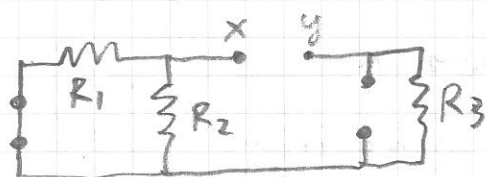

$$\Rightarrow R_{TH} = (R_1 // R_2) + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3$$


then, for  $V_{TH}$ :

approach ①, using superposition


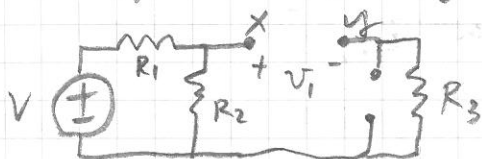


$$V_{TH} = V_1 + V_2$$


$$= \frac{R_2}{R_1 + R_2} V + (-IR_3)$$

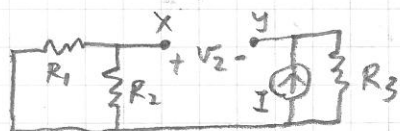
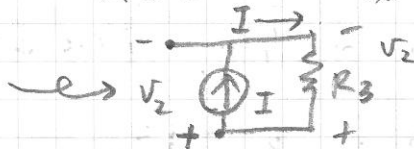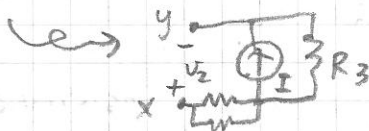
$$= \frac{R_2}{R_1 + R_2} V - IR_3 \quad \times$$



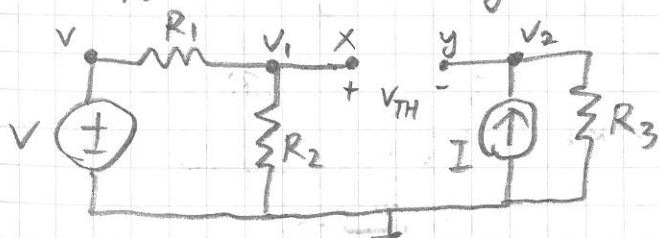approach ②, using the node method (Page 21)



$$V_{TH} = V_1 - V_2 = \frac{R_2}{R_1 + R_2} V - IR_3 \quad \times$$


$$\text{KCL: } \begin{cases} \frac{V - V_1}{R_1} + \frac{0 - V_1}{R_2} = 0 \\ I + \frac{0 - V_2}{R_3} = 0 \end{cases} \Rightarrow \begin{cases} V_1 = \frac{R_2}{R_1 + R_2} V \\ V_2 = IR_3 \end{cases}$$

P30 In the exercise on the previous page, you might wonder why we can do the following transformation:



Could it be possible that there are some current flowing through  $R_1$  and/or  $R_2$ ?

We can use KCL to figure it out:

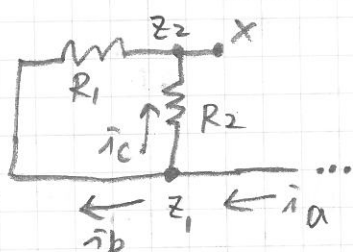

for node  $z_1$ , we have

$$\hat{i}_a - \hat{i}_b - \hat{i}_c = 0$$


for node  $z_2$ , we have

$$\hat{i}_b + \hat{i}_c = 0$$

← compare


Therefore, we see that  $\hat{i}_a = 0$ .

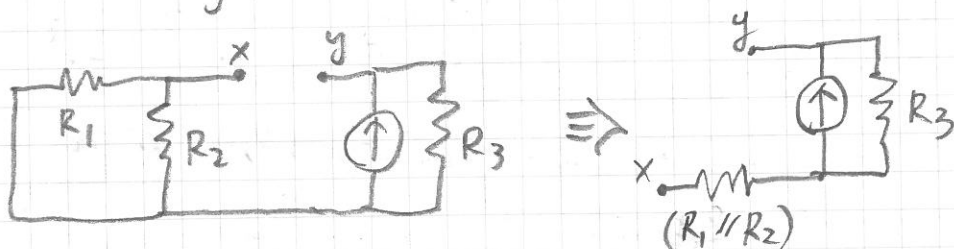In practice, it is often helpful to think in terms of equivalent resistance, which may make the situation much more obvious:




Exercise : In the following circuit, determine voltage  $V_0$  :

P31

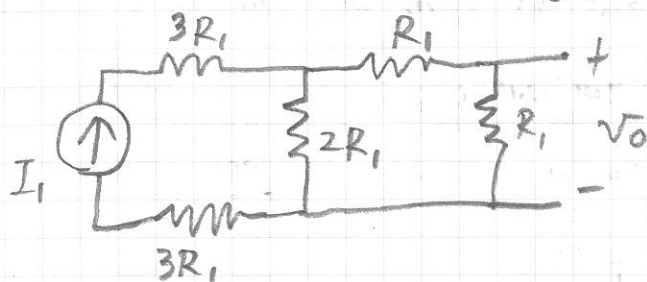


We may do the following transformation :

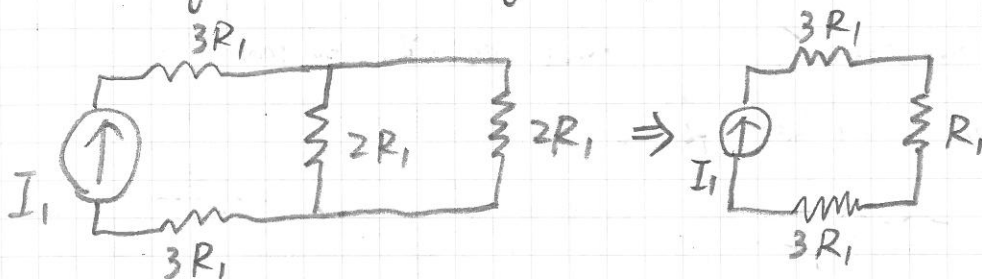

then we might conclude that  $V_0 = I_1 \cdot R_1$ , but it is wrong.

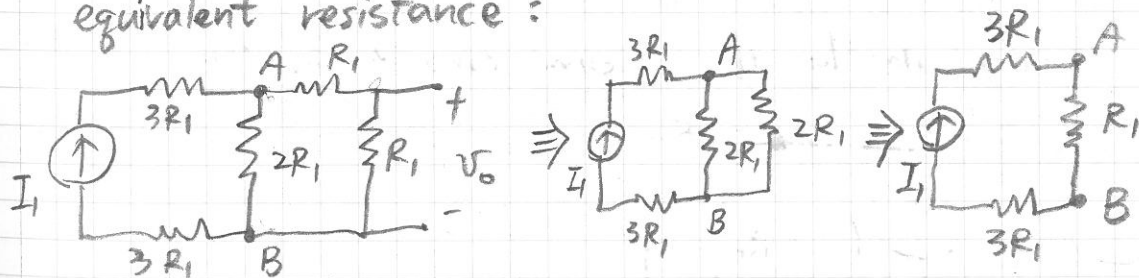To see this, it could be helpful to clearly label the nodes between which you calculate the equivalent resistance :



thus we see that  $V_0$  is not the voltage across A, B, and  $V_0 = (\text{voltage across A, B}) \times \frac{R_1}{R_1 + R_1}$

$$= (I_1 \cdot R_1) \times \frac{R_1}{R_1 + R_1} = \frac{1}{2} I_1 R_1 \text{ is the correct answer,}$$

✖