
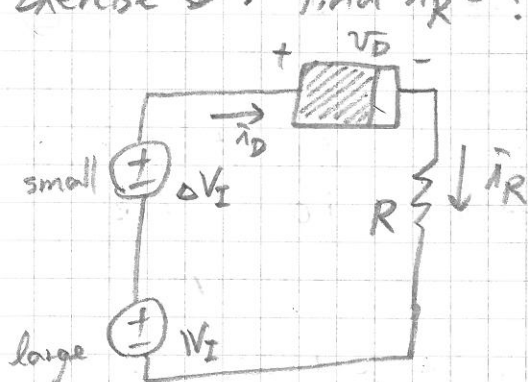


## Exercises for small-signal analysis:

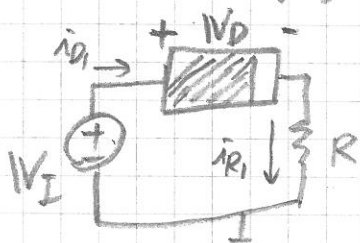Exercise ①: find  $\hat{i}_R = ?$  (The diode is defined on page 37)

$$\text{Ans: } \hat{i}_R = IK \left( \frac{-1 + \sqrt{1 + 4IKV_I R}}{2IKR} \right)^2 + \frac{\Delta V_I}{R + \left( \frac{R}{-1 + \sqrt{1 + 4IKV_I R}} \right)}$$

Solution: First of all, it is clear that  $v_D > 0$  in this case.




From analytical analysis, we have

$$\frac{V_I - V_D}{R} = IK V_D^2$$

$$\Rightarrow V_D = \frac{-1 + \sqrt{1 + 4IKV_I R}}{2IKR}$$
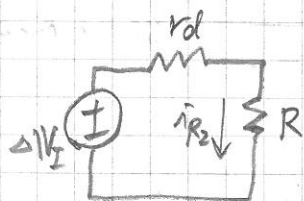
$$\Rightarrow \hat{i}_{R1} = \hat{i}_{D1} = IK V_D^2$$



$$r_d = \frac{1}{f'(v_D)|_{v_D=V_D}} = \frac{1}{2IK \cdot v_D|_{v_D=V_D}}$$


$$= \frac{R}{-1 + \sqrt{1 + 4IKV_I R}}$$

$$\hat{i}_{R2} = \frac{\Delta V_I}{R + r_d} = \frac{\Delta V_I}{R + \left( \frac{R}{-1 + \sqrt{1 + 4IKV_I R}} \right)}$$

finally,  $\hat{i}_R = \hat{i}_{R1} + \hat{i}_{R2}$  \*

P57

Exercise (2): find  $i_D = ?$

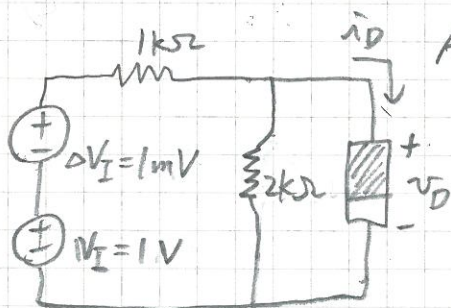


Ans: 0.2504 mA \*

$$i_D = \begin{cases} 1K v_D^2 & \text{for } v_D > 0 \\ 0 & \text{else} \end{cases}$$

$1K = 1 \text{ mA/V}^2$

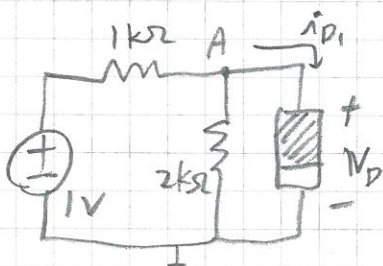
Solution: First of all, from voltage divider we know that  $v_D > 0$



Note that  $v_D \neq 1 \times \frac{2}{1+2}$

$$\begin{cases} \frac{1 - v_D}{1} = \frac{v_D - 0}{2} + i_D & (\text{KCL at A}) \\ i_D = 1K v_D^2 & (\text{element's law}) \end{cases}$$
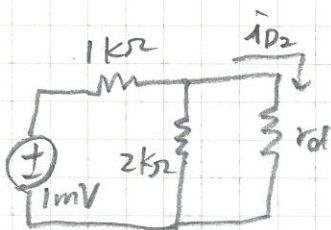
$$\Rightarrow v_D = \frac{1}{2} \text{ V} \Rightarrow i_D = 0.25 \text{ mA}$$



$$r_d = \frac{1}{f'(v_D)|_{v_D=v_D}} = \frac{1}{2 \cdot 1K v_D} = \frac{1}{1K} = 1 \text{ k}\Omega$$

$$i_{D2} = \left( \frac{2}{1+2} \right) \times \frac{1 \text{ mV}}{1 + \frac{1 \times 2}{1+2}} = 0.4 \mu\text{A}$$

current divider  $= 0.4 \times 10^{-3} \text{ mA}$


finally,  $i_D = i_{D1} + i_{D2}$

$$= 0.25 \text{ mA} + 0.0004 \text{ mA}$$

$$= 0.2504 \text{ mA}$$

\*

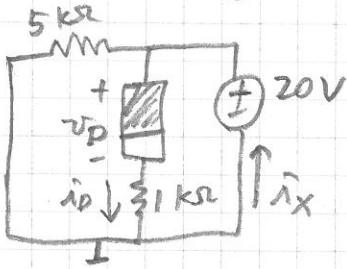
Exercise ③: find  $\bar{i}_x = ?$  Ans: 20 mA \*



Solution: It's clear that  $v_D > 0$   
Apply the node analysis method, we have


$$\begin{cases} \frac{20}{5k\Omega} + \bar{i}_D = \bar{i}_x \\ \bar{i}_D = \frac{20 - v_D}{1k\Omega} \\ \bar{i}_D = 1k \cdot v_D \end{cases} \Rightarrow \begin{cases} v_D = 4V \\ \bar{i}_D = 16mA \\ \bar{i}_x = 20mA \end{cases}$$

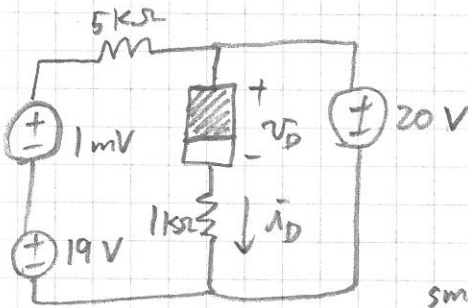Exercise ④ find  $\bar{i}_D = ?$  Ans: 16 mA \*




Solution: see the following decomposition

small signal

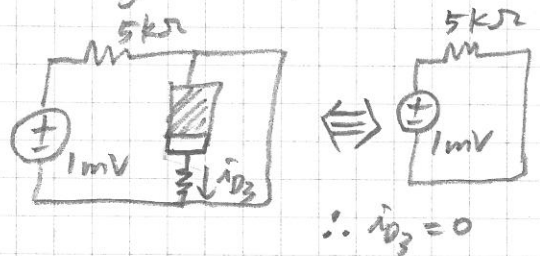

large signal

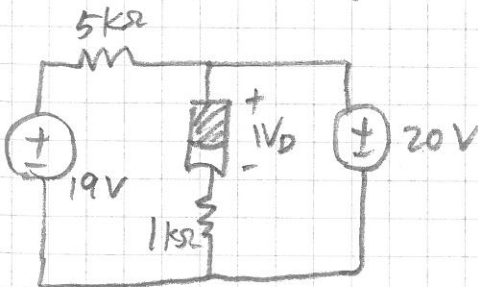

$$\bar{i}_D = \bar{i}_{D1} + \bar{i}_{D2} + \bar{i}_{D3} = 16mA$$

using superposition

