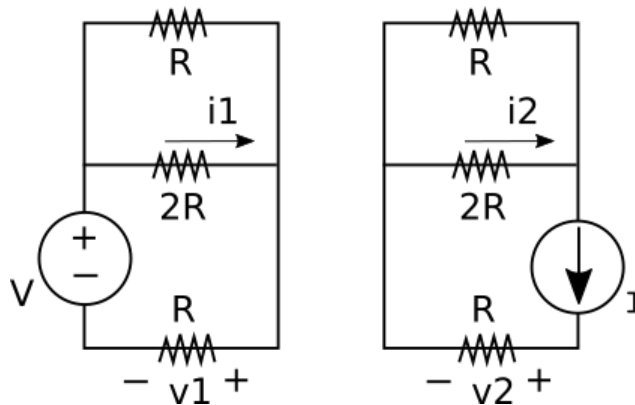


# CSU0007 Basic Electronics, Homework 2

Submit your work via Moodle before 9AM, Oct 27th.


Clearly label your answer for each question. Clearly state your calculation steps.

1. (10 points) For the following circuits, use the node analysis method to determine  $i_1$ ,  $i_2$ ,  $v_1$ , and  $v_2$ .




2. (20 points) For the following circuit,

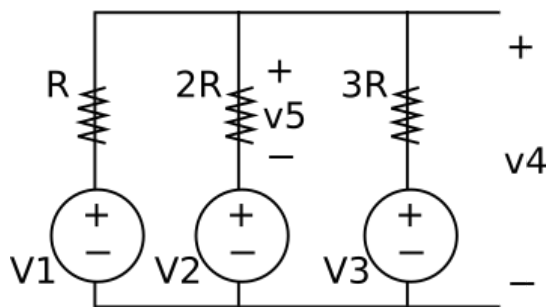1. (10 points) use the node analysis method to determine  $v_4$  and  $v_5$ ;
2. (10 points) now use superposition instead to determine  $v_4$  and  $v_5$ .




3. (10 points) For the following circuit,

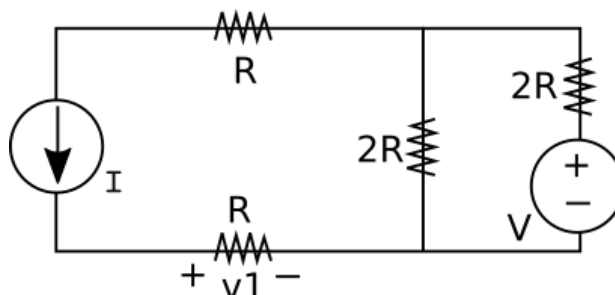1. (3 points) use the basic analysis method to determine  $v_1$ ;
2. (3 points) use the node analysis method to determine  $v_1$ ;
3. (4 points) use superposition to determine  $v_1$ .




4. (20 points) For the following circuit, consider these four separated questions:

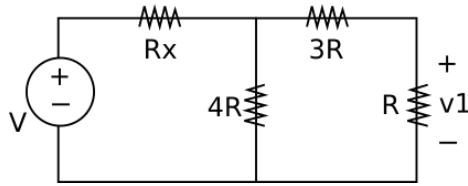1. (5 points) If  $R_x = R \, \Omega$ , what will be the value of  $v_1$ ?
2. (5 points) In order to increase  $v_1$ , shall we increase or decrease  $R_x$ ? Explain.
3. (5 points) In order to have  $v_1 = \frac{1}{5}V$ , what should be the value of  $R_x$ ?
4. (5 points) Is it possible to make  $v_1 = \frac{1}{3}V$  by setting  $R_x = y \, \Omega$  for some  $y > 0$ ? Explain.



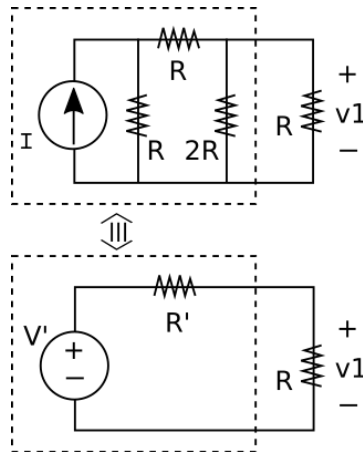5. (15 points) For the following circuit, use Thevenin's Theorem to determine  $v'$ ,  $R'$ , and  $v_1$  in the equivalent circuit. Five points each.



6. (25 points) For the following circuit,

1. (10 points) Determine  $i_1$  using either the basic analysis method, the node analysis method, superposition, or some combination of the three techniques.
2. (15 points) Use Thevenin's Theorem to determine  $v'$ ,  $R'$ , and  $i_3$  in the equivalent circuit.

