

★ Signals, Systems, and Computing

Pg


- In computing systems, information (and energy) is stored and transferred in terms of signals, which are currents or voltages as a function of time.

A circuit (or a system of circuits), as we study in this course, is used to {
① carry signals
② transform signals from one to another

Computing is also a transformation of signals; though the signals are digital and the transformation is described at a higher layer of the abstraction (Figure 1.1 in the textbook).

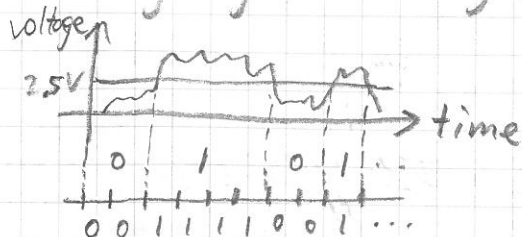Example: We use a smart phone to record this lecture (voice signal \rightarrow currents and voltages), and the recording is stored in the phone, transferred via USB to your laptop, uploaded to a cloud drive, downloaded by your friend who cannot make it to the class, and finally played by your friend's speakers/headphone (currents and voltages \rightarrow voice signals).

- Analog signal to digital signal via discretization:




P10 Section 1.8 in the textbook mentioned sinusoidal signals and the root mean square value. For your interest, the $\sqrt{2}$ ratio between the amplitude of a sinusoidal signal and its rms value comes from 三角函数 2倍角轉換.

Example: let signal $i(t) = I_m \cos(\omega t)$


$$\begin{aligned}
 i_{rms} &= \sqrt{\frac{1}{T} \int_0^T i^2(t) \cdot dt} \\
 &= \sqrt{\frac{1}{T} \int_0^T (I_m^2 \cos^2 \omega t) dt} \\
 &= \sqrt{\frac{I_m^2}{2T} \int_0^T (1 + \cos 2\omega t) dt} \\
 &= \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{T} \int_0^T (1 + \cos 2\omega t) dt} \\
 &= \frac{I_m}{\sqrt{2}} \quad \text{X}
 \end{aligned}$$

★ Resistive Networks and How to Analyze Them

- Terminology

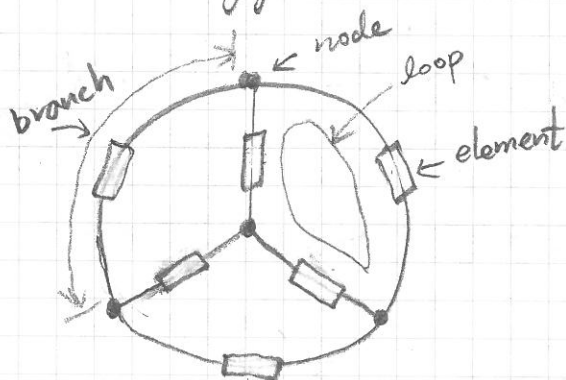

ideal wire: no resistance

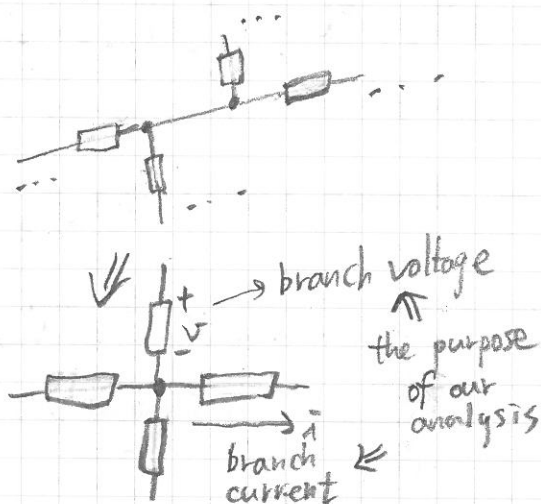

- Kirchhoff's Laws $\begin{cases} \text{KCL} \\ \text{KVL} \end{cases}$

P.11


following LMD, Kirchhoff's laws are simplifications of Maxwell's Equations (see Appendix A.2 in the textbook)

→ KCL and KVL are extremely useful tools to help us analyze a circuit!

KCL: Kirchhoff's current law

The algebraic sum of all branch currents flowing into any node must be zero.

Example:

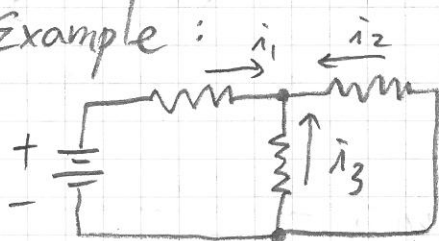

$$\sum_{n=1}^3 \hat{i}_n = 0$$

$$\sum_{n=1}^3 (-\hat{i}_n) = 0$$

In general, for integers N, M , we have

$$\sum_{n=1}^N \hat{i}_n = 0 \Rightarrow \sum_{n=1}^M \hat{i}_n + \sum_{n=M+1}^N \hat{i}_n = 0$$

$$\Rightarrow \sum_{n=1}^M \hat{i}_n = \sum_{n=M+1}^N (-\hat{i}_n)$$


⇒ Sum of total current flowing into a node

= sum of total current flowing out from a node.



P12

Example:

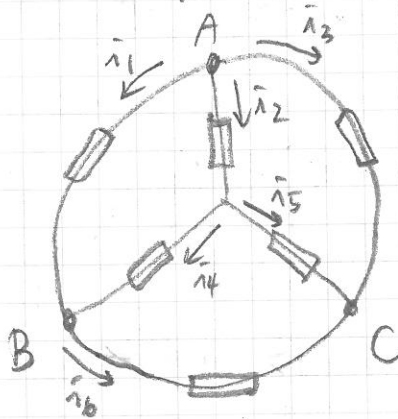

Using KCL

node A: $0 = -\hat{i}_1 - \hat{i}_2 - \hat{i}_3$

B: $0 = \hat{i}_1 + \hat{i}_4 - \hat{i}_6$


C: $0 = \hat{i}_3 + \hat{i}_5 - \hat{i}_6$

D: $0 = \hat{i}_2 + \hat{i}_4 + \hat{i}_5$


Suppose $\hat{i}_1 = 1, \hat{i}_3 = 3 \Rightarrow \hat{i}_2 = -4$

In addition, suppose $\hat{i}_5 = -2$

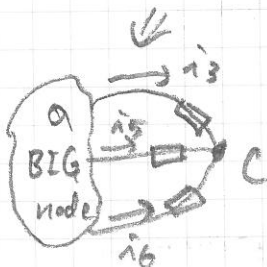$\Rightarrow \hat{i}_4 = -2, \hat{i}_6 = -1$



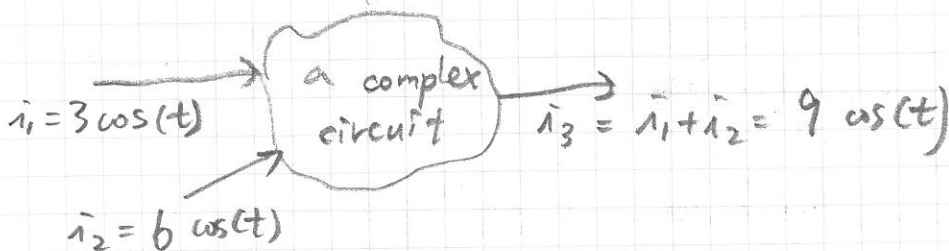
In general, for N KCL statements, only $N-1$ of them are independent. Therefore, we need $N-1$ known values to solve the circuit.



KVL: Kirchhoff's voltage law


The algebraic sum of the branch voltages around any closed path in a network must be zero.

Examples:

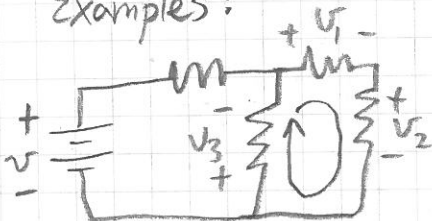

$$\sum_{n=1}^3 V_n = 0$$

並聯

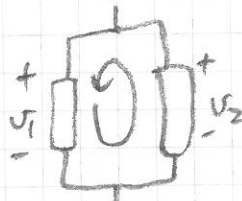

$$0 = v_1 - v_2 \Rightarrow v_1 = v_2$$

串聯




$$0 = -v + v_1 + v_2 \Rightarrow v = v_1 + v_2$$

Example:

using KVL

P13

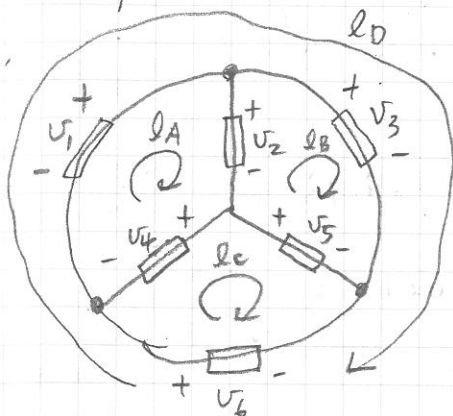

loop l_A : $0 = -V_1 + V_2 + V_4$

l_B : $0 = -V_2 + V_3 - V_5$


l_C : $0 = -V_4 + V_5 - V_6$

l_D : $0 = -V_1 + V_3 - V_6$

Suppose that $V_1 = 1$, $V_3 = 3$, $V_2 = 2$

then $V_4 = -1$, $V_5 = 1$, $V_6 = 2$

Example:

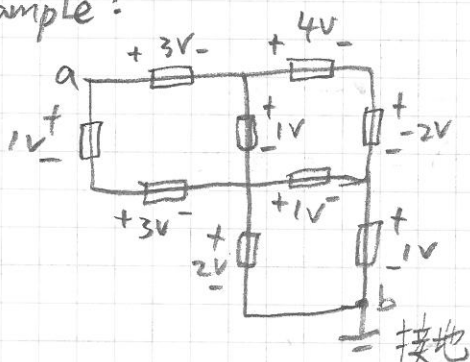

V_{ab} can be determined using KVL


(which loop(s) would you pick?)

$V_{ab} = 6 \text{ V.}$


In general, we model individual elements based on LMD assumptions and we analyze a circuit of elements using KCL and KVL.

★ Two more basic elements and their $i-v$ characteristics


① Independent voltage source

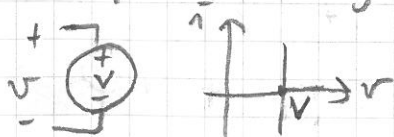

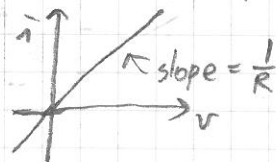for linear resistor it obeys Ohm's law $R = \frac{v}{i}$



② Independent current source


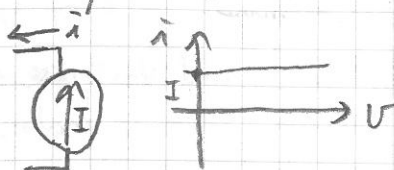


P14

★ Basic Method to Analyze A Circuit

- four steps
- 1° define branch current and voltage consistently see Page 8
 - 2° apply element laws for each elements
(e.g., Ohm's law for linear resistors)
 - 3° apply KCL and KVL
 - 4° jointly solve the equations obtained from 2° and 3°.

Example :

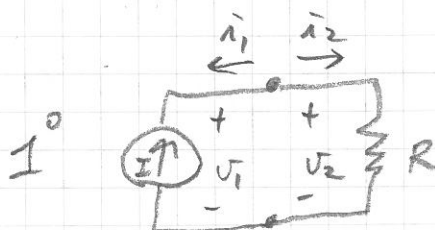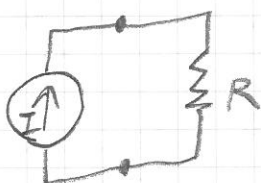


2° $i_1 = -I$, $v_2 = i_2 \cdot R$

3° KCL $\Rightarrow i_1 + i_2 = 0$
KVL $\Rightarrow -v_1 + v_2 = 0$

4° $i_2 = -i_1 = I$
 $v_2 = i_2 R = IR$
 $v_1 = v_2 = IR$ *

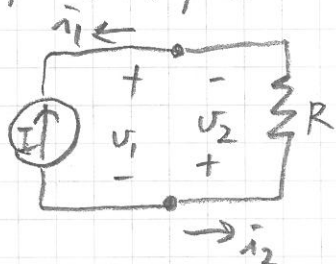if at step 1° we define v_2 inversely, we must




also define i_2 inversely, to be consistent. Applying the basic method you will find

$i_2 = -I$ and $v_2 = -IR$. This may seem to be strange. But if we recall that both i_2 and v_2 have a reversed direction, then it makes sense.

Alternatively, we may solve a circuit by considering "Energy conservation".

Example:

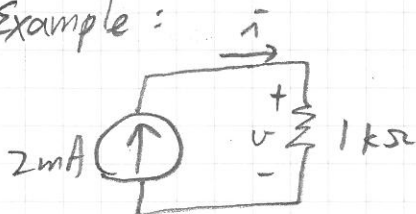

power out from the source:

$$P_{out} = 2mA \times V$$

power into the resistor:

$$P_{in} = i \times V = \frac{V^2}{R}$$


$$= \frac{V^2}{1k\Omega}$$

$$P_{out} = P_{in} \Rightarrow 2 \times 10^{-3} \cdot V = \frac{V^2}{1 \times 10^3}$$

$$\Rightarrow V = 2V$$

(Example 2.14 in the textbook has a typo saying $V = 0.5V$)

★ Voltage Divider

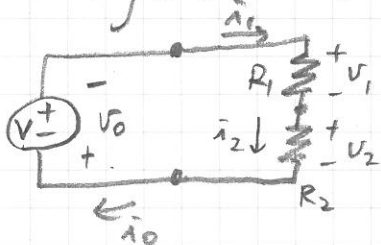

we may analyze it using the basic method:

$$\begin{cases} V_0 = V \\ V_1 = R_1 i_1 \\ V_2 = R_2 i_2 \end{cases} \quad \begin{cases} i_0 = i_1 \\ i_1 = i_2 \end{cases} \text{ KCL} \quad \begin{cases} V_0 + V_1 + V_2 = 0 \end{cases} \text{ KVL}$$

$$\Rightarrow V_2 = \frac{R_2}{R_1 + R_2} V$$

Further, from $i_2 = \frac{V_2}{R_2}$ we see $i = \frac{1}{R_1 + R_2} V$

in other word, $V = i \cdot (R_1 + R_2)$.

\Rightarrow we may replace \wedge an equivalent resistor $R' = R_1 + R_2$ R_1 and R_2 by

and the circuit is equivalent as $V \text{ --- } R'$

This lead to a general planar linear resistor analysis such as that in Example 2.21 in the textbook.