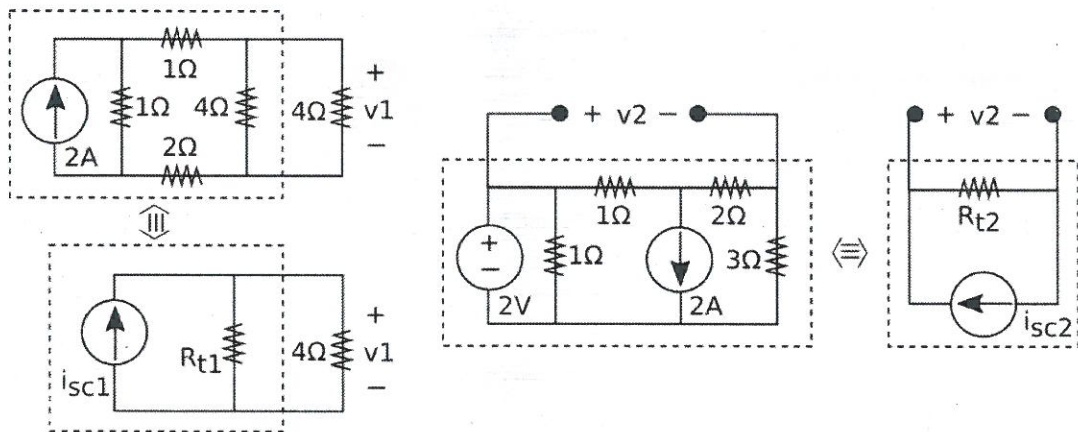


Solution attached

CSU0007 Basic Electronics, Homework 3


- **IMPORTANT!!** Submit your work via Moodle **before 9AM, Nov 10th, 2020**. We will have a review session on Nov 10th in class. The midterm exam will be on Nov 13th in class.
- Four questions in total. Please clearly label your answer for each question, and clearly state your calculation steps.

1. (42 points) Use Norton's Theorem to find $\{i_{sc1}, R_{t1}, v_1\}$ and $\{i_{sc2}, R_{t2}, v_2\}$. 7 points for each variable.




2. (40 points) For the following nonlinear circuits,



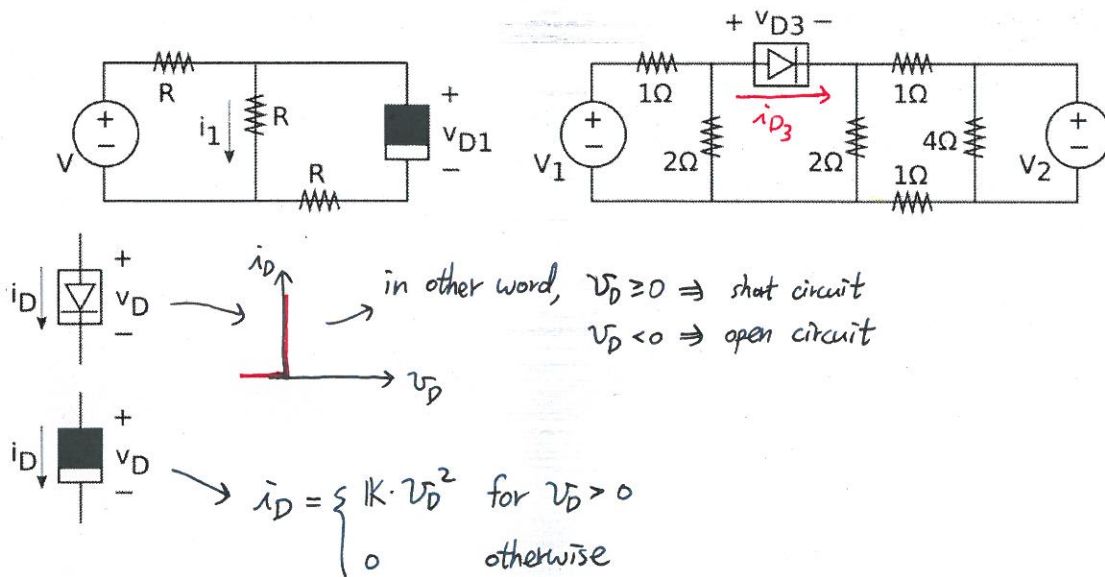
1. (20 points) use the analytical method to determine v_{D1} and i_1 (the method is covered in class and is described in Section 4.2 in the textbook);
2. (20 points) if $0 < 2V_2 < V_1$, what would be the value of i_{D3} ? Use the piecewise analysis method.





3. (10 points) Use the graphical analysis method to explain the following property: Let $v_{I1} > 0$ and $v_{I2} > 0$, and such that v_{I1} caused v_{D1} and v_{I2} caused v_{D2} . Then we have $\Delta v_I > \Delta v_D$ where $\Delta v_I = |v_{I1} - v_{I2}|$ and $\Delta v_D = |v_{D1} - v_{D2}|$. Illustrate and use your own word to explain why $\Delta v_I > \Delta v_D$.

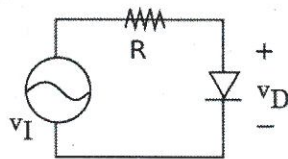

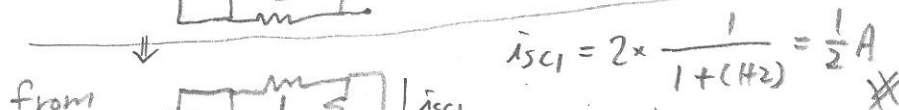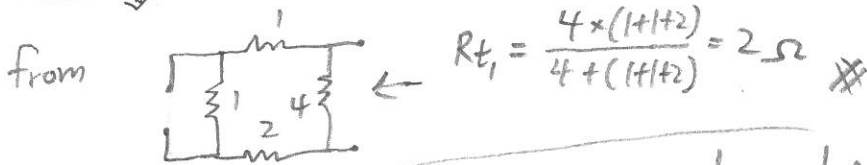
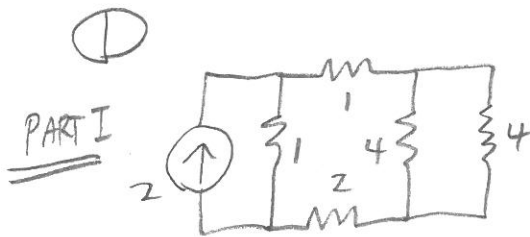
4. (8 points) In class we've talked about an approach to determine R_{TH} in Thevenin's Theorem by using a potentiometer (i.e., a variable resistor 可變電阻). Now, with the additional help of Norton's Theorem, we may determine R_{TH} without using any potentiometer. Think about it and describe an approach to determine R_{TH} by only using a multimeter (i.e., a volt-ohm-milliammeter 三用電表).



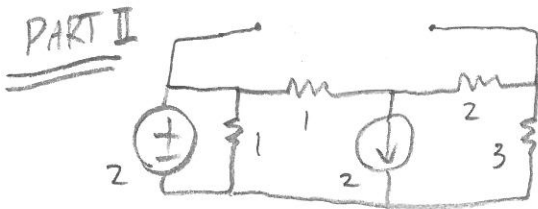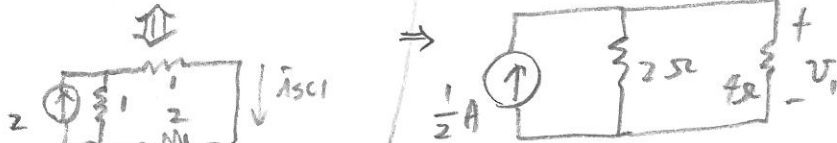
$$v_1 = \left(\frac{1}{2} \times \frac{2}{4+2} \right) \times 4 = \frac{2}{3} V$$
 ✖



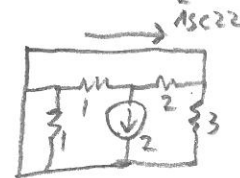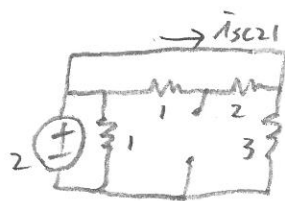
$i_{sc2} = i_{sc21} + i_{sc22}$ by superposition



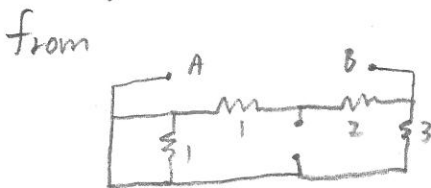$i_{sc22} = 2 \times \frac{1}{1+2} = \frac{2}{3} A$




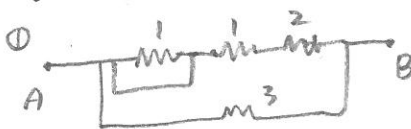There are at least two ways to analyze this:




short circuit has resistance = 0

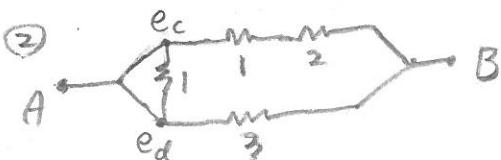$\Rightarrow R_{t2} = \frac{3 \times (\frac{1 \times 2}{1+2} + 1+2)}{3 + (\frac{1 \times 2}{1+2} + 1+2)} = \frac{3}{2} \Omega$ ✖




Since node voltage $e_c = e_d$ there will be no current flowing through $\frac{1}{3} \Omega$ if we attached A, B with a voltage source.

so, equivalently, it is like

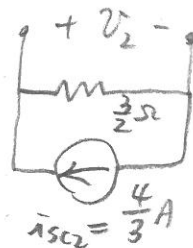

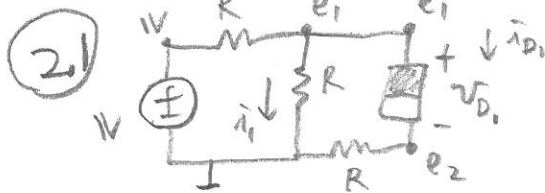$v_2 = \frac{4}{3} \times \frac{3}{2} = 2 V$ ✖



first of all, observe that v_{D1} must be larger than zero.

$$i_1 = \frac{e_1}{R} = \frac{v_{D1} + e_2}{R} = \frac{v_{D1} + R \cdot i_{D1}}{R}$$

$$= \frac{-2 + \sqrt{4 + 12 \cdot 1 \cdot 1}}{6 \cdot 1 \cdot 1^2} + 1 \cdot \left(\frac{-2 + \sqrt{4 + 12 \cdot 1 \cdot 1}}{6 \cdot 1 \cdot 1} \right)^2$$


$$= \frac{-2 + \sqrt{4 + 12 \cdot 1 \cdot 1}}{6 \cdot 1 \cdot 1^2} + \frac{4 + (4 + 12 \cdot 1 \cdot 1) - 4 \sqrt{4 + 12 \cdot 1 \cdot 1}}{36 \cdot 1 \cdot 1^2}$$

$$= -\frac{1}{3} \frac{1}{1 \cdot 1^2} + \frac{2}{9} \frac{1}{1 \cdot 1^2} + \frac{1}{3 \cdot 1} + \frac{1}{18} \sqrt{4 + 12 \cdot 1 \cdot 1}$$

$$\Rightarrow i_1 = -\frac{1}{9} \frac{1}{1 \cdot 1^2} + \frac{1}{3 \cdot 1} + \frac{1}{18} \sqrt{4 + 12 \cdot 1 \cdot 1}$$

A way to verify our derivation is to plug in some good numbers and analyze the circuit with those numbers.

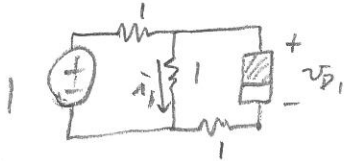For example, let $1 \text{ k}\Omega$, 1 V , $1 \text{ k}\Omega$ we have $v_{D1} = \frac{-2 + \sqrt{4 + 12}}{6} = \frac{1}{3} \text{ V}$
 $\Rightarrow i_{D1} = \frac{1}{9} \text{ mA}$




$$i_1 = \left(\frac{1}{3} + \left(\frac{1}{9} \times 1 \text{ k}\Omega \right) \right) / 1 \text{ k}\Omega = \frac{4}{9} \text{ mA}$$

$$\text{and } i_1 = -\frac{1}{9} \left(\frac{1}{1 \cdot 1^2} \right) + \frac{1}{3 \cdot 1} + \frac{1}{18} \sqrt{4 + 12 \cdot 1 \cdot 1}$$

$$= -\frac{1}{9} + \frac{1}{3} + \frac{2}{9} = \frac{4}{9} \text{ mA}$$

which gives us some assurance that equation 2 is the correct result given that equation 1 is correct.

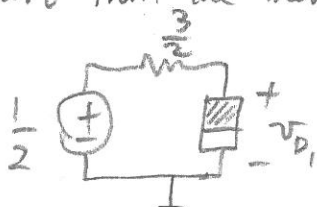To see that equation 1 is correct (and for the sake of practice), we can start from the Thévenin's equivalence:




and use the node analysis


$$\begin{cases} \frac{3}{2} i_D + v_{D1} = \frac{1}{2} \\ i_D = v_{D1}^2 \end{cases} \Rightarrow v_{D1} = \frac{1}{3} \text{ V}, \text{ which is the same as we plugged those numbers into equation 1.}$$

(2.2)

First of all, we need to determine

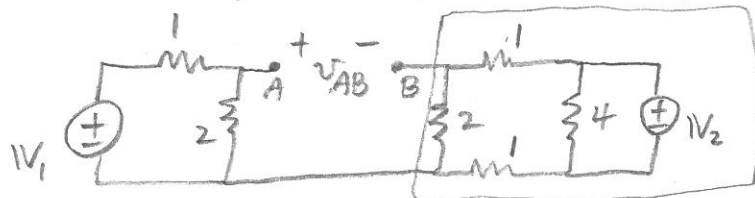


whether we can replace  by or we can replace  by We analyze this by first taking away :

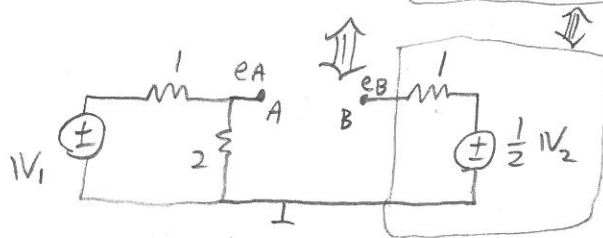→ we may use Thevenin Theorem to simplify this part.

Then we may use either the node analysis method or superposition to obtain that $V_{AB} = \frac{2}{3}V_1 - \frac{1}{2}V_2$.

Given condition $0 < 2V_2 < V_1$, we have $V_{AB} = \frac{2}{3}V_1 - \frac{1}{2}V_2$

$$\Rightarrow V_1 > 2V_2 \quad \quad \quad > \frac{4}{3}V_2 - \frac{1}{2}V_2 > 0$$

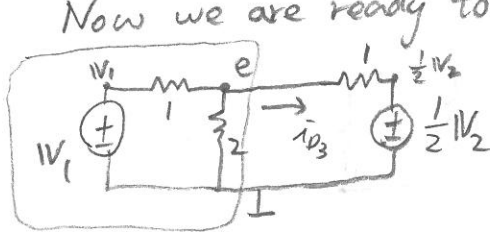Thus, we now see we should consider  as  because the i - v characteristic of the diode told us so.Now we are ready to compute i_{D3} !


$$\begin{cases} \frac{V_1 - e}{1} = \frac{e - 0}{2} + \frac{e - \frac{1}{2}V_2}{1} \\ i_{D3} = \frac{e - \frac{1}{2}V_2}{1} \end{cases}$$

$$\Rightarrow \begin{cases} 2V_1 - 2e = e + 2e - V_2 \\ i_{D3} = e - \frac{1}{2}V_2 \end{cases}$$

$$\Rightarrow \begin{cases} e = \frac{1}{5}(2V_1 + V_2) \\ i_{D3} = \frac{2}{5}V_1 - \frac{3}{10}V_2 \end{cases}$$

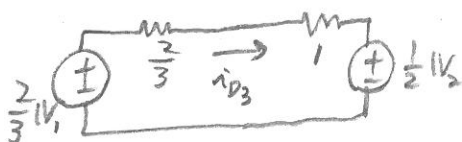
#

alternatively, you may transform the circuit further:



$$i_{D3} = \frac{\frac{2}{3}V_1 - \frac{1}{2}V_2}{\frac{2}{3} + 1} = \frac{2}{5}V_1 - \frac{3}{10}V_2$$


③

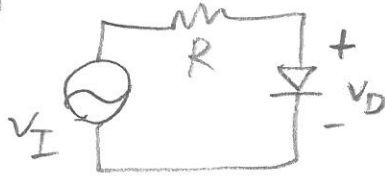

let $f(V_D)$ be the branch current flowing through ∇ (i.e., i_D)

By KCL we have $\frac{V_I - V_D}{R} = f(V_D)$

Therefore we have

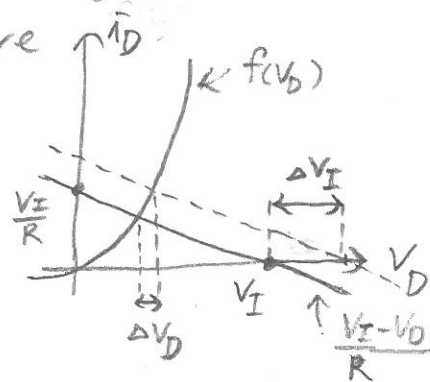

$$\Delta V_I > \Delta V_D$$

because the tangent slope of $f(V_D)$ for all $V_D > 0$ is larger than zero.

④

Refer to page 33 of the Lecture note.

Because $R_{TH} = \frac{V_{open-circuit}}{I_{short-circuit}}$, it is sufficient

to just measure $V_{open-circuit}$ and $I_{short-circuit}$:)