

Solution

CSU0007 Basic Electronics, Homework 7

- Submit your work via Moodle before **5PM, Jan. 14th**. The solution will be available right after for you to prepare for the final exam on Jan. 15th.


1. (50 points) For the following difference amplifier, suppose that $I=0.64\text{mA}$, $V_{CC}=3\text{V}$, $R_L=2\text{k}\Omega$, $K=1\text{mA/V}^2$, $V_T=1\text{V}$, and $v_{CM}=2\text{V}$.

1. (40 points) Suppose that both MOSFETs operate under the saturation discipline.

Compute large signals v_D and v_S .

2. (10 points) Determine the maximum possible v_{CM} for both MOSFET to remain in saturation.


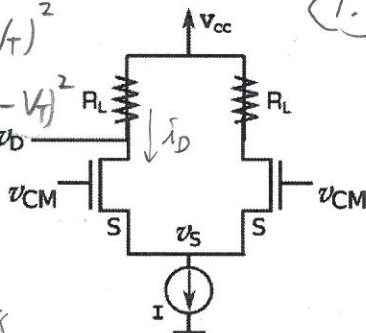
(1.1) $i_D = \frac{I}{2} = \frac{V_{CC} - v_D}{R_L} = \frac{1}{2}K(v_{GS} - V_T)^2$
 $\Rightarrow v_D = V_{CC} - \frac{I}{2}R_L = 2.36\text{V}$
 $\Rightarrow v_S = v_{CM} - V_T - \sqrt{\frac{I}{K}} = 0.2\text{V}$



(1.2) We need $v_{GS} - V_T < v_{DS}$
 $\Rightarrow (v_{CM} - v_S) - V_T < v_D - v_S$
 $\Rightarrow v_{CM} < V_T + v_D = V_T + (V_{CC} - \frac{I}{2}R_L)$
 $= 3.36\text{V}$

2. (30 points) In class, we've shown that $A_d = \frac{v_o}{v_d} = -g_m R_L$ for a difference amplifier:

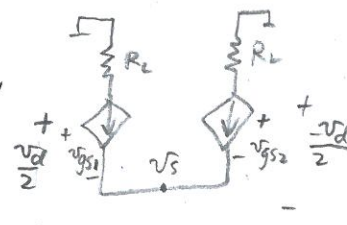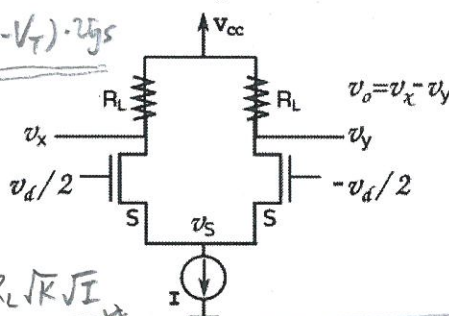(2) $\frac{I}{2} + \Delta i = \frac{1}{2}K(v_{GS} - V_T)^2 + K(v_{GS} - V_T) \cdot v_{gs}$
 $\Rightarrow v_{GS} - V_T = \sqrt{\frac{I}{K}}$
 and since $g_m = K(v_{GS} - V_T)$
 $\Rightarrow A_d = -g_m R_L = -K(v_{GS} - V_T) R_L = -R_L \sqrt{K I}$




Now, assuming both MOSFETs are identical, show that, approximately, $A_d = -R_L \sqrt{K I}$.

Hint: Consider that current $I/2 + \Delta i$ flowing through the left MOSFET and that current $I/2 - \Delta i$ flowing through the right MOSFET, where Δi is of a small quantity.

This result gives us an insight: in order to improve the small-signal voltage gain, we may choose to increase I the biasing current. In this way we keep R_L the same, and thus the output resistance remains unchanged :)

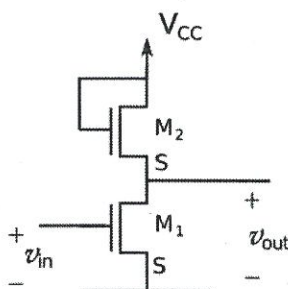3. (20 points) We've learned a way to wire a MOSFET for it to work like a resistor for a small-signal. Now, consider the following inverting amplifier, with the load resistor replaced by MOSFET M_2 (with parameter $K = K_2$). Suppose that M_1 (with parameter $K = K_1$) operates under the saturation discipline:




Show that the small-signal voltage gain, $\frac{v_{out}}{v_{in}}$, is equal to $-\sqrt{\frac{K_1}{K_2}}$.

Hint: The same amount of current should flow through both M_1 and M_2 .

This result suggests a cool feature: recall that parameter K for a MOSFET is in portion to the geometric length (L) and width (W) of the channel between source and drain, i.e., $K = K'(\frac{W}{L})$. Assuming that the two MOSFETs have identical K' and L , then essentially, we may setup the voltage gain of this circuit by building the MOSFETs with the calculated relative channel widths :)

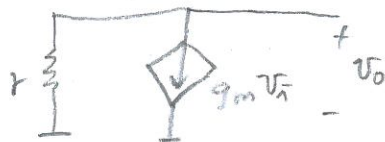③ The small-signal resistance, r , from M_2 is $\frac{1}{1K_2(V_{GS_2} - V_T)}$



$$\frac{v_o}{v_i} = -g_m \cdot r$$

$$= -1K_1(V_{GS_1} - V_T) \cdot \frac{1}{1K_2(V_{GS_2} - V_T)}$$

since $i_{D_1} = i_{D_2}$

$$\Rightarrow \frac{1K_1(V_{GS_1} - V_T)^2}{2} = \frac{1K_2(V_{GS_2} - V_T)^2}{2}$$

$$\Rightarrow \frac{V_{GS_1} - V_T}{V_{GS_2} - V_T} = \sqrt{\frac{1K_2}{1K_1}}$$

$$\Rightarrow \frac{v_o}{v_i} = -\sqrt{\frac{1K_1}{1K_2}}$$

#