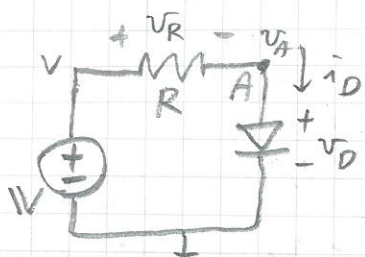


P38 Motivation for graphical analyses:
Consider the following example



KCL at node A:

$$\frac{v_A - V}{R} + I_S (e^{v_D/V_{TBE}} - 1) = 0$$

$$\Rightarrow \frac{v_D - V}{R} + I_S (e^{v_D/V_{TBE}} - 1) = 0$$

Solving for v_D is like solving for

x for $ax + be^x + c = 0$ for some constants a, b , and c .

→ May be solved by trial-and-error

→ little insight, however.

What if we want to know the impact of increasing/decreasing V to the value of v_D ?

And, how would v_D change with the change of R ? These are critical questions to ask when designing an electronic circuit.

Now, graphical analyses can be very helpful in this aspect!

For concreteness, suppose $V = 3\text{ V}$

P39

in the example on P38.

$$R = 500\ \Omega$$

$V_{THE} = 0.025\text{ V}$ in room temperature

We can leverage KCL and KVL to state two equations for i_D :

$$\begin{cases} i_D = I_s (e^{v_D/V_{THE}} - 1) = 10^{-12} (e^{v_D/0.025} - 1) \\ i_D = \frac{V_R}{R} = \frac{V - v_D}{R} = -\frac{1}{R} v_D + 0.006 \quad (\text{unit: A}) \end{cases}$$

then graphically speaking, the solution of i_D and v_D lies at the intersection point of the two curves on the i_D - v_D plane:

i_D

v_D

slope $= -\frac{1}{R}$

0.6

0.5

0.6

3

$i_D = -\frac{1}{R} v_D + \frac{V}{R}$

i_D

$\frac{V}{R}$

solution for (v_D, i_D)

v_D

V

if R changes

i_D

v_D

if V increases

then we see $\Delta v_D \ll \Delta V$
(exercise: try to explain why)

Δv_D

ΔV

V

V_{new}

R



$R + \Delta R$

V

which give much insight in how the circuit would behave!

P₄₀ Another example (half-wave voltage rectifier)

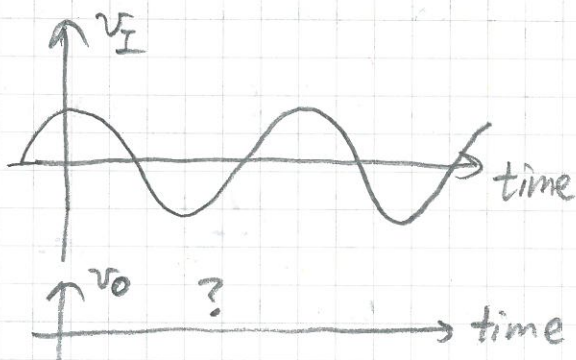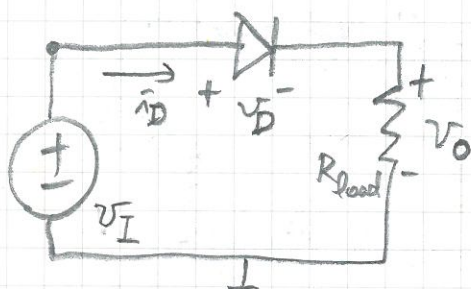In the following circuit,
given a time-varying voltage source v_I ,
what will be the output voltage v_O across
a resistor?




From KVL, $v_I - v_D - v_O = 0$

$$\Rightarrow v_O = v_I - v_D$$

From KCL, element law, and
the i-v characteristic of the diode:
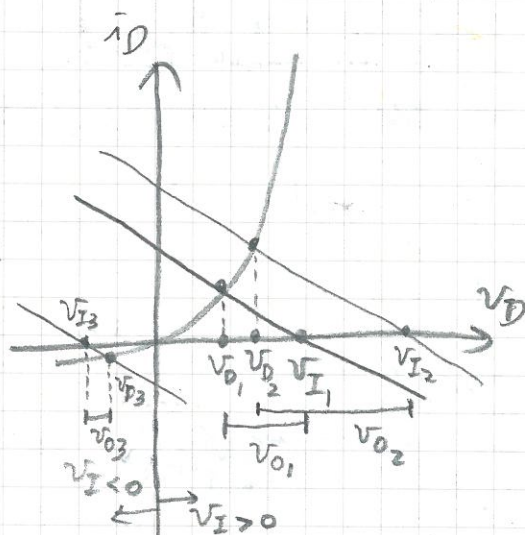
$$\begin{cases} i_D = I_S (e^{v_D/V_{TNE}} - 1) \\ i_D = \frac{v_O}{R} = \frac{v_I - v_D}{R} \end{cases}$$



We see $v_{D3} \approx 0$ when $v_D < 0$
because the curve is
very close to the X axis

