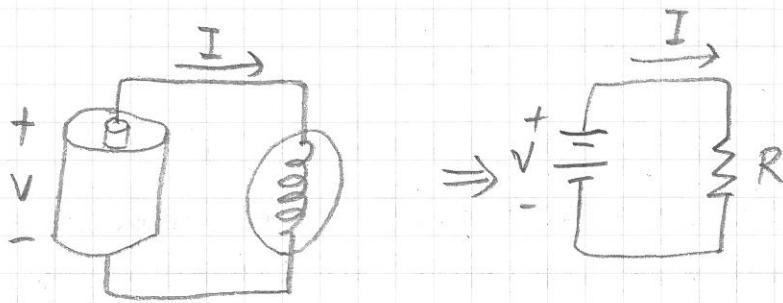


P1

- The lumped circuit abstraction



for now, let's just consider elements having two terminals, e.g,



We may ignore the internal structure of an element and consider it as a "lump", where we may completely describe relevant properties (such as voltage and current) by only observing its terminals.


For example, if a resistor with resistance R obeys Ohm's law, then we may compute the current flowing through the resistor by the voltage across its terminals : $I = V/R$.

The lumped circuit abstraction works only under certain constraints, which we call the lumped matter discipline (LMD).

From Physics to Electronic Circuit:


- ★ The lumped matter discipline (LMD) → a set of rules that control an activity or situation.
- simplify the analysis of electronic circuit
 - modularize a complex circuit into analyzable elements

Derivation of LMD:

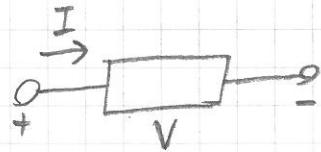

goal #1:

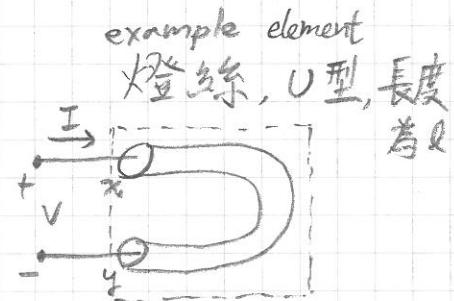able to ascribe a unique voltage across the terminals X and Y



definition of voltage:

$$V_{yx} = - \int_x^y \mathbf{E} \cdot d\mathbf{l}$$

where \mathbf{E} is the electrical field (a vector)

$d\mathbf{l}$ is a tiny portion of \mathbf{l}

and Faraday's law of induction:

$$\oint \mathbf{E} \cdot d\mathbf{l} = - \frac{\partial \Phi_B}{\partial t}$$

where Φ_B is the magnetic flux.

\oint represents a closed path integral


Then we see that if there's no time-varying magnetic flux,

$$\oint \mathbf{E} \cdot d\mathbf{l} = 0 \Rightarrow \int_x^y \mathbf{E} \cdot d\mathbf{l} + \int_y^x \mathbf{E} \cdot d\mathbf{l} = 0$$

along path 1 path 2

$$\Rightarrow \int_x^y \mathbf{E} \cdot d\mathbf{l} = \int_x^y \mathbf{E} \cdot d\mathbf{l}$$

path 1 path 2

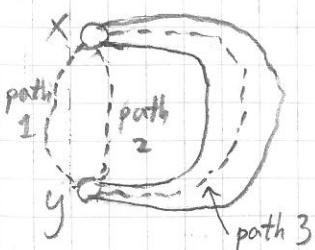

也就是說 $\int_x^y \mathbf{E} \cdot d\mathbf{l}$ 的值和路徑無關! ($= \int_{\text{path } 3}^y \mathbf{E} \cdot d\mathbf{l}$)

P3

Therefore, the constraint for goal #1 is

$$\frac{\partial \phi_B}{\partial t} = 0,$$

and we assumed that holds for all time.

(To make sure this constraint holds, we may need to revise

goal #2:

able to define a unique current
through the terminals X and Y

the model and introduce
an element called
"inductor".)

First of all, the definition of current:

$$I = \int_{S_z} J \cdot dS$$




where J is the current density at a given point within the filament and S_z is the cross-sectional surface of the filament at point z .

Due to the conservation of charge, we have

$$\oint J \cdot dS = -\frac{\partial \phi}{\partial t} \quad \text{for a closed surface}$$

~~~~~      ~~~~

流出的电量      減少的电量

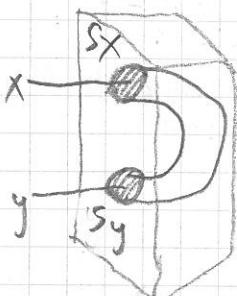

Thus, if there's no time-varying charge within the closed surface, we have

$$\oint J \cdot dS = 0 \Rightarrow -\int_{S_x} J \cdot dS + \int_{S_y} J \cdot dS = 0$$

假設  $S_x$  為唯一入口  
 $S_y$  為唯一出口。

$$\Rightarrow \int_{S_y} J \cdot dS = \int_{S_x} J \cdot dS$$



$$I_{in} = I_{out}$$

Therefore, the constraint for goal #2 is

P<sub>4</sub>

$$\frac{\partial g}{\partial t} = 0,$$

and we assume that holds for all time.

(To make sure this constraint holds, we may need to revise the model and introduce an element called "capacitor".)


Besides goals #1 and #2, we also need to assume that the signal timescale must be much

↳ ...0110100... for example

larger than the propagation delay of electromagnetic waves across the lumped elements. (Otherwise, ... see textbook P<sub>II</sub>)

⇒ the size of our lumped elements must be much smaller than the wavelength associated with the V and I signals, and such a condition may be challenging to hold as we reduce the element size and increase the operating frequency (e.g., a 2 GHz CPU).

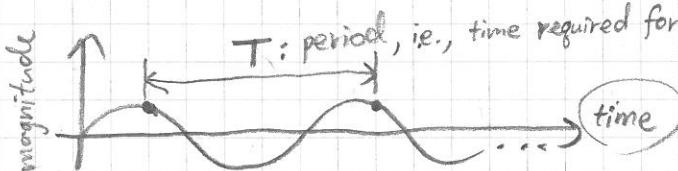definition of wavelength: the <sup>(λ)</sup> distance between two adjacent points in the wave having the same phase.



$$\lambda = v \cdot T = v \cdot \frac{1}{f} \Rightarrow f \uparrow \text{ then } \lambda \downarrow$$

wavelength    wave speed    period    ↑  
frequency

for example, electromagnetic waves travel at about  $15 \times 10^4$  km/s, or  $15 \times 10^9$  cm/s, within a microprocessor (to be specific, through silicon dioxide).

Now, suppose that the microprocessor operates at a clock rate of 2 GHz. This translates to the wavelength equal to  $\lambda = 15 \times 10^9 / 2 \times 10^9 = 7.5$  cm,

which means that LMD may not hold if the microprocessor chip is larger than 7.5 cm on a side.

Think about it : what if ① clock rate  $\uparrow$  ?  
 ② wave speed  $\uparrow$  ?

In general, in computer engineering, people are often working to meet various constraints (such as this) so that they may apply a previously established model (such as LMD) and make use of known results/properties that depend on the given model. This is like "Standing on the shoulders of giants."


- Basic lumped element 1: batteries

Two key properties  
 | energy 能量 (unit: joule <sup>or</sup> ampere-hours)  
 | power 功率 (unit: watt)

能量轉換或使用的速率

$$P = V \cdot I$$

| watt = 1 volt  $\cdot$  1 ampere

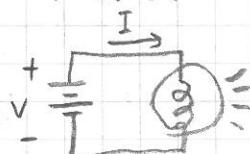

P6

Let  $\Sigma$  be the amount of energy supplied to an element over an interval  $T$ , then we have  $\Sigma = P \cdot T$ . In general, the amount of energy supplied is the time integral of the power.

$$1 \text{ joule} = 1 \text{ watt-second}$$

Example: Suppose a Raspberry Pi consumes 2W of power and its energy is supplied by a 3.7V, 2600 mA-h battery. For how long can the battery power the Raspberry Pi?

$$\begin{aligned} P = V \cdot I &= 3.7 \times 2600 \times 10^{-3} \text{ W-h} \\ &= 9.62 \text{ W-h} \end{aligned}$$

$$\frac{9.62 \text{ W-h}}{2 \text{ W}} = 4.81 \text{ hours} *$$

- Basic lumped element 2: resistors (linear)

Ohm's law: the voltage measured across the terminals of a resistor is linearly proportional to the current flowing through the resistor.

That is,  $V = i \cdot R$


Further,

$$R = \rho \frac{l}{a}$$


we call it the resistance of a resistor.

(see Appendix A.3  
in the textbook)


resistivity

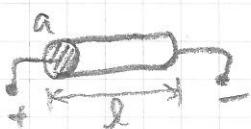

also,  $R = \rho \frac{l}{wh}$

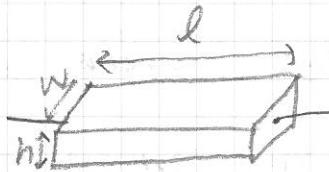

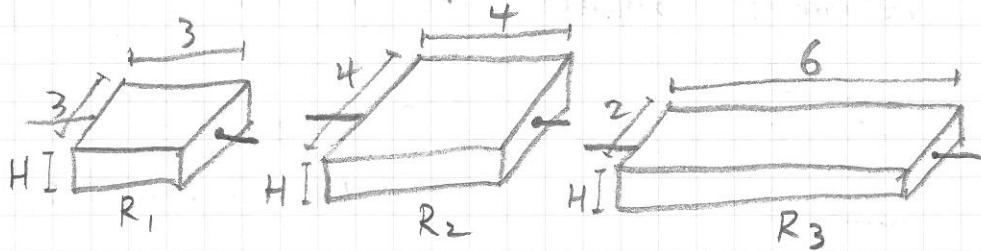Example : Consider three planar resistors as follows



Let  $R_0 = \rho_0 \frac{1}{1 \cdot H} = 2 k\Omega$  and assume  $\rho_0 = \rho_1 = \rho_2 = \rho_3$

Then  $R_1 = \rho_1 \frac{3}{3 \cdot H} = R_0 = 2 k\Omega$

$$\frac{R_1}{R_2} = \frac{\rho_1 \frac{3}{3H}}{\rho_2 \frac{4}{4H}} = 1 \text{ and } R_2 = R_1 = 2 k\Omega$$

$$\frac{R_2}{R_3} = \frac{\rho_2 \frac{4}{4H}}{\rho_3 \frac{6}{6H}} = \frac{1}{3} \Rightarrow R_3 = 6 k\Omega$$

exercise : you can verify that  $\frac{R_1}{R_3} = \frac{R_2}{R_3}$ .

$\Rightarrow$  等比例縮小長及寬，則相對電阻值 \_\_\_\_\_ ?


$\Rightarrow$  缩小晶片的大小不會改變相對電阻值 A.  $\downarrow$  B.  $\uparrow$  C. 不變

$\Rightarrow$  Often, signal values are derived as a function of resistance ratios. Therefore, by such a process shrink the chip may continue to function as before!

example : a voltage divider, which we will study later this semester.



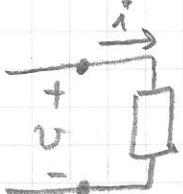
# - Associated Variable Convention : (约定俗成)

For a two-terminal lumped element,  
define current to flow in at the element  
terminal assigned to be positive in voltage.



$v$  and  $i$  are called  
"terminal variables".

Example :

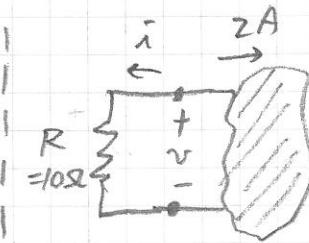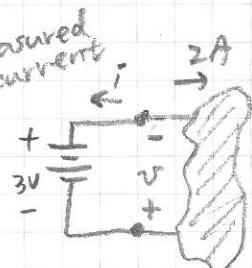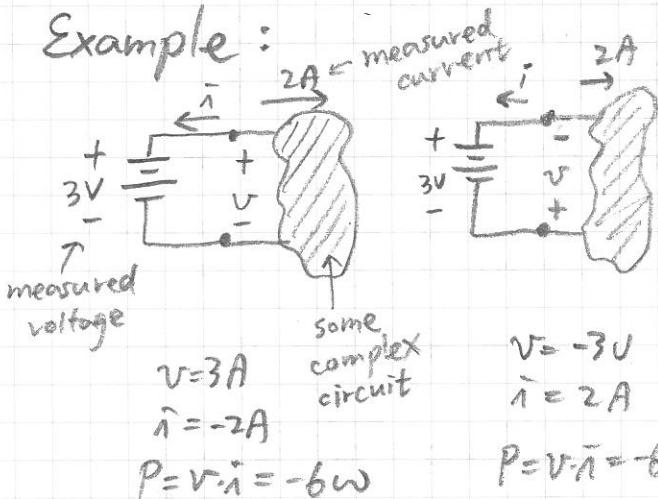


$$\begin{aligned} i &= -2A \\ v &= iR = -20V \\ P &= v.i = 40W \end{aligned}$$

$\Rightarrow$  power supplied "from" battery  
by

$\Rightarrow$  power supplied "to" resistor

(and then is  
dissipated in  
the form of heat)

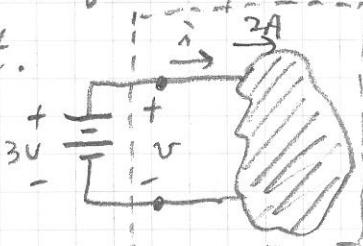Note that the above is from the viewpoint of the battery ; from the viewpoint of that complex circuit, you may try and see that now power is supplied "to" it.



# ★ Signals, Systems, and Computing

- In computing systems, information (and energy) is stored and transferred in terms of signals, which are currents or voltages as a function of time.

A circuit (or a system of circuits), as we study in this course, is used to

{ ① carry signals  
② transform signals from  
one to another

Computing is also a transformation of signals; though the signals are digital and the transformation is described at a higher layer of the abstraction (Figure 1.1 in the textbook).

Example: We use a smart phone to record this lecture (voice signal  $\rightarrow$  currents and voltages), and the recording is stored in the phone, transferred via USB to your laptop, uploaded to a cloud drive, downloaded by your friend who cannot make it to the class, and finally played by your friend's speakers/headphone (currents and voltages  $\rightarrow$  voice signals).

- Analog signal to digital signal via discretization:




P10 Section 1.8 in the textbook mentioned sinusoidal signals and the root mean square value. For your interest, the  $\sqrt{2}$  ratio between the amplitude of a sinusoidal signal and its rms value comes from 三角函數 2 倍角轉換.

Example: Let signal  $i(t) = I_m \cos(\omega t)$



$$\begin{aligned} i_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T i^2(t) \cdot dt} \\ &= \sqrt{\frac{1}{T} \int_0^T (I_m^2 \cos^2 \omega t) dt} \\ &= \sqrt{\frac{I_m^2}{2T} \int_0^T (1 + \cos 2\omega t) dt} \\ &= \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{T} \int_0^T (1 + \cos 2\omega t) dt} \\ &= \frac{I_m}{\sqrt{2}} \times \end{aligned}$$

## ★ Resistive Networks and How to Analyze Them

### - Terminology

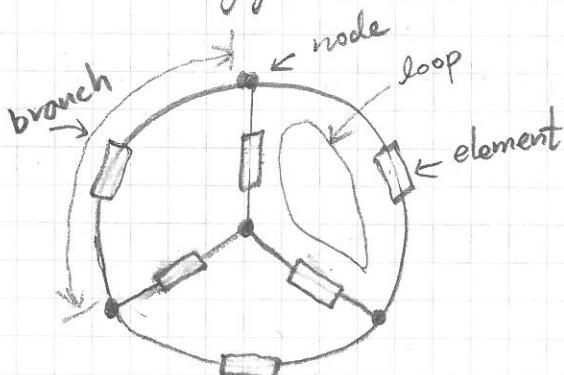

ideal wire : no resistance

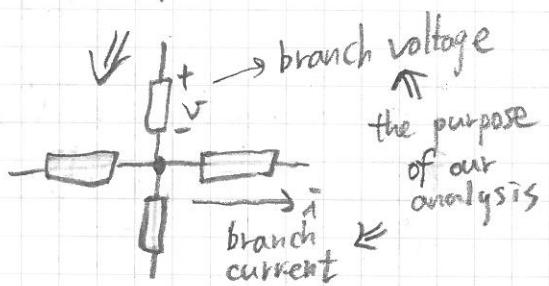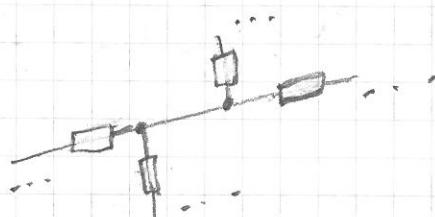

the purpose  
of our  
analysis

- Kirchhoff's Laws  $\left\{ \begin{array}{l} \text{KCL} \\ \text{KVL} \end{array} \right.$

following LMD, Kirchhoff's laws are simplifications of Maxwell's Equations


(see Appendix A.2 in the textbook)

→ KCL and KVL are extremely useful tools to help us analyze a circuit!

KCL : Kirchhoff's current law —

The algebraic sum of all branch currents flowing into any node must be zero.

Example :

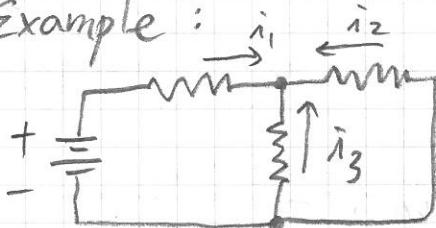

$$\sum_{n=1}^3 i_n = 0$$

$$\sum_{n=1}^3 (-i_n) = 0$$

In general, for integers  $N, M$ , we have

$$\sum_{n=1}^N i_n = 0 \Rightarrow \sum_{n=1}^M i_n + \sum_{n=M+1}^N i_n = 0$$

$$\Rightarrow \sum_{n=1}^M i_n = \sum_{n=M+1}^N (-i_n)$$


⇒ Sum of total current flowing into a node

= sum of total current flowing out from a node.



P12

Example:

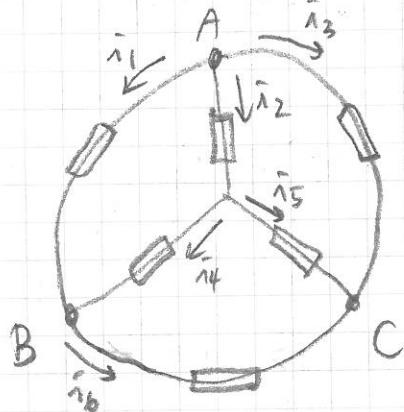

Using KCL

$$\text{node A: } 0 = -i_1 - i_2 + i_3$$

$$B: 0 = i_1 + i_4 - i_6$$


$$C: 0 = i_2 + i_4 - i_5$$

$$D: 0 = i_3 + i_5 + i_6$$


$$\text{Suppose } i_1 = 1, i_3 = 3 \Rightarrow i_2 = -4$$

In addition, suppose  $i_5 = -2$
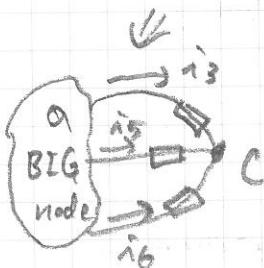
$$\Rightarrow i_4 = -2, i_6 = -1 \times$$



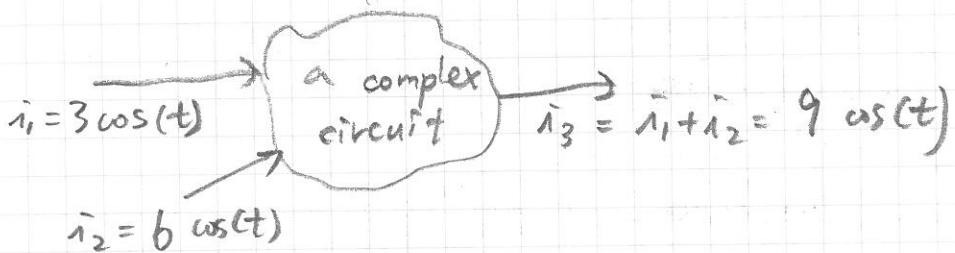
In general, for  $N$  KCL statements, only  $N-1$  of them are independent. Therefore, we need  $N-1$  known values to solve the circuit.



KVL: Kirchhoff's voltage law


The algebraic sum of the branch voltages around any closed path in a network must be zero.

Examples:

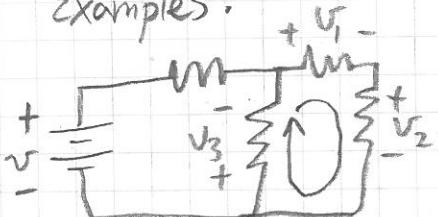

$$\sum_{n=1}^3 V_n = 0$$

並聯

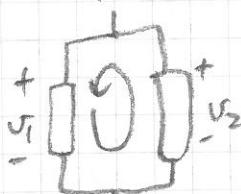


$$0 = V_1 - V_2 \\ \Rightarrow V_1 = V_2$$

串聯



$$0 = -V + V_1 + V_2 \\ \Rightarrow V = V_1 + V_2$$

Example:

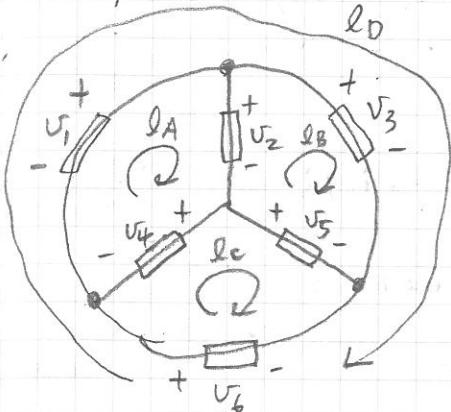

Using KVL

$$\text{loop } l_A: 0 = -V_1 + V_2 + V_4$$

$$l_B: 0 = -V_2 + V_3 - V_5$$


$$l_C: 0 = -V_4 + V_5 - V_6$$

$$l_D: 0 = -V_1 + V_3 - V_6$$

Suppose that  $V_1 = 1$ ,  $V_3 = 3$ ,  $V_2 = 2$

then  $V_4 = -1$ ,  $V_5 = 1$ ,  $V_6 = 2$

Example:

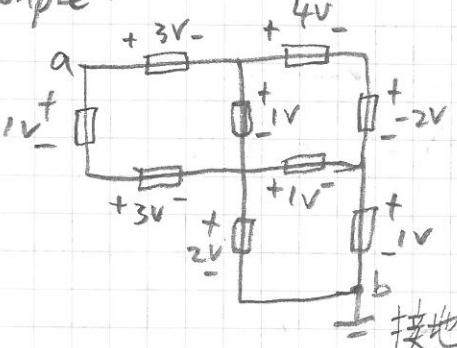


$V_{ab}$  can be determined using KVL  
(which loop(s) would you pick?)

$$V_{ab} = 6 \text{ V.}$$


In general, we model individual elements based on LMD assumptions and we analyze a circuit of elements using KCL and KVL.

★ Two more basic elements and their  $i-v$  characteristics

① Independent voltage source

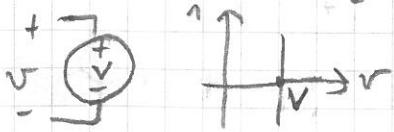

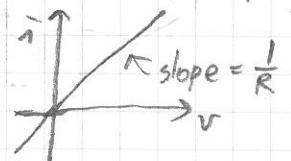for linear resistor it obeys Ohm's law  $R = \frac{V}{I}$



② Independent current source




# \* Basic Method to Analyze A Circuit

four steps


see Page 8

- 1° define branch current and voltage consistently
- 2° apply element laws for each elements  
(e.g., Ohm's law for linear resistors)
- 3° apply KCL and KVL
- 4° jointly solve the equations obtained from 2° and 3°.

Example :

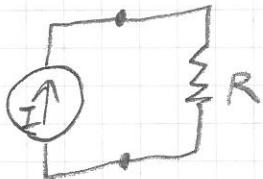

1°

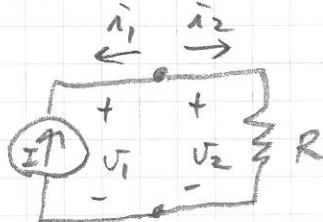

2°

$$i_1 = -I, \quad v_2 = i_2 \cdot R$$

3°

$$\text{KCL} \Rightarrow i_1 + i_2 = 0$$


$$\text{KVL} \Rightarrow -v_1 + v_2 = 0$$

4°  $i_2 = -i_1 = I$

$$v_2 = i_2 R = IR$$

$$v_1 = v_2 = IR *$$

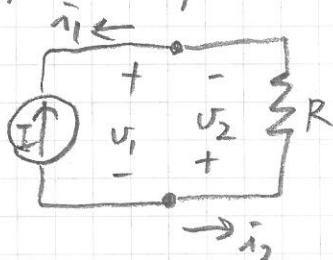if at step 1° we define  $v_2$  inversely, we must




also define  $i_2$  inversely, to be consistent. Applying the basic method you will find

$i_2 = -I$  and  $v_2 = -IR$ . This may seem to be strange. But if we recall that both  $i_2$  and  $v_2$  have a reversed direction, then it makes sense.

Alternatively, we may solve a circuit by considering "Energy conservation".

Example :

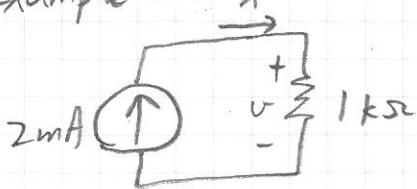

power out from the source :

$$P_{out} = 2 \text{ mA} \times V$$

power into the resistor :

$$P_{in} = i \times V = \frac{V^2}{R}$$


$$= \frac{V^2}{1 \text{ k}\Omega}$$

$$P_{out} = P_{in} \Rightarrow 2 \times 10^{-3} \cdot V = \frac{V^2}{1 \times 10^3}$$

$$\Rightarrow V = 2 \text{ V} *$$

(Example 2.14 in the textbook has a typo saying  $V = 0.5 \text{ V}$ )

## \* Voltage Divider

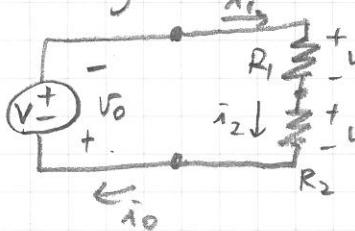

We may analyze it using the basic method:

$$\begin{cases} V_0 = V \\ V_1 = R_1 i_1 \\ V_2 = R_2 i_2 \end{cases} \quad \begin{cases} i_0 = i_1 \\ i_1 = i_2 \end{cases} \quad \begin{cases} V_0 + V_1 + V_2 = 0 \\ KCL \end{cases} \quad KVL$$

$$\Rightarrow V_2 = \frac{R_2}{R_1 + R_2} V$$

Further, from  $i_2 = \frac{V_2}{R_2}$  we see  $i = \frac{1}{R_1 + R_2} V$

in other word,  $V = i \times (R_1 + R_2)$ .



$\Rightarrow$  We may replace  $R_1$  and  $R_2$  by an equivalent resistor  $R' = R_1 + R_2$

and the circuit is equivalent as  $V \xrightarrow{\parallel} R'$

This lead to a general planar linear resistor analysis such as that in Example 2.21 in the textbook.

P16

★ Current Divider

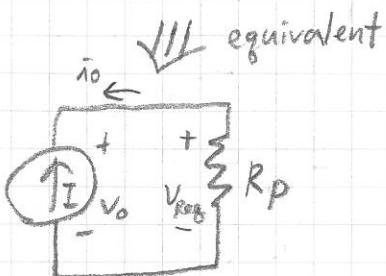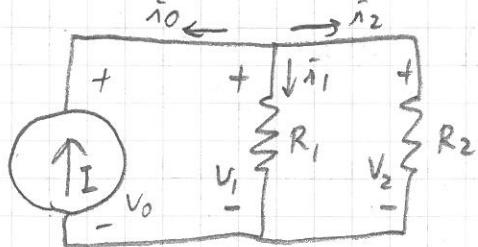

$$V_1 = R_1 \bar{i}_1 = \frac{R_1 R_2}{R_1 + R_2} I$$

"

$$V_0 = \text{Req} \cdot I$$

$$\Rightarrow \boxed{R_P = \frac{R_1 R_2}{R_1 + R_2}}$$

$$\Rightarrow \frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2}$$

Using the "basic method"

$$\begin{cases} \bar{i}_0 = -I \\ V_1 = R_1 \bar{i}_1 \\ V_2 = R_2 \bar{i}_2 \end{cases} \quad \begin{cases} \bar{i}_0 + \bar{i}_1 + \bar{i}_2 = 0 \\ V_0 = V_1 = V_2 \end{cases}$$


$$\Rightarrow \bar{i}_1 + \bar{i}_2 = I$$

$$\begin{aligned} \bar{i}_1 + \bar{i}_2 &= \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_0 R_2 + V_0 R_1}{R_1 R_2} \\ &= \frac{R_1 + R_2}{R_1 R_2} V_0 \end{aligned}$$

$$\Rightarrow V_0 = \frac{R_1 R_2}{R_1 + R_2} \cdot I$$



$$\Rightarrow \boxed{\begin{aligned} \bar{i}_1 &= \frac{V_1}{R_1} = \frac{R_2}{R_1 + R_2} I \\ \bar{i}_2 &= \frac{V_2}{R_2} = \frac{R_1}{R_1 + R_2} I \end{aligned}}$$

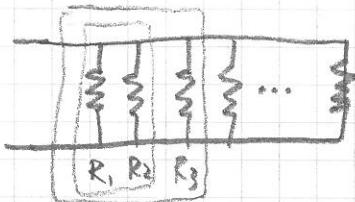In general, for  $N$  resistors connected in parallel,






$$\frac{1}{R_P} = \sum_{n=1}^N \frac{1}{R_n} \quad \text{then}$$

this can be proved by induction.

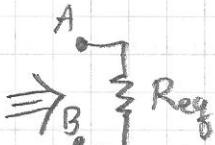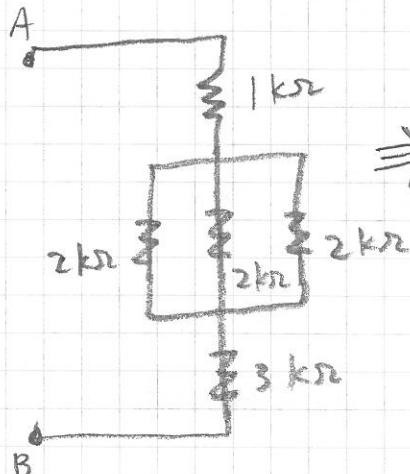
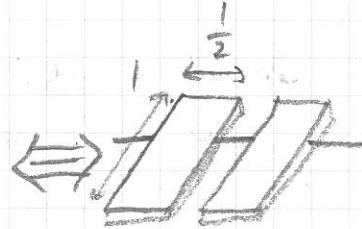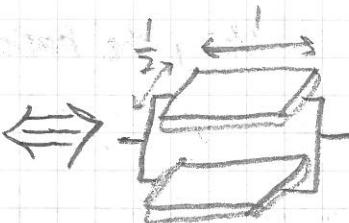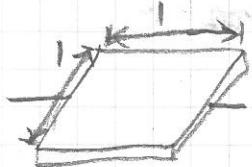
$$\begin{aligned} \text{Req} &= 1 + \frac{1}{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} + 3 \\ &= \frac{14}{3} \Omega \end{aligned}$$




$$\text{let } R_1 = R_{\square}$$

$$R_2 = \frac{2R_{\square} \cdot 2R_{\square}}{2R_{\square} + 2R_{\square}}$$

$$= R_{\square} = R_1$$

$$R_3 = \frac{1}{2}R_{\square} + \frac{1}{2}R_{\square}$$

$$= R_{\square} = R_1$$

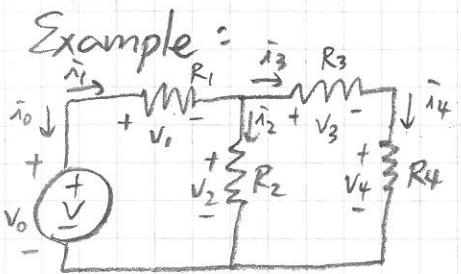

Determine  $V_1, V_2, V_3, V_4$   
and  $i_1, i_2, i_3, i_4$ .


Way ①: we may use the basic method

2° element law ...

3° KCL & KVL ...

4° 解聯立方程式

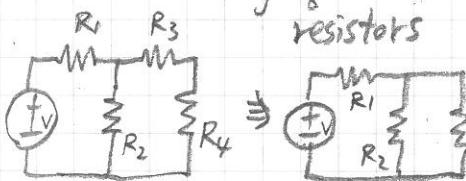Way ②: transformation using equivalent resistors



$$\frac{V_2}{V_0} = \frac{R_2(R_3+R_4)}{R_2+R_3+R_4}$$

$$i_1 = \frac{V_0}{R_1 + \frac{R_2(R_3+R_4)}{R_2+R_3+R_4}}$$

$$i_1 = V_0 / \left( R_1 + \frac{R_2(R_3+R_4)}{R_2+R_3+R_4} \right)$$

$$V_1 = i_1 R_1 = \underline{\hspace{2cm}}$$

$$V_2 = \underline{\hspace{2cm}} \quad (\text{voltage divider})$$


$$i_2 = V_2 / R_2, \quad i_3 = V_2 / (R_3+R_4)$$

$$V_3 = i_3 R_3, \quad V_4 = i_3 R_4$$

give it a try yourself here :

P18 Sometime we may leverage symmetry to greatly reduce the complexity of analysis:

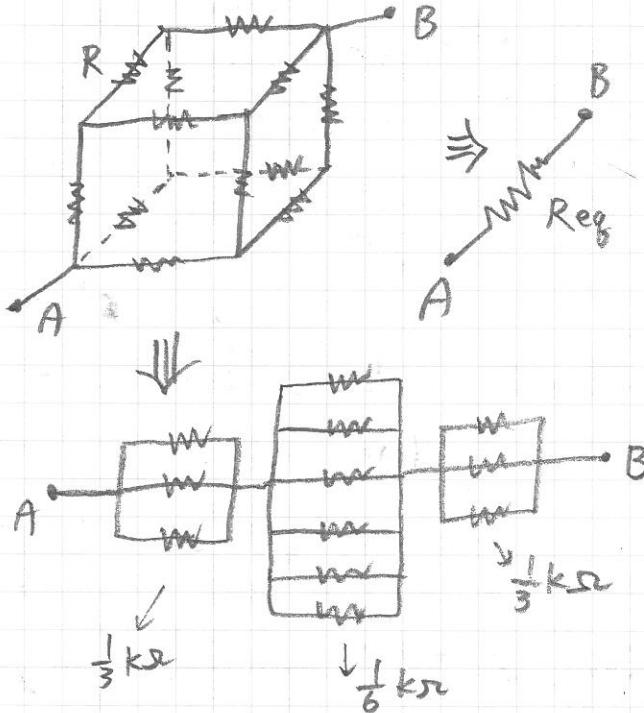Example: assuming all resistors are the same on a cube, with resistance  $R = 1 \text{ k}\Omega$ , determine  $\text{Req}$




(see example 2.24  
in the textbook)


$$\begin{aligned}\text{Req} &= \frac{1}{3} + \frac{1}{6} + \frac{1}{3} \\ &= \frac{5}{6} \text{ k}\Omega\end{aligned} *$$

Often, we still need to apply the basic method after reducing a circuit by using equivalent resistors and symmetry !!


Example:

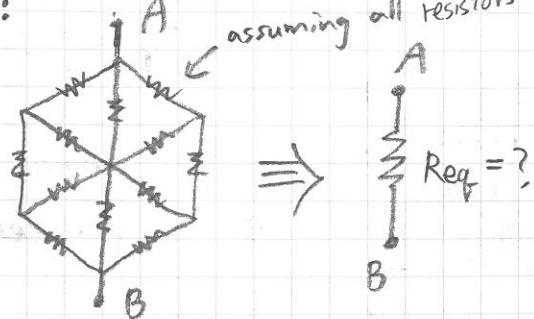

following P18,

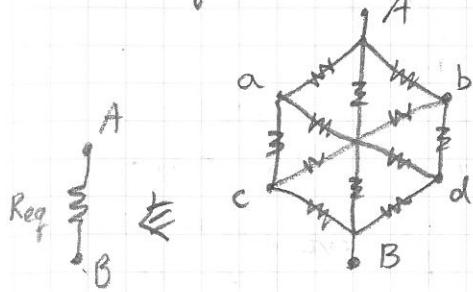

24

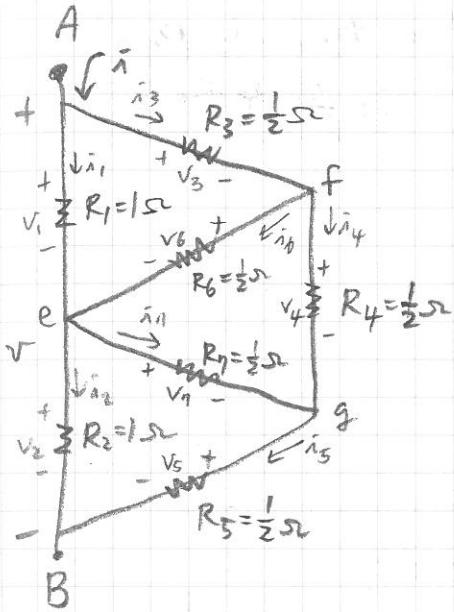

$$KVL: \begin{cases} ⑤ V_1 + V_2 = V_3 + V_4 + V_5 \\ ⑥ V_1 = V_3 + V_6 \\ ⑦ V_2 = V_1 + V_5 \end{cases}$$

$$Req = \frac{V}{i} = \frac{V_1 + V_2}{i_1 + i_3} = \frac{i_1 + i_2}{i_1 + i_3}$$


$$\begin{matrix} ① & \begin{bmatrix} 1 & -1 & 1 & 0 & -1 & 0 & 0 \\ ② & \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 1 & -1 \\ ③ & \begin{bmatrix} 0 & 0 & 1 & 1 & 0 & -1 & 0 \\ ④ & \begin{bmatrix} 0 & 0 & 0 & -1 & 1 & 0 & -1 \\ ⑤ & \begin{bmatrix} 2 & 2 & -1 & -1 & -1 & 0 & 0 \\ ⑥ & \begin{bmatrix} 2 & 0 & -1 & 0 & 0 & -1 & 0 \\ ⑦ & \begin{bmatrix} 0 & 2 & 0 & 0 & -1 & 0 & -1 \end{bmatrix} \end{bmatrix} \end{bmatrix} \end{bmatrix} \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

note: equation ④ is dependent.

使用高斯消去法 可得  $\begin{cases} i_1 = 2i_7 \\ i_2 = 2i_7 \\ i_3 = 3i_7 \end{cases}$

or [www.mathworks.com](http://www.mathworks.com) Matrix Calculator

P19

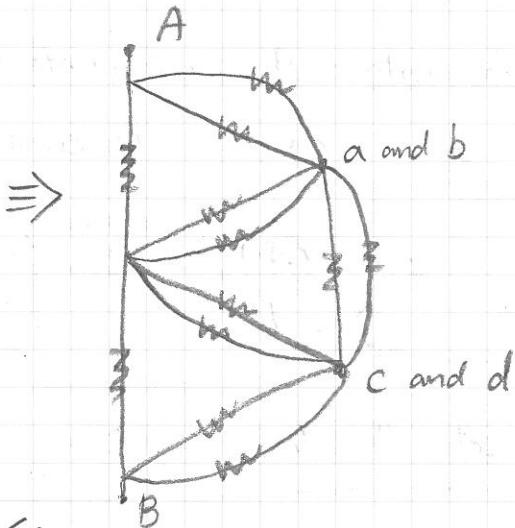

element laws:

$$\begin{cases} V_1 = i_1, V_2 = i_2, V_3 = \frac{1}{2}i_3 \\ V_4 = \frac{1}{2}i_4, V_5 = \frac{1}{2}i_5, V_6 = \frac{1}{2}i_6 \\ V_7 = \frac{1}{2}i_7 \end{cases}$$


$$\begin{aligned} KCL: & ① i = i_1 + i_3 = i_2 + i_5 \quad (\text{node } A \& B) \\ & ② i_1 + i_6 = i_2 + i_7 \quad (\text{node } e) \\ & ③ i_3 = i_6 + i_4 \quad (\text{node } f) \\ & ④ i_5 = i_7 + i_4 \quad (\text{node } g) \end{aligned}$$

therefore, 我們可將所有電壓值代換為電流值, 去解電流的聯立方程式!!)

$$\therefore Req = \frac{i_1 + i_2}{i_1 + i_3} = \frac{2+2}{2+3} = \frac{4}{5} \Omega *$$

Calculation is a necessary part in engineering!

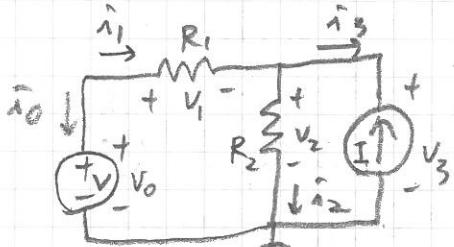P20 Example : A circuit with two independent sources




Determine  $i_2$ .

$$\begin{aligned} \text{element law} & \left\{ \begin{array}{l} V_0 = V \\ V_1 = R_1 i_1 \\ V_2 = R_2 i_2 \\ i_3 = -I \end{array} \right. & \text{KCL} & \left\{ \begin{array}{l} \hat{i}_0 = -i_1 \\ i_1 = i_2 + i_3 \end{array} \right. \\ \text{KVL} & \left\{ \begin{array}{l} V_0 = V_1 + V_2 \\ V_2 = V_3 \end{array} \right. & & \end{aligned}$$

then solve these linear equations (see textbook Pg5).



Exercise:  $V_x = ?$

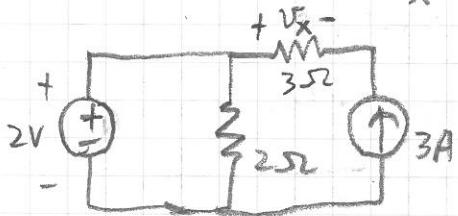

(ans:  $V_x = -9V$ )


$$i_2 = \frac{R_1}{R_1 + R_2} I + \frac{1}{R_1 + R_2} V$$

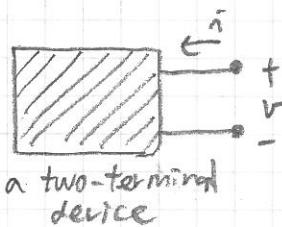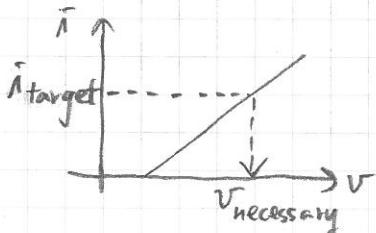\* \* \* The I-V characteristic of a circuit




我們可藉由給定  $v$  量測  $i$   
(or vice versa) 來繪製  
I-V relation.

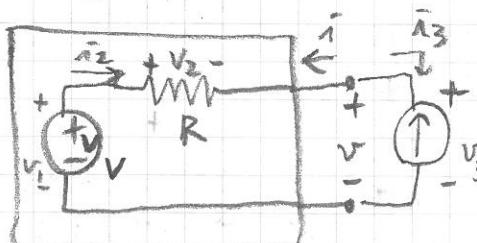If we know the device's internals,  
we may also determine its I-V relation:



using the basic method, we have
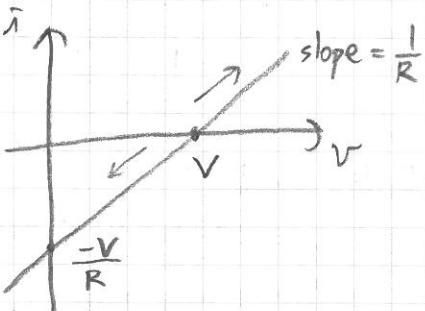
$$V = V + iR \Rightarrow i = \frac{1}{R}V - \frac{V}{R}$$



example usage:  
預測電流流向


$$\left\{ \begin{array}{l} V \geq V \rightarrow i \geq 0 \\ V < V \rightarrow i < 0 \end{array} \right.$$

# \* Circuit Analysis using the Node Method

## Motivation:

Often, the number of nodes in a circuit is much smaller than that of branches. Node method thus involves fewer number of variables, which means it is often easier to solve.

- definition of node voltage:

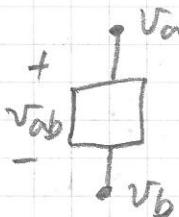

$$V_{ab} = V_a - V_b$$

node voltage

Procedure of the node method:

1° select a reference node (接地,  $v=0$ )


2° assign node variables

3° apply KCL

4° solve equations

5° back-solve the needed branch voltage/current.

Example: find  $V_0 = ?$

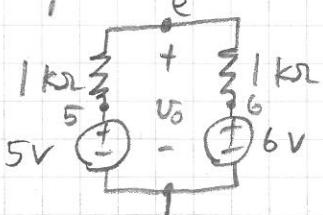

e have

if using the basic method,

$$\begin{aligned} i_1 &= \frac{V_1}{1k\Omega} \\ i_2 &= \frac{V_2}{1k\Omega} \end{aligned}$$

using the node method,

$$\frac{5-e}{1k\Omega} + \frac{6-e}{1k\Omega} = 0$$

$$e = 5.5V \quad V_0 = e - 0 = 5.5V$$


$$\begin{aligned} i_1 + i_2 &= 0 \\ \Rightarrow V_1 + V_2 &= 0 \\ \text{using KVL,} \quad 5 - V_1 + V_2 - 6 &= 0 \\ \Rightarrow V_1 - V_2 &= -1 \end{aligned}$$

$$\begin{cases} V_1 = -0.5 \\ V_2 = 0.5 \end{cases}$$

$$V_0 = 6 - V_2 \quad (\text{KVL})$$

$$= 5.5V$$

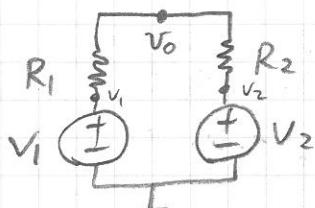P22 Symbolic Computation can give us some insights:



$$\text{KCL: } \frac{V_1 - V_0}{R_1} + \frac{V_2 - V_0}{R_2} = 0$$

$$\Rightarrow R_2(V_1 - V_0) + R_1(V_2 - V_0) = 0$$

$$\Rightarrow V_0 = \frac{1}{R_1 + R_2} (R_2 V_1 + R_1 V_2)$$

$$= \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$


Insights ①  $V_0$  is a linear combination of  $V_1$  and  $V_2$ .

The circuit acts as an adder that gives a weighted sum of  $V_1$  and  $V_2$ .

② if set  $V_2 = 0$ , then  $V_{01} = \frac{R_2}{R_1 + R_2} V_1$ ,

which is equivalent to the result of a voltage divider:

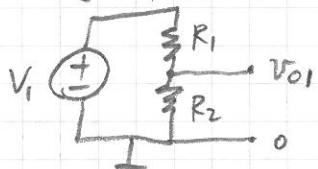i.e., having the same i-V characteristic.



③ similarly, if set  $V_1 = 0$ , then

$V_{02} = \frac{R_1}{R_1 + R_2} V_2$ , equivalent to the


result of a voltage divider:



⇒ from ② and ③, the original circuit can be thought of as a superposition of two voltage dividers, with  $V_0 = V_{01} + V_{02}$ .

Another example:

P23

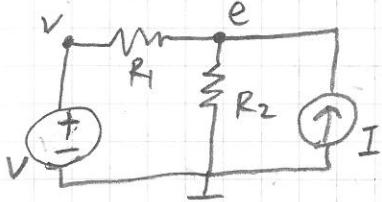




$$KCL: \frac{V-e}{R_1} + \frac{0-e}{R_2} + I = 0$$

$$\Rightarrow R_2(V-e) + R_1(-e) + I R_1 R_2 = 0$$

$$\Rightarrow e = \frac{1}{R_1+R_2} (R_2 V + I R_1 R_2)$$

$$= \frac{R_2}{R_1+R_2} V + \frac{R_1 R_2}{R_1+R_2} I$$

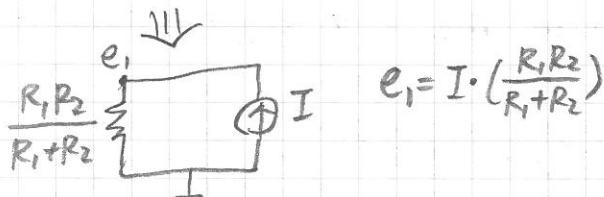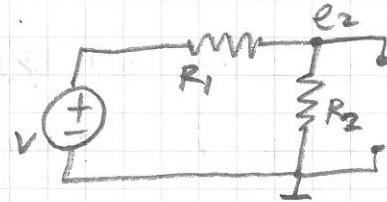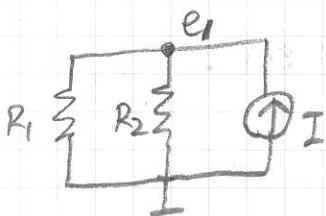Study the case of  $V=0$  and  $I=0$ , respectively, we see that the original circuit can be thought of as a superposition of one current divider and one voltage divider, where  $e = e_1 + e_2$ :



$$e_1 = I \cdot \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$e_2 = \frac{R_2}{R_1 + R_2} V.$$

(Note: set  $V=0$  相當於將 短路 (short circuit))  
 set  $I=0$  相當於將 斷路 (open circuit))

In general, for a linear circuit, we can use the concept of superposition to simplify our analysis, by first considering one independent source at a time and then adding up the result.

P24

Why does the concept of "superposition" make sense in circuit analysis?

- Because ① each independent source contributes to the response of circuit "individually" and the contribution is independent from the contribution of any other independent source, and  
② independent sources are assumed to have no resistance (see P13 of this note).

Why does the concept of "equivalence" make sense in circuit analysis?


- Because as long as the i-v characteristic are identical, from input/output viewpoint of a system, what's inside doesn't matter.

Therefore, we may replace some part of a circuit by its equivalence, solely for the purpose of simplifying our analysis. It is an extremely useful trick in engineering!

For example, we may use 設號產生 to feed an equivalent input to a system, emulating some physical input circuit.

Example of the use of superposition:

find  $V_o = ?$

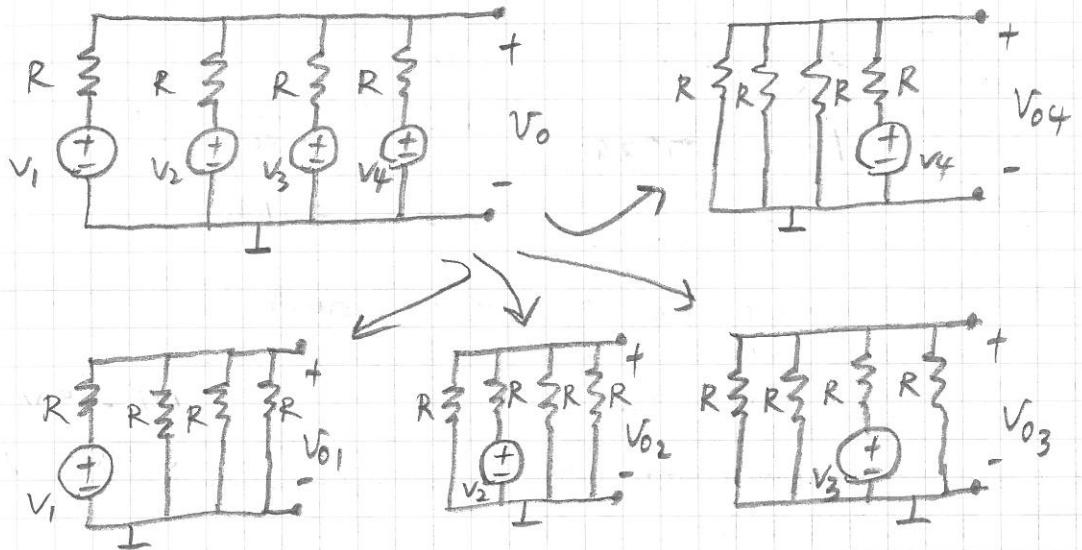


$$V_{o1} = \frac{\frac{1}{3}}{1 + \frac{1}{3}} V_1, \quad V_{o2} = \frac{\frac{1}{3}}{1 + \frac{1}{3}} V_2, \quad V_{o3} = \frac{\frac{1}{3}}{1 + \frac{1}{3}} V_3, \quad V_{o4} = \frac{\frac{1}{3}}{1 + \frac{1}{3}} V_4$$

$$= \frac{1}{4} V_1 \quad = \frac{1}{4} V_2 \quad = \frac{1}{4} V_3 \quad = \frac{1}{4} V_4$$


$$\Rightarrow V_o = V_{o1} + V_{o2} + V_{o3} + V_{o4} = \frac{1}{4}(V_1 + V_2 + V_3 + V_4) *$$

Another example: find  $I = ?$

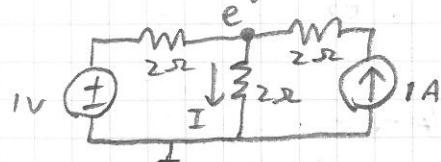

$$e = e_v + e_i = \frac{3}{2}$$


$$I = \frac{e - 0}{2\Omega} = 0.75 A *$$

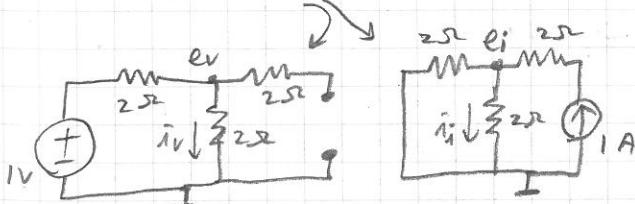

Alternatively, we may compute  $I$  directly:

$$i_v = \frac{1}{4} \quad i_i = \frac{2}{2+2} \times 1 = \frac{1}{2}$$

current divider

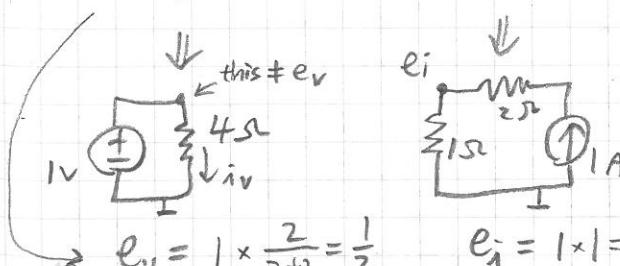


$$\Rightarrow e_v = 1 \times \frac{2}{2+2} = \frac{1}{2}$$

$$e_i = 1 \times 1 = 1$$

$$\Rightarrow I = i_v + i_i$$

$$= \frac{1}{4} + \frac{1}{2} = 0.75 A *$$

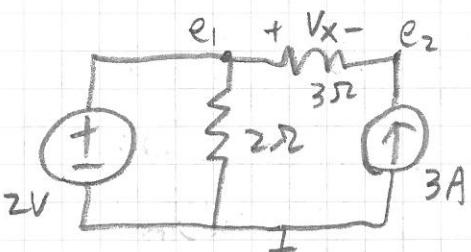P26 Some further of the use of node method : example



find  $v_x = ?$

$$e_1 = 2V$$


$$KCL: \frac{e_1 - e_2}{3\Omega} + 3 = 0$$

$$\Rightarrow e_2 = 11V$$

$$\Rightarrow v_x = e_1 - e_2 = -9V$$

Compare this with the use of basic method  
as we did on P20 of this note ! ( $v_x = -9V$  there)

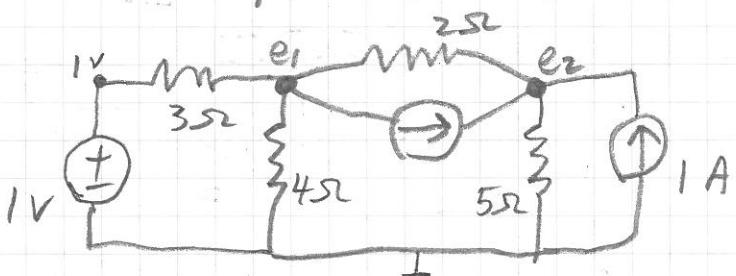Another example : find  $e_1$  and  $e_2$



$$KCL \text{ on } e_1: \frac{e_1 - 1}{3} + \frac{e_1}{4} + \frac{e_1 - e_2}{2} + 2 = 0$$

$$KCL \text{ on } e_2: -2 + \frac{e_2 - e_1}{2} + \frac{e_2}{5} - 1 = 0$$

$$\Rightarrow \begin{cases} 4e_1 - 4 + 3e_1 + 6e_1 - 6e_2 + 24 = 0 \\ -20 + 5e_2 - 5e_1 + 2e_2 - 10 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} 13e_1 - 6e_2 = -20 \\ -5e_1 + 7e_2 = 30 \end{cases}$$

$$\Rightarrow 13e_1 - 6\left(\frac{1}{7}(30 + 5e_1)\right) = -20$$

$$\Rightarrow 91e_1 - 180 - 30e_1 = -140$$

$$\Rightarrow 61e_1 = 40 \Rightarrow e_1 \approx 0.655, e_2 = \frac{1}{6}(13e_1 + 20)$$


$$= \frac{1}{6}(13 \times 0.655 + 20) = 4.75$$

d: ★ Thévenin's Theorem

P27

Goal: Given an arbitrary linear circuit, we would like to know how it would respond to external excitation; in other word, we'd like to know its  $i$ - $V$  characteristic.

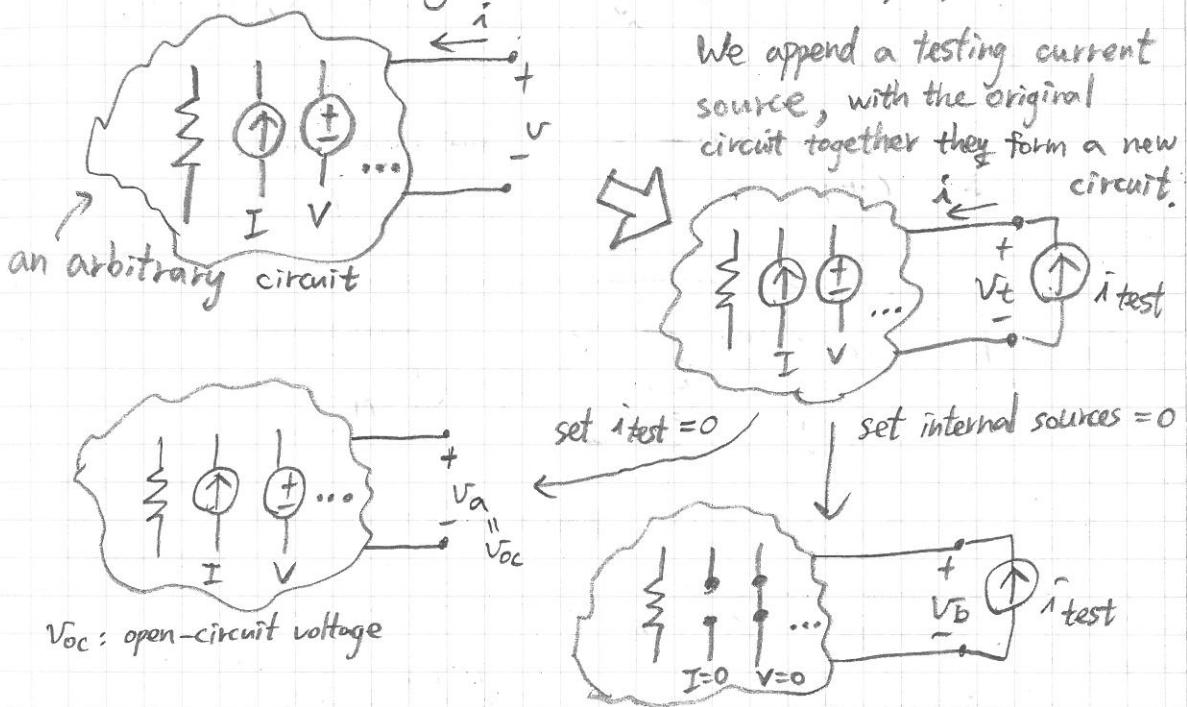
Approach: leverage the concept of superposition!




By superposition,

$$V_t = V_a + V_b$$

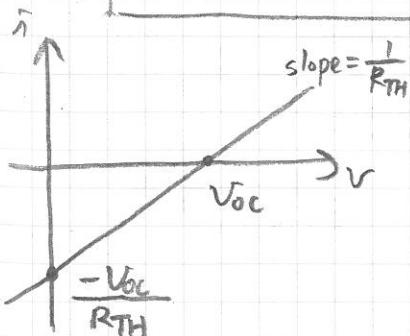
$$\Rightarrow V_t = V_{oc} + i_{test} R_{TH}$$



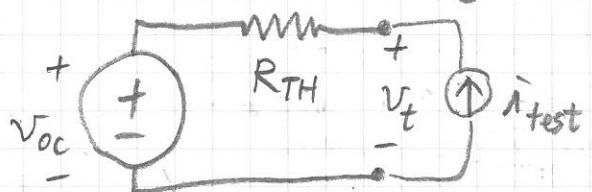⇒ equivalently, this relation describes the following circuit:



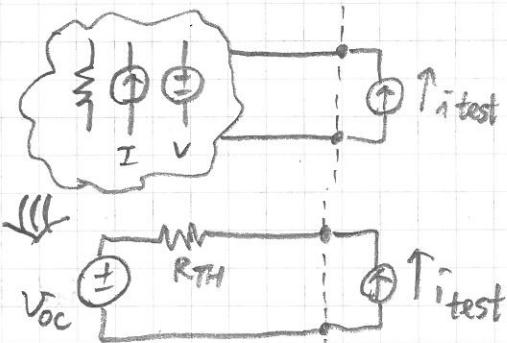P28 Therefore, we have the following equivalence:




linear

In other word, we may reduce an arbitrary circuit to an equivalent circuit of the form:



We name  $V_{TH} = V_{oc}$   
in honor of Thévenin.


Example:

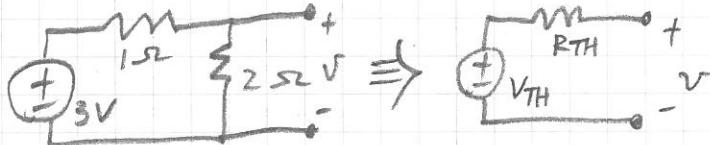

$$V_{TH} = V = 3 \times \frac{2}{1+2} = 2V, R_{TH} = \frac{1.2}{1+2} = \frac{2}{3}\Omega \text{ from } \boxed{\frac{1.2}{\frac{1.2+2.5}{2.5}}} = \frac{2}{3}\Omega$$



Another example: find  $I = ?$

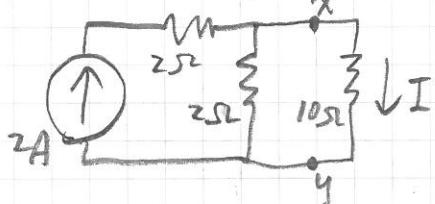


calculating  $V_{TH}$ :




$$V_{TH} = 2A \times 2.5\Omega = 4V$$

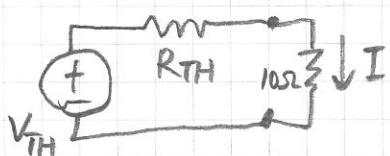We may replace the left side of x-y by an equivalent circuit:



calculating  $R_{TH}$ :

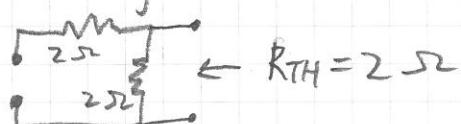


$$\Rightarrow I = \frac{4}{2+10} = \frac{1}{3}A \quad *$$

$$\text{Then } I = \frac{V_{TH}}{R_{TH} + 10\Omega}$$

Exercise : create the Thévenin Equivalent Circuit  
for the following circuit :

P29

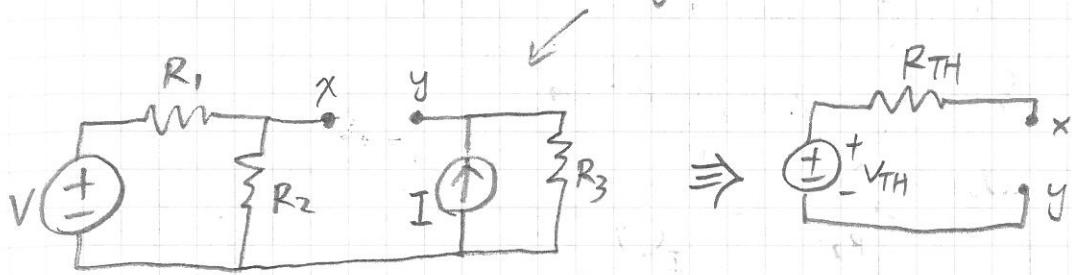

first of all, for  $R_{TH}$ :

$$\text{Circuit diagram: } R_1 \parallel R_2 \parallel R_3 \quad \Rightarrow \quad R_{TH} = (R_1 \parallel R_2) + R_3 \\ = \frac{R_1 R_2}{R_1 + R_2} + R_3$$

then, for  $V_{TH}$ :


approach ①, using superposition

$$\begin{aligned} \text{Circuit diagram: } & R_1 \parallel R_2 \parallel R_3 \quad V_{TH} = V_1 + V_2 \\ & = \frac{R_1}{R_1 + R_2} V + (-IR_3) \\ & = \frac{R_1}{R_1 + R_2} V - IR_3 \quad \times \\ \text{Circuit diagram: } & R_1 \parallel R_2 \parallel R_3 \quad \rightarrow V_2 \\ & \rightarrow V_2 \end{aligned}$$

approach ②, using the node method (Page 21)


$$\begin{aligned} \text{Circuit diagram: } & R_1 \parallel R_2 \parallel R_3 \quad V_{TH} = V_1 - V_2 \\ & = \frac{R_2}{R_1 + R_2} V - IR_3 \quad \times \\ \text{KCL: } & \left\{ \begin{array}{l} \frac{V - V_1}{R_1} + \frac{0 - V_1}{R_2} = 0 \\ I + \frac{0 - V_2}{R_3} = 0 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} V_1 = \frac{R_2}{R_1 + R_2} V \\ V_2 = IR_3 \end{array} \right. \end{aligned}$$

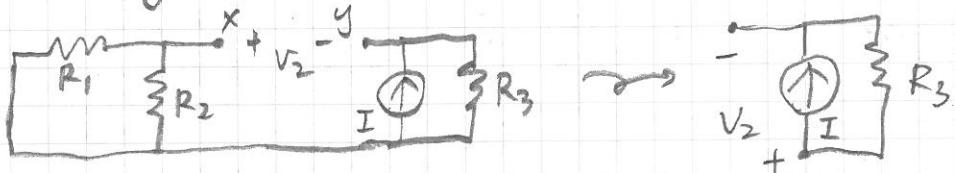P30 In the exercise on the previous page, you might wonder why we can do the following transformation:



Could it be possible that there are some current flowing through  $R_1$  and/or  $R_2$ ?

We can use KCL to figure it out:

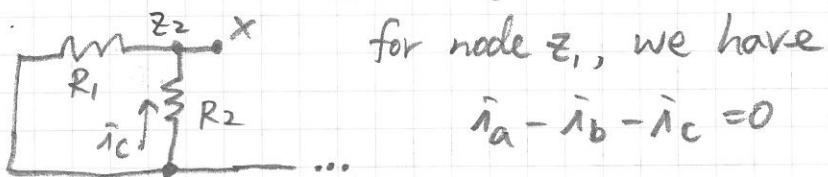

for node  $Z_1$ , we have  
 $i_a - i_b - i_c = 0$


$$i_a - i_b - i_c = 0$$

for node  $Z_2$ , we have


$$i_b + i_c = 0 \quad \text{compare}$$

Therefore, we see that  $i_a = 0$ .

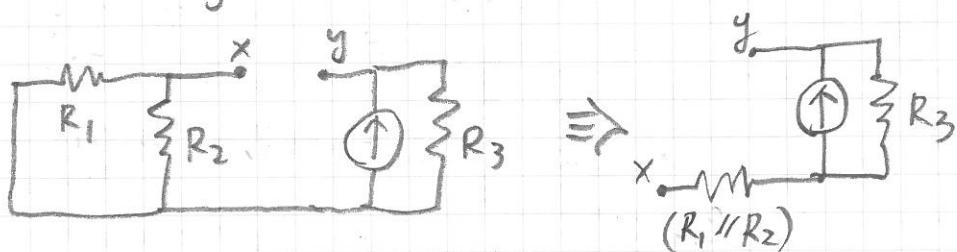
In practice, it is often helpful to think in terms of equivalent resistance, which may make the situation much more obvious:



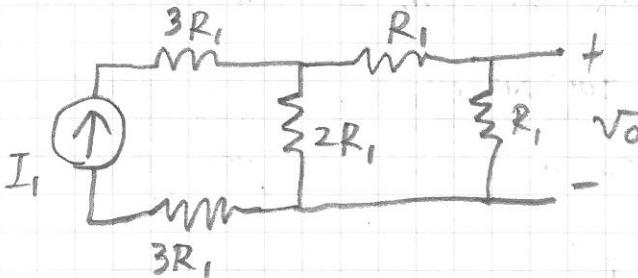Exercise : In the following circuit, determine voltage  $V_o$  :




We may do the following transformation :

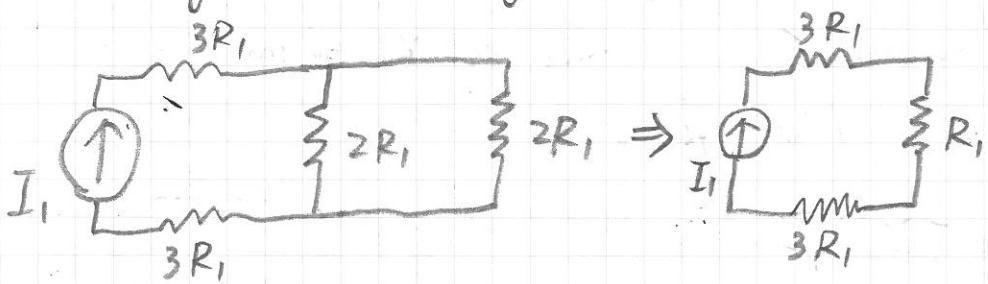

then we might conclude that  $V_o = I_1 \cdot R_1$ ,  
but it is wrong.

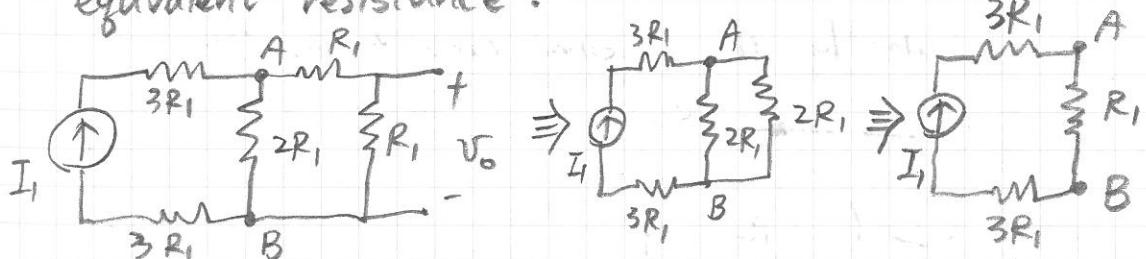To see this, it could be helpful to clearly label the nodes between which you calculate the equivalent resistance :




thus we see that  $V_o$  is not the voltage across A, B,  
and  $V_o = (\text{voltage across } A, B) \times \frac{R_1}{R_1 + R_1}$

$$= (I_1 \cdot R_1) \times \frac{R_1}{R_1 + R_1} = \frac{1}{2} I_1 R_1 \text{ is the correct answer.}$$
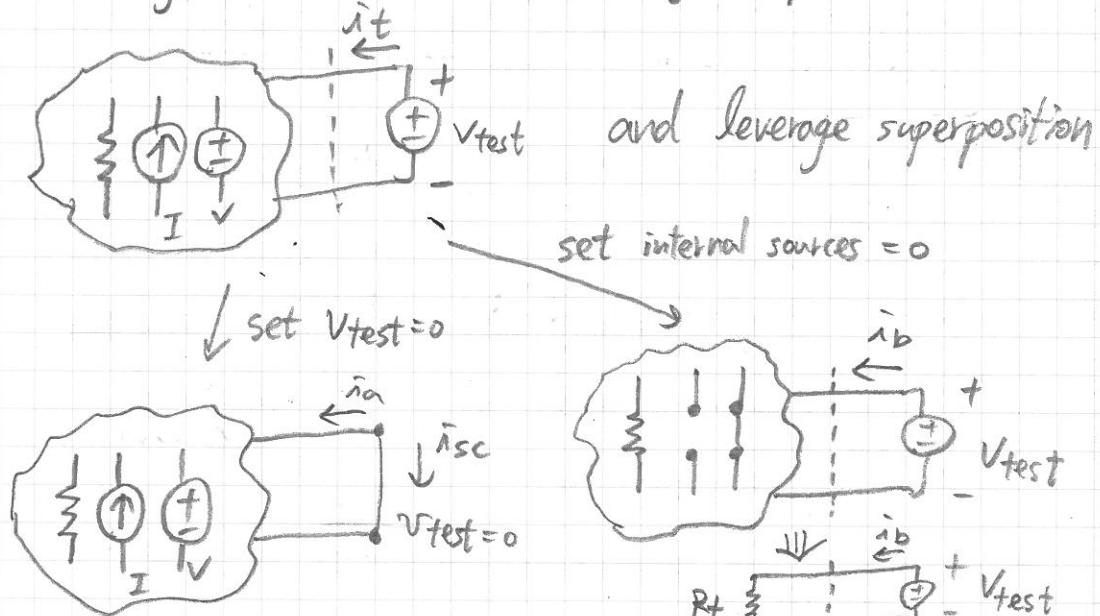
## P32 ★ Norton's Theorem


For the same goal as that of Thévenin's Theorem, here we choose to attach a testing independent voltage source to a possibly complex circuit:



$$\text{then } i_t = i_a + i_b = -i_{\text{sc}} + \frac{V_{\text{test}}}{R_t}$$

$$\Rightarrow i_t + i_{\text{sc}} - \frac{V_{\text{test}}}{R_t} = 0$$

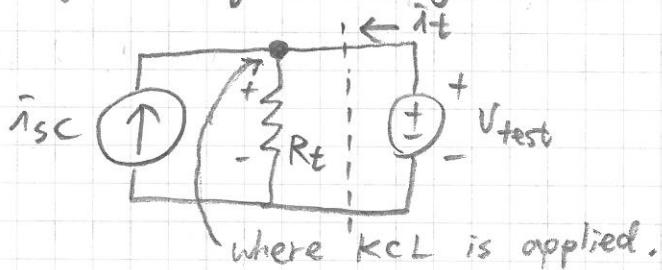Think of above in terms of KCL, then, equivalently the original circuit is like



where KCL is applied.

And  $R_t = R_{\text{TH}}$ , since we applied same procedure of decomposition as we did in Thévenin's Theorem.

Relation between  
Norton's Equivalent Circuit  
and  
Thévenin's Equivalent Circuit:



since  $V_1 = V_2$ , we have

$$i_{sc} \cdot R_t = V_2 = V_{TH}$$

$$\Rightarrow R_t = \frac{V_{TH}}{i_{sc}} = \frac{V_{oc}}{i_{sc}}$$

(recall that  
 $V_{TH} = V_{oc}$   
page 28)

in other word,

$$\text{等效電阻} = \frac{\text{開路電壓}}{\text{短路電流}}$$

Example: find  $V = ?$



approach ①: voltage divider

$$V = 3 \times \frac{2}{1+2} = \frac{2}{3} V$$

approach ②: Thévenin's Theorem

$$V_{TH} = 2V$$

$$V = V_{TH} = 2V$$

approach ③: Norton's Theorem


$$i_{sc} = 3A$$

$$R_t = \frac{1+2}{1+2} = \frac{2}{3} \Omega$$


$$V = 3 \times \frac{2}{3} = \frac{2}{3} V$$

⇒ these three agree in one.


P34 Example : find  $V_{xy} = ?$

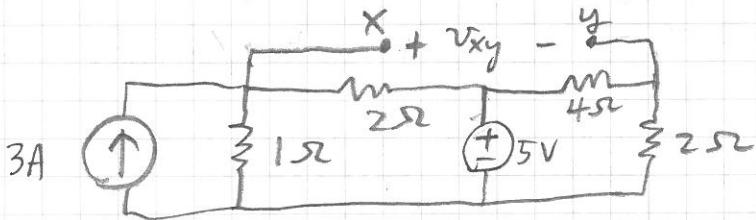

Using Norton's Theorem, we have

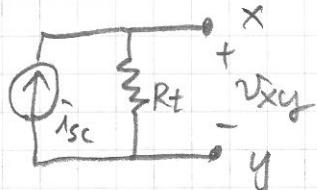


to calculate  $R_t$ :

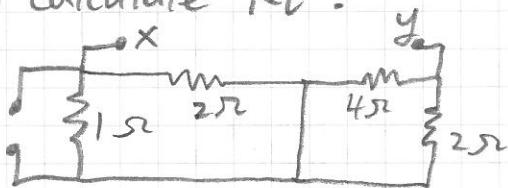

$$R_t = \left( \frac{1}{2} + \frac{1}{4} \right) = 2 \Omega$$

to calculate  $i_{sc}$ :

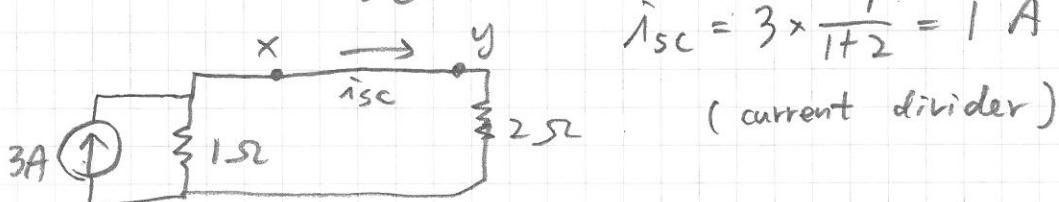


$$i_{sc} = 3 \times \frac{1}{1+2} = 1 \text{ A}$$

(current divider)

$$\text{Therefore } V_{xy} = i_{sc} \times R_t = 2 \text{ V}$$

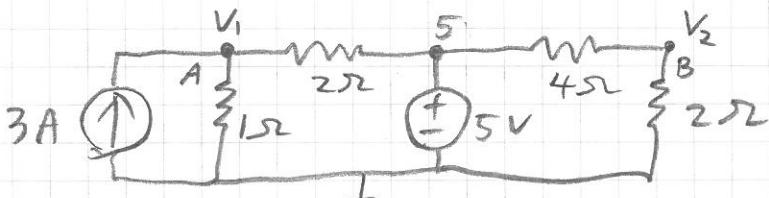Alternatively, we may use the node method:





$$\text{KCL at node A : } 3 + \frac{0 - V_1}{1} + \frac{5 - V_1}{2} = 0 \Rightarrow V_1 = \frac{11}{3}$$

$$\text{KCL at node B : } \frac{5 - V_2}{4} + \frac{0 - V_2}{2} = 0 \Rightarrow V_2 = \frac{5}{3}$$

$$V_{xy} = V_1 - V_2 = \frac{11}{3} - \frac{5}{3} = 2 \text{ V}$$

# \* Nonlinear Devices

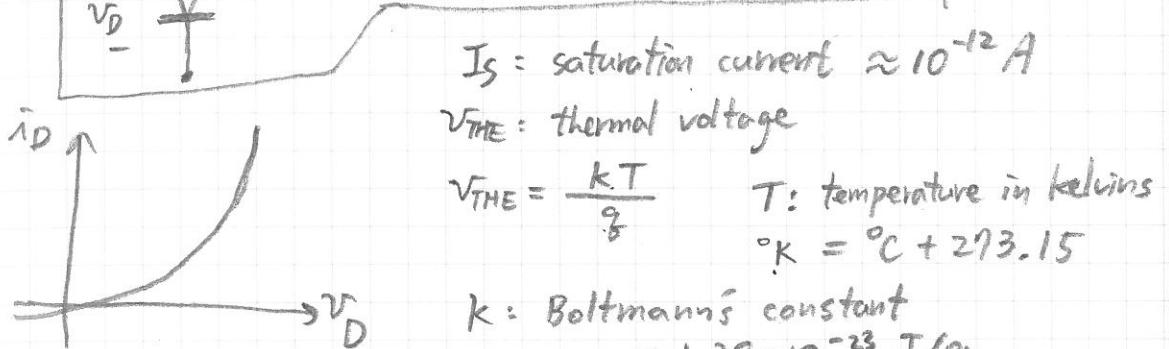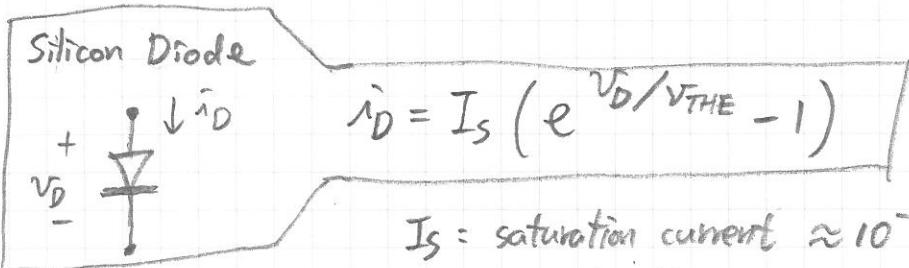

$I_s$ : saturation current  $\approx 10^{-12} \text{ A}$

$V_{THE}$ : thermal voltage


$$V_{THE} = \frac{kT}{q} \quad T: \text{temperature in kelvins}$$

$$^{\circ}\text{K} = ^{\circ}\text{C} + 273.15$$


$$k: \text{Boltmann's constant} \\ = 1.38 \times 10^{-23} \text{ J/}^{\circ}\text{K}$$

$$q: \text{charge of an electron} \\ = 1.602 \times 10^{-19} \text{ C}$$

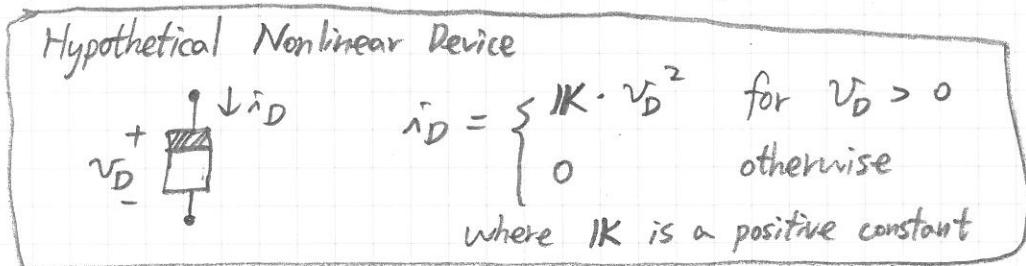Example: CPU 温度  $\hat{s}$ t, see example 16.1 in the textbook.



Example: find  $V_D$  and  $i_D$ :

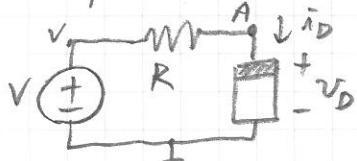

$$\text{KCL at A: } \frac{V - V_D}{R} + (-i_D) = 0$$

Plug in the  $i$ - $v$  relation, we have


$$\begin{cases} \frac{V - V_D}{R} - IK V_D^2 = 0 & \text{for } V_D > 0 \\ \frac{V - V_D}{R} = 0 & \text{otherwise} \end{cases}$$

$$\Rightarrow V_D = \frac{-1 + \sqrt{1 + 4RIKV}}{2RK}$$

$$\text{and } i_D = IK \left( \frac{-1 + \sqrt{1 + 4RIKV}}{2RK} \right)^2 \text{ for } V_D > 0$$

Exercise: find  $i_3 = ?$


(hint: Page 29 and the above example)

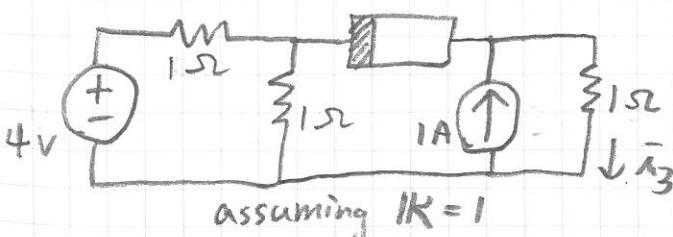

You can do it!

$$\text{Ans: } i_3 = \left( \frac{\sqrt{7} - 1}{3} \right)^2 + 1$$

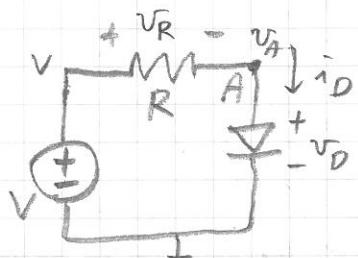P36 Motivation for graphical analyses:  
Consider the following example



KCL at node A:

$$\frac{v_A - v}{R} + I_s(e^{\frac{v_D}{V_{THE}}} - 1) = 0$$

$$\Rightarrow \frac{v_D - v}{R} + I_s(e^{\frac{v_D}{V_{THE}}} - 1) = 0$$

Solving for  $v_D$  is like solving for

$x$  for  $ax + be^x + c = 0$  for some constants  
 $a, b$ , and  $c$ .

→ May be solved by trial-and-error

→ little insight, however.

What if we want to know the impact of increasing/decreasing  $V$  to the value of  $v_D$ ?

And, how would  $v_D$  change with the change of  $R$ ? These are critical questions to ask when designing a electronic circuit.

Now, graphical analyses can be very helpful in this aspect!

For concreteness, suppose  $V = 3V$   
 $R = 500\ \Omega$


in the example.

$V_{THE} = 0.025\ V$  in room temperature

We can rearrange the KCL equation  
 to give two equations for  $i_D$ :



$$\begin{cases} i_D = I_s (e^{v_D/v_{THE}} - 1) = 10^{-12}(e^{v_D/0.025} - 1) \\ i_D = \frac{V - v_D}{R} = -\frac{1}{R}v_D + 0.006 \quad (\text{unit: A}) \end{cases}$$

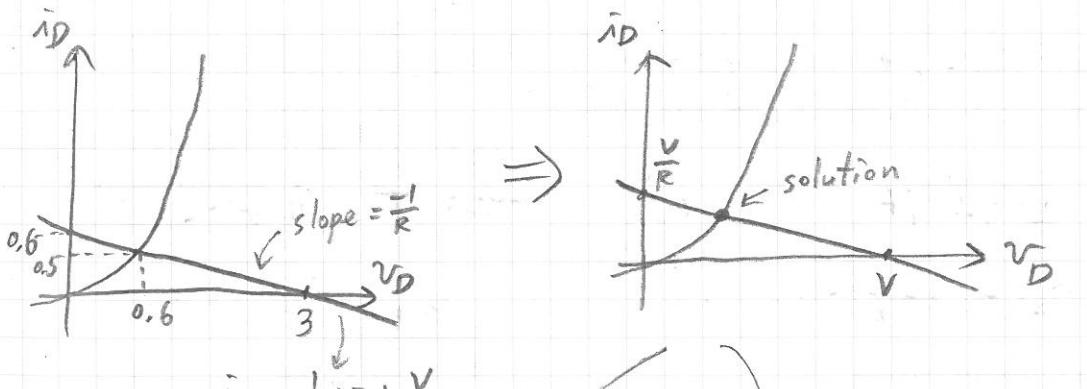then graphically speaking, the solution  
 of  $i_D$  and  $v_D$  lies at the intersection point  
 of the two curves on a  $v_D$ - $i_D$  plot:



if  $R$  changes

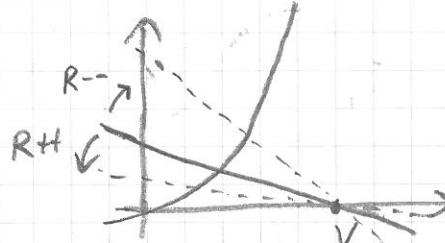
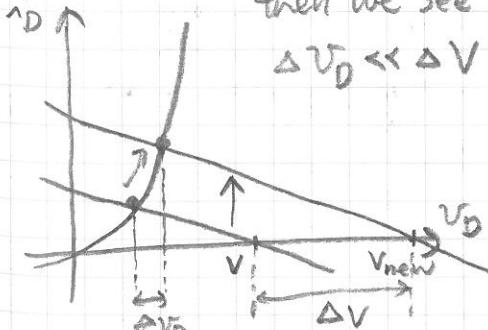
if  $V$  increases  
 then we see  
 $\Delta v_D \ll \Delta V$



which give much insight  
 in how the circuit behaves!
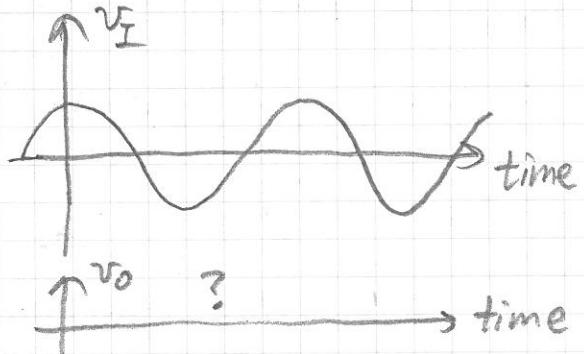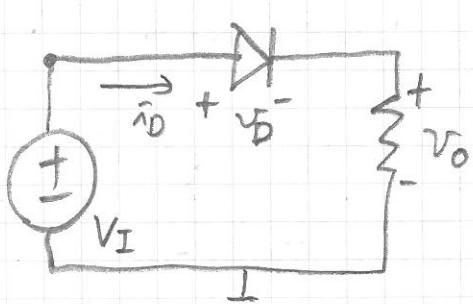
# P38 Another example (half-wave voltage rectifier)

In the following circuit, given a time-varying voltage source  $V_I$ , what will be the output voltage  $V_O$  across a resistor?




$$\text{from KVL, } V_I - V_D - V_O = 0$$




$$\Rightarrow V_O = V_I - V_D$$

from KCL, element law, and the  $i-v$  characteristic of the diode:
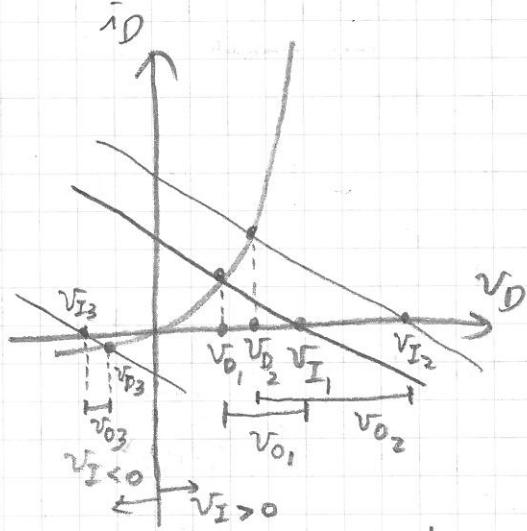
$$\begin{cases} i_D = I_s (e^{V_D/V_{THE}} - 1) \\ i_D = \frac{V_I - V_D}{R} \end{cases}$$



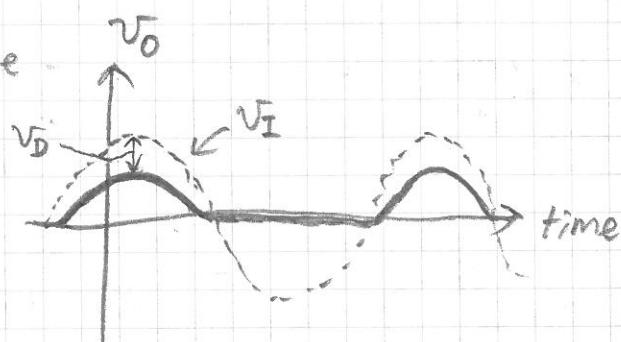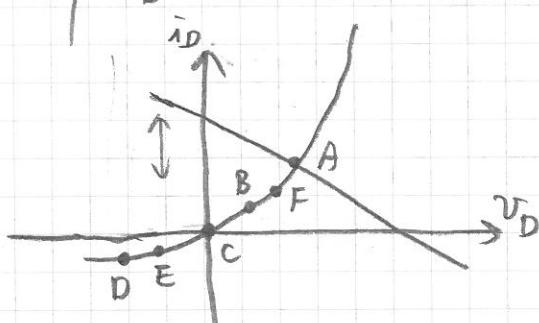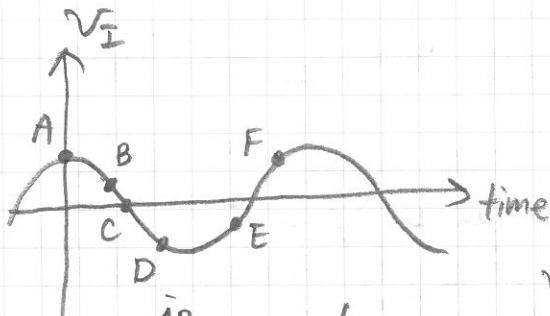
we see  $V_{O_3} \approx 0$  when  $V_D < 0$



Besides the graphical analysis,


in some occasion we may simplify our analysis of a nonlinear circuit by considering an approximated version of the  $i-v$  characteristic of a given nonlinear element.

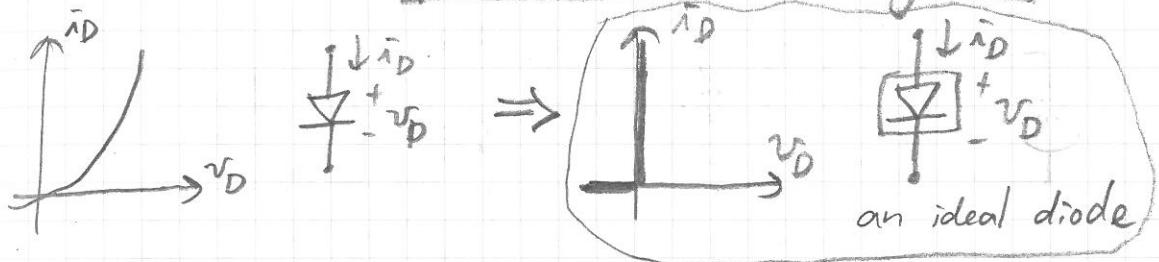This is called the piecewise linear analysis.




For an ideal diode, depending on the actual voltage (or the actual current direction), we may replace the diode by either a short circuit or an open circuit.

Example:

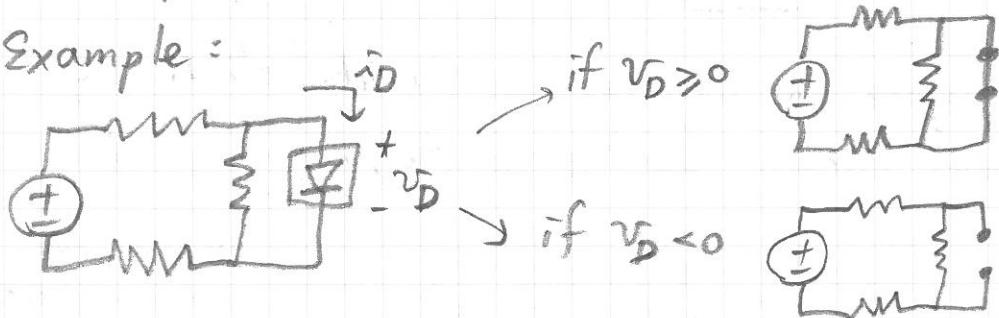


(Note: in class I conditioned on the direction of the current flowing through the diode, but perhaps it makes more sense to condition on  $v_D$ . Either way, we follow the associated variable convention (see page 8 of this note).)

P40 Example :

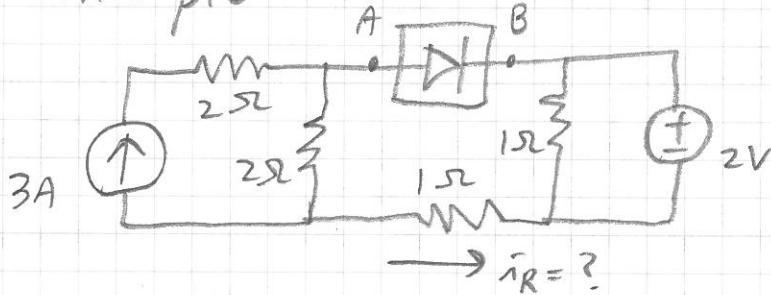

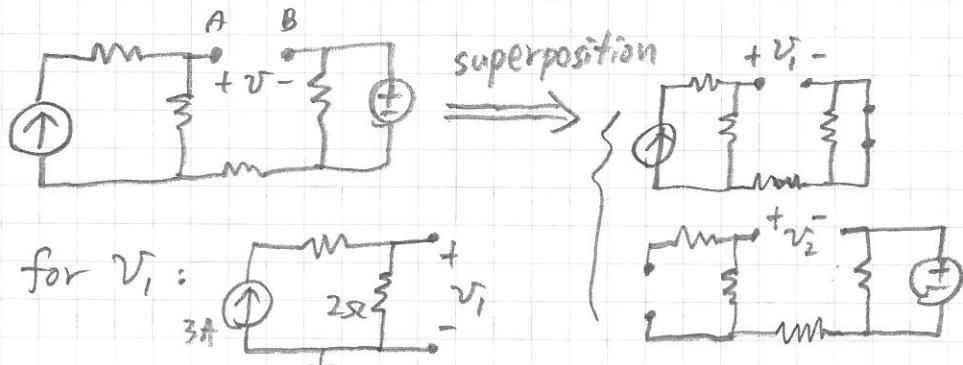
We first find the voltage across A and B.



$$V_1 = 3A \times 2\Omega = 6V$$

$$\text{for } V_2 : \quad \begin{array}{c} + \\ \text{---} \\ - \\ | \\ 2V \end{array} \quad V_2 = -2V \quad \rightarrow V = V_1 + V_2 = 6 - 2 = 4V$$

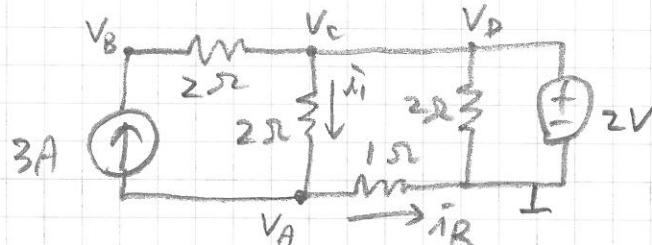therefore we may replace the ideal diode by a short circuit, leading to the following equivalence:



in class we used superposition; here, let's try using the node method!

$$V_C = V_D = 2$$

$$i_1 = 3 + i_R$$

$$\Rightarrow \frac{2 - V_A}{2} = 3 + \frac{V_A - 0}{1}$$


$$2 - V_A = 6 + 2V_A$$

$$\Rightarrow V_A = -\frac{4}{3}$$

$$\Rightarrow i_R = \frac{V_A - 0}{1} = \frac{-4}{3} A$$


Some exercise problems since P32:

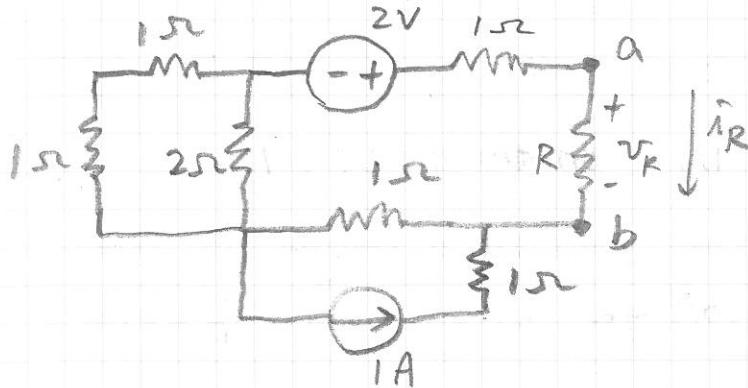- A. Use Norton's Theorem to find  $i_R$  and  $v_K$  for ①  $R=2$  and ②  $R=4$




- B. Following A, rather than using Norton's Theorem, directly apply superposition to find  $i_R$  for  $R=2$ .

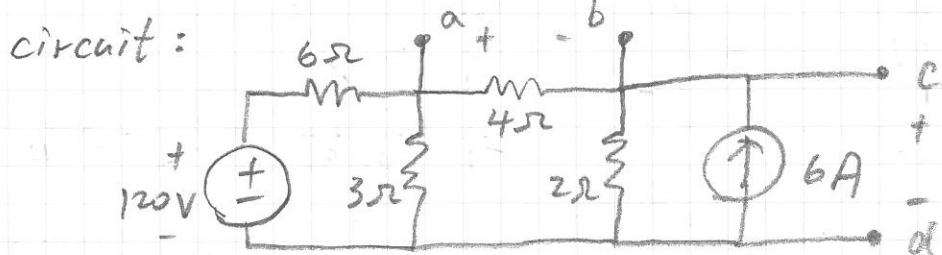- C. Determine the Norton equivalent at terminals a,b and at terminals c,d, for the following circuit:



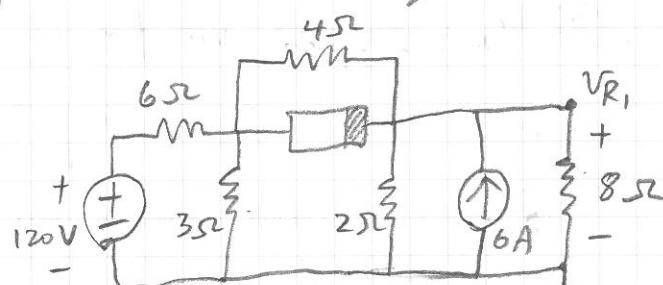- D. For the following nonlinear circuit, determine  $v_{R_1}$ .

$$i_D = \begin{cases} 2 \cdot V_D^2 & \text{for } V_D > 0 \\ 10 & \text{otherwise} \end{cases}$$




(hint: compare this with that in C.)

P42 E. For the following nonlinear circuit, with some initial analysis of its  $i_D - v_D$  relation at hand, try to answer three questions:

① if for some need we changed the input voltage  $v_I$ , so that  $v_I > 1$ , would that lead to a change to the output voltage  $v_O > 0.4$  or  $v_O < 0.4$ ?

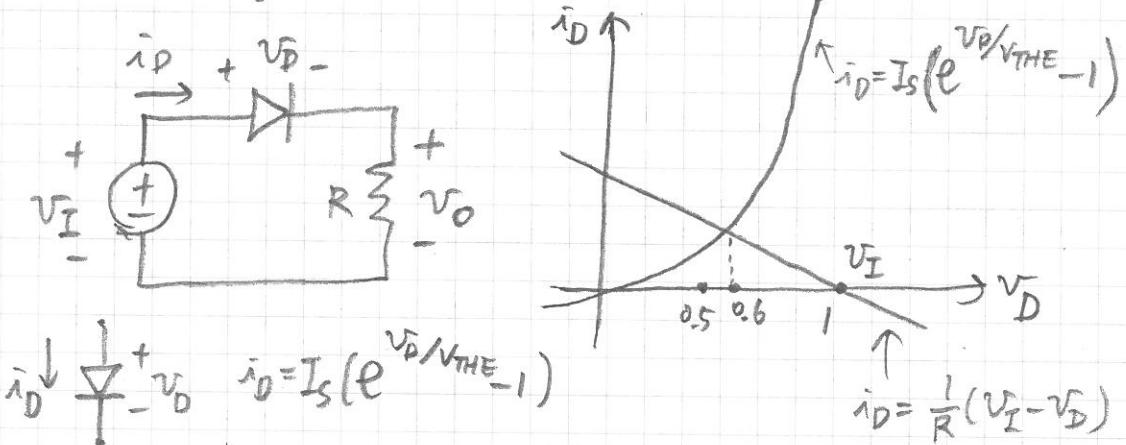② Now, suppose we operate the circuit at region  $v_I \gg 1$ . What can we say about  $v_O$ ?



③ Now, suppose we fix  $v_I$  but replace the linear resistor by a very heavy load, such that  $R \gg 1$ . What would  $i_D$  become?

Answers to Problems A, B, C, D:

A. ①  $i_R = \frac{1}{5}A$ ,  $v_R = \frac{2}{5}V$  ②  $i_R = \frac{1}{7}A$ ,  $v_R = \frac{4}{7}V$  B. same as A.


C.  $R_{tab} = 2\Omega$ ,  $I_{scab} = 7A$   
 $R_{tcd} = \frac{3}{2}\Omega$ ,  $I_{scd} = \frac{38}{3}A$

D. 16 V \*
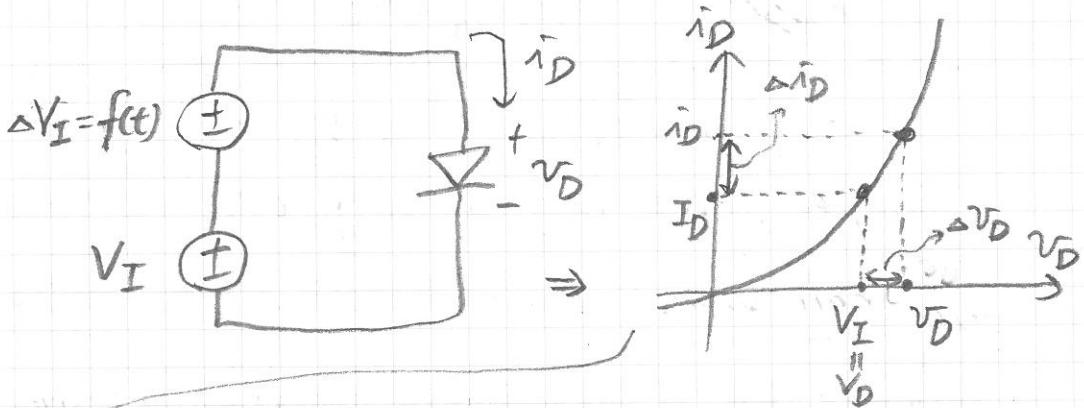
# ★ Small-Signal Analysis for Nonlinear Devices P43

- In many sensor applications and most audio amplifiers, the input voltage/current to a circuit often consists of two parts:


- { ① a time-invariant source (large signal)
- ② a time-varying source (small signal)



The large signal is used to determine the region of operation (i.e., which part of the  $i_D - V_D$  curve), and the small signal is the "real" input (e.g., those induced by human voice, as in the case of a microphone).

$$\begin{aligned}V_D &= V_I + \Delta V_D \\&\quad \begin{matrix} \uparrow & \uparrow \\ \text{large} & \text{small signal} \end{matrix} \\i_D &= I_D + \Delta i_D\end{aligned}$$

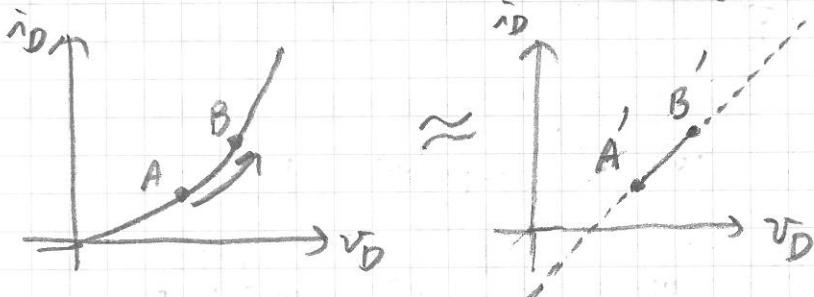P44 as we will see, moving along a small distance on "the  $i_D$ - $v_D$  curve" can be approximated as moving along a small distance on "a straight line"




Therefore, we may simplify our analysis of small signal by considering the signal's response on a nonlinear device as if it is the response on a linear device (resistor).


Review P13, where we've shown that the  $i$ - $v$  characteristic of a resistor on the  $i$ - $v$  plot is a straight line; further, the slope of the line is equal to the reciprocal of the resistance ( $R$ ) of the resistor.

Now, a question is : how do we determine the resistance of that linear device ?

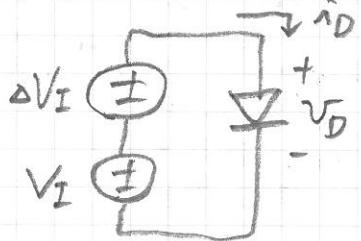Let  $r_d$  be the resistance of the linear device. Using small-signal analysis, we essentially transform the original circuit



into an approximately equivalence:

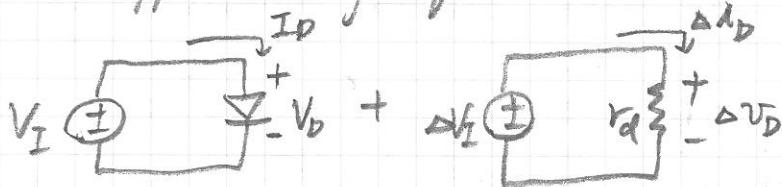


$$\text{where } i_D = I_D + \Delta i_D$$

$$\frac{V_{THE}}{I_D}$$

Now, let's see how to determine  $r_d$ !

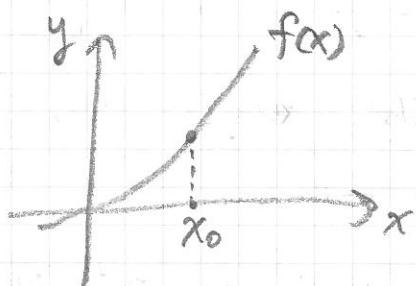We use Taylor's Theorem, which provides a way to approximate a curve near a certain point  $x = x_0$ :



$$\begin{aligned} y &= f(x) = f(x_0) \Big|_{x=x_0} + f'(x) \Big|_{x=x_0} (x-x_0) \\ &\quad + \frac{1}{2!} f''(x) \Big|_{x=x_0} (x-x_0)^2 + \frac{1}{3!} f'''(x) \Big|_{x=x_0} (x-x_0)^3 + \dots \end{aligned}$$

P46 in our case of a nonlinear diode,  
recall that

$$i_D = I_s \left( e^{\frac{v_D}{V_{THE}}} - 1 \right) = f(v_D)$$

we define it

$$\Rightarrow i_D \underset{v_D \text{ near } V_D}{=} f(v_D) \Big|_{v_D=V_D} + f'(v_D) \Big|_{v_D=V_D} (v_D - V_D)$$

$$+ \frac{1}{2!} f''(v_D) \Big|_{v_D=V_D} (v_D - V_D)^2$$

$$+ \frac{1}{3!} f'''(v_D) \Big|_{v_D=V_D} (v_D - V_D)^3 + \dots$$

$$= f(v_D) \Big|_{v_D=V_D} + (v_D - V_D) \left( f'(v_D) \Big|_{v_D=V_D} \right)$$

we choose to  
ignore these terms

$$\left. \begin{array}{l} + \frac{1}{2!} f''(v_D) \Big|_{v_D=V_D} (v_D - V_D) \\ + \frac{1}{3!} f'''(v_D) \Big|_{v_D=V_D} (v_D - V_D)^2 \\ + \dots \end{array} \right\}$$

using the chain rule, we get  $f'(v_D) = \frac{I_s}{V_{THE}} e^{\frac{v_D}{V_{THE}}}$

$$\Rightarrow i_D \underset{v_D \text{ near } V_D}{\approx} \underbrace{f(v_D) \Big|_{v_D=V_D}}_{\sim} + \underbrace{(v_D - V_D) \cdot \frac{I_s}{V_{THE}} e^{\frac{v_D}{V_{THE}}}}_{\sim} \Big|_{v_D=V_D}$$

$$= \underbrace{I_s \left( e^{\frac{v_D}{V_{THE}}} - 1 \right)}_{\sim} + \underbrace{\Delta v_D \cdot \frac{I_s}{V_{THE}} e^{\frac{v_D}{V_{THE}}}}$$

since we know that

$$e^{\frac{V_D}{V_{THE}}} \gg 1$$

so we can think of  $e^{\frac{V_D}{V_{THE}}} \approx e^{\frac{V_D}{V_{THE}}} - 1$

With that, we may rewrite the equation as

$$\frac{i_D}{v_D \text{ near } V_D} = I_S (e^{\frac{V_D}{V_{THE}}} - 1) + \Delta v_D \frac{I_S}{V_{THE}} (e^{\frac{V_D}{V_{THE}}} - 1)$$

Now, by observation we see  $I_S (e^{\frac{V_D}{V_{THE}}} - 1) = I_D$

$$\text{Thus, } \frac{i_D}{v_D \text{ near } V_D} = I_D + \frac{\Delta v_D}{V_{THE}} I_D$$

Compare to  $i_D = I_D + \Delta i_D$ , we have  $\Delta i_D = \underbrace{\frac{\Delta v_D}{V_{THE}} I_D}_{-V_D}$

Think in terms of relation of  $\Delta i_D$  and  $\Delta v_D$   
and we may choose to define

$$r_d = \frac{V_{THE}}{I_D}$$

\*\*

In the hindsight, we may generalize our result by saying that for an arbitrary nonlinear element, we have


$$r_d = \frac{1}{f'(v_D)} \Big|_{v_D=v_D} = \frac{1}{\frac{df(v_D)}{dv_D}} \Big|_{v_D=v_D}$$

\*\* (finally!)

P48

Example :

find  $i_D = ?$

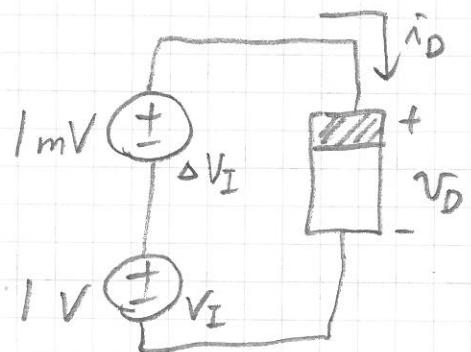

recall that for  $\square$  (P35)

$$i_D = K \cdot V_D^2 \text{ for } V_D > 0$$

and here we suppose

$$K = 1 \text{ mA/V}^2$$

Ans:

$$\left. \begin{array}{l} i_D \\ \downarrow \\ \text{circuit diagram} \end{array} \right\} \quad V_{D_1} = 1 \quad (\text{KVL})$$

$$\left. \begin{array}{l} 1 \text{ V} \\ \downarrow \\ \text{circuit diagram} \end{array} \right\} \Rightarrow i_{D_1} = K \cdot V_{D_1}^2 = 1 \text{ mA}$$

$$V_{D_2} = 1 \text{ mV} \quad (\text{KVL})$$

$$\left. \begin{array}{l} 1 \text{ mV} \\ \downarrow \\ \text{circuit diagram} \end{array} \right\} \quad r_d = \frac{1}{f(V_D)|_{V_D=V_D}} = \frac{1}{2 \cdot K \cdot V_D|_{V_D=1 \text{ V}}} \\ = 500 \Omega$$

$$\Rightarrow i_{D_2} = \frac{V_{D_2}}{r_d} = 2 \mu\text{A}$$

$$\Rightarrow i_D = i_{D_1} + i_{D_2} = 1.002 \text{ mA}$$

\*

## \* The digital abstraction

So far, we've been studying analog signals like voltage and current, and we focus on how these signals, being transformed by a circuit, will impact the behavior of a certain element in a circuit. The impact manifests itself in terms of analog signals on the element, and we also called it the "response" of the element with respect to the analog signals from a voltage source  or a current source .


Now, how does an analog signal relate to the "digital world", the world built using some meaningful combinations of 0s and 1s?

The digital abstraction serves this purpose. It specifies a transformation that interprets the analog signals into a series of binary digits, the so-called "digital signals."


P50

Review Section 1.8 in the textbook.

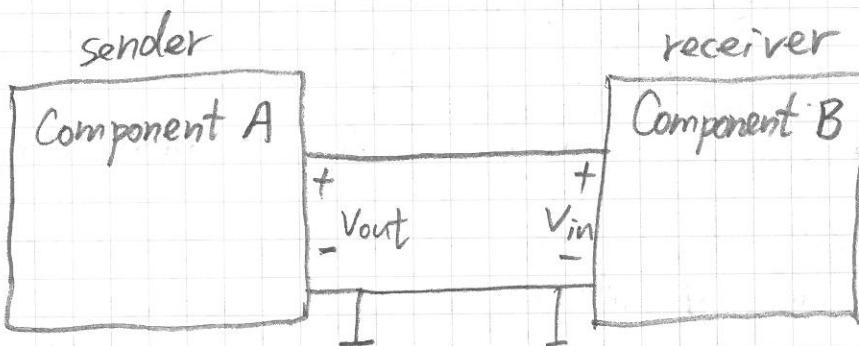- Digital signals are "interpretations" of analog signals, so that they can be understood and be used by a digital system (such as a computer).
- Between physical components in a system, it is still analog signals that are transferred.
- How to transform digital signals into analog ones?




Our first attempt :

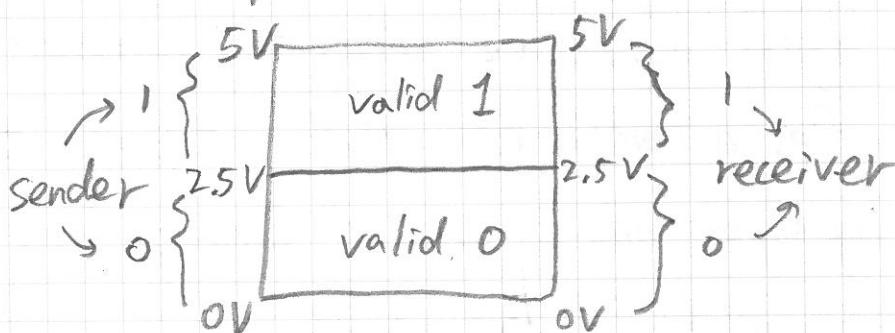


A serious problem :

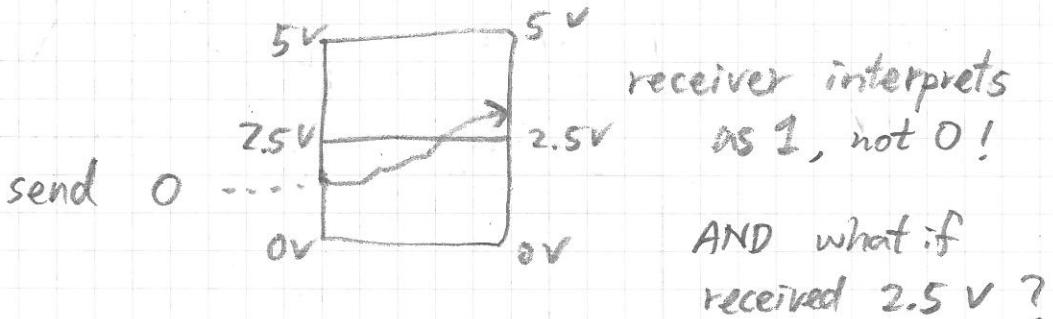there could be noise / interference  
during signal transmissions



An improved design :

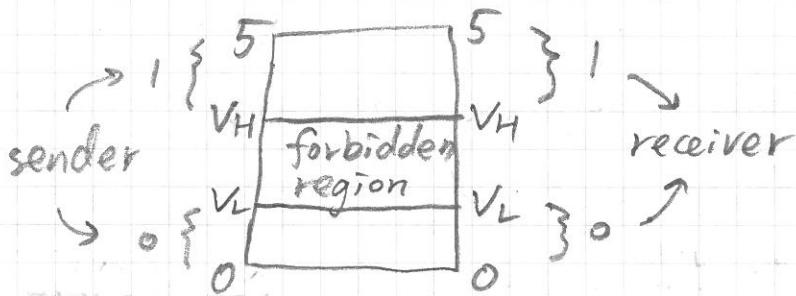

$V_H$  and  $V_L$  are high / low voltage thresholds.


A further question :

how to quantify the immunity  
to noise ?

and if we can do that, this can serve  
as a contract, and accordingly it would  
ensure device manufacturers to meet consumers'  
need, and components can be connected  
to form a system.

P52

## A better design :

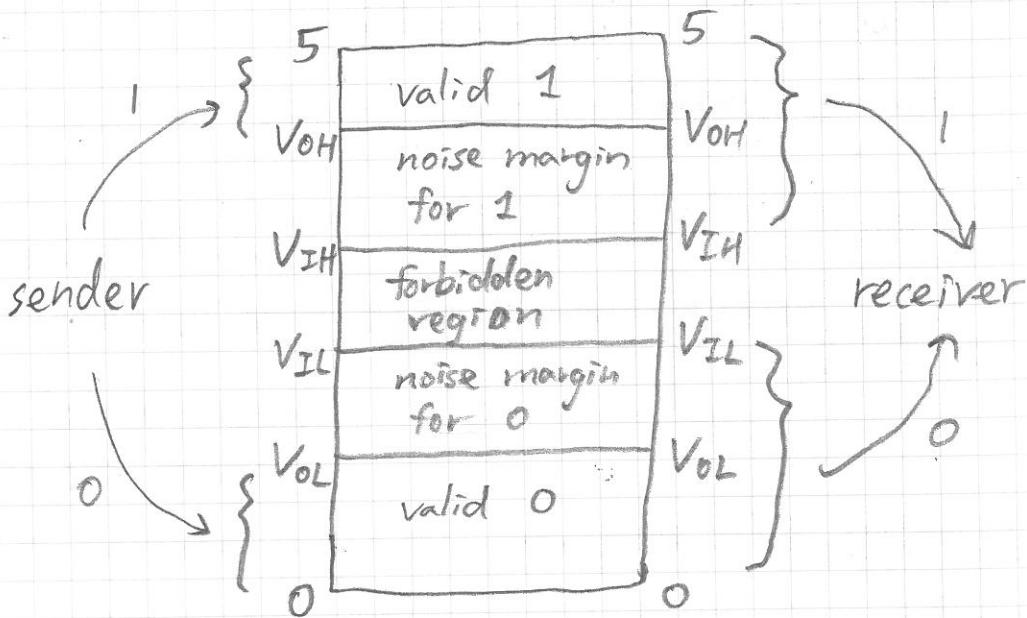

### - The static discipline (principle) —

A device must interpret correctly voltage inputs falling within the  $V_{IL}$  or  $V_{IH}$  threshold; with a valid input, the device must produce a valid voltage output that falls within the  $V_{OL}$  or  $V_{OH}$  threshold.

~ A specification of digital devices.

Sections 5.2, 5.3, 5.6 in the textbook  
are very good learning materials.

Be sure to study them yourselves.

We will briefly cover some of them  
at some appropriate opportunity in this course.


Logic gates (<sup>i.e.</sup> combinational gates):



AND gate




OR gate

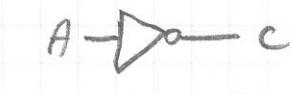


NOT gate
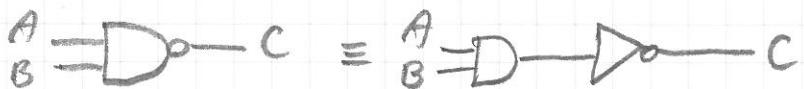
$$\begin{array}{r} A \quad C \\ \hline 1 \rightarrow 0 \\ 0 \rightarrow 1 \end{array}$$



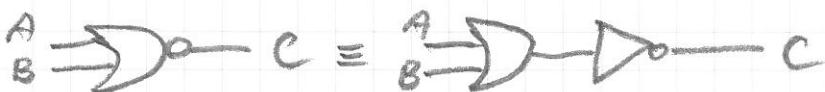NAND gate  $\equiv$  AND gate plus NOT gate



NOR gate  $\equiv$  OR gate plus NOT gate



### Truth table

| inputs |   | output (C) |    |      |     |
|--------|---|------------|----|------|-----|
| A      | B | AND        | OR | NAND | NOR |
| 0      | 0 | 0          | 0  | 1    | 1   |
| 0      | 1 | 0          | 1  | 1    | 0   |
| 1      | 0 | 0          | 1  | 1    | 0   |
| 1      | 1 | 1          | 1  | 0    | 0   |

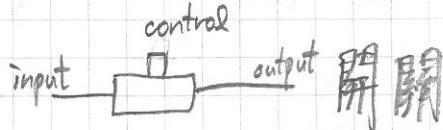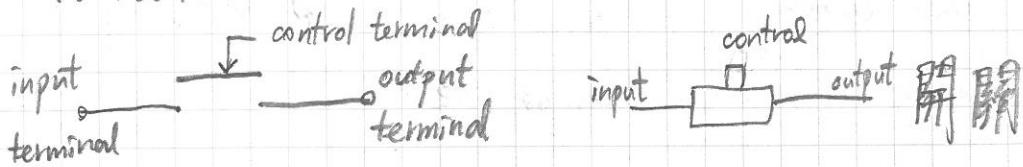
## P54 ★ The MOSFET switch

(Metal Oxide Semiconductor Field-Effect Transistor)

A switch is a three-terminal element in a circuit.



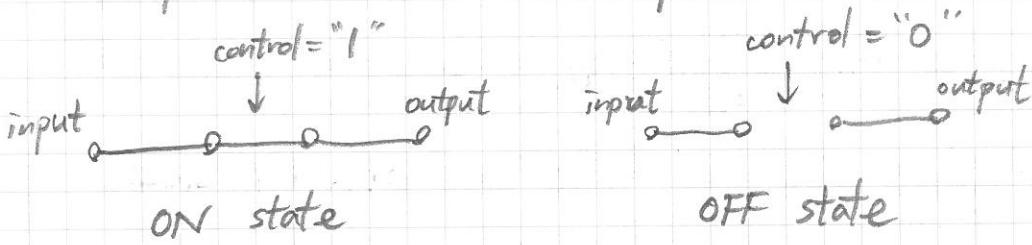
Ideally, input to the control terminal determines whether or not there is a short circuit between the input terminal and the output terminal:



(compare this with an ideal diode  $\text{---}$ , P39)

Such a simple idea of a switch enables many ways to control the response of certain elements in a circuit. First, let's look at two examples showing how a switch may impact the response of another element in a circuit:

## Example 1.

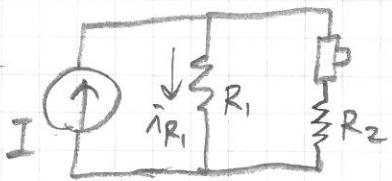


A switch connected in series with resistor  $R_2$  will impact the current flowing through resistor  $R_1$ .

$$\text{ON state: } i_{R_1} = I \times \frac{R_2}{R_1 + R_2}$$

$$\text{OFF state: } i_{R_1} = I$$

## Example 2.

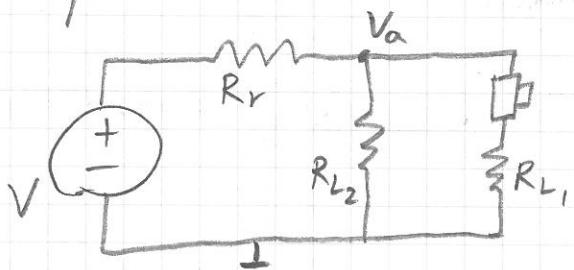

$$\text{ON state: } V_a = V \times \frac{R_{L_2} // R_{L_1}}{R_r + R_{L_2} // R_{L_1}}$$


$$\text{OFF state: } V_a = V \times \frac{R_{L_2}}{R_r + R_{L_2}}$$

The voltage across the resistor  $R_{L_2}$  will drop if the switch is in the ON state, because of the existence of  $R_r$ .

Conceptually, by connecting two switches in series we may implement the AND logic; by connecting two switches in parallel, we may implement the OR logic. In both cases, the control terminals take the input logical values.

P56


The symbol of a MOSFET

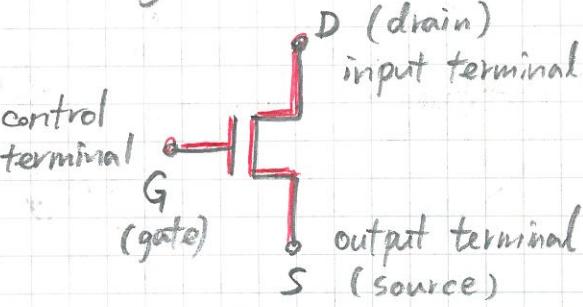


Let  $i_{DS}$  be the current flowing from the drain to the source,  $V_{GS}$  be the voltage across the gate and the source, and  $V_T$  be a threshold voltage.

In its simplest model ( $\underline{s}$  model), the MOSFET behaves as follows :

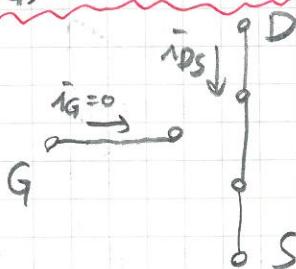
$$V_{GS} \geq V_T \Rightarrow \text{ON state}$$


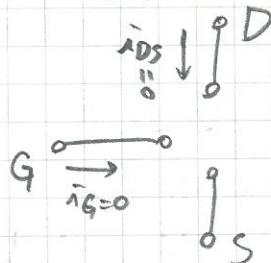
$$V_{GS} < V_T \Rightarrow \text{OFF state}$$




And in terms of input/output ports:

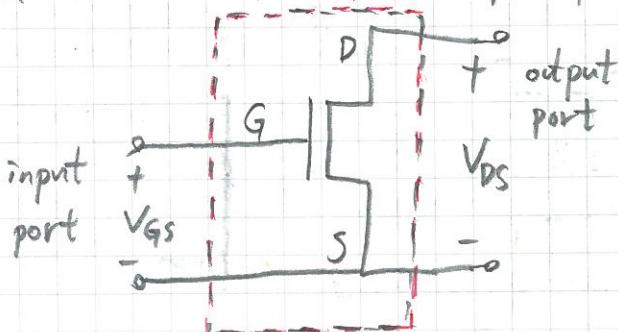

Later, we will study some more realistic models of MOSFET (for example, explicitly consider its internal resistance). For now, let's focus on the S model and its switching behavior. P57

We may use a MOSFET to construct a logical NOT gate  $\rightarrow \text{D}\circlearrowleft$ , so-called an "inverter":


(review P53)

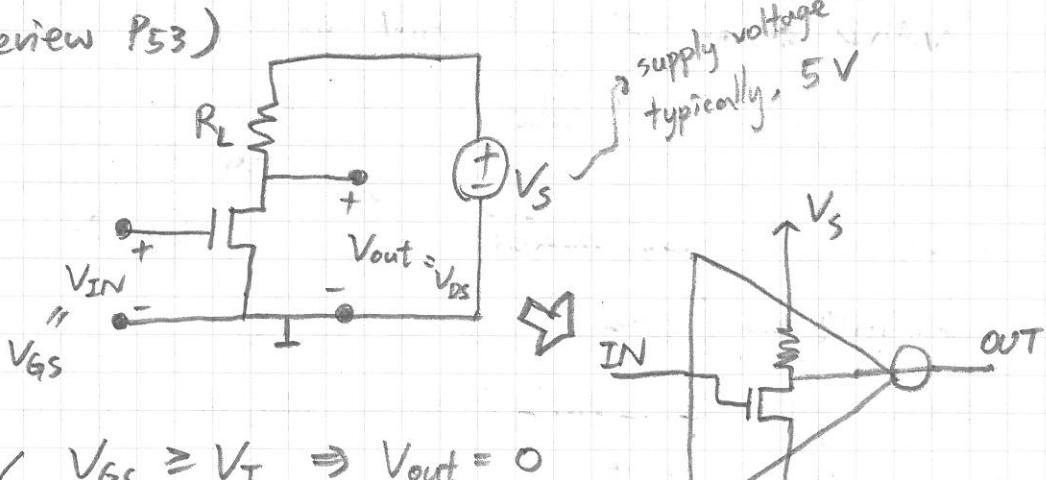

$$\left. \begin{array}{l} V_{GS} \geq V_T \Rightarrow V_{out} = 0 \\ (\text{logic 1}) \quad (\text{logic 0}) \end{array} \right\}$$

$$\left. \begin{array}{l} V_{GS} < V_T \Rightarrow V_{out} = V_S \\ (\text{logic 0}) \quad (\text{logic 1}) \end{array} \right\}$$

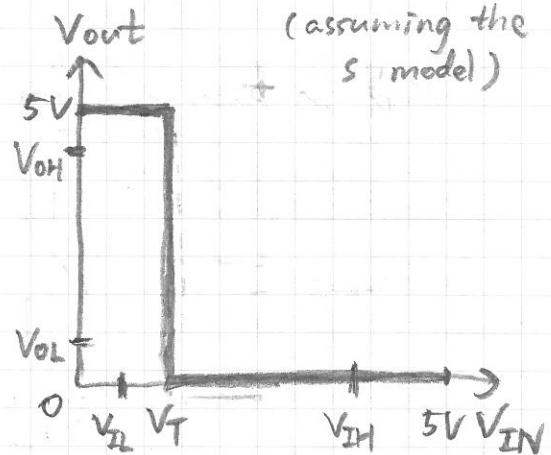transfer characteristic of an inverter (assuming the S model)




A valid mapping of voltage levels specified in the static discipline  $\rightarrow V_{OL}$


(review P52)

P58

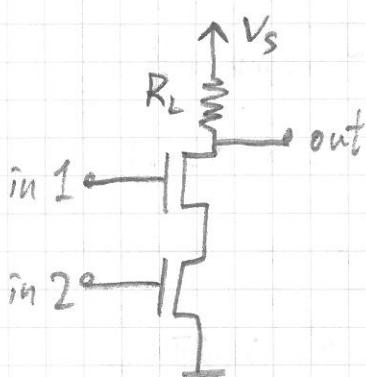
Similarly, we may use MOSFETs to construct other logic gates:



NAND gate

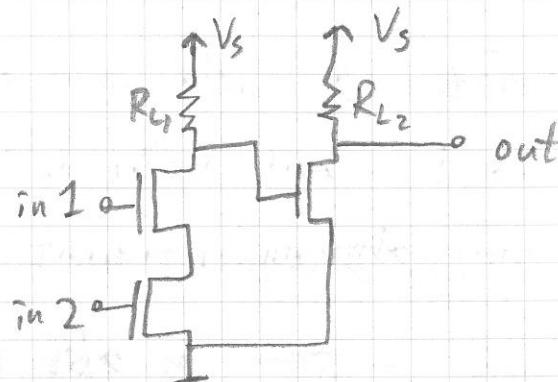


AND gate ( $\text{NAND} + \text{NOT}$ )

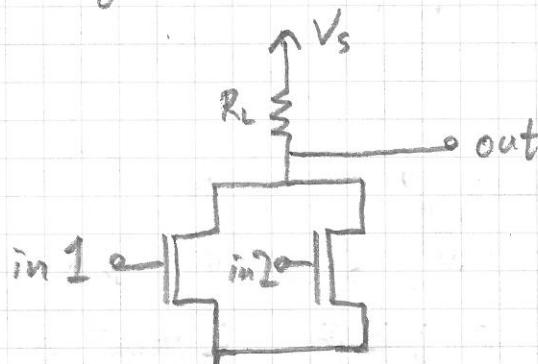


NOR gate

Exercise:  
OR gate

★ Physical structure of a MOSFET

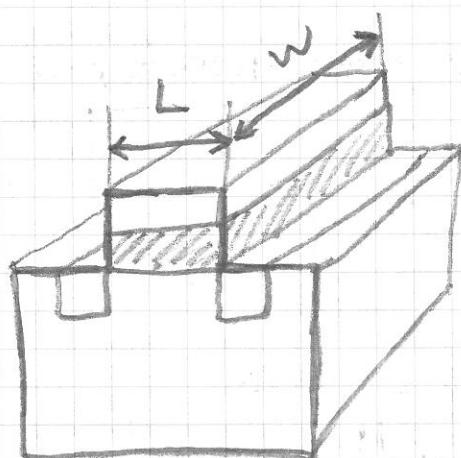

3D view

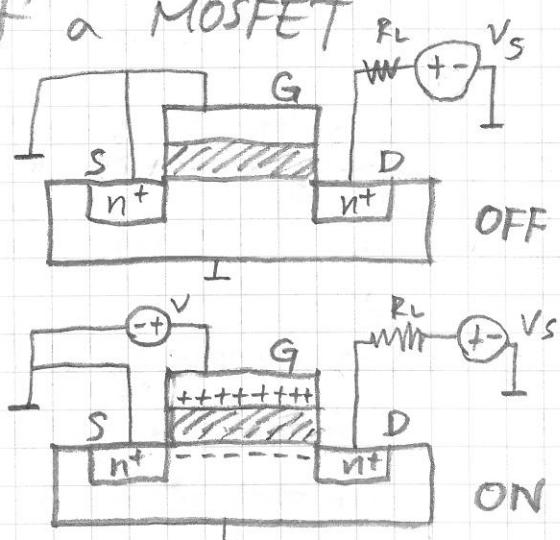

2D view

P59

When a positive voltage is applied at the control terminal G, a conducting channel will be built up between the two  $n^+$  regions, and therefore some nontrivial current may flow from D to S. Read Section 6.7 in the textbook for a more detailed account.

The physical structure also implies that in the ON state there really will exist some resistance between D and S, and the value of the resistance is characterised by the dimensions of that conducting channel. Let  $R_N$  be the resistance per square of the channel, and L be the channel length and W the channel width.


We have

$$R_{ON} = R_N \cdot \frac{L}{W} \quad (\text{review P6})$$

→ the resistance of the channel

The S model neglects  $R_{ON}$ . A more realistic model takes  $R_{ON}$  into account, and we call it the SR model:
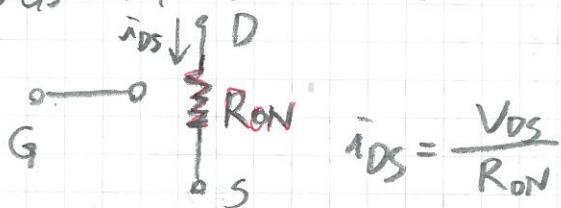
$$V_{GS} \geq V_T \Rightarrow \text{ON state}$$




(the OFF state is same as that in the S model)

$$i_{DS} = \frac{V_{DS}}{R_{ON}}$$
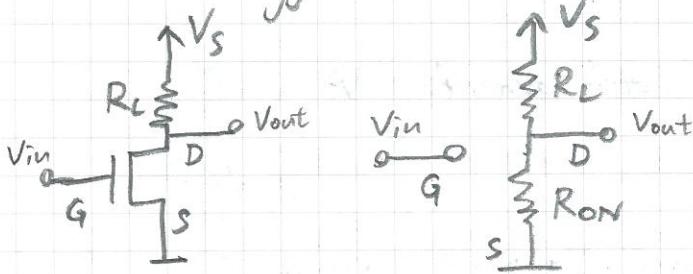
## P60 \* Analyzing a MOSFET circuit using the SR model

Taking into account the impact from  $R_{ON}$ , the analysis may seem complicated, but it is still based on what we've learned so far.

Let's analyze an inverter to illustrate this:




Because now we consider  $R_{ON}$ , the output voltage  $V_{out}$  will not be zero when  $V_{GS} \geq V_T$ ;

instead,

$$V_{out} = V_s \times \frac{R_{on}}{R_L + R_{on}}$$

following the voltage-divider relationship.

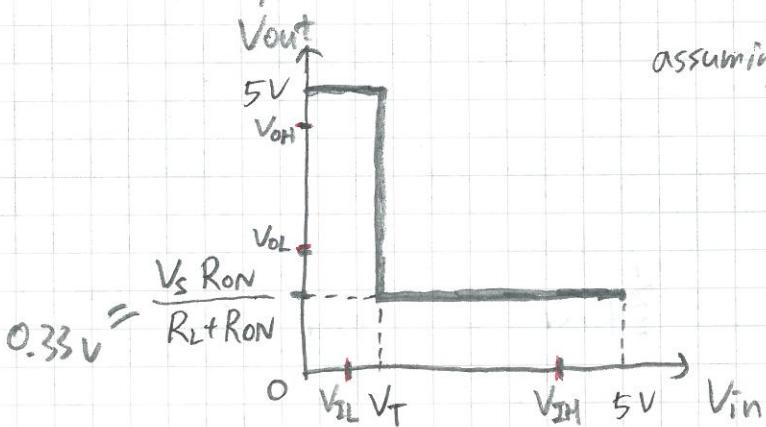And thus the transfer characteristic will become as follows (compare to one on P51):



assuming  $V_s = 5V$

$V_T = 1V$

$R_{on} = 1k\Omega$

$R_L = 14k\Omega$

This change of  $V_{out}$  value has at least two impacts:


in ON state

① To meet the static discipline,  $V_{out}$  needs to be lower than  $V_{OL}$ ; otherwise, we may observe that even though the magnitude of noise is within the specified margin, the value of  $V_{in}$  still exceeds  $V_{IL}$ .

→ solution A: redesign to reduce  $V_{out}$ .  
(from the manufacturer's viewpoint)

→ solution B: replace by a compatible device.  
(from the consumer's viewpoint)

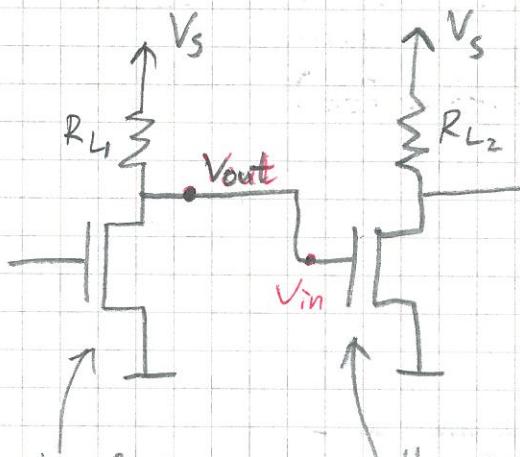② To drive another MOSFET,  $V_{out}$  in ON state needs to be lower than  $V_T$ , since  $V_{out}$  in OFF state equals  $V_s \geq V_T$ .  
usually



(As another example,  
see the AND gate)  
on P58

the driving  
MOSFET

the MOSFET whose ON/OFF state  
is driven by the preceding MOSFET.

P62

study Examples 6.5 and 6.6 in the textbook.

In general, since  $V_{out} = V_s \times \frac{R_{on}}{R_L + R_{on}}$ ,

to change  $V_{out}$ , we may {  
① change  $V_s$   
② change  $R_L$   
③ change  $R_{on}$

①  $\Rightarrow$  as a side-effect, it will also  
change  $V_{out}$  in OFF state!



②  $\Rightarrow$  { larger resistance is hard to achieve in VLSI;  
larger resistance would cause nontrivial  
voltage drop in the presence of leakage current;

③  $\Rightarrow$  may be achieved by changing the W/L ratio  
of the MOSFET.

$\Rightarrow$  An engineer's job often involves in finding  
the best solution among "multiple" options !!


\* Signal restoration, gain, and nonlinearity (Section 6.9 in the textbook) P63

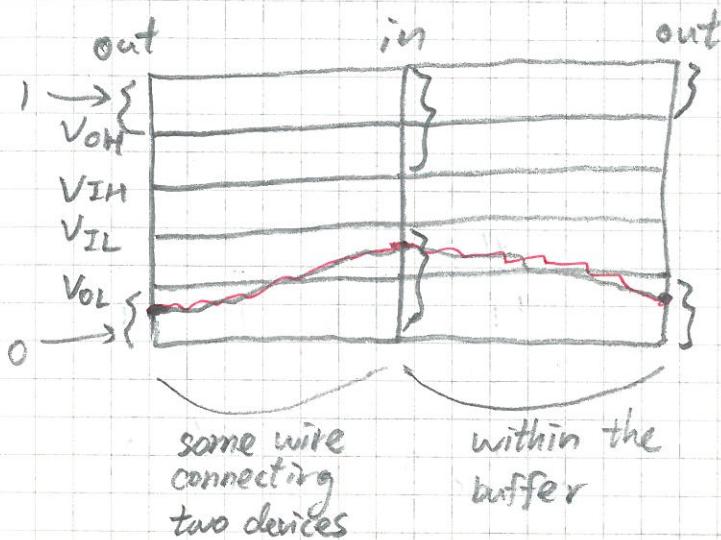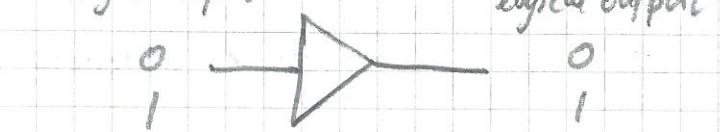We may use a device called "buffer" to restore a distorted signal (distorted by noise, logical input logical output for example):




As long as the system follows the static discipline, the output of a buffer will be closer to the output of the device that precedes it.

A rough implementation of a buffer:

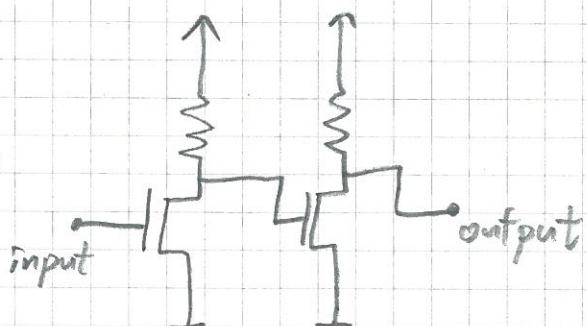

P64

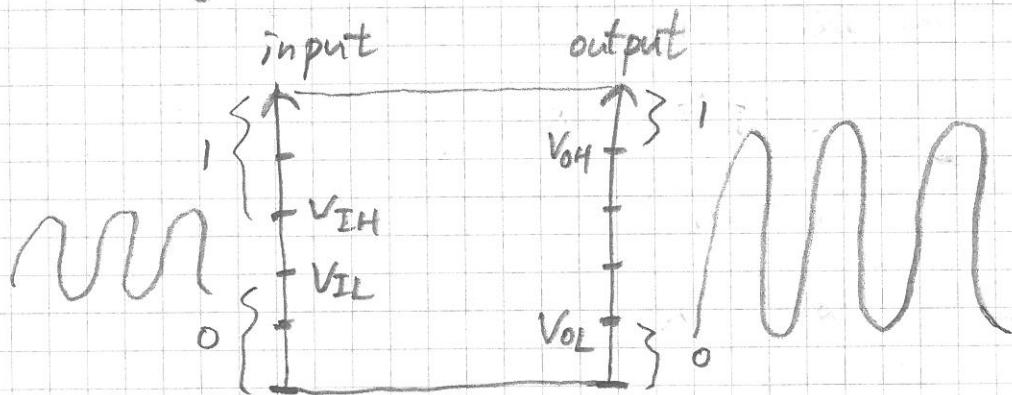In order for an electronic device to satisfies the system's specification of the static discipline, it turns out that such a device must be capable of amplifying an input signal. Why? Because a signal may fluctuate between logic 0 and logic 1:




Definition :


$$\text{Gain} = \frac{V_{OH} - V_{OL}}{V_{IH} - V_{IL}} \quad \text{for } V_{IL} \rightarrow V_{IH} \text{ transition}$$

for example, if  $V_{OH}=4$ ,  $V_{IH}=3$ ,  $V_{IL}=2$ ,  $V_{OL}=1$   
then the gain is 3.

The transfer characteristic of a buffer:

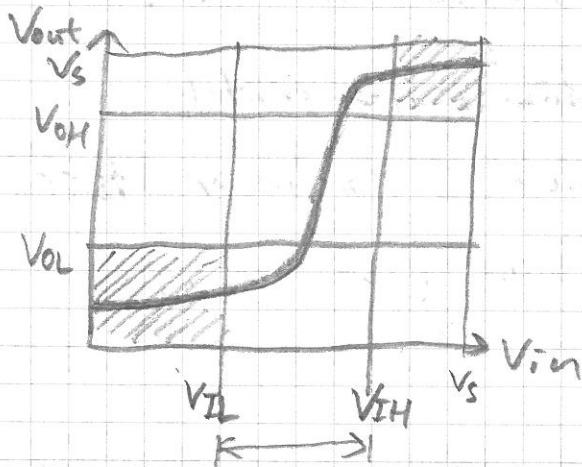

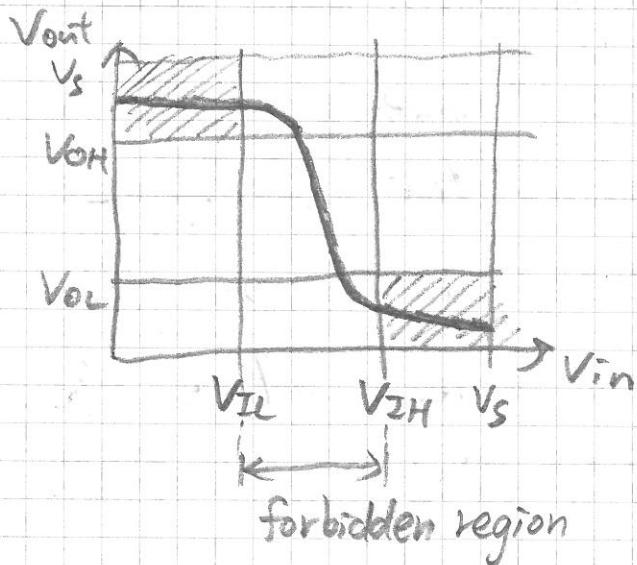The transfer characteristic of an inverter:



In both cases, the shaded region represents the valid region for the transfer curve.

Note that since  $V_{OL} < V_{IL}$  and  $V_s - V_{OH} < V_s - V_{IH}$ , the magnitude of the slope of the curve in the valid region is smaller than 1.



P66

So far, our discussion of MOSFET

include its behavior as a switch  
(S model) as well as its linear  $V_{DS} - i_{DS}$   
relation in its ON state (SR model, with  
resistor  $R_{ON}$ ).


In science and engineering, we are often curious about how a system would behave should we increase/decrease the value of a certain parameter. We have seen that a MOSFET will go from OFF state to ON state as we increase voltage  $V_{GS}$ .

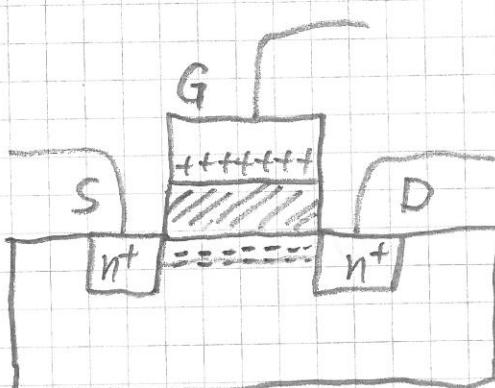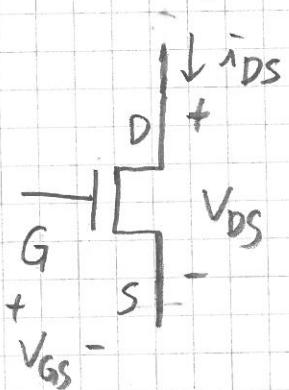Now, let's consider what will happen if we gradually increase  $V_{DS}$ .




As we increase  $V_{DS}$ , the difference in electrical potentials between G and D decreases. → 電位差

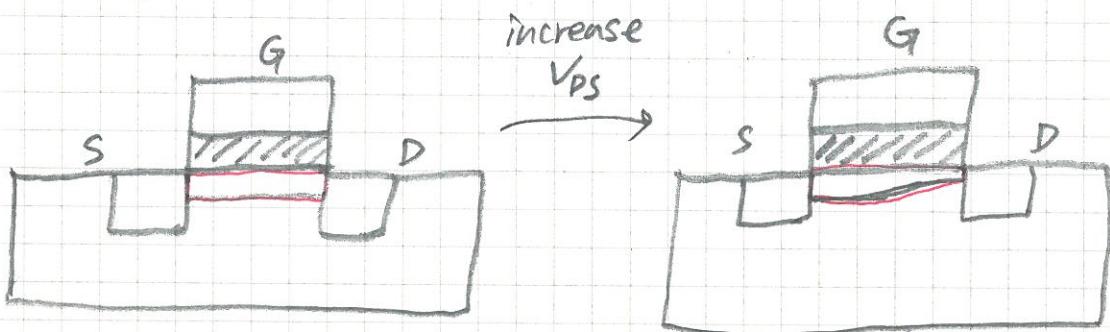This in turn will reduce the amount of free electrons near D, essentially shrinking the thickness of the conductible channel near D :



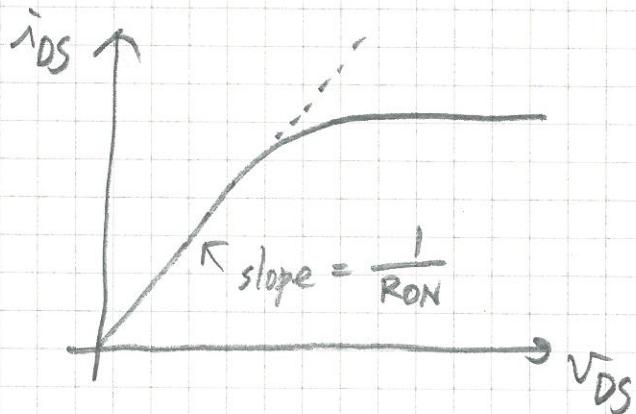Therefore we will see a bending of the curve on the  $i_{DS}$ - $V_{DS}$  plot :





電阻截面積 ↓  
 $\Rightarrow$  電阻值 ↑  
 $\Rightarrow$  slope ↓

# P68 \* The SCS model of a MOSFET

switch-current source

Compared to the S model and the SR model, the SCS model is a more accurate MOSFET model (closer to the real physical characteristic).

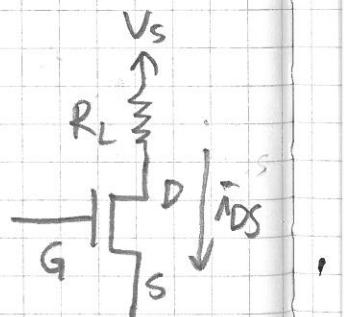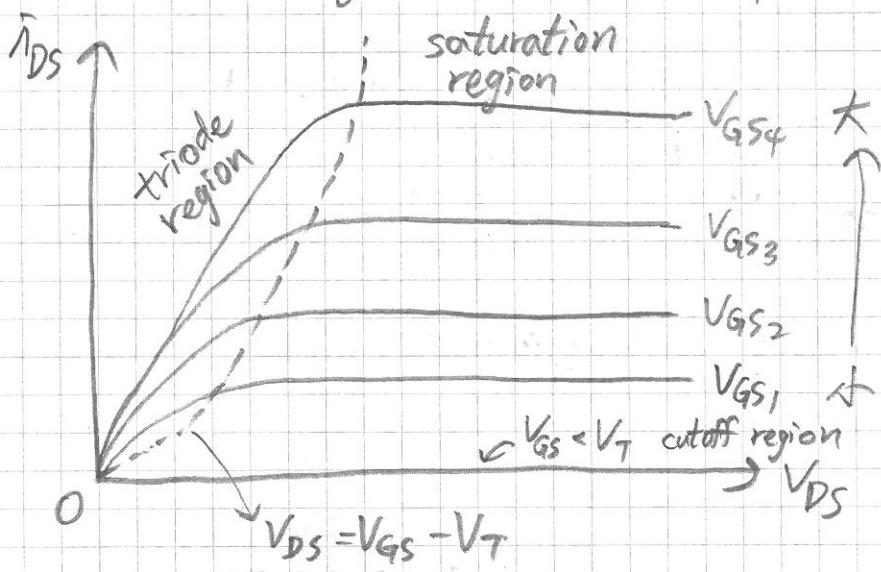In the SCS model, a MOSFET can operate with three very different behaviors, and we say it has three "operational regions".




Conditions for each region:

$$\left. \begin{array}{l} \text{cutoff: } V_{GS} < V_T, \text{ i.e., } \underline{\underline{V_{GS} - V_T}} < 0 \\ \text{saturation: } 0 \leq \underline{\underline{V_{GS} - V_T}} \leq V_{PS} \\ \text{triode: } V_{DS} < \underline{\underline{V_{GS} - V_T}} \end{array} \right\}$$

$$\left. \begin{array}{l} \text{cutoff: } V_{GS} < V_T, \text{ i.e., } \underline{\underline{V_{GS} - V_T}} < 0 \\ \text{saturation: } 0 \leq \underline{\underline{V_{GS} - V_T}} \leq V_{PS} \\ \text{triode: } V_{DS} < \underline{\underline{V_{GS} - V_T}} \end{array} \right\}$$



$$\left. \begin{array}{l} \text{cutoff: } V_{GS} < V_T, \text{ i.e., } \underline{\underline{V_{GS} - V_T}} < 0 \\ \text{saturation: } 0 \leq \underline{\underline{V_{GS} - V_T}} \leq V_{PS} \\ \text{triode: } V_{DS} < \underline{\underline{V_{GS} - V_T}} \end{array} \right\}$$

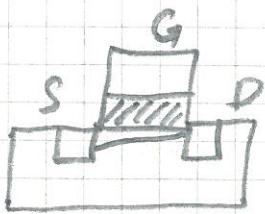In the saturation region, current  $i_{DS}$  would stay the same as we keep increasing  $V_{DS}$ , because the channel between source and drain has become stable : P69



(review P58, P66-67)

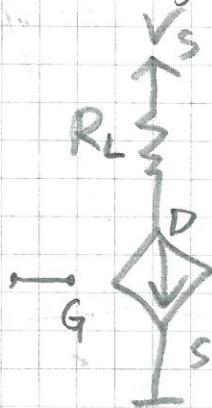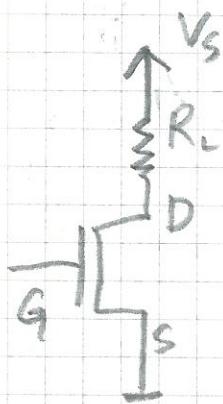Therefore, we may consider such a behavior as if there is a "current source" (P13). But  $i_{DS}$  would depend on voltage  $V_{GS}$ , and thus we say it is like a "voltage-controlled current source". symbol:



if  $0 \leq V_{GS} - V_T \leq V_{DS}$   
→ in saturation region

$$i_{DS} = f(V_{GS}) = \frac{K(V_{GS} - V_T)^2}{2}$$


(according to physics)

Note that  $K$  is a coefficient ;

unit : mA/V<sup>2</sup>

Pno

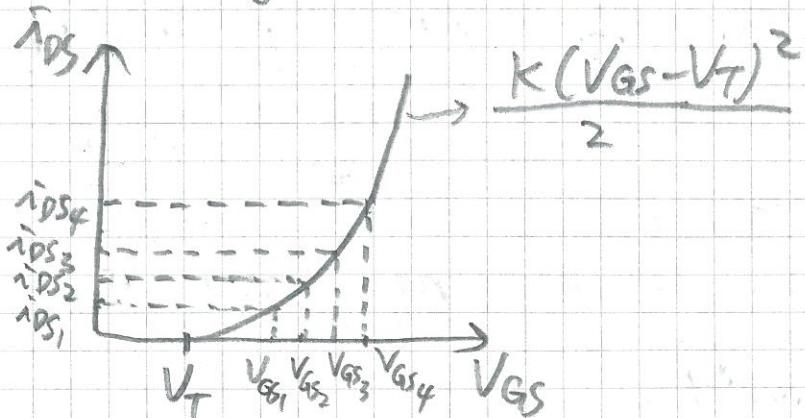
Plotting the  $i_{DS}$  -  $V_{GS}$  relation, we see:



$$\begin{aligned}\text{Therefore, if } |V_{GS_1} - V_{GS_2}| &= |V_{GS_2} - V_{GS_3}| \\ &= |V_{GS_3} - V_{GS_4}|\end{aligned}$$


we will have

$$|i_{DS_1} - i_{DS_2}| < |i_{DS_2} - i_{DS_3}| < |i_{DS_3} - i_{DS_4}|$$

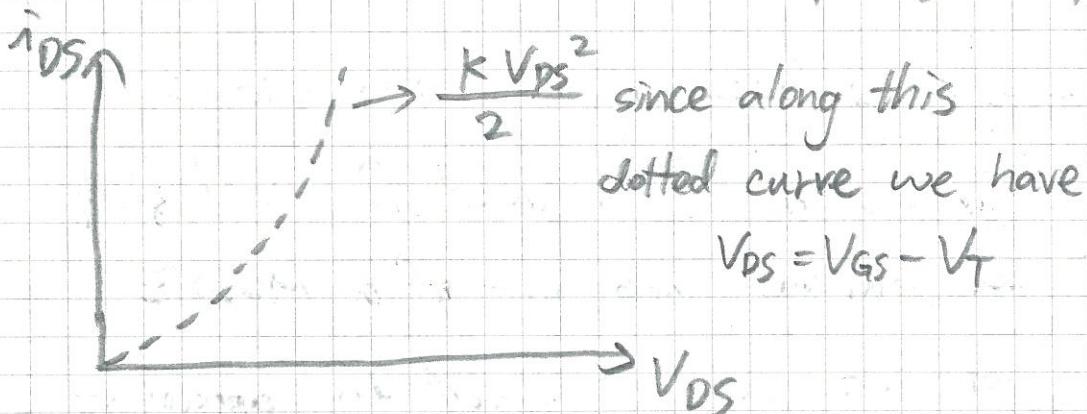

$$\Rightarrow i_{DS} = \begin{cases} 0 & \text{for } V_{GS} < V_T \\ \frac{K(V_{GS}-V_T)^2}{2} & \text{for } 0 \leq V_{GS}-V_T \leq V_{DS} \end{cases}$$

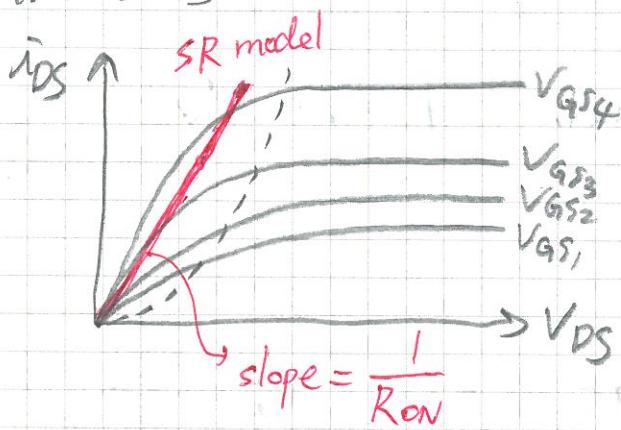From the aspect of the SCS model,  
 the  $R_{ON}$  in the SR model can be thought  
 of as a piecewise approximation of the  
 $i_{DS}$ - $V_{DS}$  relation in the triode region in  
 the SCS model :




We may summarize in this way :

The S model is good for analyzing  
 the ON/OFF behavior of a MOSFET.

The SR model is good for approximating  
 the MOSFET's behavior in the triode  
 region.

P72 Let's work on two examples to get ourselves familiar with the SCS model and its analysis:

Example 1.

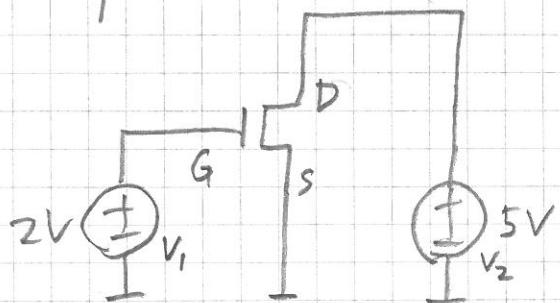

Assuming

$$V_T = 1 \text{ V}$$

$$K = 1 \text{ mA/V}^2$$

①  $i_{DS} = ?$  since  $V_{GS} = 2 \text{ V} > V_T$

$$\text{and } V_{DS} = 5 \text{ V} > V_{GS} - V_T = 1,$$

we see the MOSFET is operating in the saturation region  $\Rightarrow i_{DS} = \frac{K(V_{GS}-V_T)^2}{2} = 0.5 \text{ mA}$

② If we keep  $V_1$  and decrease  $V_2$ , at what condition of  $V_2$  will the MOSFET enter the triode region?

$\rightarrow$  As long as  $V_{DS} \geq V_{GS} - V_T$  the MOSFET will stay in the saturation region

$\rightarrow$  if  $V_2 = V_{DS} < V_{GS} - V_T = 1 \text{ V}$ , the MOSFET will enter the triode region.

③ If we keep  $V_2$ , what would be the range of  $V_1$  for the MOSFET to stay in the saturation region?

$$\rightarrow V_{DS} \geq V_{GS} - V_T$$


$$\rightarrow 5 \geq V_{GS} - 1 \rightarrow V_{GS} \leq 6$$

$$\rightarrow V_1 = V_{GS} \leq 6 *$$

Example 2.

Assuming  $V_T = 1$  V

$$k = 4 \text{ mA/V}^2$$

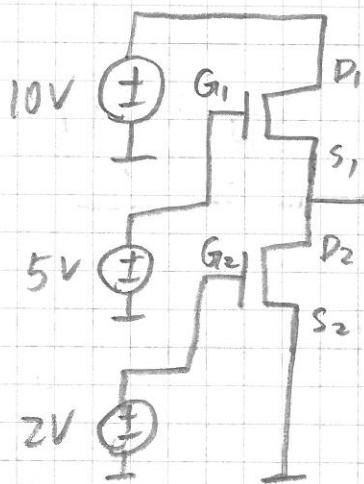

If  $V_0 = 3$ , are both MOSFETs operating in the saturation region?

Yes, since  $V_{G_1S_1} - V_T = (5 - 3) - 1 = 1 > 0$

and  $\underbrace{V_{G_1S_1} - V_T}_{=1} \leq \underbrace{V_{DS_1}}_{=10 - 3 = 7}$

And  $V_{G_2S_2} - V_T = 2 - 1 = 1 > 0$

and  $\underbrace{V_{G_2S_2} - V_T}_{=1} \leq \underbrace{V_{DS_2}}_{=5 - 3 = 2}$



And  $V_{G_1S_1} = V_{G_2S_2}$  correctly implies  $i_{D_1S_1} = i_{D_2S_2} *$

P74 (Note on 2020/6/1 3PM :

I apologize for the confusion regarding whether  $V_0=2$  in Example 2 makes sense or not.

After some more thoughts, I think what I said this morning is wrong.

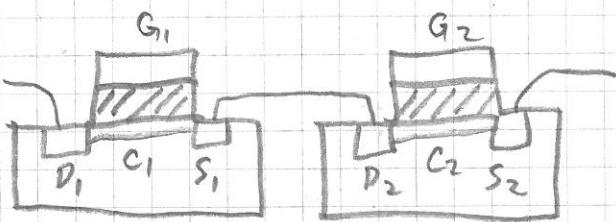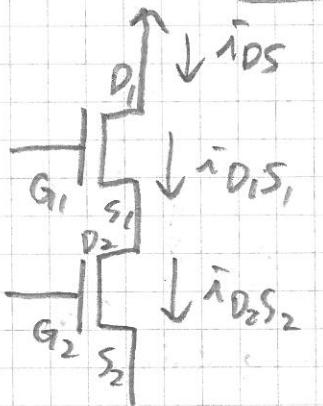It is wrong that  $\bar{i}_{DS} = \bar{i}_{D_1S_1} + \bar{i}_{D_2S_2}$



In physics,  $\bar{i}_{D_1S_1}$  is constrained by channel  $C_1$ , and  $\bar{i}_{D_2S_2}$  is constrained by channel  $C_2$ . It should be that


$$\bar{i}_{DS} = \bar{i}_{D_1S_1} = \bar{i}_{D_2S_2}.$$

And therefore  $V_0=2$  does NOT make sense.)

Now let's see how we may leverage a MOSFET operating in the saturation region for some useful purposes. P75

It turns out that in the saturation region a MOSFET may be used to amplify a signal. Amplifiers are used in many real-world applications and systems. Headphones and speakers are two examples.

### - MOSFET Amplifier, Version 1

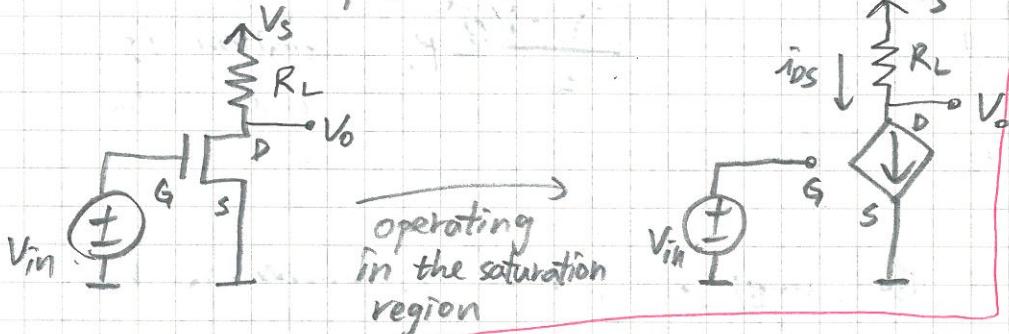

The voltage-controlled current source gives


$$i_{DS} = \frac{K(V_{GS} - V_T)^2}{2} \quad (\text{see P69})$$

and in addition, by Ohm's law  $i_{DS} = \frac{V_s - V_o}{R_L}$

$$\Rightarrow \frac{K(V_{GS} - V_T)^2}{2} = \frac{V_s - V_o}{R_L} \Rightarrow V_o = V_s - K \cdot \frac{(V_{in} - V_T)^2}{2} \cdot R_L$$

and that  $V_{GS} = V_{in}$

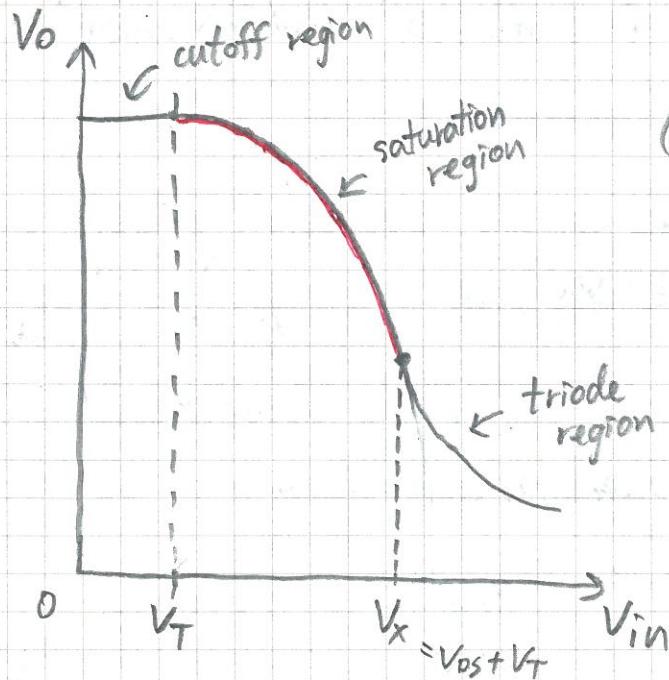P76 following the equation on P75, we have



( compare this  
to the plots on  
P57 and P65 )

The  $V_o = V_s - \frac{K(V_{in}-V_T)^2}{2} R_L$  relation is  
only valid when  $V_T \leq V_{in} \leq V_x$ .

Later we will study how to determine  $V_x$ .  
( P81 )

The slope  $\frac{V_o}{V_{in}}$  is also the ratio between  $V_{in}$  and  $V_o$ . We see that in some part of the saturation region the magnitude of the slope is greater than one. Therefore we may amplify  $V_{in}$  by  $\frac{V_o}{V_{in}}$  times and output the result as  $V_o$ .

The "gain" of the amplifier is defined to be  $\frac{V_o}{V_{in}}$ .

Using this MOSFET amplifier, however,


the output will be inverted, which might not be what we want:

$$\begin{cases} V_{in} \downarrow \Rightarrow V_o \uparrow \\ V_{in} \uparrow \Rightarrow V_o \downarrow \end{cases}$$

(can be verified by the sign of the slope in the  $V_o - V_{in}$  plot.)


Let's study an alternative design ↴

### - MOSFET Amplifier, Version 2

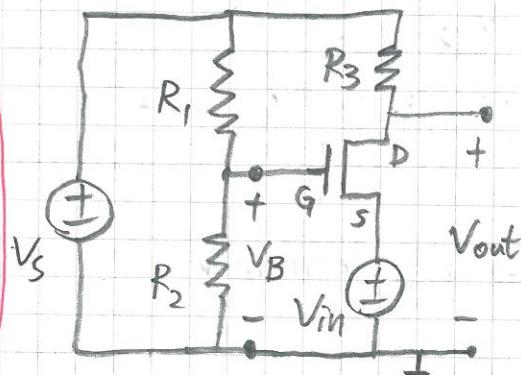

In this configuration, we use one voltage source to provide voltages to the gate and the drain.

This is equivalent to :

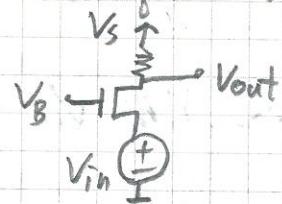

$$V_{GS} = V_B - V_{in}$$

$$= \left( V_s \times \frac{R_2}{R_1 + R_2} \right) - V_{in}$$

Therefore, we have

$$\frac{k(V_{GS} - V_T)^2}{2} = \frac{V_s - V_{out}}{R_3}$$

Given saturation region, we have

$$I_{DS} = \frac{k(V_{GS} - V_T)^2}{2}$$

and by Ohm's law


$$I_{DS} = \frac{V_s - V_{out}}{R_3}$$

$$\Rightarrow \frac{k\left(V_s \times \frac{R_2}{R_1 + R_2} - V_{in} - V_T\right)^2}{2} = \frac{V_s - V_{out}}{R_3}$$

Pn8 following the equation on P77, suppose that

$$\begin{cases} V_S = 10 \text{ V} \\ R_1 = 84 \text{ k}\Omega, R_2 = 16 \text{ k}\Omega, R_3 = 20 \text{ k}\Omega \\ V_T = 1 \text{ V}, K = 1 \text{ mA/V}^2 \end{cases}$$

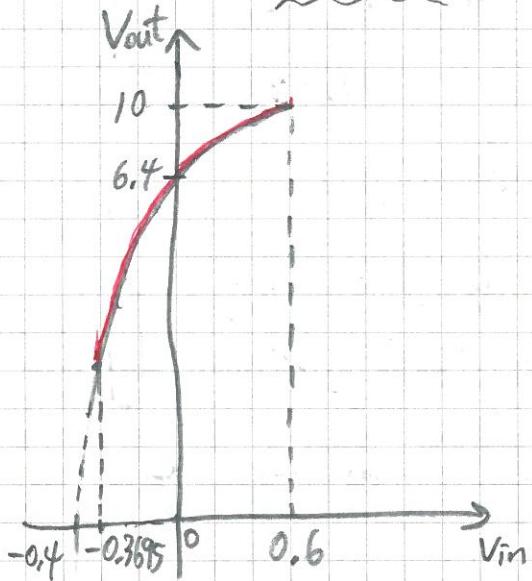then  $V_B = 1.6$  and  $V_{out} = 10 - 10(0.6 - V_{in})^2$



To operate in the saturation region, both of the following conditions must be satisfied:

$$\begin{cases} V_{GS} \geq V_T \quad \text{--- (1)} \\ V_{GS} - V_T \leq V_{DS} \quad \text{--- (2)} \end{cases}$$

from (1),  $1.6 - V_{in} \geq 1 \Rightarrow V_{in} \leq 0.6 \text{ V}$

from (2),  $(1.6 - V_{in}) - 1 \leq V_{out} - V_{in}$

$$\Rightarrow V_{out} \geq 0.6 \text{ V}$$

$$\Rightarrow 10 - 10(0.6 - V_{in})^2 \geq 0.6$$

$$\Rightarrow -0.3695 \text{ V} \leq V_{in} \leq 1.5695 \text{ V}$$

$$-0.3695 \text{ V} \leq V_{in} \leq 0.6 \text{ V}$$

Thus we see that

it is an amplifier ( $\frac{V_{out}}{V_{in}} > 0$ )

and  $\begin{cases} V_{in} \uparrow \Rightarrow V_{out} \uparrow \\ V_{in} \downarrow \Rightarrow V_{out} \downarrow \end{cases}$

$\begin{cases} V_{in} \downarrow \Rightarrow V_{out} \downarrow \end{cases} *$

P79

For the purpose of signal amplification, and for the SCS model in general, we would want to make sure that the MOSFET operates in the saturation region. Given the circuit's parameters, in order to determine whether the MOSFET will operate in the saturation region (or to determine the valid range of values of parameters), we may use the conditions listed on P68 or use graphical analysis.

For example, for the MOSFET amplifier on P75, suppose  $V_S = 5V$ ,  $R_L = 1k\Omega$ ,  $V_T = 0.8V$ ,  $V_{in} = 2.5V$  is the MOSFET in the saturation region?

Answer:  $V_{GS} = V_{in} = 2.5V$ .

$$V_{DS} = V_D = V_S - K \frac{(V_{in} - V_T)^2}{2} R_L = 4.28V$$

and we see that both



$$\left. \begin{array}{l} V_{GS} \geq V_T \\ V_{DS} \geq V_{GS} - V_T \end{array} \right\}$$

Therefore, it is indeed in the saturation region. #


P80 Using graphically analysis, we first observe that, by Ohm's law, we first

$$i_{DS} = \frac{V_S - V_{DS}}{R_L}$$

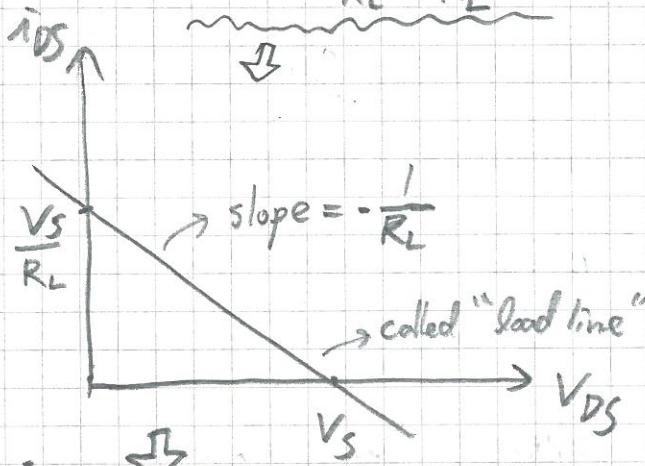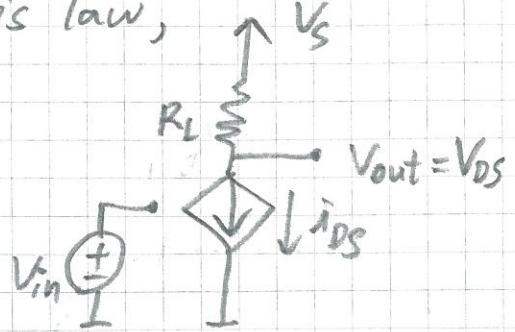
$$\Rightarrow i_{DS} = \frac{V_S}{R_L} - \frac{1}{R_L} V_{DS}$$




(see the plot on P68)

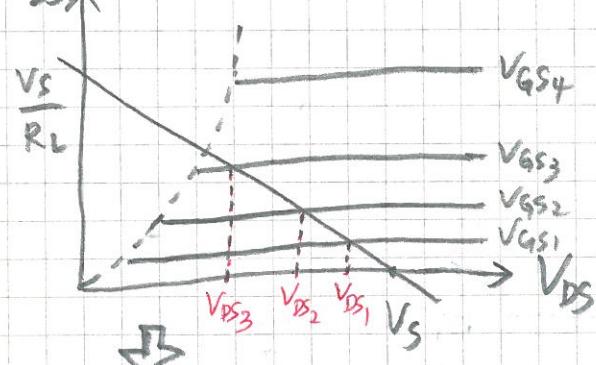
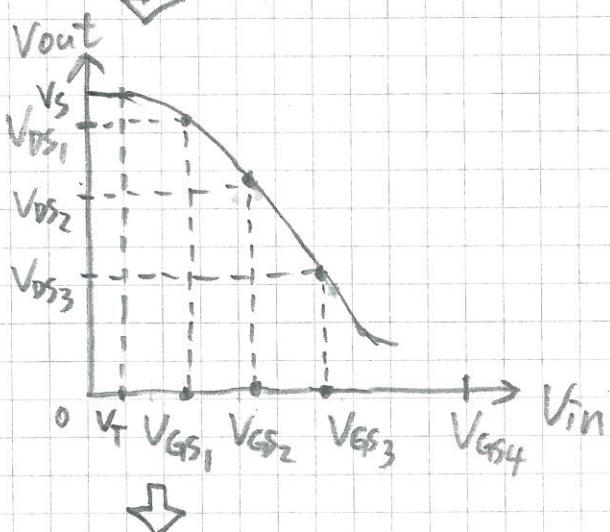
$$\begin{cases} V_{in} = V_{GSx} & x=1 \sim 4 \\ V_{out} = V_{DSx} & x=1 \sim 3 \end{cases}$$



(see the plot on P76)

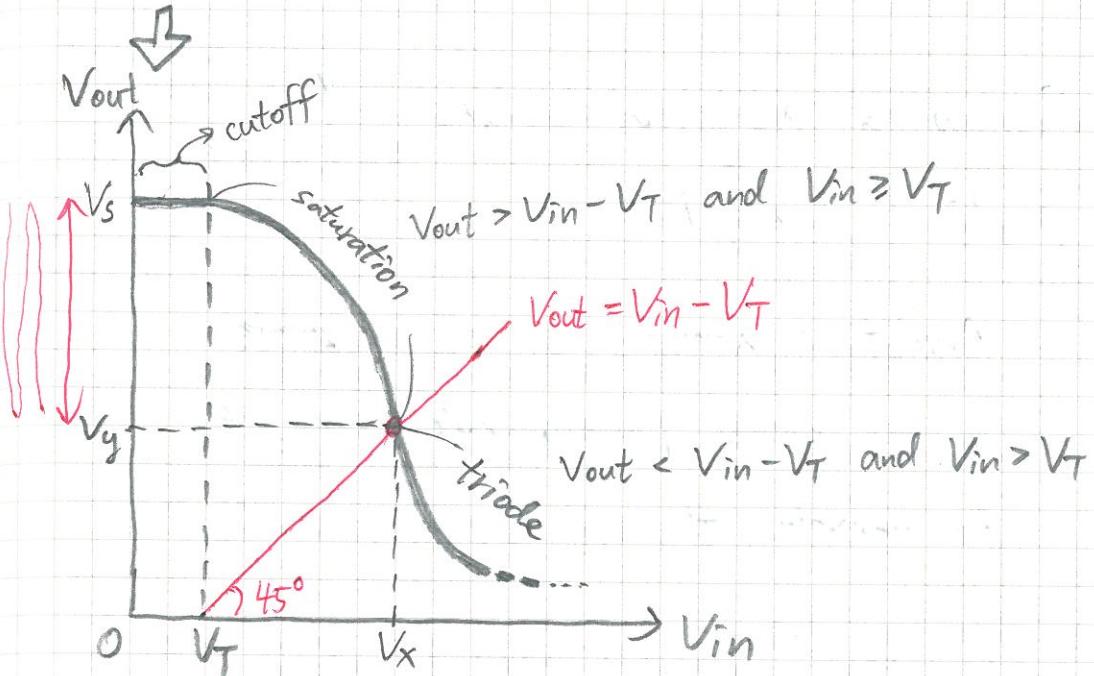

To compute  $V_x$ , we have

$$\begin{cases} V_{out} = V_{in} - V_T \\ V_{out} = V_s - K \frac{(V_{in} - V_T)^2}{2} R_L \end{cases} \quad (\text{P75})$$

$$\Rightarrow V_{in} - V_T = V_s - K \frac{(V_{in} - V_T)^2}{2} R_L$$

$$\Rightarrow \frac{K R_L}{2} (V_{in} - V_T)^2 + (V_{in} - V_T) - V_s = 0$$

$$\Rightarrow V_{in} - V_T = \frac{-1 + \sqrt{1 + 2V_s R_L K}}{K R_L}$$

$$\Rightarrow V_x = \frac{-1 + \sqrt{1 + 2V_s K R_L}}{K R_L} + V_T$$

$$V_y = V_x - V_T$$

P82


## Comparing analytical analysis and graphical analysis:

- Analytical analysis is as accurate as the model (and formula) can be.

For example, the use of  $i_{DS} = \frac{k(V_{DS}-V_T)^2}{2}$

- Graphical analysis may be more accurate, provided that the manufacturer of the electronic device often gives "data sheet", which includes the actual measured physical values of, for example,  $i_{DS}$ - $V_{DS}$  characteristics.
- Graphical analysis also provides more insights (for example, see P39, 38).

Example:

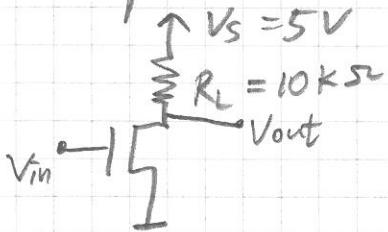


Assuming VT = 1V

$$K = 1 \text{ mA/V}^2$$

What would be the maximum Vin that the MOSFET can still stay in the saturation region?

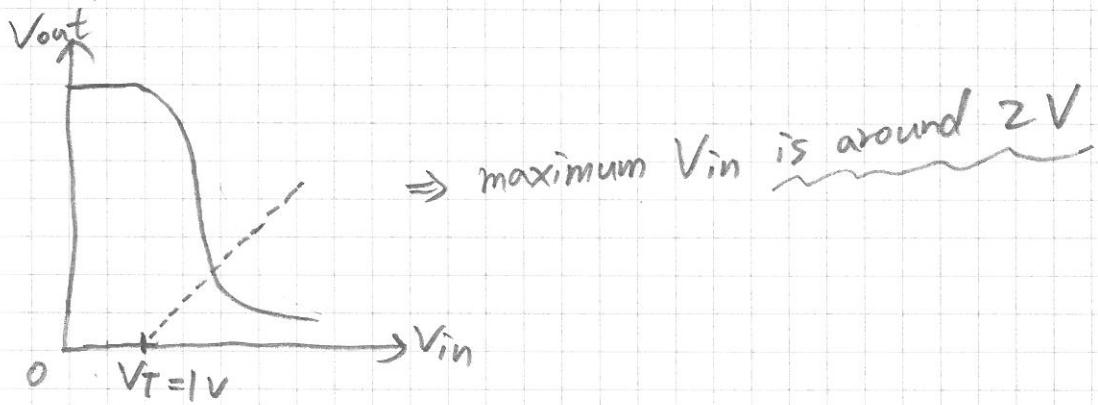If the Vout - Vin plot is accurate, we may directly estimate the maximum Vin:




Applying analytical analysis, we have

$$\begin{aligned} V_{in} &= \frac{-1 + \sqrt{1 + 2VsKR_L}}{KR_L} + VT \\ &= \frac{-1 + \sqrt{1 + 2 \times 5 \times 10^{-3} \times 10 \times 10^3}}{1 \times 10^{-3} \times 10 \times 10^3} + 1 \approx 1.9 \text{ V} \end{aligned}$$

$$I_{DS} \uparrow$$

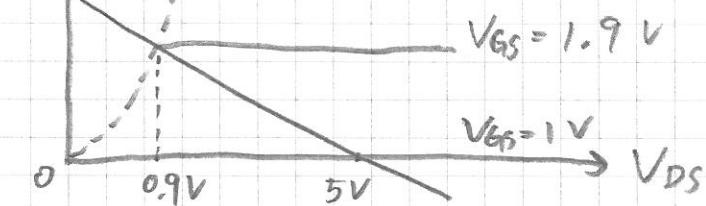$V_{out} = V_{in} - V_T \approx 0.9 \text{ V}$



## P84 \* The Small-Signal Model

We have learned some small-signal analysis when we were studying diode circuits early this semester (P43 - P48; Section 4.5 in the textbook).

Small-signal model and its analysis play a critical role in both design and usage of MOSFET amplifiers because



- ① many real-world input signals are small signals;
- ② the small-signal gain  $\frac{V_o}{V_i}$  is "linear", which implies less signal distortion caused by the amplifier;
- ③ the circuit under the small-signal model is "linear", which means we may apply existing linear circuit analysis techniques, for example Thévenin's Theorem, to help us understand the circuit's behavior and its response to input signal!

It is important to remember that small-signal model is an "approximation" of the original non-linear model. In practice, it may be needed to estimate the quality of such an approximation. That part is beyond the scope of this course, but you may study P218 in the textbook to get some idea. It is interesting to recall that the original non-linear model is itself an approximated description of how a circuit behaves in the real world.

In essence, the small-signal model describes how a circuit responds to a small, time-varying signal. The large, time-invariant signal is used to determine the operating point around which the small signal oscillates. Take our familiar MOSFET amplifier, for example:

$$V_I = V_{I_0} + \Delta V_I$$

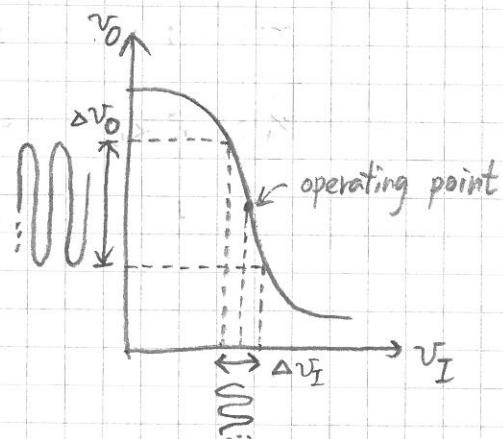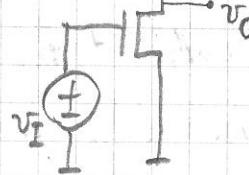↓      ↓      ↓  
total    large    small  
input    signal    signal



P86


The large, time-invariant signal in this case is call the DC bias, or the DC offset.

直流偏壓

In the small-signal model, we consider that all of the independent current sources  $\oplus$  and independent voltage sources are shut off, because their impact to the circuit does not change along with the small signal; in other word, their impact to the circuit is time-invariant.

In this sense, the voltage-controlled current source  $\diamond$  is not considered shut off for our MOSFET amplifier, because the current depends on the small-signal  $V_i$  (and depends on the large-signal  $V_I$ , too).

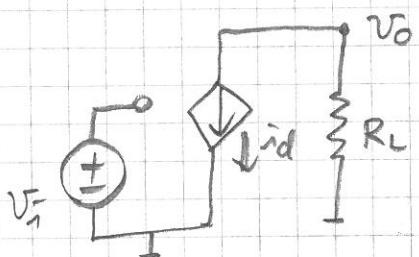The small-signal model of our MOSFET amplifier:



where  $i_d = g_m \cdot V_i$ ,  
and  $g_m = k(V_I - V_T)$

is called the  
incremental transconductance.

To obtain the small-signal gain  $\frac{V_o}{V_i}$ , we P87  
may apply linear circuit analysis :

$$\frac{V_o - 0}{R_L} = -i_d$$

$$\Rightarrow V_o = -i_d \cdot R_L = -(g_m \cdot V_i) \cdot R_L$$


$$\Rightarrow \frac{V_o}{V_i} = -g_m \cdot R_L$$

and the magnitude of the gain is

$$\left| \frac{V_o}{V_i} \right| = g_m R_L$$

In class, we've used the Taylor series expansion to derive that relation  $i_d = K(V_I - V_T)V_i$ .

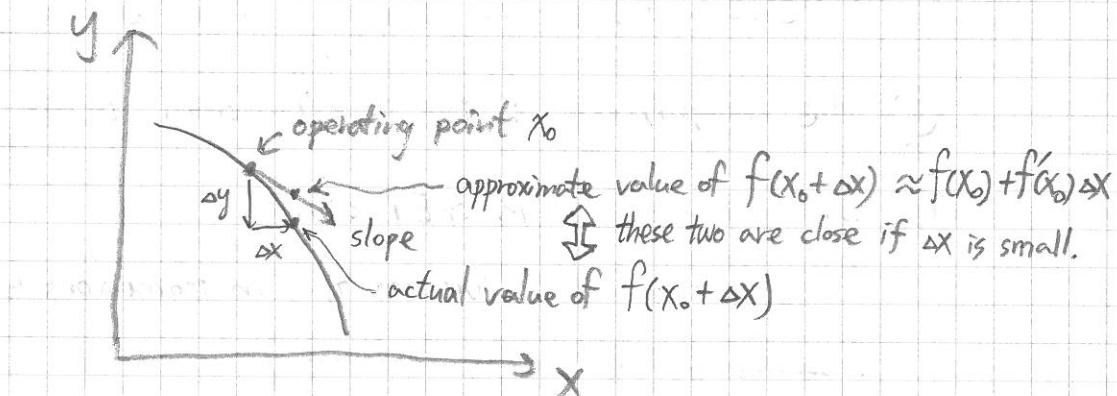
The take-home message of such a derivation is that we may, in general, compute the first derivative (-一次微分) of a function at the operating point to get a reasonable small-signal relation :



Study textbook Chapter 8 and Homework 6 for some examples of the small-signal analysis and the model. Finally, from a practical viewpoint, we may summarize four criteria regarding how to select an appropriate operating point, or in other word, how to set a proper DC bias:

- ① determine the range of input signal  $V_I$  such that the MOSFET would operate in the saturation region; (P356 in textbook)
- ② if the large-signal is also time-varying, we may want to maximize the peak-to-peak swing of the input signal by setting the operating point at the middle of the valid range of  $V_I$  for operation in the saturation regions; (review P351 and P369 in the textbook)
- ③ the magnitude of the small-signal gain;
- ④ driving another MOSFET circuit; (P61 in this note; Questions 4, 5 in Homework 4) (Section 8.2.3 in the textbook)

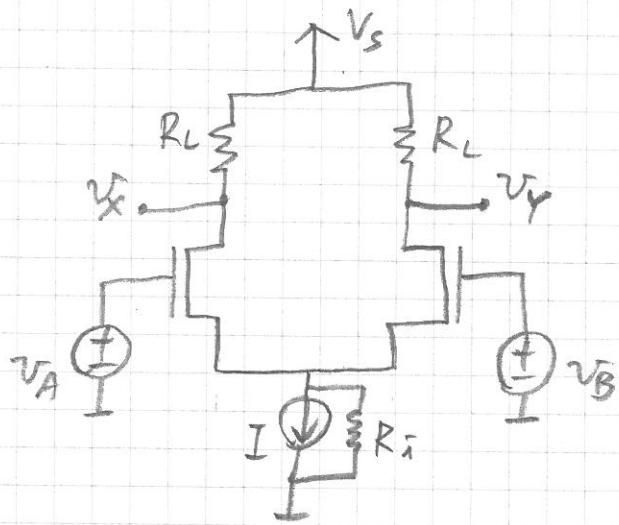We will discuss more on the difference amplifier after the final exam. It will not be included in the exam.



(\*)

q,