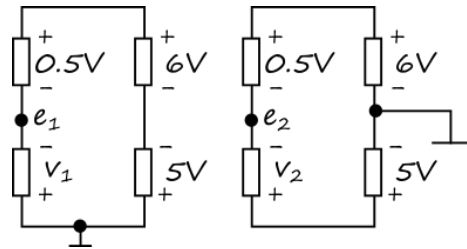


National Taiwan Normal University  
Department of Computer Science and Information Engineering  
CSU0007 - Basic Electronics


## Homework 2

Seven questions. 100 points total. Due on 10PM, Tuesday, 3/31/2020. Submit your answer via Moodle  
Clearly state each step of your calculation to receive full score.


1. (20 points) Find the node voltages  $e_1$  and  $e_2$  and the branch voltages  $v_1$  and  $v_2$ . 5 points each.



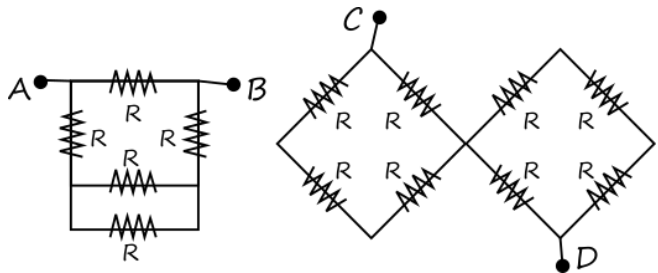
2. (10 points) Find the equivalent resistance from the viewpoint of A-B and from that of C-D. 5 points each.



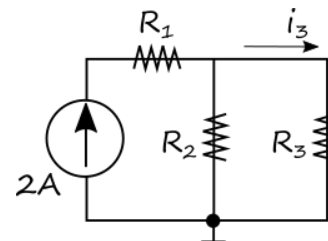
3. (10 points) Find the current  $i_3$ . -----



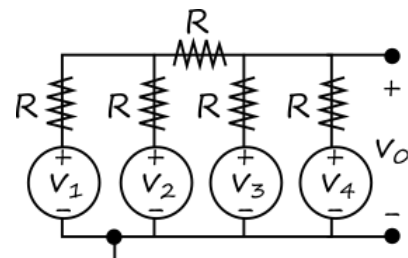
4. (10 points) Find the voltage  $v_0$ . -----



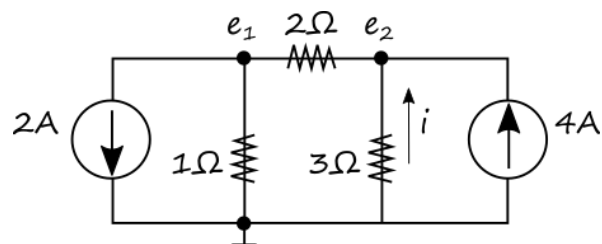
5. (15 points) Find node voltage  $e_1$  and  $e_2$ , and then find the current  $i$ . 5 points each.



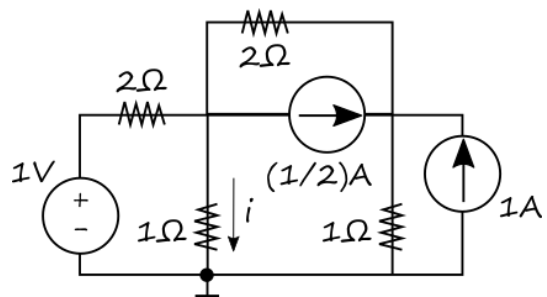
6. (10 points) Find the current  $i$ . -----



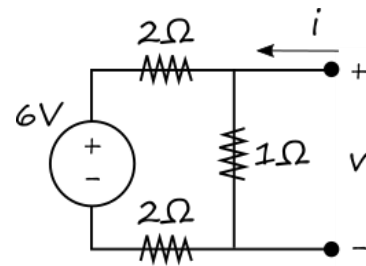7. (25 points) Thévenin's Theorem and its application:  
 7a. (10 points) Find  $R_{TH}$  and  $V_{TH}$  of the following circuit:



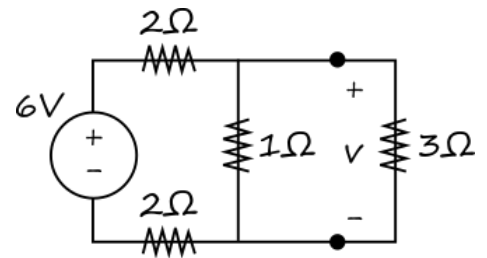- 7b. (5 points) Use the result from 7a to find the voltage  $v$  here. -----



- 7c. (10 points) In the following circuit, find the current  $i$ . (Hint: study Example 3.22 in the textbook)

