

National Taiwan Normal University
CSU0007 - Basic Electronics Homework 6

100 points total. Due on 11:59PM, Friday, 6/12/2020.

Submit your answer via Moodle. Clearly state your analysis to earn full score.

Please tweak your image files to help save some ink! For example, grey-out the background color. Thanks!

請影像處理您的作業照片以節省列印墨水 (例如把背景顏色調淡)~ 謝謝!

By default, we assume that all MOSFETs have $V_T=1$ V, $K=1$ mA/V², and we use the SCS model.

- 1 Consider the MOSFET amplifier in Figure 8.1 in the textbook.
 - 1.1 (20 points) Explain in your own words why in the small-signal model of this amplifier (Figure 8.16 in the textbook page 419), we would treat one end of the R_L as grounded (為何 R_L 的一端視為接地)?
 - 1.2 (20 points) Suppose we want to make the magnitude of the small-signal gain equal to 10, and suppose that we are given $V_S=15$ V and $R_L=15$ k Ω . What should be the value of V_I for this purpose?
 - 1.3 (20 points) Following Question 1.2, verify that with such a configuration, the MOSFET is indeed operating in the saturation region.
- 2 We have discussed the use of a *buffer* circuit to restore a distorted signal (page 63 in the lecture note; Section 6.9 in the textbook). We may implement a buffer circuit using a MOSFET circuit that is also called a *source follower* (the output signal would *follow* the change in the input signal). Before working on the following questions, be sure to study examples 7.8, 7.10, 7.11, and 8.4 in the textbook.
 - 2.1 (20 points) Consider the source-follower circuit in Figure 7.24 on page 349, and instead we suppose that $v_{IN}=3$ V, $K=1$ mA/V², and $V_T=1$ V, and that the resistor has resistance equal to 2 k Ω . Assume that the MOSFET is operating in the saturation region. Determine the value of current i_D .
 - 2.2 (10 points) Now, consider the circuit in Figure 7.45 on page 369. Suppose that we chose the DC voltage offset $V_B=5$ V and that v_A is a sinusoidal large signal. What could be the maximum possible peak-to-peak swing of v_A so that v_{OUT} will not be clipped? (Review the phenomenon of clipping on page 351 in the textbook; note that on that page the example does not have any DC voltage offset).
 - 2.3 (10 points) Now, suppose that v_A is a small signal. Further, suppose that a resistor R_L is attached to the output port, and therefore the circuit becomes as that of Figure 8.38 on page 436 in the textbook (Think of $v_I=V_B+v_A$ where v_A is a small signal). Assuming that the MOSFET operates in the saturation region, and $R_S=R_L=1$ k Ω , $V_{GS}=3$ V, $V_T=1$ V, and $K=1$ mA/V². Determine the small-signal gain $|v_o/v_i|$.

(1.1) 參考 p86 in the note.

(1.2) $\left| \frac{v_o}{v_i} \right| = 10$

$$\Rightarrow K(V_{GS}-V_T)R_L = 10$$

$$\Rightarrow 1 \times 10^{-3} (V_I - 1) \cdot 15 \times 10^3 = 10$$

$$\Rightarrow V_I \approx 1.66$$

(1.3) In this configuration,

$$V_{GS} = V_I \text{ and } V_{DS} = v_O$$

$$i_D = \frac{K(V_I - V_T)^2}{2} \approx 0.21$$

$$\text{and since } i_D = \frac{V_S - v_O}{R_L} \Rightarrow v_O = V_S - i_D R_L = 11.93$$

so indeed $V_{GS} - V_T < V_{DS}$

(2.1) $\frac{v_{OUT}}{2 \times 10^3} = \frac{1 \times 10^{-3} [(3 - v_{OUT}) - 1]^2}{2}$

$\Rightarrow v_{OUT} = 1 \text{ or } 4$ this is invalid
for saturation region
we must have

$$\Rightarrow i_D = \frac{v_{OUT}}{2 \times 10^3} = 0.5 \text{ mA}$$


$$V_{GS} \geq V_T = 1$$

$\hookrightarrow v_{IN} - v_{OUT}$


(2.2) Following Examples 7.10 and 7.11, we see that if $v_{IN} \leq 1$ the MOSFET will enter the cutoff region and v_{OUT} will equal to 0. Therefore, the maximum peak-to-peak swing of v_A is

$$(5 - 1) \times 2 = 8 \text{ V}$$


2.3

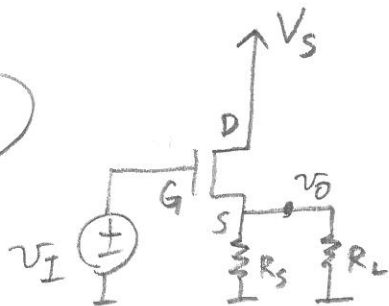





operating in the saturation region

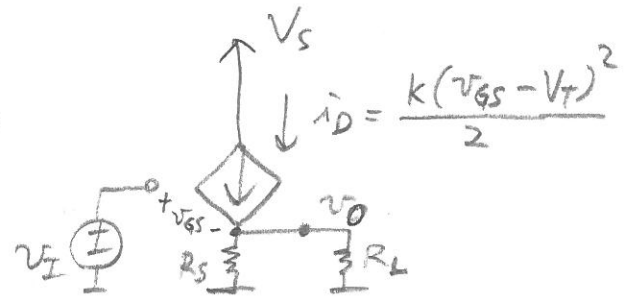

small-signal model

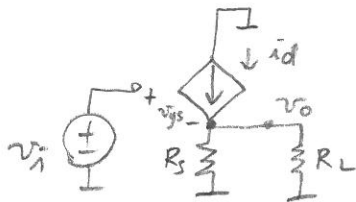

equivalently

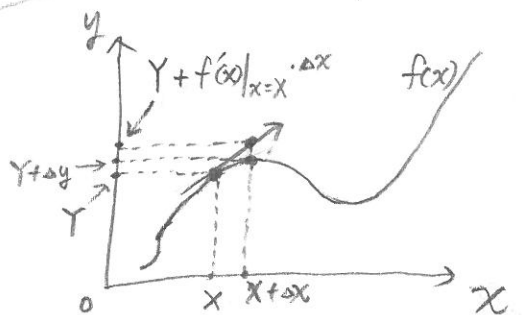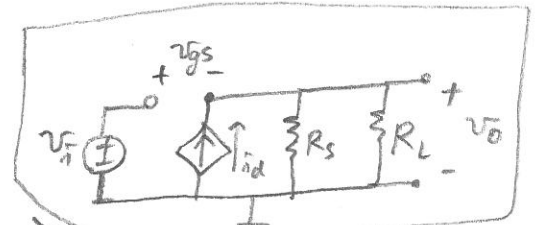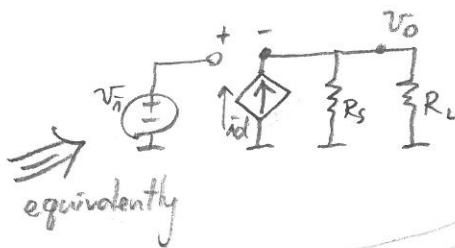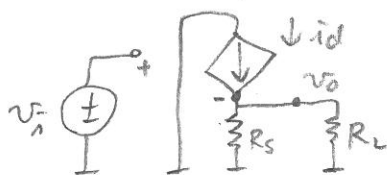

Now, let $f(v_{GS}) = i_D$, which is $\frac{k(V_{GS} - V_T)^2}{2}$

then $i_D = f'(v_{GS})|_{v_{GS}=V_{GS}} \cdot v_{GS}$

$= k(V_{GS} - V_T) \cdot v_{GS}$ where $v_{GS} = V_{GS} + v_{GS}$

define $g_m = k(V_{GS} - V_T)$

then we have $i_D = g_m \cdot v_{GS}$

($x = X + \Delta x$) think this way

then $v_o = i_D \cdot (R_s \parallel R_L)$

$= g_m \cdot v_{GS} \cdot (R_s \parallel R_L)$

$= g_m \cdot (v_i - v_o) \cdot (R_s \parallel R_L)$

$\Rightarrow v_o \left(\frac{1}{R_s \parallel R_L} + g_m \right) = g_m \cdot v_i$

$\Rightarrow \frac{v_o}{v_i} = \frac{g_m}{\frac{R_s + R_L}{R_s R_L} + g_m} = \frac{R_s R_L g_m}{R_s + R_L + R_s R_L g_m} = \frac{10^3 \times 10^3 \times [10^{-3}(3-1)]}{10^3 + 10^3 + 10^3 \cdot 10^3 \cdot [10^{-3}(3-1)]}$

$= 0.5$

Note: $\frac{v_o}{v_i} < 1$ in such a source-follower circuit also explains why it can be used as a buffer (reduce voltage level) (see P63 in the note).