
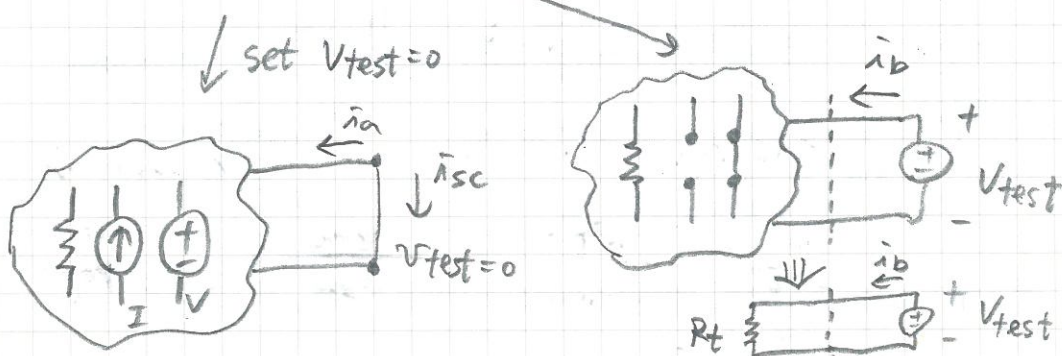

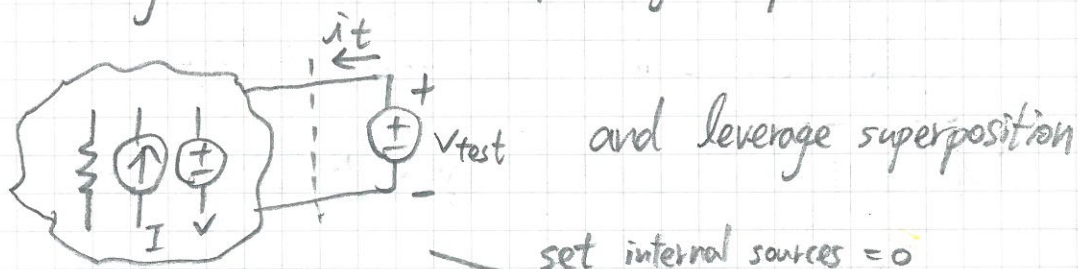
# P32 ★ Norton's Theorem


For the same goal as that of Thévenin's Theorem, here we choose to attach a testing independent voltage source to a possibly complex circuit:



$$\text{then } i_t = i_a + i_b = -i_{sc} + \frac{V_{test}}{R_t}$$

$$\Rightarrow i_t + i_{sc} - \frac{V_{test}}{R_t} = 0$$

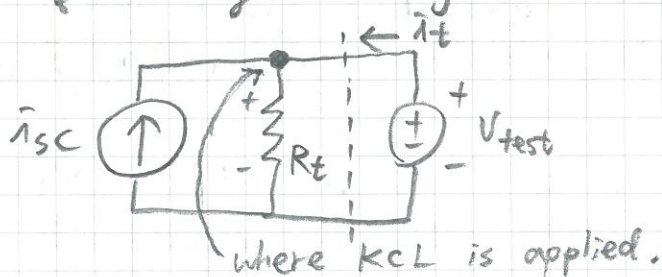Think of above in terms of KCL, then, equivalently the original circuit is like




And  $R_t = R_{TH}$ , since we applied same procedure of decomposition as we did in Thévenin's Theorem.

## Relation between

Norton's Equivalent Circuit

and

Thévenin's Equivalent Circuit:

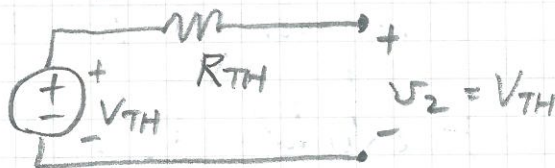

since  $V_1 = V_2$ , we have

$$i_{sc} \cdot R_t = V_2 = V_{TH}$$

$$\Rightarrow R_t = \frac{V_{TH}}{i_{sc}} = \frac{V_{oc}}{i_{sc}}$$

(recall that  
 $V_{TH} = V_{oc}$   
 page 28)

in other word,

$$\text{等效電阻} = \frac{\text{開路電壓}}{\text{短路電流}}$$


Example: find  $V = ?$




approach ①: voltage divider

$$V = 3 \times \frac{2}{1+2} = 2V$$

approach ②: Thévenin's Theorem

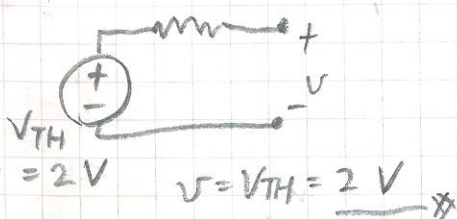


approach ③: Norton's Theorem

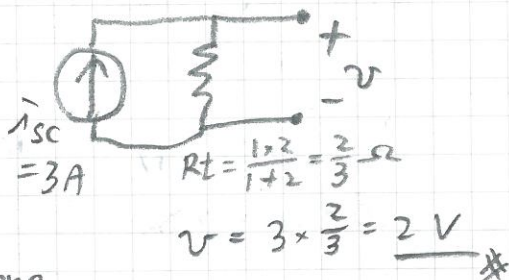


$\Rightarrow$  these three agree in one.




P34 Example: find  $V_{xy} = ?$

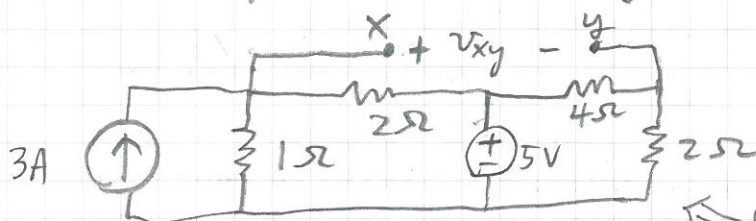

Using Norton's Theorem, we have:

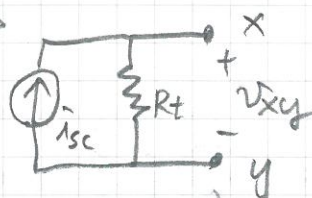

Now, to calculate  $R_t$ :

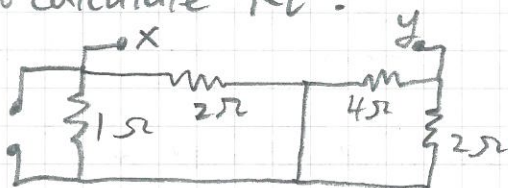


$$R_t = (1\Omega // 2\Omega) + (4\Omega // 2\Omega) = 2\Omega$$

To calculate  $i_{sc}$ , we may use superposition:

$$i_{sc} = i_{sc1} + i_{sc2}$$


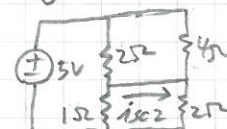
$$i_{sc1} = 3 \times \frac{\frac{2}{3}}{\frac{2}{3} + \frac{4}{3}} = 1A$$




from KCL, we may see that  $i_{sc2} = 0$

therefore,  
 $i_{sc} = 1A$

$$V_{xy} = i_{sc} \times R_t = 2V$$

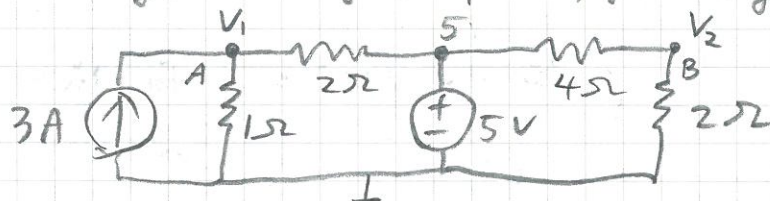Alternatively, we may compute  $V_{xy}$  directly, using the node analysis method:



$$\text{KCL at node A: } 3 + \frac{0 - V_1}{1} + \frac{5 - V_1}{2} = 0 \Rightarrow V_1 = \frac{11}{3}$$

$$\text{KCL at node B: } \frac{5 - V_2}{4} + \frac{0 - V_2}{2} = 0 \Rightarrow V_2 = \frac{5}{3}$$


$$V_{xy} = V_1 - V_2 = \frac{11}{3} - \frac{5}{3} = 2V$$

P35

From the above example, we see that in order to use Norton's Theorem correctly, we need to be very careful when determining the short-circuit current  $\hat{i}_{sc}$ .

KCL is a great tool here to help us.

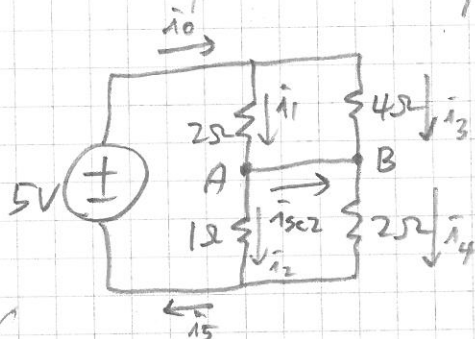To be specific, when we were determining  $\hat{i}_{sc2}$  in the previous example:




Applying KCL at nodes A and B, we have

$$\hat{i}_{sc2} = \hat{i}_2 - \hat{i}_1$$

$$\hat{i}_{sc2} = \hat{i}_4 - \hat{i}_3$$

The above two equalities must hold, and we can use one of them to calculate  $\hat{i}_{sc2}$  and then use the other one to verify our answer.

equivalently

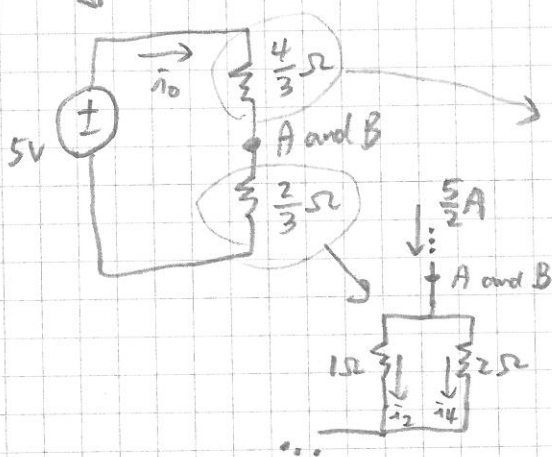

$$\text{Hence, } \hat{i}_0 = \frac{5}{\frac{4}{3} + \frac{2}{3}} = \frac{5}{2} \text{ A}$$

according to Ohm's law.

$$\hat{i}_1 = \hat{i}_0 \times \frac{4}{2+4} = \frac{5}{3} \text{ A}$$


$$\hat{i}_3 = \hat{i}_0 \times \frac{2}{2+4} = \frac{5}{6} \text{ A}$$

$$\hat{i}_2 = \frac{5}{2} \times \frac{2}{1+2} = \frac{5}{3} \text{ A}$$

$$\hat{i}_4 = \frac{5}{2} \times \frac{1}{1+2} = \frac{5}{6} \text{ A}$$
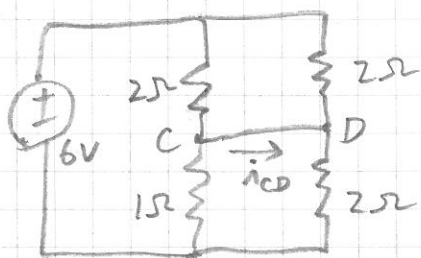
#

Interestingly, if we have the following circuit instead, the current flowing from node C to node D would be non-zero:




You can verify, as an exercise, that  $i_{CD} = -\frac{3}{5} \text{ A}$

In essence, the condition to have no current flowing from node X to node Y is to have the node voltage at node X equal to that at node Y. Starting from here and using the symbolic computation, you might rediscover the "Wheatstone Bridge" circuit :)


One final note on circuit transformation:

When we are using either Thévenin's Theorem or Norton's Theorem to transform a circuit into its equivalence, it is possible that we might define the  $V_{oc}$  or  $i_{sc}$  variable in the direction opposite to what's really happening in the circuit, since for a complex circuit we might not readily perceive the real direction of the voltage or current. But that's fine, because our computed result will have a negative sign if the direction was wrong.

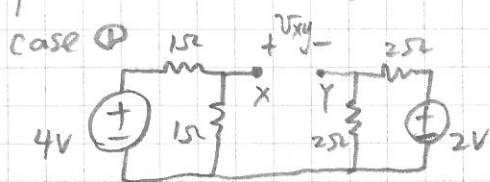Example: determine  $V_{xy}$  in these two cases:



(ans:  $V_{xy} = 1 \text{ V}$ )

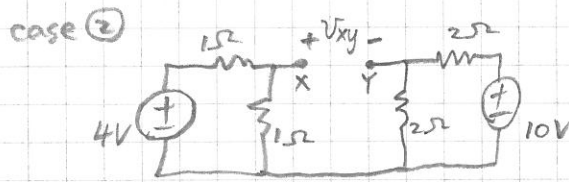

(ans:  $V_{xy} = -3 \text{ V}$ )