

Solution

National Taiwan Normal University  
Department of Computer Science and Information Engineering  
CSU0007 - Basic Electronics

Homework 1

(Five questions. 100 points total. Due on 10PM, Tuesday, 3/17/2020. Submit your answer via Moodle)  
Clearly state each step of your calculation to receive full score.


1. (15 points) Let  $r$  be the resistance of a linear planar resistor with width=length= $5 \times 10^{-6}$ m and thickness of  $10^{-6}$ m. What are the resistance of the following resistors of the same material (and of the same thickness)?

1a. (5 points)

1b. (5 points)

1c. (5 points) (Hint: study Example 2.21 in the textbook)


$$R = \rho \frac{l}{a}$$

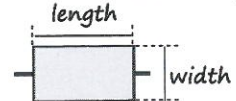

1a.  $r$

1b. 串聯  $\frac{1}{5}r + r = \frac{6}{5}r$

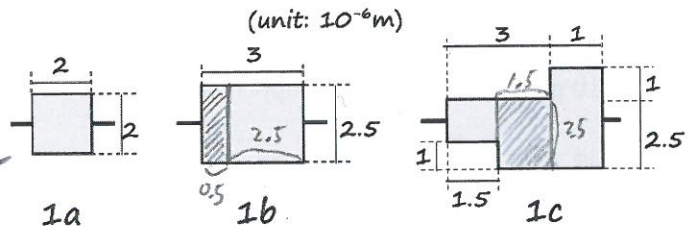1c. 三個串聯  $1.5r + \frac{1.5}{2.5}r + \frac{1}{3.5}r = \frac{161}{90}r$



2. (20 points) Mr. Wang was learning to make some yogurt. In the making process, it is critical to make sure the temperature of the yogurt stays between  $32.2^\circ\text{C}$  and  $48.9^\circ\text{C}$ . He used an Arduino Uno (<https://store.arduino.cc/usa/arduino-uno-rev3>) to monitor the temperature. His Arduino Uno consumes 250mW of power in average.

2a. (10 points) For how long can a full 5V, 500mAh battery sustain this Arduino Uno? (Hint: study the related example in note1 for lecture on 3/2/2020)

2b. (10 points) To keep powering the Arduino Uno for a whole week, what is the minimum required battery capacity (in terms of mAh)?

2a.  $5 \times 500 \times 10^{-3} = 2.5 \text{ Wh}$

$$\frac{2.5}{250 \times 10^{-3}} = 10 \text{ hours} *$$

2b. power demand

$$= 24 \times 7 \times 250 = 42000 \text{ mWh}$$

for a 5V battery, the capacity should be at least  $42000/5 = 8400 \text{ mAh}$  \*

3. (20 points) Mrs. Wang brought an LED light for her night reading. Within the light there is a resistor with resistance  $R = 1\text{k}\Omega$ . The resistor can dissipate a maximum of 0.4W of power, and it will overheat if the power dissipation exceeds 0.4W.

3a. (10 points) Mrs. Wang used a battery rated at 7.2V to power the LED light. Would that overheat the light? (Hint: study Example 1.16 in the textbook)

3b. (10 points) Mr. Wang Jr. plugged the light into a 110V wall plug. Would that overheat the light?

3a.  $P = VI = V \left( \frac{V}{R} \right) = \frac{V^2}{R}$

$$= \frac{7.2^2}{10^3} = 51.84 \text{ mW} < 0.4 \text{ W} \Rightarrow \text{safe}$$

3b.  $P = \frac{110^2}{10^3} = 12.1 \text{ W} > 0.4 \text{ W} \Rightarrow \text{that would overheat the light!}$

4. (30 points) In the following, use KCL and KVL to determine the branch current and branch voltage with respect to each lumped element.

4a. (10 points) In Figure 4a, suppose  $i_1=5A$ ,  $i_2=2A$ ,  $i_5=4A$ ,  $i_8=1A$ . Determine  $i_3$ ,  $i_4$ ,  $i_6$ , and  $i_7$ .

using KCL:

node A:  $i_1 + i_4 + i_5 = 0 \Rightarrow i_4 = -9A$

node B:  $i_7 - i_5 - i_8 = 0 \Rightarrow i_7 = 5A$

node C:  $i_6 + i_8 - i_2 = 0 \Rightarrow i_6 = 1A$

node D:  $-i_3 + i_2 - i_1 = 0 \Rightarrow i_3 = -3A$

可用其它 node 驗算, 例如 node E:  $i_3 - i_4 - i_7 - i_6 = 0$

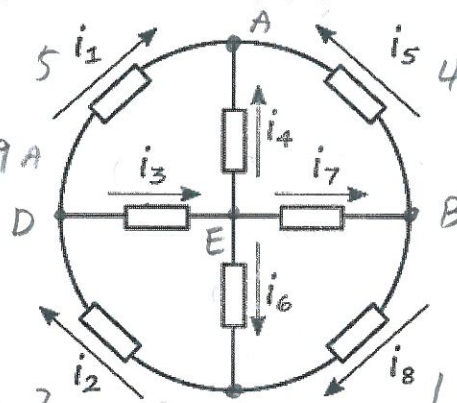


Figure 4a

4b. (10 points) In Figure 4b, suppose  $v_1=6V$ ,  $v_2=3V$ ,  $v_6=2V$ ,  $v_8=1V$ . Determine  $v_3$ ,  $v_4$ ,  $v_5$ , and  $v_7$ .

using KVL:

loop  $l_1$ :  $v_2 + v_1 + v_5 - v_8 = 0 \Rightarrow v_5 = -8V$

loop  $l_2$ :  $v_2 - v_3 + v_6 = 0 \Rightarrow v_3 = 5V$

loop  $l_3$ :  $v_1 - v_4 + v_3 = 0 \Rightarrow v_4 = 11V$

loop  $l_4$ :  $v_4 + v_5 - v_7 = 0 \Rightarrow v_7 = 3V$

loop  $l_5$  驗算:  $v_6 + v_8 - v_7 = 0$

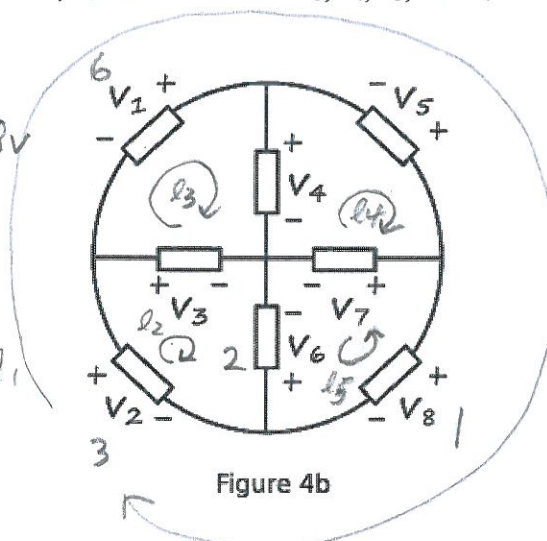


Figure 4b

4c. (10 points) In Figure 4c, suppose  $i_1=3A$  and  $R_2=15\Omega$ . Determine  $v_1$ ,  $v_2$ ,  $R_1$ , and  $i_2$ .

using KVL for loop  $l_1$ , we see

$$v_1 = v_2$$

using KVL for loop  $l_2$ , we see

$$v_1 = 30V, \text{ thus } v_2 = 30V$$

using Ohm's law,

$$R_1 = \frac{v_1}{i_1} = \frac{30}{3} = 10\Omega$$

$$i_2 = \frac{v_2}{R_2} = \frac{30}{15} = 2A$$


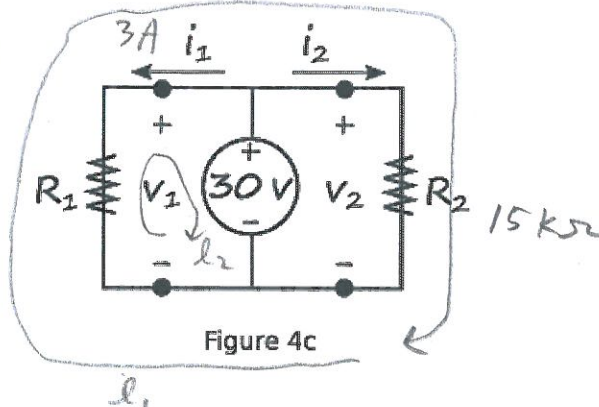


Figure 4c

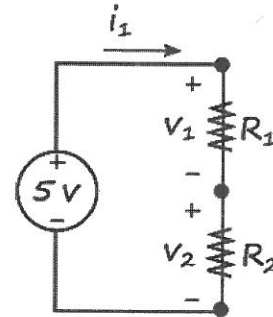5. (15 points) Consider the following voltage dividers.

5a. (10 points) Suppose  $R_1=7k\Omega$  and  $R_2=8k\Omega$ . What is the branch voltage across resistor  $R_2$ ?

$$V_2 = \frac{R_2}{R_1 + R_2} \times 5V = \frac{8}{3} V$$



5b. (5 points) Suppose  $R_1=10k\Omega$ . If we want to have a branch voltage of 3V across resistor  $R_2$ . What should be the resistance of  $R_2$ ?

$$\begin{aligned} 3 &= \frac{R_2}{R_1 + R_2} \times 5 \\ &= \frac{R_2}{10 + R_2} \times 5 \end{aligned}$$

$$\Rightarrow 30 + 3R_2 = 5R_2$$

$$\Rightarrow R_2 = 15 k\Omega$$

