

Solution sketch

National Taiwan Normal University
Department of Computer Science and Information Engineering
CSU0007 - Basic Electronics

Homework 3


100 points total. Due on 9AM, Monday, 5/11/2020.

Submit your answer via Moodle. Clearly state your analysis to earn full score.

1 (40 points) Answer the following two questions:

- 1.1 (20 points) In the midterm exam, the corrected answer of Question 5c shows that $v_D = 1.75V$, not $2V$. Why does the voltage across the diode become smaller than $2V$? State your qualitative opinion.
- 1.2 (20 points) For the following circuit, apply the small-signal analysis to find current i_D . Recall that you may apply Thévenin's theory to help simplify the analysis.

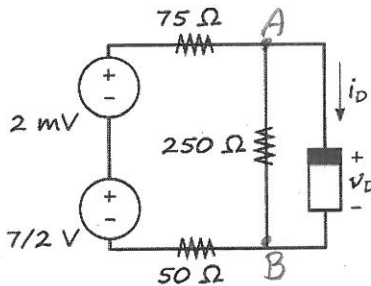1.1 In general, 並聯後的等效電阻值會下降, and thus voltage divider 分到的電壓會較低.



$$i_D = \begin{cases} K \cdot v_D^2 & \text{for } v_D > 0 \\ 0 & \text{otherwise} \end{cases}$$


Assuming $K = 1 \text{ mA/V}^2$

Now, by small signal analysis

$$r_d = \frac{1}{2K v_D} \bigg|_{v_D=2} = \frac{1}{2 \times 1 \times 2} = \frac{1}{4} \text{ k}\Omega = 250 \Omega$$

$$\Rightarrow \bar{i}_{D2} = \frac{2 \text{ mV} \times \frac{250 \parallel 250}{75 + 50 + 250 \parallel 250}}{250} = 4 \mu\text{A}$$

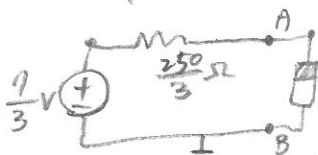1.2 Using Thévenin's theory, we see the following is an equivalence: (with respect to the $7.2V$ signal)



and by analysis we know $v_D > 0$

Now, by KCL + element law:

$$\frac{7.2 - v_D}{\frac{250}{3}} = i_D = K \cdot v_D^2$$

$$\Rightarrow v_D = 2V$$

$$\Rightarrow \bar{i}_{D1} = 4 \text{ mA}$$

$$\Rightarrow \bar{i}_D = \bar{i}_{D1} + \bar{i}_{D2} = 4.004 \text{ mA}$$

2 (60 points) Answer the following two questions regarding the mapping between voltage levels and logic values in the static discipline, given thresholds $V_{IL}=1.8V$, $V_{IH}=2.3V$, $V_{OL}=1V$, and $V_{OH}=4V$, and assume the highest voltage level is $5V$:

- 2.1 (30 points) Suppose a sender sent a logic 0 by placing $V_{OUT}=0.9V$, and the noise during transmission added $0.7V$ to the signal. Would its receiver be able to correctly interpret the signal as a logic 0? Give a quantitative reason.
- 2.2 (30 points) For the electronic system working under the given static discipline, can the following electronic device work correctly with the system? The device produces voltage level $V_{OUT}=0.8V$ for sending a logic 0 and $V_{OUT}=4.5V$ for sending a logic 1. The device will interpret all input signals between $0V$ and $2V$ as a logic 0 and all input signals between $2.5V$ and $5V$ as a logic 1. Show your quantitative analysis.

2.1 Yes. $0.9 + 0.7 = 1.6 < V_{IL}$.

2.2 No. ✓(1) $0.8V < V_{OL}$

✓(2) $4.5V > V_{OH}$

✓(3) $0V \sim 2V$ as a logic 0 \Rightarrow it can interpret V_{IL} and below as a logic 0.

X(4) $2.5V \sim 5V$ as a logic 1 \Rightarrow it might not interpret $2.3V \sim 2.5V$ as a logic 1.