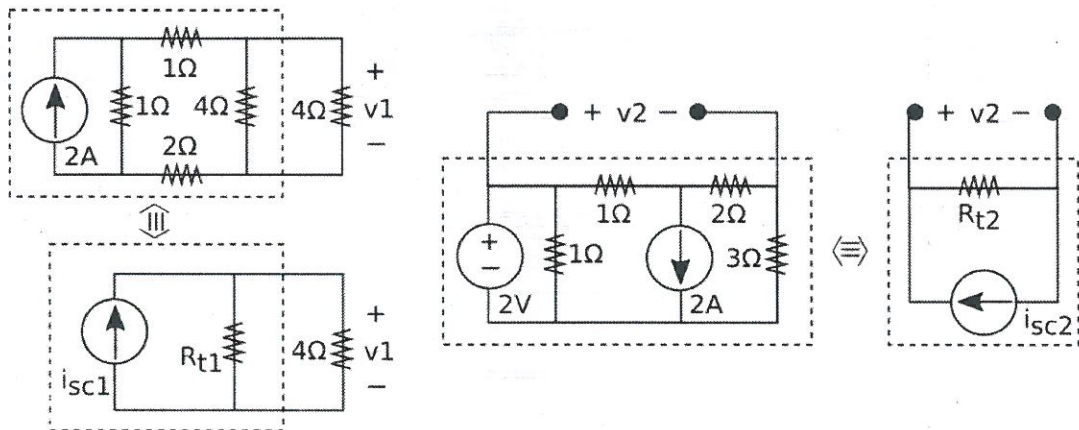


Solution attached

CSU0007 Basic Electronics, Homework 3


- **IMPORTANT!!** Submit your work via Moodle **before 9AM, Nov 10th, 2020**. We will have a review session on Nov 10th in class. The midterm exam will be on Nov 13th in class.
- Four questions in total. Please clearly label your answer for each question, and clearly state your calculation steps.

1. (42 points) Use Norton's Theorem to find $\{i_{sc1}, R_{t1}, v_1\}$ and $\{i_{sc2}, R_{t2}, v_2\}$. 7 points for each variable.




2. (40 points) For the following nonlinear circuits,

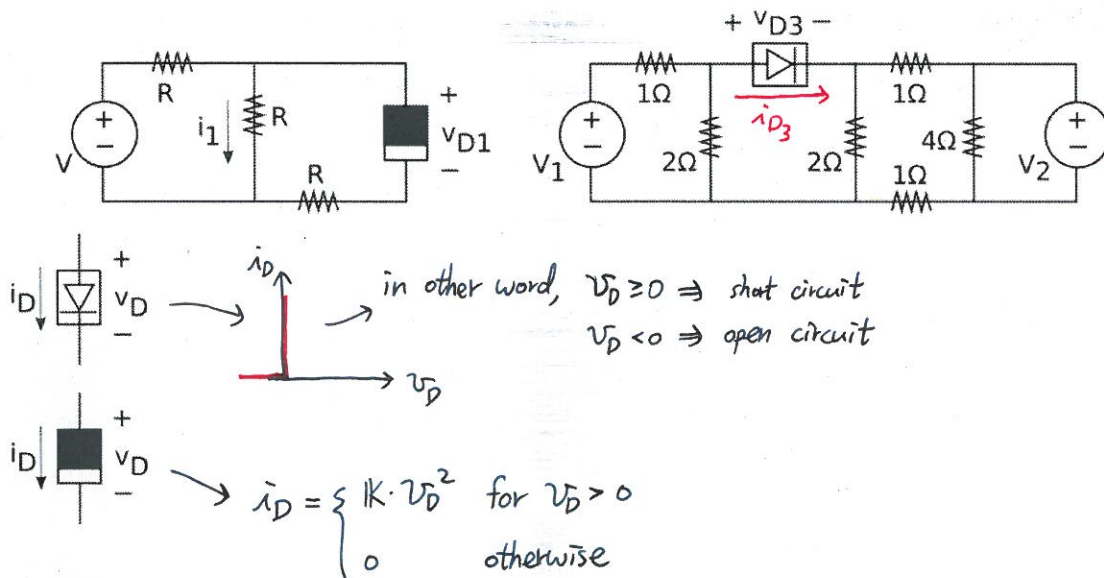1. (20 points) use the analytical method to determine v_{D1} and i_1 (the method is covered in class and is described in Section 4.2 in the textbook);
2. (20 points) if $0 < 2V_2 < V_1$, what would be the value of i_{D3} ? Use the piecewise analysis method.




3. (10 points) Use the graphical analysis method to explain the following property: Let $v_{I1} > 0$ and $v_{I2} > 0$, and such that v_{I1} caused v_{D1} and v_{I2} caused v_{D2} . Then we have $\Delta v_I > \Delta v_D$ where $\Delta v_I = |v_{I1} - v_{I2}|$ and $\Delta v_D = |v_{D1} - v_{D2}|$. Illustrate and use your own word to explain why $\Delta v_I > \Delta v_D$.

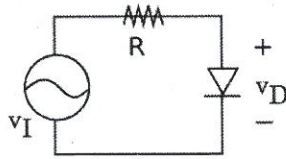


4. (8 points) In class we've talked about an approach to determine R_{TH} in Thevenin's Theorem by using a potentiometer (i.e., a variable resistor 可變電阻). Now, with the additional help of Norton's Theorem, we may determine R_{TH} without using any potentiometer. Think about it and describe an approach to determine R_{TH} by only using a multimeter (i.e., a volt-ohm-milliammeter 三用電表).

①

PART I

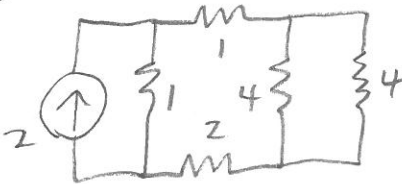

from

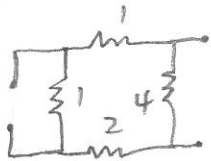

$$R_{t1} = \frac{4 \times (1+1+2)}{4 + (1+1+2)} = 2 \Omega$$

from




$$\bar{I}_{SC1} = 2 \times \frac{1}{1 + (1+2)} = \frac{1}{2} A$$

$$V_1 = \left(\frac{1}{2} \times \frac{2}{4+2} \right) \times 4$$



$$= \frac{2}{3} V$$





PART II

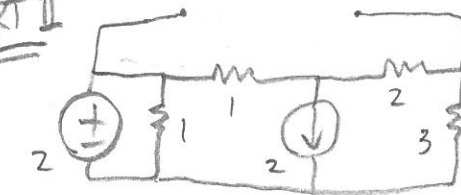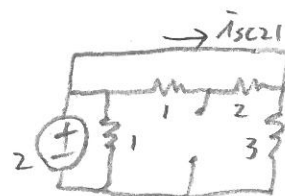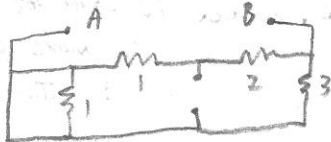 $\bar{I}_{SC2} = \bar{I}_{SC21} + \bar{I}_{SC22}$ by superposition

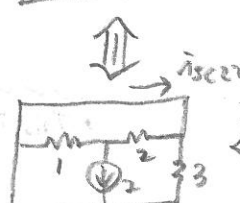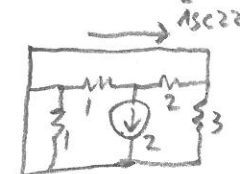
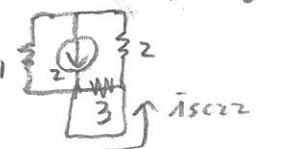
from




$$\bar{I}_{SC21} = \frac{2}{3} A$$



$$\bar{I}_{SC22} = 2 \times \frac{1}{1+2} = \frac{2}{3} A$$



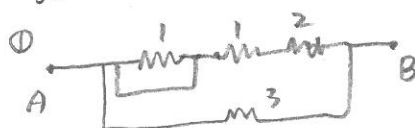
There are at least two ways to analyze this:



short circuit has resistance = 0

$$\Rightarrow R_{t2} = \frac{3 \times \left(\frac{1 \times 0}{1+0} + 1+2 \right)}{3 + \left(\frac{1 \times 0}{1+0} + 1+2 \right)} = \frac{3}{2} \Omega$$

②

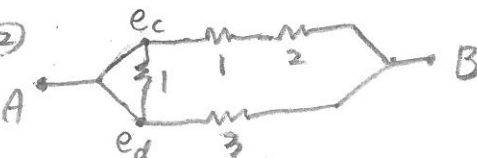

Since node voltage $e_c = e_d$


there will be no current flowing through $\frac{1}{2} \Omega$ if we attached A, B with a voltage source.

so, equivalently, it is like



$$R_{t2} = \frac{3}{2} \Omega$$

5

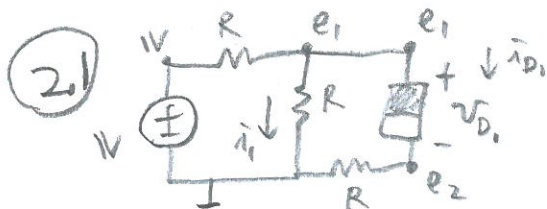

first of all, observe that v_{D1} must be larger than zero.

$$i_1 = \frac{e_1}{R} = \frac{v_{D1} + e_2}{R} = \frac{v_{D1} + R K v_{D1}^2}{R}$$

$$= \frac{-2 + \sqrt{4 + 12 K V R}}{6 K R^2} + K \left(\frac{-2 + \sqrt{4 + 12 K V R}}{6 K R} \right)^2$$


$$= \frac{-2 + \sqrt{4 + 12 K V R}}{6 K R^2} + \frac{4 + (4 + 12 K V R) - 4 \sqrt{4 + 12 K V R}}{36 K R^2}$$

$$= -\frac{1}{3} \frac{1}{K R^2} + \frac{2}{9} \frac{1}{K R^2} + \frac{V}{3 R} + \frac{1}{18} (\sqrt{4 + 12 K V R}) / (K R^2)$$

$$\Rightarrow i_1 = -\frac{1}{9} \frac{1}{K R^2} + \frac{V}{3 R} + \frac{1}{18} (\sqrt{4 + 12 K V R}) / (K R^2) \quad \leftarrow \text{equation 2}$$

A way to verify our derivation is to plug in some good numbers and analyze the circuit with those numbers.

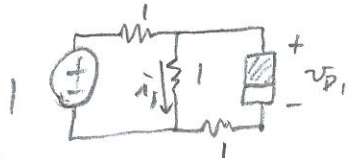For example, let $K=1$, $V=1$, $R=1$ we have $v_{D1} = \frac{-2 + \sqrt{4 + 12}}{6} = \frac{1}{3} \text{ V}$



$\Rightarrow i_{D1} = \frac{1}{9} \text{ mA}$
This is actually a poor choice in this case, because it could not catch the above error.

$$i_1 = \left(\frac{1}{3} + \left(\frac{1}{9} \times 1 \text{ k}\Omega \right) \right) / 1 \text{ k}\Omega = \frac{4}{9} \text{ mA}$$


A better choice we should pick $K \neq V \neq R$.

and $i_1 = -\frac{1}{9} \left(\frac{1}{1 \times 1^2} \right) + \frac{1}{3 \times 1} + \frac{1}{18} \sqrt{4 + 12 \cdot 1 \cdot 1 \cdot 1}$

$$= -\frac{1}{9} + \frac{1}{3} + \frac{2}{9} = \frac{4}{9} \text{ mA}$$

which gives us some assurance that equation 2 is the correct result given that equation 1 is correct.

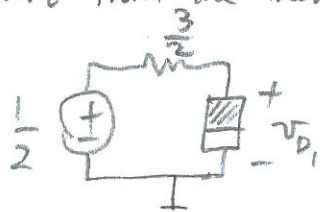To see that equation 1 is correct (and for the sake of practice), we can start from the Thévenin's equivalence:



and use the node analysis

$$\begin{cases} \frac{3}{2} i_D + v_{D1} = \frac{1}{2} \\ i_D = v_{D1}^2 \end{cases} \Rightarrow v_{D1} = \frac{1}{3} \text{ V}, \text{ which is the same as we plugged those numbers into equation 1.}$$


2.2

First of all, we need to determine


whether we can replace  by 

or we can replace  by 

We analyze this by first taking away :

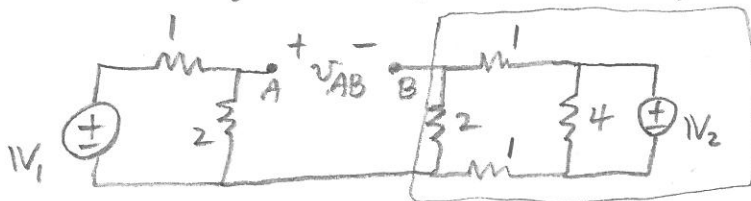

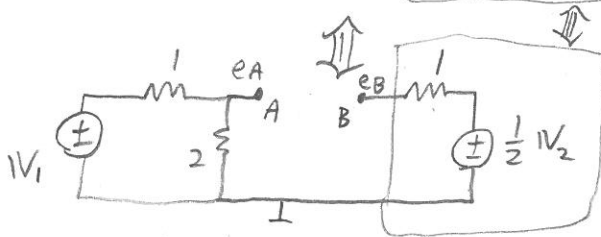

→ we may use Thevenin Theorem to simplify this part.




Then we may use either the node analysis method or superposition to obtain that $V_{AB} = \frac{2}{3}V_1 - \frac{1}{2}V_2$.

Given condition $0 < 2V_2 < V_1$, we have $V_{AB} = \frac{2}{3}V_1 - \frac{1}{2}V_2$
 $\Rightarrow V_1 > 2V_2$ $> \frac{4}{3}V_2 - \frac{1}{2}V_2 > 0$

Thus, we now see we should consider  as  because the $i-v$ characteristic of the diode told us so.

Now we are ready to compute i_{D3} !

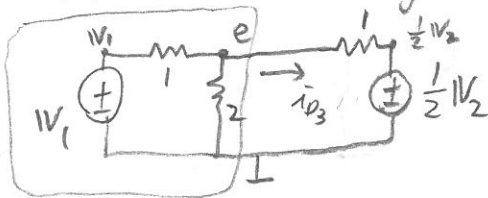

alternatively, you may transform the circuit further:




$$\begin{cases} \frac{V_1 - e}{1} = \frac{e - 0}{2} + \frac{e - \frac{1}{2}V_2}{1} \\ i_{D3} = \frac{e - \frac{1}{2}V_2}{1} \end{cases}$$

$$\Rightarrow \begin{cases} 2V_1 - 2e = e + 2e - V_2 \\ i_{D3} = e - \frac{1}{2}V_2 \end{cases}$$

$$\Rightarrow \begin{cases} e = \frac{1}{5}(2V_1 + V_2) \\ i_{D3} = \frac{2}{5}V_1 - \frac{3}{10}V_2 \end{cases}$$

$$i_{D3} = \frac{\frac{2}{3}V_1 - \frac{1}{2}V_2}{\frac{2}{3} + 1} = \frac{2}{5}V_1 - \frac{3}{10}V_2$$


③

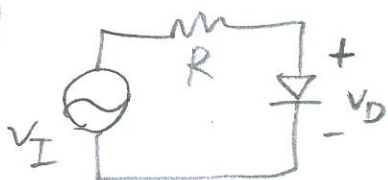

Let $f(V_D)$ be the branch current flowing through ∇ (i.e., i_D)

By KCL we have $\frac{V_I - V_D}{R} = f(V_D)$

Therefore we have

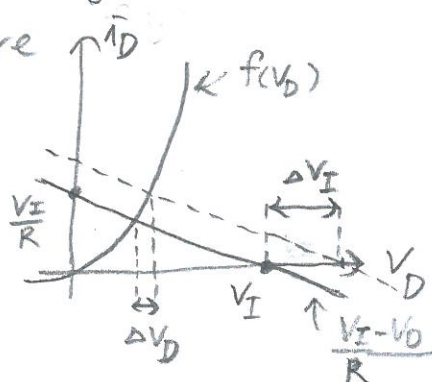

$$\Delta V_I > \Delta V_D$$

because the tangent slope of $f(V_D)$ for all $V_D > 0$ is larger than zero.

④

Refer to page 33 of the Lecture note.

Because $R_{TH} = \frac{V_{open-circuit}}{I_{short-circuit}}$, it is sufficient

to just measure $V_{open-circuit}$ and $I_{short-circuit}$:)