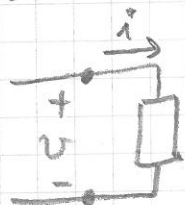





# $P_9$ - Associated Variable Convention: (約定俗成)

For a two-terminal lumped element,  
define current to flow in at the element  
terminal assigned to be positive in voltage.



$v$  and  $i$  are called  
"terminal variables."

Example:

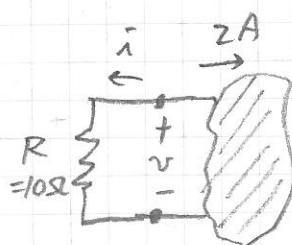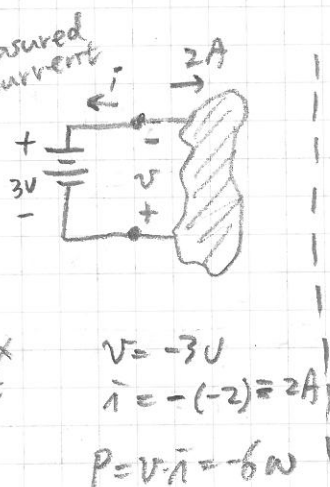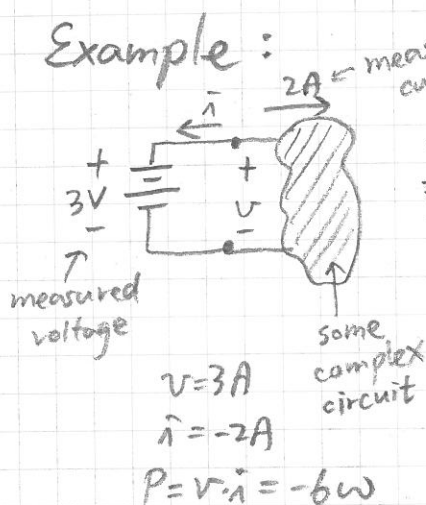


$$\begin{aligned}
 i &= -2A \\
 v &= iR = -20V \\
 P &= v \cdot i = 40W
 \end{aligned}$$

⇒ power supplied "from" battery  
by

⇒ power supplied  
"to" resistor  
(and then is  
dissipated in  
the form of heat)

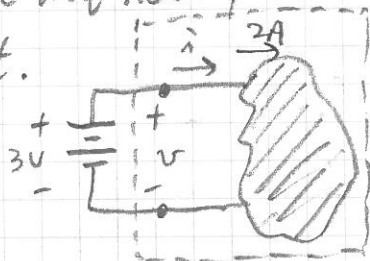Note that the above is from the  
viewpoint of the battery; from the  
viewpoint of that complex circuit,  
you may try and see that now power  
is supplied "to" it.




P10 Section 1.8 in the textbook mentioned sinusoidal signals and the root mean square value. For your interest, the  $\sqrt{2}$  ratio between the amplitude of a sinusoidal signal and its rms value comes from 三角函数 2 倍角轉換.

Example: let signal  $i(t) = I_m \cos(\omega t)$


$$\begin{aligned}
 i_{rms} &= \sqrt{\frac{1}{T} \int_0^T i^2(t) \cdot dt} \\
 &= \sqrt{\frac{1}{T} \int_0^T (I_m^2 \cos^2 \omega t) dt} \\
 &= \sqrt{\frac{I_m^2}{2T} \int_0^T (1 + \cos 2\omega t) dt} \\
 &= \frac{I_m}{\sqrt{2}} \sqrt{\frac{1}{T} \int_0^T (1 + \cos 2\omega t) dt} \\
 &= \frac{I_m}{\sqrt{2}} \quad \text{※}
 \end{aligned}$$

## ★ Resistive Networks and How to Analyze Them

### - Terminology

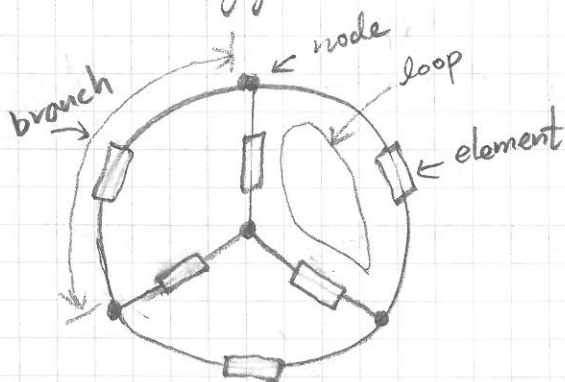

ideal wire: no resistance

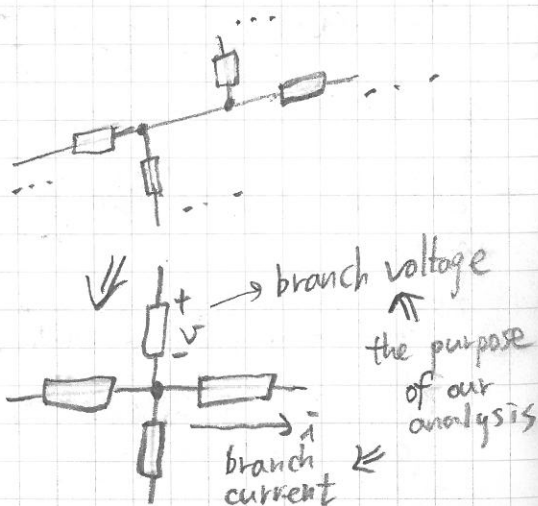

# - Kirchhoff's Laws $\begin{cases} \text{KCL} \\ \text{KVL} \end{cases}$


P11

following LMD, Kirchhoff's laws are simplifications of Maxwell's Equations (see Appendix A.2 in the textbook)

→ KCL and KVL are extremely useful tools to help us analyze a circuit!
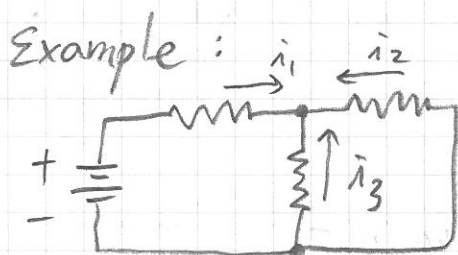
## KCL: Kirchhoff's current law

The algebraic sum of all branch currents flowing into any node must be zero.



$$\sum_{n=1}^3 \hat{i}_n = 0$$

$$\sum_{n=1}^3 (-\hat{i}_n) = 0$$


In general, for integers  $N, M$ , we have

$$\sum_{n=1}^N \hat{i}_n = 0 \Rightarrow \sum_{n=1}^M \hat{i}_n + \sum_{n=M+1}^N \hat{i}_n = 0$$

$$\Rightarrow \sum_{n=1}^M \hat{i}_n = \sum_{n=M+1}^N (-\hat{i}_n)$$

⇒ Sum of total current flowing into a node

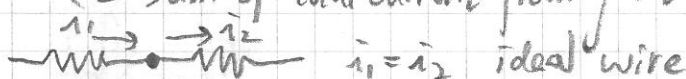= sum of total current flowing out from a node.



P12

Example:


Using KCL

node A:  $0 = -\hat{i}_1 - \hat{i}_2 - \hat{i}_3$

B:  $0 = \hat{i}_1 + \hat{i}_4 - \hat{i}_6$

C:  $0 = \hat{i}_2 - \hat{i}_4 - \hat{i}_5$

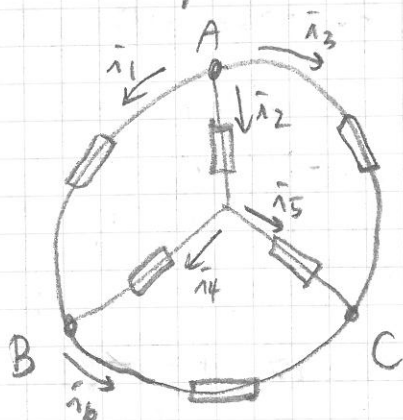
D:  $0 = \hat{i}_3 + \hat{i}_5 + \hat{i}_6$




Suppose  $\hat{i}_1 = 1, \hat{i}_3 = 3 \Rightarrow \hat{i}_2 = -4$

In addition, suppose  $\hat{i}_5 = -2$

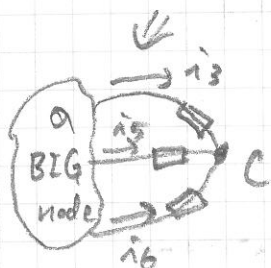$\Rightarrow \hat{i}_4 = -2, \hat{i}_6 = -1$



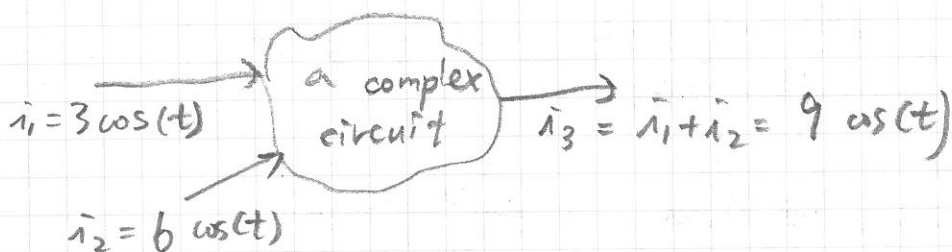
In general, for  $N$  KCL statements, only  $N-1$  of them are independent. Therefore, we need  $N-1$  known values to solve the circuit.



KVL: Kirchhoff's voltage law


The algebraic sum of the branch voltages around any loop (i.e., closed path) in a network must be zero.

Examples:

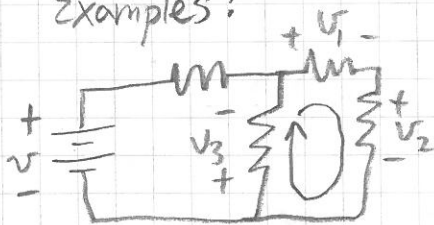

$$\sum_{n=1}^3 V_n = 0$$

並聯 (Parallel)

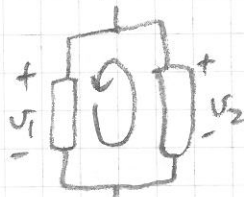


$$0 = V_1 - V_2 \Rightarrow V_1 = V_2$$

串聯 (Series)



$$0 = -V + V_1 + V_2 \Rightarrow V = V_1 + V_2$$

Example:

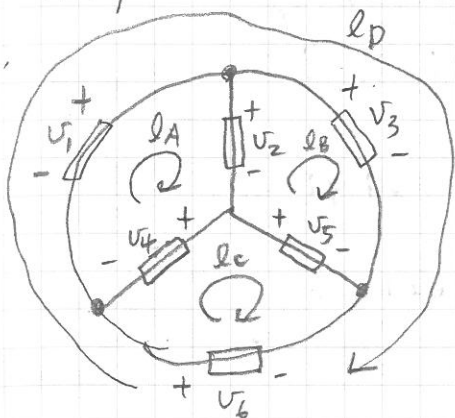

using KVL

loop  $l_A$ :  $0 = -V_1 + V_2 + V_4$


$l_B$ :  $0 = -V_2 + V_3 - V_5$

$l_C$ :  $0 = -V_4 + V_5 - V_6$

$l_D$ :  $0 = -V_1 + V_3 - V_6$

Suppose that  $V_1 = 1$ ,  $V_3 = 3$ ,  $V_2 = 2$   
then  $V_4 = -1$ ,  $V_5 = 1$ ,  $V_6 = 2$

Example:

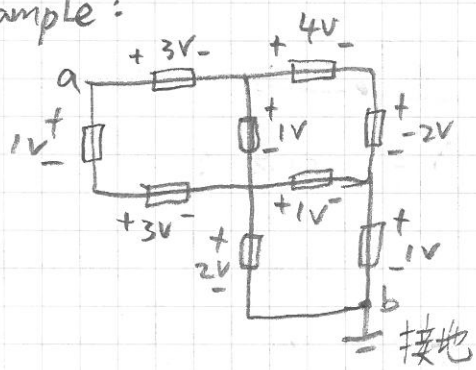

$V_{ab}$  can be determined using KVL


(which loop(s) would you pick?)

$V_{ab} = 6 \text{ V.}$


In general, we model individual elements based on LMD assumptions and we analyze a circuit of elements using KCL and KVL.

★ Two more basic elements and their  $i-v$  characteristics


① Independent voltage source

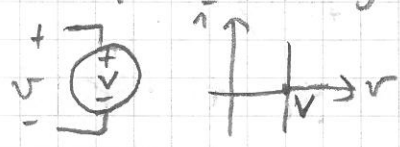

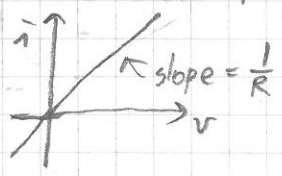for linear resistor it obeys Ohm's law  $R = \frac{v}{i}$



② Independent current source

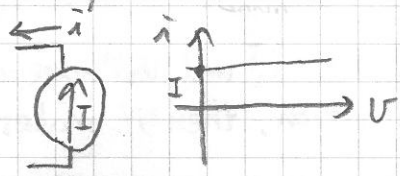





P14

# ★ Basic Method to Analyze A Circuit

four steps

- 1° define branch current and voltage consistently see Page 9
- 2° apply element laws for each elements  
(e.g., Ohm's law for linear resistors)
- 3° apply KCL and KVL
- 4° jointly solve the equations obtained from 2° and 3°

Example :

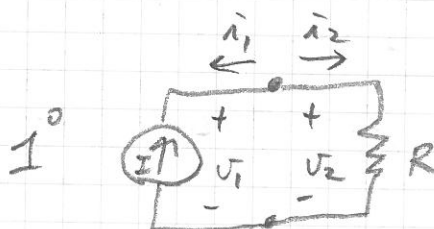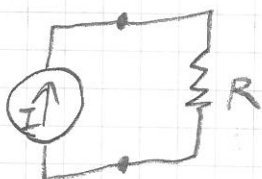

2°  $i_1 = -I$ ,  $v_2 = i_2 \cdot R$

3° KCL  $\Rightarrow i_1 + i_2 = 0$


KVL  $\Rightarrow -v_1 + v_2 = 0$

4°  $i_2 = -i_1 = I$

$v_2 = i_2 R = IR$

$v_1 = v_2 = IR$  \*

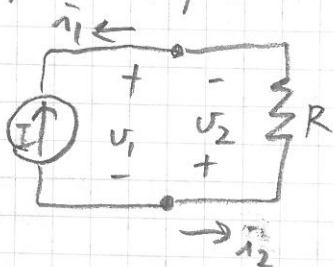if at step 1° we define  $v_2$  inversely, we must




also define  $i_2$  inversely, to be consistent. Applying the basic method you will find

$i_2 = -I$  and  $v_2 = -IR$ . This may seem to be strange. But if we recall that both  $i_2$  and  $v_2$  have a reversed direction, then it makes sense.

Alternatively, we may solve a circuit by considering "Energy conservation".

Example:

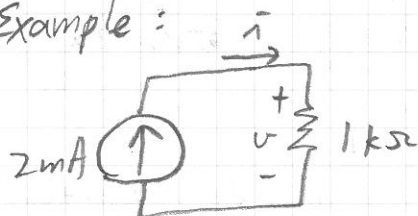

power out from the source:

$$P_{out} = 2mA \times V$$

power into the resistor:


$$P_{in} = i \times V = \frac{V^2}{R} = \frac{V^2}{1k\Omega}$$

$$P_{out} = P_{in} \Rightarrow 2 \times 10^{-3} \cdot V = \frac{V^2}{1 \times 10^3}$$

$$\Rightarrow V = 2V$$

(Example 2.14 in the textbook has a typo saying  $V = 0.5V$ )

### ★ Voltage Divider

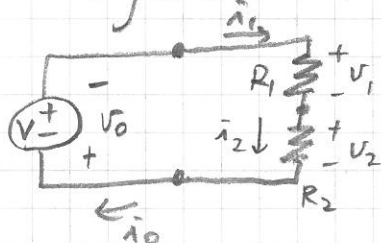

we may analyze it using the basic method:

$$\begin{cases} V_0 = -V \\ V_1 = R_1 i_1 \\ V_2 = R_2 i_2 \end{cases} \quad \begin{cases} \hat{i}_0 = \hat{i}_1 \\ \hat{i}_1 = \hat{i}_2 \end{cases} \text{ KCL} \quad \begin{cases} V_0 + V_1 + V_2 = 0 \end{cases} \text{ KVL}$$

$$\Rightarrow V_2 = \frac{R_2}{R_1 + R_2} V$$

Further, from  $i_2 = \frac{V_2}{R_2}$  we see  $i = \frac{1}{R_1 + R_2} V$


in other word,  $V = i \times (R_1 + R_2)$ .

$\Rightarrow$  we may replace  $R_1$  and  $R_2$  by an equivalent resistor  $R' = R_1 + R_2$

and the circuit is equivalent as  $V \oplus R'$

This lead to a general planar linear resistor analysis, such as that in Example 2.21 in the textbook.

# P16 \* Current Divider

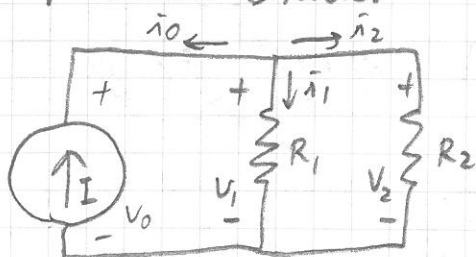

Using the "basic method"

$$\begin{cases} \hat{i}_0 = -I \\ V_1 = R_1 \hat{i}_1 \\ V_2 = R_2 \hat{i}_2 \end{cases} \quad \begin{cases} \hat{i}_0 + \hat{i}_1 + \hat{i}_2 = 0 \\ V_0 = V_1 = V_2 \end{cases}$$

$$\Rightarrow \hat{i}_1 + \hat{i}_2 = I$$

$$\hat{i}_1 + \hat{i}_2 = \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_0 R_2 + V_0 R_1}{R_1 R_2}$$

$$= \frac{R_1 + R_2}{R_1 R_2} V_0$$

$$\Rightarrow V_0 = \frac{R_1 R_2}{R_1 + R_2} \cdot I$$

$$\Rightarrow \begin{cases} \hat{i}_1 = \frac{V_1}{R_1} = \frac{R_2}{R_1 + R_2} I \\ \hat{i}_2 = \frac{V_2}{R_2} = \frac{R_1}{R_1 + R_2} I \end{cases}$$


$$V_1 = R_1 \hat{i}_1 = \frac{R_1 R_2}{R_1 + R_2} I$$

$$V_0 = R_{eq} \cdot I$$

$$\Rightarrow R_p = \frac{R_1 R_2}{R_1 + R_2}$$


$$\Rightarrow \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

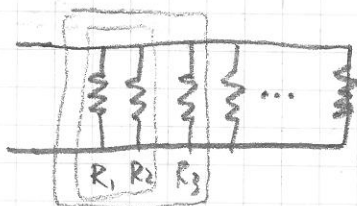In general, for N resistors connected in parallel,





$$\frac{1}{R_p} = \sum_{n=1}^N \frac{1}{R_n}$$

this can be proved by induction.

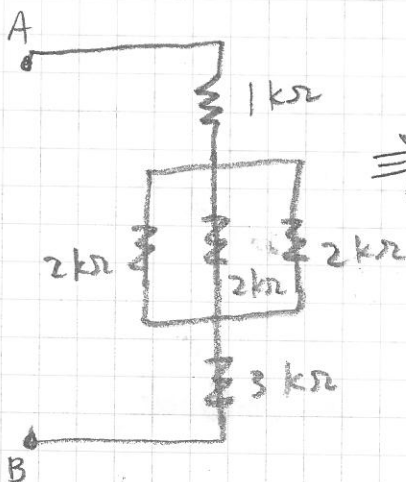
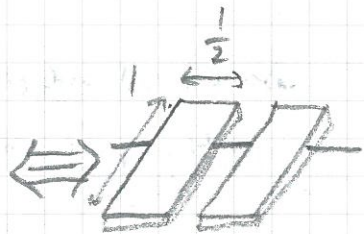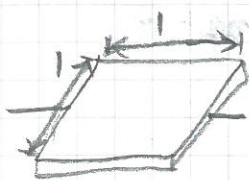
$$\begin{aligned} R_{eq} &= 1 + \frac{1}{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} + 3 \\ &= \frac{14}{3} \text{ k}\Omega \end{aligned}$$





P.17

let  $R_1 = R_0$


$$R_2 = \frac{2R_0 \cdot 2R_0}{2R_0 + 2R_0}$$

$$R_3 = \frac{1}{2}R_0 + \frac{1}{2}R_0$$

$$= R_0 = R_1$$


$$= R_0 = R_1$$

Example:

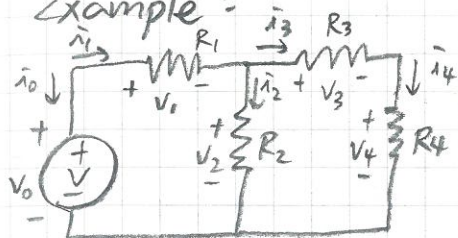

Determine  $V_1, V_2, V_3, V_4$   
and  $i_1, i_2, i_3, i_4$ .

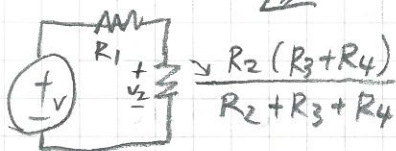Way ②: transformation  
using equivalent  
resistors



$$i_1 = V / \left( R_1 + \frac{R_2(R_3+R_4)}{R_2+R_3+R_4} \right)$$

$$V_1 = i_1 R_1 = \dots$$

$$V_2 = \dots \text{ (voltage divider)}$$

$$i_2 = V_2 / R_2, \quad i_3 = V_2 / (R_3 + R_4)$$

$$V_3 = i_3 R_3, \quad V_4 = i_3 R_4$$

Way ①: we may use the  
basic method

2° element law ...


3° KCL & KVL ...

4° 解聯立方程式


give it a try yourself here:

P18 Sometimes we may leverage symmetry to greatly reduce the complexity of analysis:

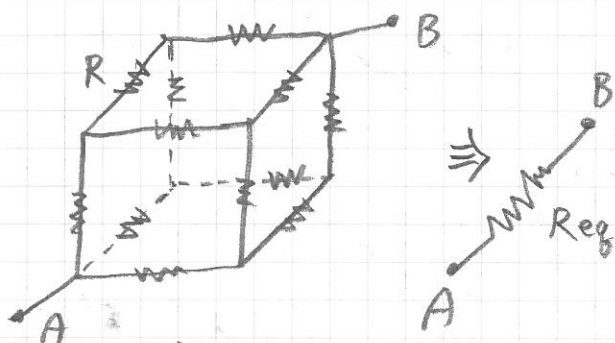Example: assuming all resistors are the same on a cube, with resistance  $R = 1\text{ k}\Omega$ , determine  $R_{eq}$




(See example 2.24 in the textbook)

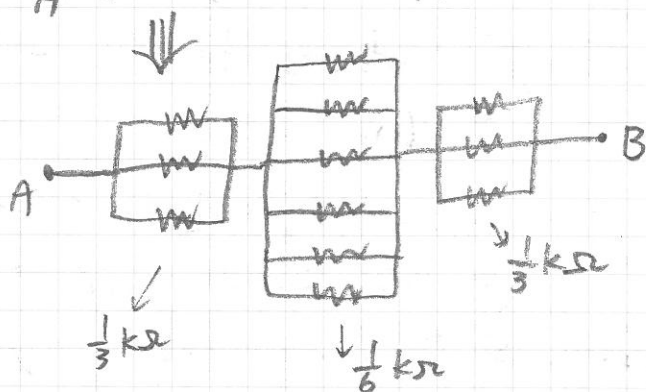

$$R_{eq} = \frac{1}{3} + \frac{1}{6} + \frac{1}{3} = \frac{5}{6}\text{ k}\Omega *$$




Often, we still need to apply the basic method after reducing a circuit by using equivalent resistors and symmetry !!

Example:

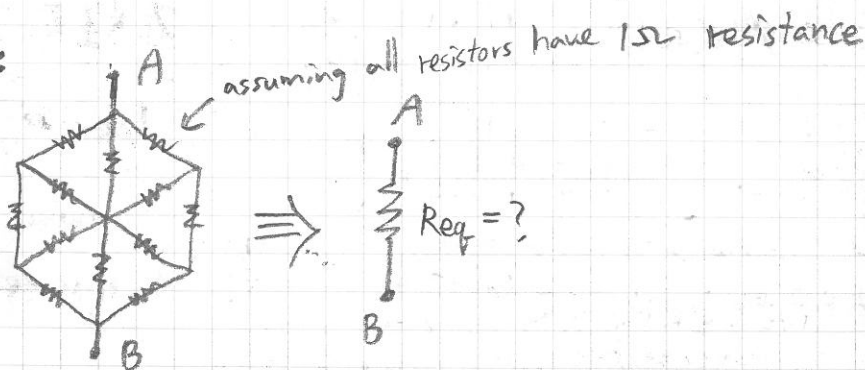

following P18,

P19

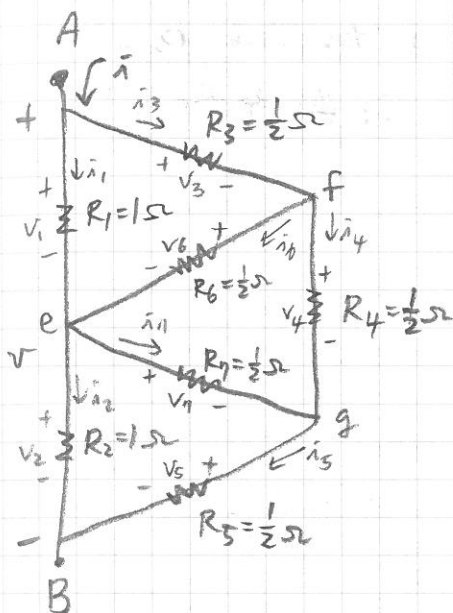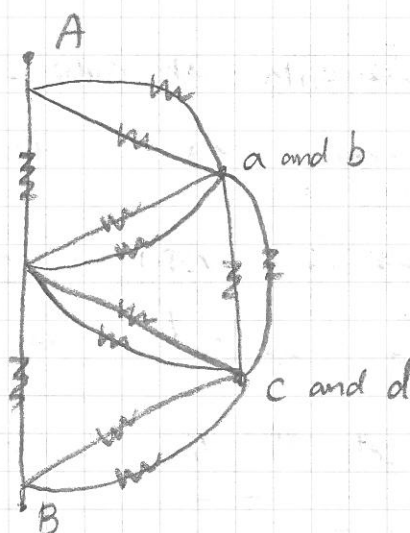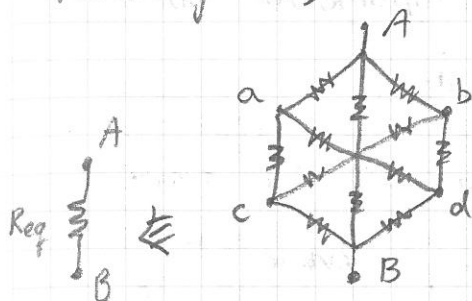

element laws:

$$\begin{cases} v_1 = i_1, v_2 = i_2, v_3 = \frac{1}{2} i_3 \\ v_4 = \frac{1}{2} i_4, v_5 = \frac{1}{2} i_5, v_6 = \frac{1}{2} i_6 \\ v_7 = \frac{1}{2} i_7 \end{cases}$$

KCL:

- ①  $i_1 + i_3 = i_2 + i_5$  (node A & B)
- ②  $i_1 + i_6 = i_2 + i_7$  (node e)
- ③  $i_3 = i_6 + i_4$  (node f)
- ④  $i_5 = i_7 + i_4$  (node g)

KVL:

- ⑤  $v_1 + v_2 = v_3 + v_4 + v_5$
- ⑥  $v_1 = v_3 + v_6$
- ⑦  $v_2 = v_7 + v_5$

$$Req = \frac{V}{i} = \frac{v_1 + v_2}{i_1 + i_3} = \frac{i_1 + i_2}{i_1 + i_3}$$

therefore, 我們可將所有電壓值代換為電流值, 去解電流的聯立方程式!!


$$\begin{bmatrix} 1 & -1 & 1 & 0 & -1 & 0 & 0 \\ 1 & -1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & 1 & 0 & -1 & 0 \\ 0 & 0 & 0 & -1 & 1 & 0 & -1 \\ 2 & 2 & -1 & -1 & -1 & 0 & 0 \\ 2 & 0 & -1 & 0 & 0 & -1 & 0 \\ 0 & 2 & 0 & 0 & -1 & 0 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

note: equation ④ is dependent,  
使用高斯消去法可得  $\begin{cases} i_1 = 2 i_7 \\ i_2 = 2 i_7 \\ i_3 = 3 i_7 \end{cases}$   
or [www.mathstools.com](http://www.mathstools.com) Matrix Calculator

$$\therefore Req = \frac{i_1 + i_2}{i_1 + i_3} = \frac{2+2}{2+3} = \frac{4}{5} \Omega$$

Calculation is a necessary part in engineering!

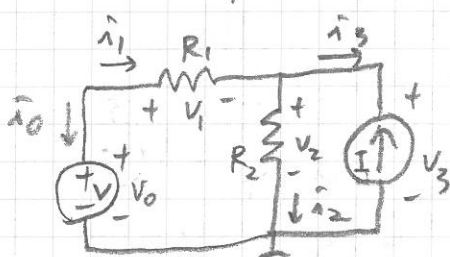P<sub>20</sub> Example: A circuit with two independent sources



Determine  $\hat{i}_2$ .

element law

$$\begin{cases} V_0 = V \\ V_1 = R_1 \hat{i}_1 \\ V_2 = R_2 \hat{i}_2 \\ \hat{i}_3 = -I \end{cases}$$

KCL

$$\begin{cases} \hat{i}_0 = -\hat{i}_1 \\ \hat{i}_1 = \hat{i}_2 + \hat{i}_3 \end{cases}$$


KVL

$$\begin{cases} V_0 = V_1 + V_2 \\ V_2 = V_3 \end{cases}$$

then solve these linear equations (see textbook P95).



$$\hat{i}_2 = \frac{R_1}{R_1 + R_2} I + \frac{1}{R_1 + R_2} V$$

Exercise:  $V_x = ?$

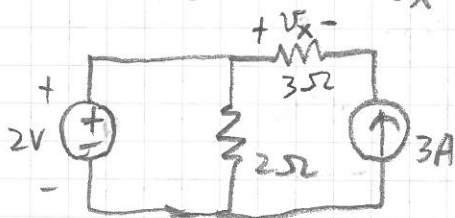


(ans:  $V_x = -9V$ )

★★ The I-V characteristic of a circuit

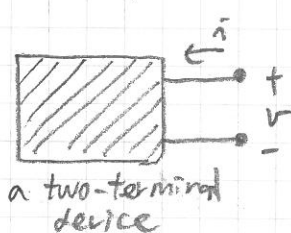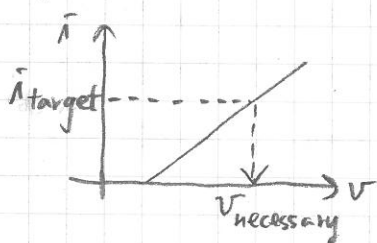


我們可藉由給定  $V$  量測  $\hat{i}$   
(or vice versa) 來繪製  
I-V relation.

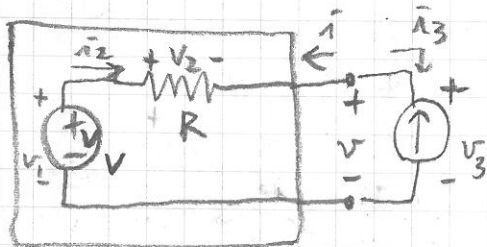If we know the device's internals,  
we may also determine its I-V relation:



using the basic method, we have
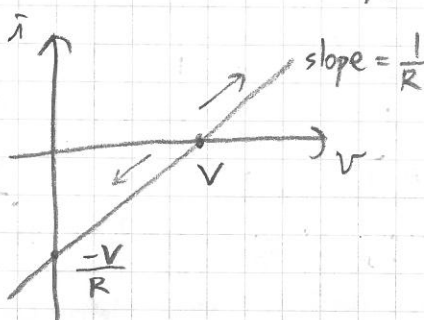
$$V = V + iR \Rightarrow \hat{i} = \frac{1}{R} V - \frac{V}{R}$$



example usage:  
預測電流流向

$$\begin{cases} V \geq V \rightarrow \hat{i} \geq 0 \\ V < V \rightarrow \hat{i} < 0 \end{cases}$$