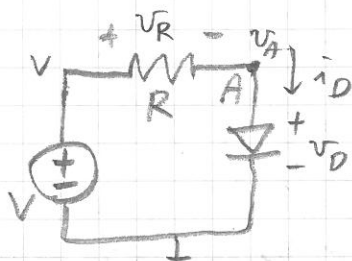


P36 Motivation for graphical analyses:  
Consider the following example



KCL at node A:

$$\frac{v_A - V}{R} + I_S(e^{v_D/V_{TBE}} - 1) = 0$$

$$\Rightarrow \frac{v_D - V}{R} + I_S(e^{v_D/V_{TBE}} - 1) = 0$$

Solving for  $v_D$  is like solving for

$x$  for  $ax + be^x + c = 0$  for some constants  $a, b$ , and  $c$ .

→ May be solved by trial-and-error

→ little insight, however.

What if we want to know the impact of increasing/decreasing  $V$  to the value of  $v_D$ ?

And, how would  $v_D$  change with the change of  $R$ ? These are critical questions to ask when designing an electronic circuit.

Now, graphical analyses can be very helpful in this aspect!

For concreteness, suppose  $\begin{cases} V = 3\text{ V} \\ R = 500\ \Omega \end{cases}$  in the example.


P37

$V_{THER} = 0.025\text{ V}$  in room temperature


We can rearrange the KCL equation to give two equations for  $i_D$ :

$$\begin{cases} i_D = I_s (e^{v_D/V_{THER}} - 1) = 10^{-12} (e^{v_D/0.025} - 1) \\ i_D = \frac{V - v_D}{R} = -\frac{1}{R} v_D + 0.006 \quad (\text{unit} = \text{A}) \end{cases}$$

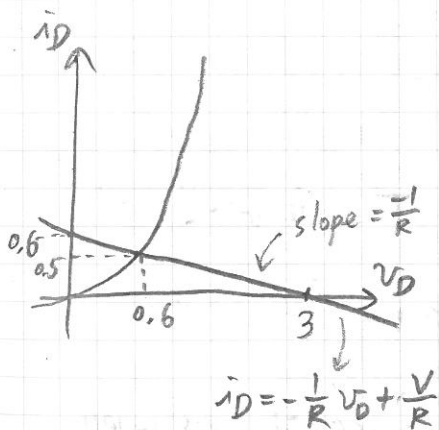then graphically speaking, the solution of  $i_D$  and  $v_D$  lies at the intersection point of the two curves on a  $v_D$ - $i_D$  plot:





$\Rightarrow$

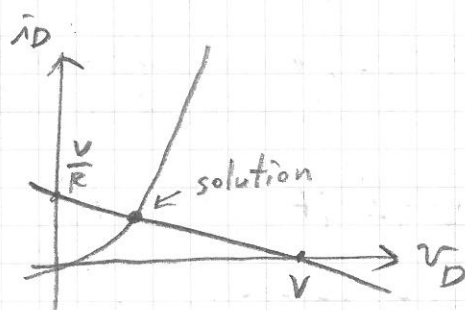

if  $R$  changes

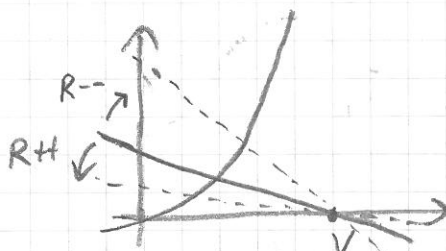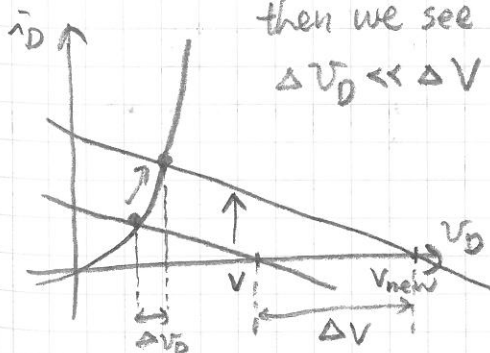if  $V$  increases then we see  $\Delta v_D \ll \Delta V$





which give much insight in how the circuit behaves!

# P38 Another example (half-wave voltage rectifier)

In the following circuit,

given a time-varying voltage source  $v_I$ ,

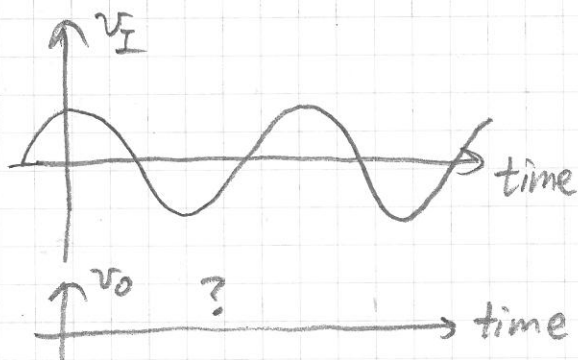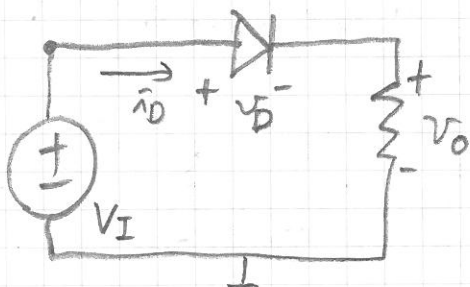what will be the output voltage  $v_O$  across a resistor?




from KVL,  $v_I - v_D - v_O = 0$




$$\Rightarrow v_O = v_I - v_D$$

from KCL, element law, and the i-v characteristic of the diode:
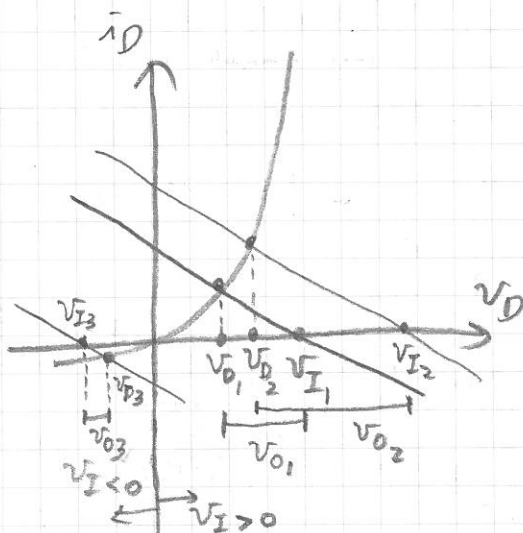
$$\begin{cases} i_D = I_S (e^{v_D/V_{TNE}} - 1) \\ i_D = \frac{v_I - v_D}{R} \end{cases}$$




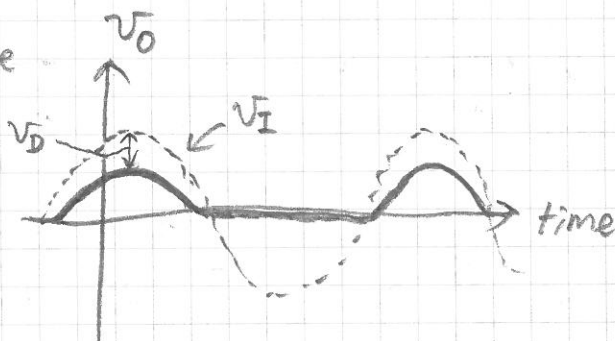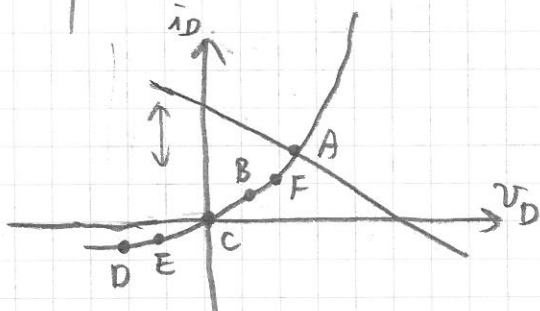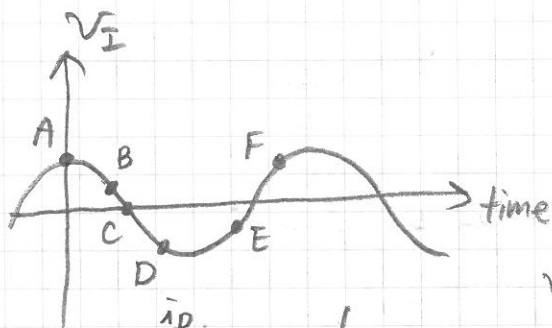We see  $v_{O3} \approx 0$  when  $v_D < 0$




Besides the graphical analysis, in some occasion we may simplify our analysis of a nonlinear circuit by considering an approximated version of the  $i$ - $v$  characteristic of a given nonlinear element.

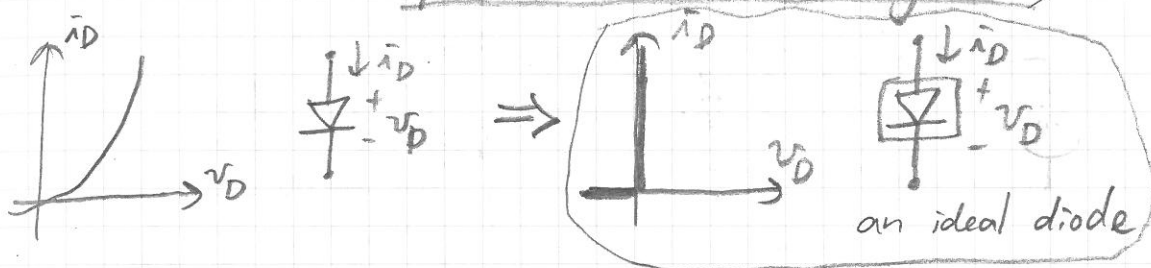This is called the piecewise linear analysis.




For an ideal diode, depending on the actual voltage (or the actual current direction), we may replace the diode by either a short circuit or an open circuit.

Example:

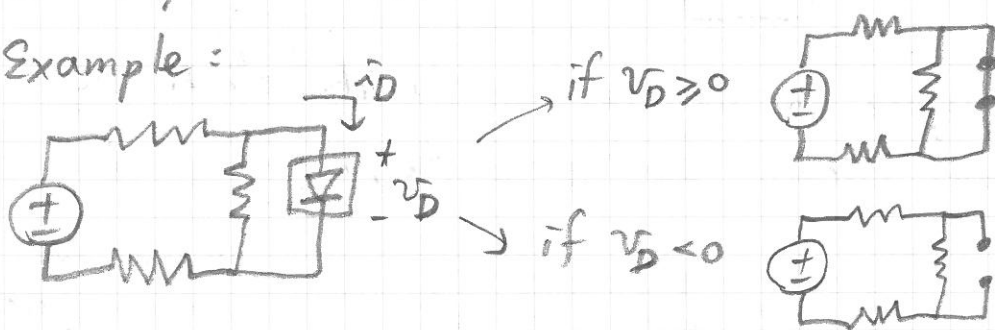


(Note: in class  $\checkmark$  conditioned on the direction of the current flowing through the diode, but perhaps it makes more sense to  <sup>$i_D$</sup>  condition on  $v_D$ . Either way, we follow the associated variable convention (see page 8 of this note).)

P40 Example:

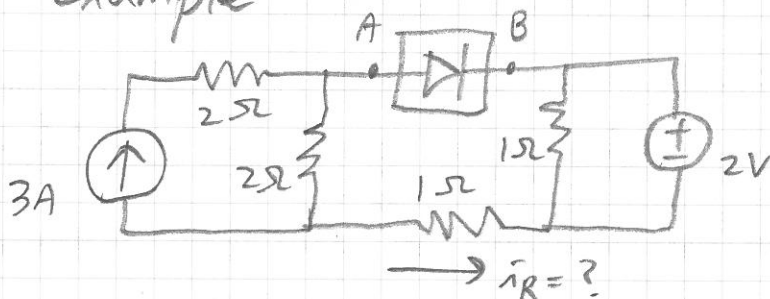

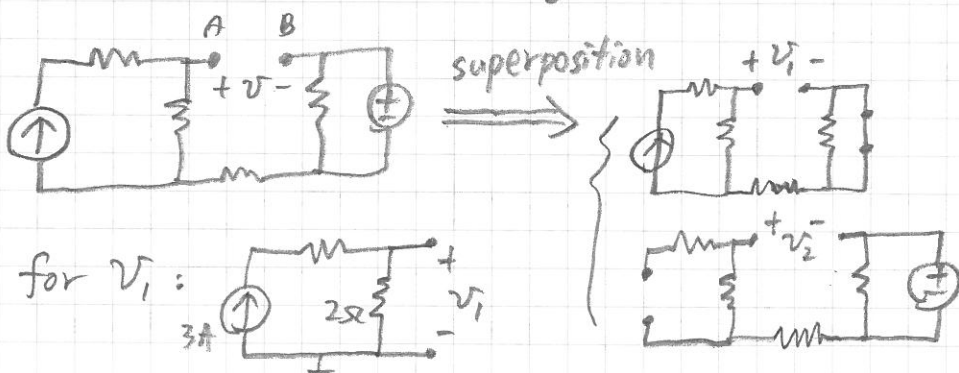We first find the voltage across A and B.




$$v_1 = 3A \times 2\Omega = 6V$$

$$\text{for } v_2: \quad v_2 = -2V$$

$$v = v_1 + v_2 = 6 - 2 = 4V$$

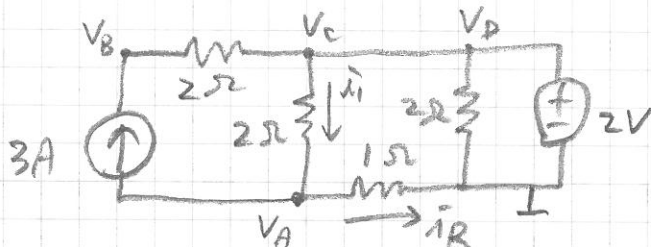→ therefore we may replace the ideal diode by a short circuit, leading to the following equivalence:



in class we used superposition; here, let's try using the node method!

$$V_C = V_D = 2$$

$$\hat{i}_1 = 3 + \hat{i}_R$$

$$\Rightarrow \frac{2 - V_A}{2} = 3 + \frac{V_A - 0}{1}$$

$$2 - V_A = 6 + 2V_A$$

$$\Rightarrow V_A = \frac{-4}{3}$$

$$\Rightarrow \hat{i}_R = \frac{V_A - 0}{1} = \frac{-4}{3} A$$