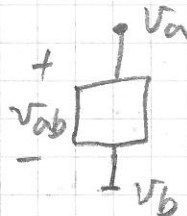


★ Circuit Analysis using the Node Method

P21

Motivation:


Often, the number of nodes in a circuit is much smaller than that of branches. Node method thus involves fewer number of variables, which means it is often easier to solve.

- definition of node voltage:  $V_{ab} = V_a - V_b$
node voltage

Procedure of the node method:

- 1° select a reference node (接地, $v=0$)
- 2° assign node variables
- 3° apply KCL
- 4° solve equations
- 5° back-solve the needed branch voltage/current.

Example: find $V_0 = ?$

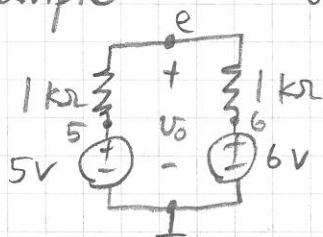


using the node method,

$$\frac{5-e}{1k\Omega} + \frac{6-e}{1k\Omega} = 0$$

$$e = 5.5V \quad V_0 = e - 0 = 5.5V$$

if using the basic method,

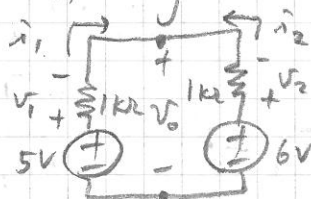

$$\hat{I}_1 = \frac{V_1}{1k\Omega}$$

$$\hat{I}_2 = \frac{V_2}{1k\Omega}$$

$$\hat{I}_1 + \hat{I}_2 = 0$$

$$\Rightarrow V_1 + V_2 = 0$$

using KVL,

$$5 - V_1 + V_2 - 6 = 0$$


$$\Rightarrow V_1 - V_2 = -1$$

$$\begin{cases} V_1 = -0.5 \\ V_2 = 0.5 \end{cases}$$

$$V_0 = 6 - V_2 \text{ (KVL)}$$

$$= 5.5V$$

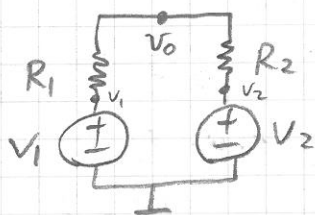P22 Symbolic Computation can give us some insights:



$$\text{KCL: } \frac{V_1 - V_0}{R_1} + \frac{V_2 - V_0}{R_2} = 0$$

$$\Rightarrow R_2(V_1 - V_0) + R_1(V_2 - V_0) = 0$$

$$\Rightarrow V_0 = \frac{1}{R_1 + R_2} (R_2 V_1 + R_1 V_2)$$

$$= \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$

Insights ① V_0 is a linear combination of V_1 and V_2 .


The circuit acts as an adder that gives a weighted sum of V_1 and V_2 .

② if set $V_2 = 0$, then $V_{01} = \frac{R_2}{R_1 + R_2} V_1$,

which is equivalent to the result

of a voltage divider:

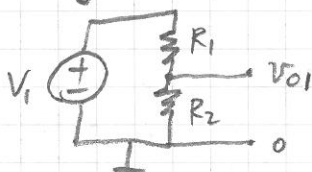
i.e., having the same $i-v$ characteristic.



③ similarly, if set $V_1 = 0$, then

$$V_{02} = \frac{R_1}{R_1 + R_2} V_2, \text{ equivalent to the}$$

result of a voltage divider:

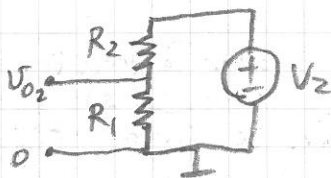

\Rightarrow from ② and ③, the original circuit can be thought of as a superposition of two voltage dividers, with $V_0 = V_{01} + V_{02}$.

\rightarrow we will talk more about it on October 6!