

Name: \_\_\_\_\_

Solution

Student ID: \_\_\_\_\_

National Taiwan Normal University  
Department of Computer Science and Information Engineering  
CSU0007 - Basic Electronics  
Midterm Exam (Apr. 27, 2020)

Five group questions; exam time: 2 hours 50 minutes (9:20am-12:10pm)  
Clearly state each step of your answer.

1. (15 points) **Foundations.** Answer the following two questions:

- 1a. (8 points) In Figure 1a, suppose  $v_1=2V$ ,  $v_4=3V$ , and  $v_7=1V$ . Determine  $v_2$ ,  $v_3$ ,  $v_5$ , and  $v_6$ .  
1b. (7 points) In Figure 1b, find the equivalent resistance,  $R_{AB}$ , from the viewpoint of A-B.

1a. Using KVL

$$V_3 = 1 \text{ V}$$

$$V_6 = -3 \text{ V}$$

$$V_5 = 1 \text{ V}$$

$$V_2 = -2 \text{ V}$$

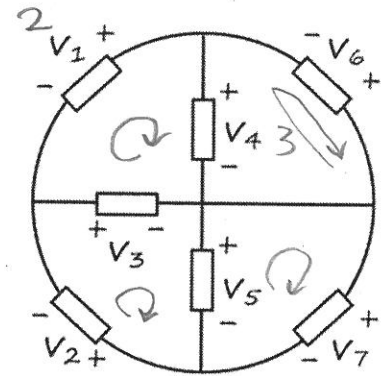


Figure 1a

1b.

$$R_{AB} = (4R // 4R) + (3R // 3R) + (3R // 3R) + (4R // 4R)$$

$$= 2R + \frac{3}{2}R + \frac{3}{2}R + 2R$$

$$= 7R$$

\*

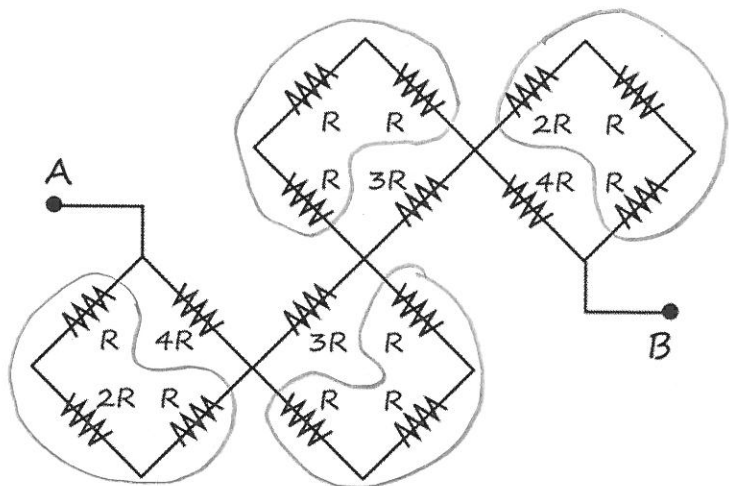


Figure 1b

Name: Solution

Student ID: \_\_\_\_\_

2. (30 points) **Elementary Analysis Techniques.** Answer the following three questions:

- 2a. (10 points) In Figure 2a, given the branch variables, perform symbolic computation to find current  $i_4$  in terms of  $V_0$  and  $R_1 \sim R_4$ . You may use equivalent resistors to simplify the process.
- 2b. (10 points) In Figure 2b, find current  $i$  by *applying the node method only*.
- 2c. (10 points) Following Question 2b, this time apply the concept of superposition to find  $i$ .

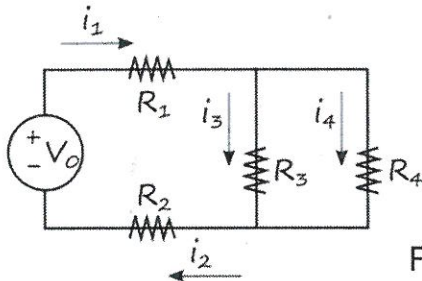


Figure 2a


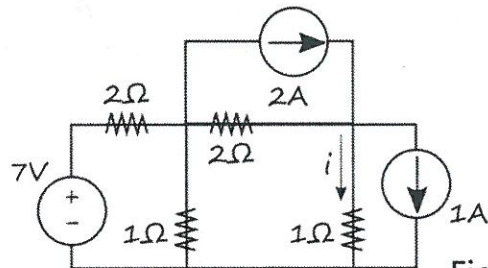


Figure 2b

$$2a. \quad i_4 = \frac{1}{R_4} \left( V_0 \times \frac{\frac{R_3 R_4}{R_3 + R_4}}{R_1 + R_2 + \frac{R_3 R_4}{R_3 + R_4}} \right)$$
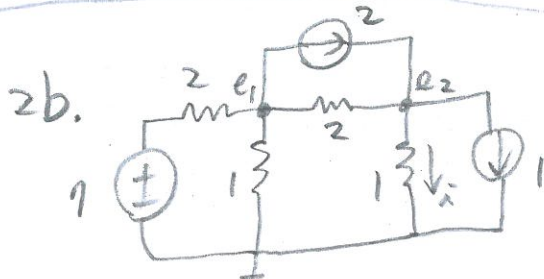
$$= \frac{R_3 V_0}{(R_1 + R_2)(R_3 + R_4) + R_3 R_4} \quad \#$$





KCL at  $e_1$ :  $\frac{e_1 - 1}{2} + e_1 + 2 + \frac{e_1 - e_2}{2} = 0$

KCL at  $e_2$ :  $-2 + \frac{e_2 - e_1}{2} + e_2 + 1 = 0$

$\Rightarrow e_2 = 1$

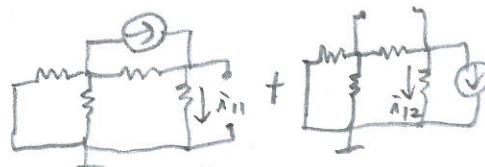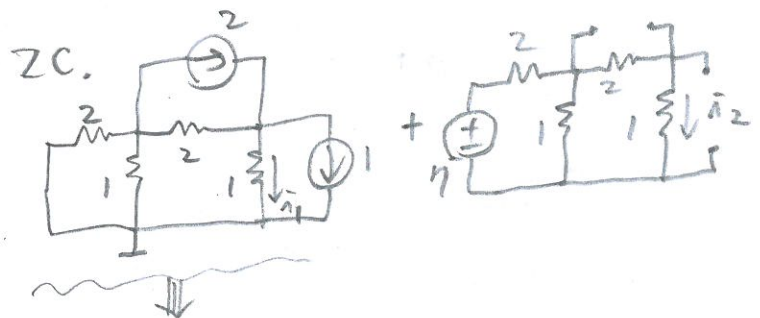$i = \frac{e_2}{1} = 1 \text{ A} \quad \#$



$$i = i_1 + i_2$$

$$= i_{11} + i_{12} + i_2$$

$$i_2 = \left( 1 \times \frac{\frac{3}{4}}{2 + \frac{3}{4}} \times \frac{1}{2 + 1} \right) / 1 = \frac{7}{11} \text{ A}$$

$$i_{11} = 2 \times \frac{2}{\frac{5}{3} + 2} = \frac{12}{11} \text{ A}$$

$$i_{12} = (-1) \times \frac{\frac{8}{3}}{\frac{8}{3} + 1} = -\frac{8}{11} \text{ A}$$

→ voltage divider + element law

→ current divider

$$\Rightarrow i = \frac{12}{11} - \frac{8}{11} + \frac{7}{11} = 1 \text{ A} \quad \#$$

Name: \_\_\_\_\_

Solution

Student ID: \_\_\_\_\_

3. (15 points) **Circuit Transformations.** Consider the circuit shown in Figure 3 and answer the following two questions:

3a. (7 points) Find resistance  $R_{TH}$  in the Thévenin equivalent (Figure 3a).

3b. (8 points) Find current  $i_{SC}$  in the Norton equivalent (Figure 3b).

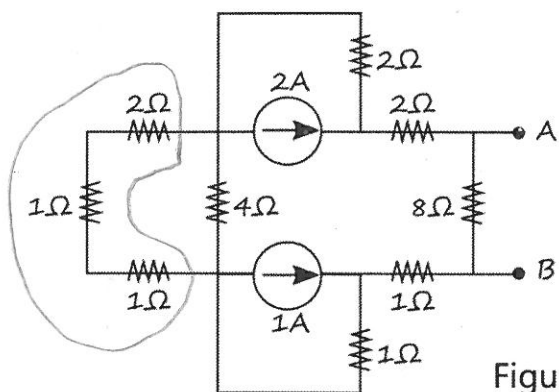


Figure 3

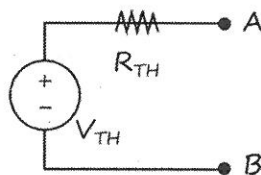


Figure 3a



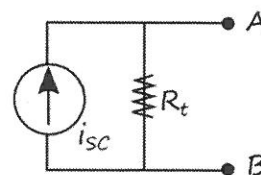


Figure 3b

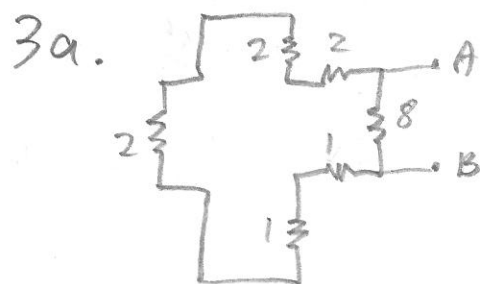


$$\Rightarrow R_{TH} = 4 \Omega$$

3b.

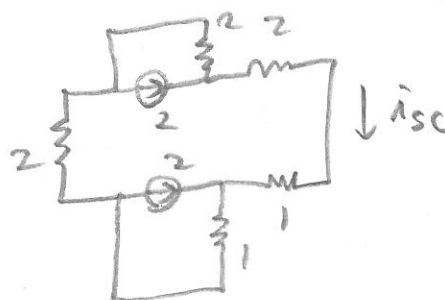

using superposition

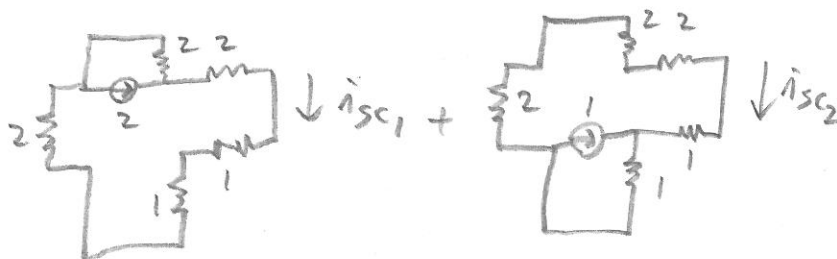

$$\hat{i}_{SC} = \hat{i}_{SC1} + \hat{i}_{SC2}$$

$$\hat{i}_{SC1} = 2 \times \frac{2}{6+2} = \frac{1}{2} A$$

$$\hat{i}_{SC2} = (-1) \times \frac{1}{7+1} = -\frac{1}{8} A$$

both using  
current  
divider

$$\Rightarrow \hat{i}_{SC} = \frac{1}{2} - \frac{1}{8} = \frac{3}{8} A$$

Name: Solution

Student ID: \_\_\_\_\_

4. (15 points) **Applications.** Answer the following two questions:

- 4a. (7 points) As shown in Figure 4a, we have an embedded electronic system that can supply 5V voltage to power some other electronic devices. We have a sensor device that can only operate at ~~3.2-3.4V~~ <sup>3.1~3.5V</sup>. Given a set of linear resistors, you are asked to use some of those resistors to construct a circuit that connects the four wires with some appropriate voltage transformation. Draw your answer directly on Figure 4a.

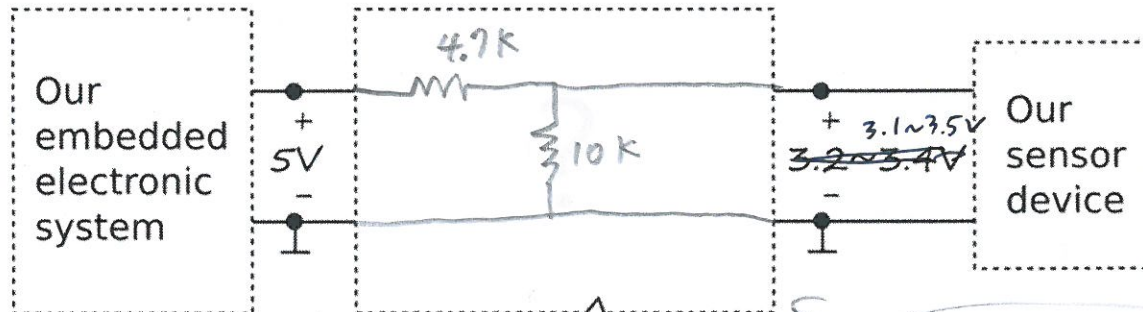


Figure 4a

voltage divider

$$5 \times \frac{10}{4.7 + 10} \approx 3.4$$

	1k $\Omega$	x2
	3.5k $\Omega$	x2
	4.7k $\Omega$	x2
	10k $\Omega$	x2

- 4b. (8 points) Given an arbitrary linear circuit, we may determine its Thévenin equivalent in two steps. First, we connect the circuit with a linear resistor and measure the branch voltage across that resistor. Then, we replace the resistor by a different linear resistor and again measure its branch voltage. Think about why that would help us determine the Thévenin equivalent. Now, with the two steps shown in Figure 4b, determine resistance  $R_{TH}$  of the Thévenin equivalent of our target linear circuit.


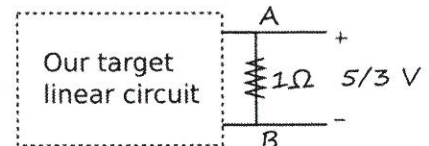
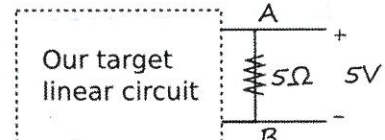
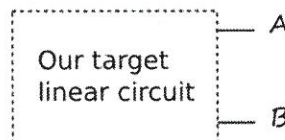


Figure 4b

It is indeed a voltage divider :
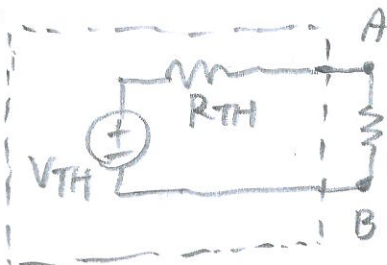
$$\begin{cases} 5 = V_{TH} \times \frac{5}{5 + R_{TH}} \\ \frac{5}{3} = V_{TH} \times \frac{1}{1 + R_{TH}} \end{cases} \Rightarrow \begin{cases} R_{TH} = 5 \\ V_{TH} = 10 \end{cases}$$



Name: \_\_\_\_\_

Solution

Student ID: \_\_\_\_\_

5. (25 points) **Nonlinear Analysis.** Answer the following three questions:

- 5a. (7 points) For the circuit in Figure 5a, if we changed the linear resistor so that  $R$  decreased, would  $i_D$  increase or decrease? Give your reason based on the graphical analysis.
- 5b. (8 points) In Figure 5b, apply the analytical method to find current  $i$ .
- 5c. (10 points) In Figure 5c, apply the small-signal analysis to find current  $i_D$ .

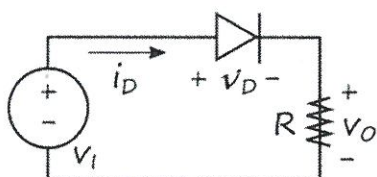


Figure 5a


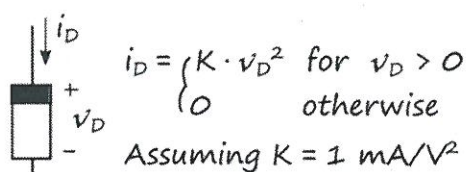
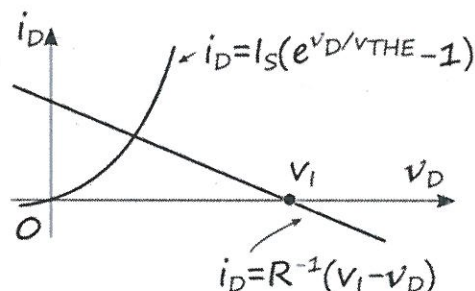


Figure 5b

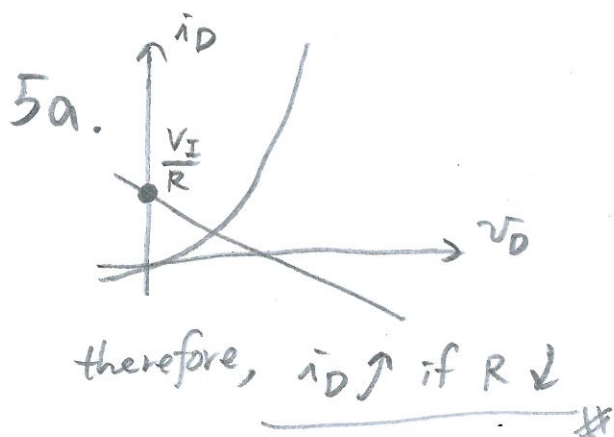

for small signal:

$$r_d = \frac{1}{\left. \frac{d i_D(V_D)}{d V_D} \right|_{V_D = V_D}}$$



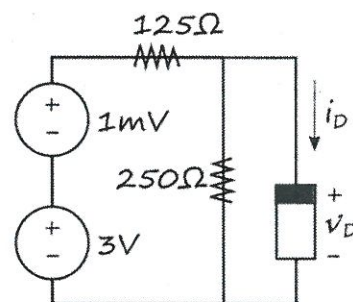


Figure 5c

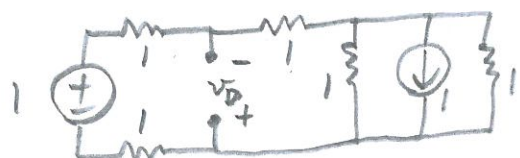5b. First, we need to determine whether  $V_D > 0$ :



using superposition (I prefer that)

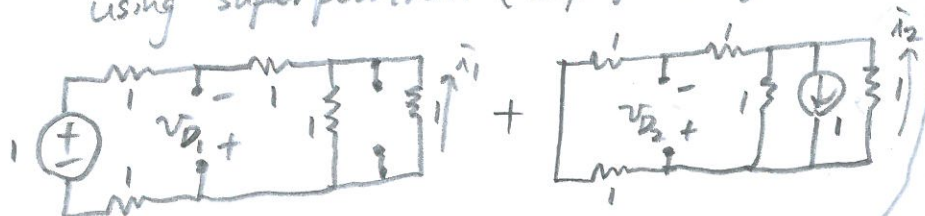

$$V_D = V_{D1} + V_{D2}$$

$$V_{D1} = (-1) \times \frac{\frac{3}{2}}{2 + \frac{3}{2}} = -\frac{3}{7} V$$

$$V_{D2} = 2 \times \left( 1 \times \frac{1}{\frac{3}{4} + 1} \right) \times \frac{1}{3 + 1} = \frac{2}{7}$$

$$\Rightarrow V_D = \frac{3}{7} + \frac{2}{7} = \frac{5}{7} < 0$$

$$\Rightarrow i_D = 0$$


Then we may reuse the superposition

$$i = i_1 + i_2 = \frac{(-1)}{1} \times \frac{\frac{3}{2}}{3 + \frac{1}{2}} + 1 \times \frac{\frac{3}{4}}{\frac{3}{4} + 1} = \frac{2}{7} A$$

Name: Solution



Student ID: \_\_\_\_\_

5c.

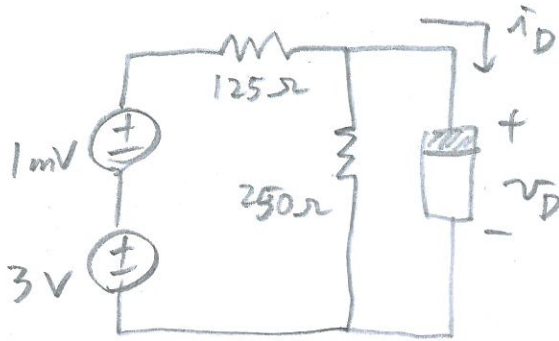

$$i_D = \begin{cases} IK \cdot v_D^2 & \text{if } v_D > 0 \\ 0 & \text{otherwise} \end{cases}$$

and  $IK = 1 \text{ mA/V}^2$

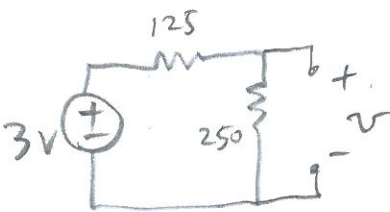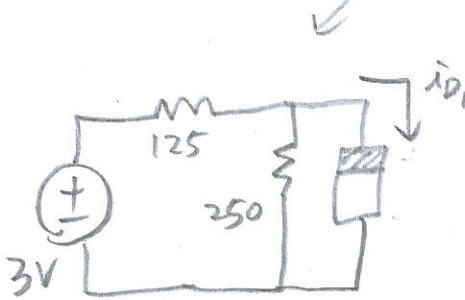

$$V = 3 \times \frac{250}{125 + 250} = 2 \text{ V}$$

$V > 0$  ensures that the diode is ON

$$\Rightarrow \cancel{i_{D1}} = 1 \times 10^{-3} \times 2$$

$\cancel{= 4 \text{ mA}}$

To compute  $i_{D1}$ , it is wrong to directly apply  $i_D = IK \cdot v_D^2$  because  $v_D \neq V$

The correct way is as follows:




KCL on A:  $\frac{3 - v_D}{125} + \frac{0 - v_D}{250} - i_{D1} = 0$

Diode characteristic:  $i_{D1} = IK \cdot v_D^2$

$$\Rightarrow v_D = -6 + 2\sqrt{15} \approx 1.75 \text{ V (not 2V)}$$
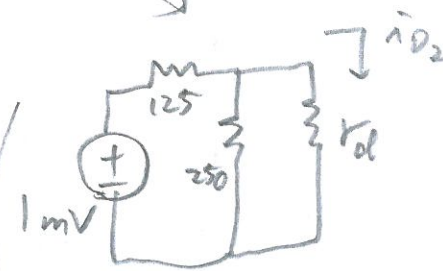
$$\Rightarrow i_{D1} = 10^{-3} \times v_D^2 = 3.0625 \text{ mA}$$



$$r_d = \frac{1}{\left. \frac{d(IK v_D^2)}{d v_D} \right|_{v_D = V_D}} = \frac{1}{2IK v_D} \bigg|_{v_D = V_D} = \cancel{1.75}$$

$$= \frac{1}{2 \times 10^{-3} \times \cancel{1.75}} \approx \frac{1}{2 \times 10^{-3} \times 1.75} = \frac{286 \Omega}{1.75} \approx 163.4 \Omega$$

$$\Rightarrow i_{D2} = \frac{1 \times 10^{-3} \times \frac{250 \times 250}{250 + 250}}{250 + 286} = \frac{1 \times 10^{-3} \times 133.4}{536} \approx 0.000249 \text{ mA}$$

$\cancel{= 2 \mu A}$   
 $\cancel{1.79}$

$$\cancel{i_D = i_{D1} + i_{D2} = 4.002 \text{ mA}}$$

$$= 3.0625 \text{ mA} + 0.00179 \text{ mA} \approx 3.0643 \text{ mA}$$