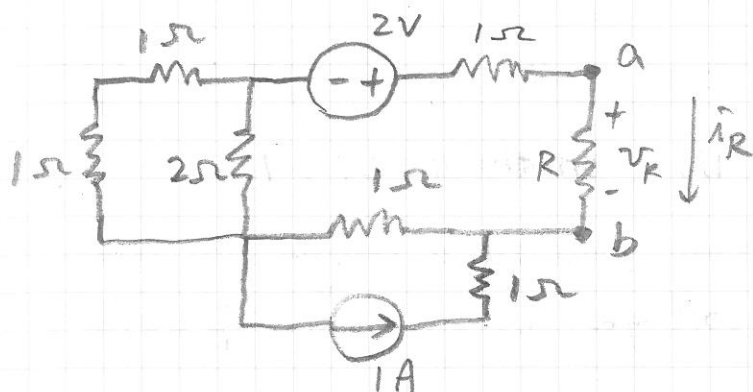


Some exercise problems since P32:


P41

- A. Use Norton's Theorem to find i_R and v_R for ① $R=2$ and ② $R=4$




- B. Following A, rather than using Norton's Theorem, directly apply superposition to find i_R for $R=2$.

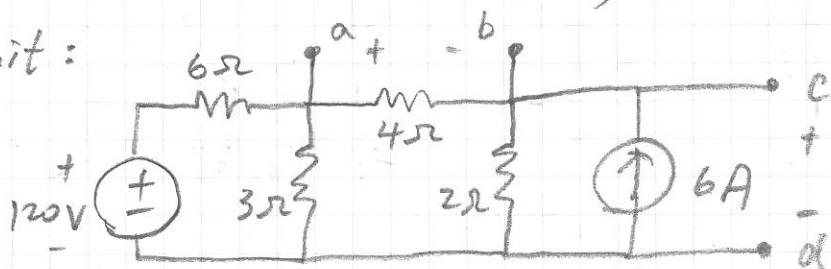- C. Determine the Norton equivalent at terminals a, b and at terminals c, d, for the following circuit:



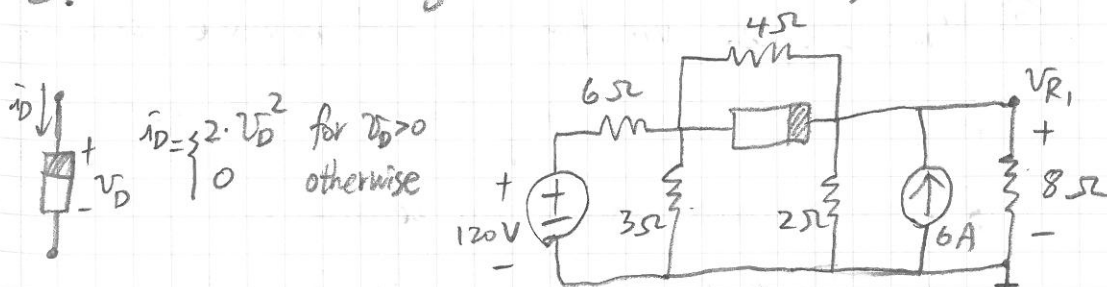- D. For the following nonlinear circuit, determine v_{R_1} .




$i_D = \begin{cases} 2 \cdot v_D^2 & \text{for } v_D > 0 \\ 0 & \text{otherwise} \end{cases}$

(hint: compare this with that in C.)

P42 E. For the following nonlinear circuit, with some initial analysis of its i_D - v_D relation at hand, try to answer three questions:

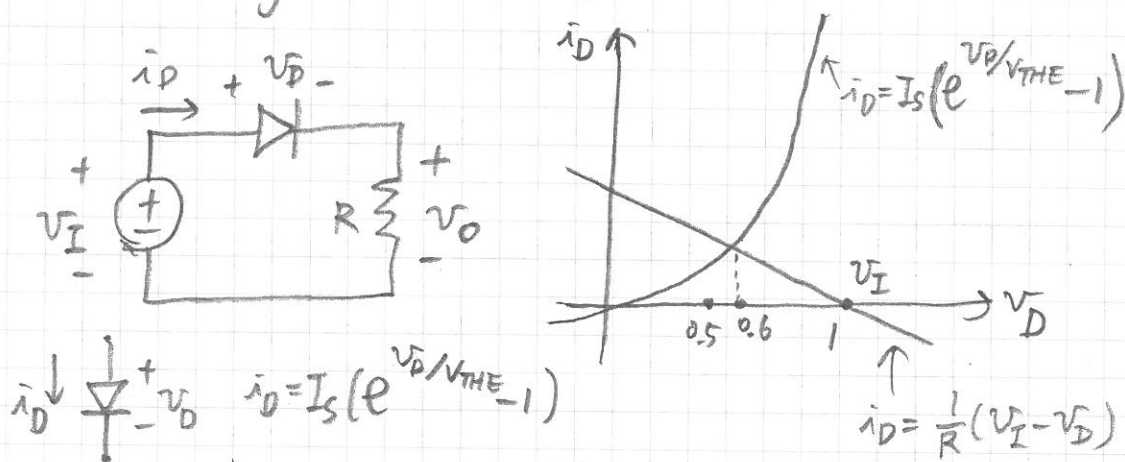- ① if for some need we changed the input voltage v_I , so that $v_I > 1$, would that lead to a change to the output voltage $v_O > 0.4$ or $v_O < 0.4$?
- ② Now, suppose we operate the circuit at region $v_I \gg 1$. What can we say about v_O ?



- ③ Now, suppose we fix v_I but replace the linear resistor by a very heavy load, such that $R \gg 1$. What would i_D become?

Answers to Problems A, B, C, D:

A. ① $i_R = \frac{1}{5}A$, $v_R = \frac{2}{5}V$ ② $i_R = \frac{1}{7}A$, $v_R = \frac{4}{7}V$ B. same as A. C. $R_{tob} = 2\Omega$, $i_{scab} = 1A$
 $R_{tcd} = \frac{3}{2}\Omega$, $i_{sccd} = \frac{38}{3}A$ D. $16V$ ✱