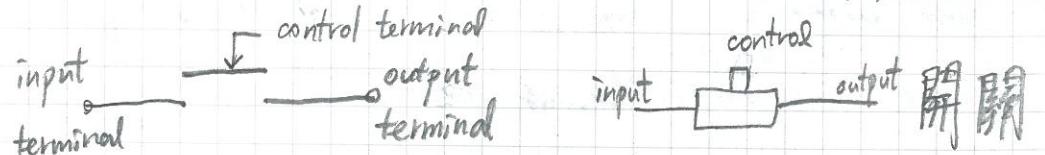



## P54 \* The MOSFET switch

(Metal Oxide Semiconductor Field-Effect Transistor)

A switch is a three-terminal element in a circuit.



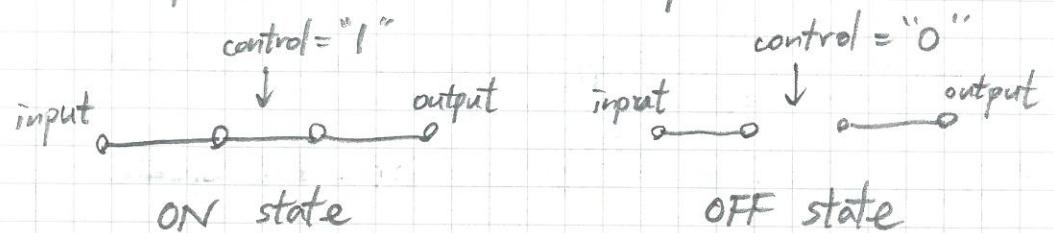
Ideally, input to the control terminal determines whether or not there is a short circuit between the input terminal and the output terminal:



(compare this with an ideal diode  $\text{\textcircled{D}}$ , P39)

Such a simple idea of a switch enables many ways to control the response of certain elements in a circuit. First, let's look at two examples showing how a switch may impact the response of another element in a circuit:

## Example 1.

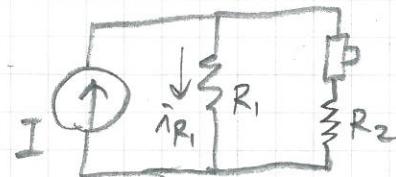


A switch connected in series with resistor  $R_2$  will impact the current flowing through resistor  $R_1$ .

$$\text{ON state: } i_{R_1} = I \times \frac{R_2}{R_1 + R_2}$$

$$\text{OFF state: } i_{R_1} = I$$

## Example 2.

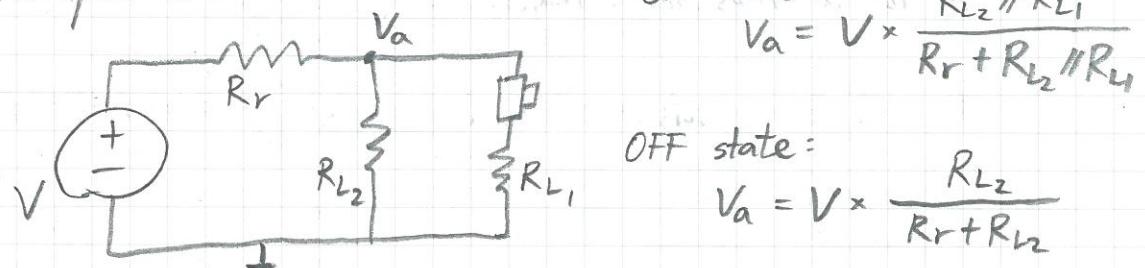

$$\text{ON state: } V_a = V \times \frac{R_{L2} // R_{L1}}{R_r + R_{L2} // R_{L1}}$$

$$\text{OFF state: } V_a = V \times \frac{R_{L2}}{R_r + R_{L2}}$$


The voltage across the resistor  $R_{L2}$  will drop if the switch is in the ON state, because of the existence of  $R_r$ .

Conceptually, by connecting two switches in series we may implement the AND logic; by connecting two switches in parallel, we may implement the OR logic. In both cases, the control terminals take the input logical values.

## P55

P56


The symbol of a MOSFET

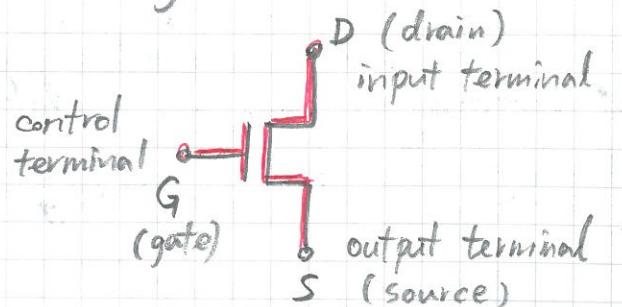


Let  $i_{DS}$  be the current flowing from the drain to the source,  $V_{GS}$  be the voltage across the gate and the source, and  $V_T$  be a threshold voltage.

In its simplest model (S model), the MOSFET behaves as follows :

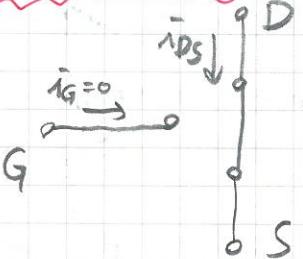
$$V_{GS} \geq V_T \Rightarrow \text{ON state}$$


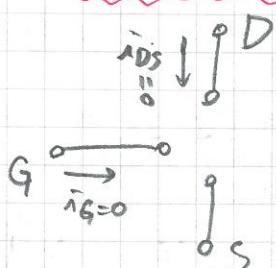
$$V_{GS} < V_T \Rightarrow \text{OFF state}$$



And in terms of input/output ports:

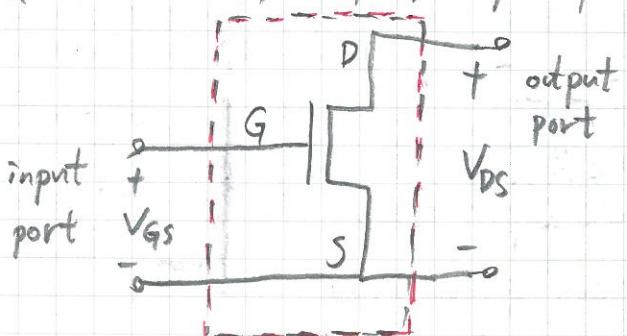


Later, we will study some more realistic models of MOSFET (for example, explicitly consider its internal resistance). For now, let's focus on the S model and its switching behavior.

P57

We may use a MOSFET to construct a logical NOT gate  $\rightarrow \neg$ , so-called an "inverter":


(review P53)

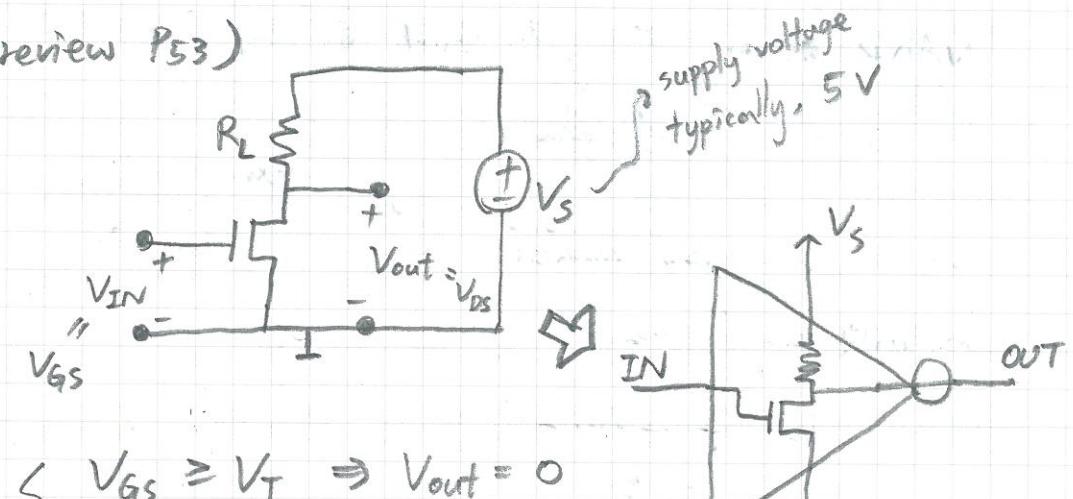

$$\left\{ \begin{array}{l} V_{GS} \geq V_T \Rightarrow V_{out} = 0 \\ (\text{logic 1}) \end{array} \right. \quad \left. \begin{array}{l} V_{GS} < V_T \Rightarrow V_{out} = V_S \\ (\text{logic 0}) \end{array} \right.$$

$$\left. \begin{array}{l} V_{GS} < V_T \Rightarrow V_{out} = V_S \\ (\text{logic 0}) \end{array} \right. \quad \left. \begin{array}{l} V_{out} = V_S \\ (\text{logic 1}) \end{array} \right.$$

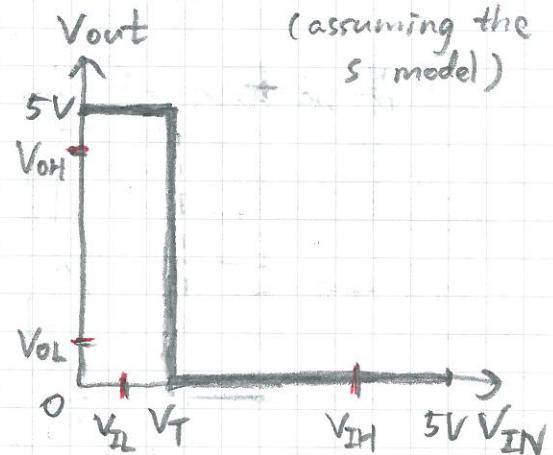transfer characteristic of an inverter (assuming the S model)




A valid mapping of voltage levels specified in the static discipline  $\rightarrow$   $V_{OL}$


(review P52)

P58

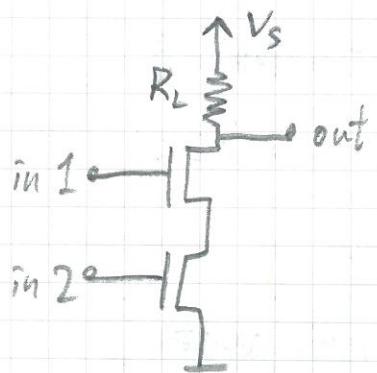
Similarly, we may use MOSFETs to construct other logic gates:



NAND gate

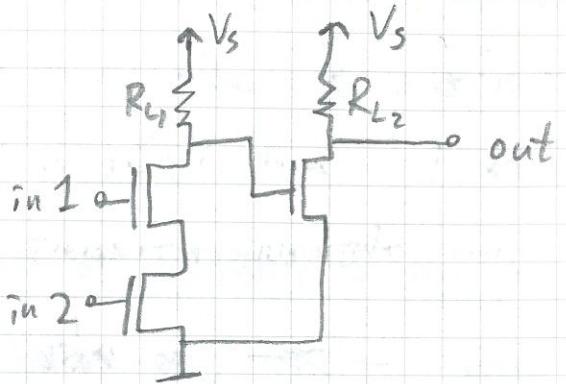

AND gate (NAND + NOT)

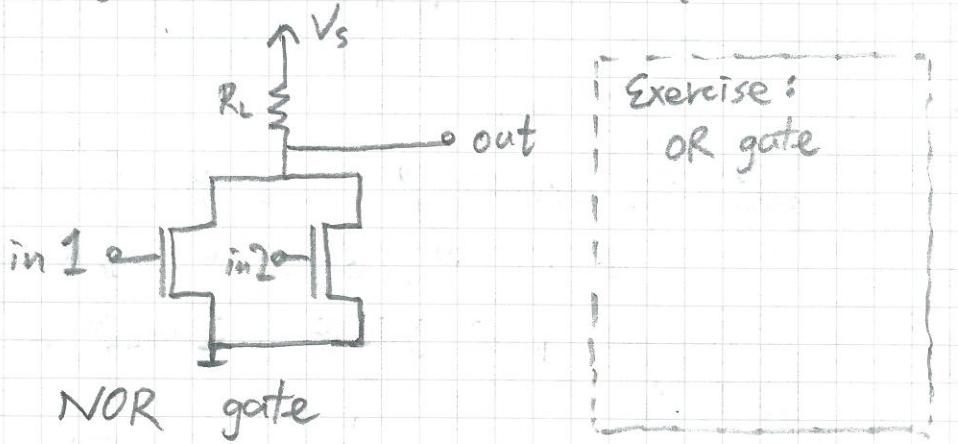

NOR gate

When a positive voltage is applied

P59

at the control terminal G, a conducting channel will be built up between the two  $n^+$  regions, and therefore some nontrivial current may flow from D to S. Read Section 6.7 in the textbook for a more detailed account.

The physical structure also implies that in the ON state there really will exist some resistance between D and S, and the value of the resistance is characterised by the dimensions of that conducting channel. Let  $R_{ON}$  be the resistance per square of the channel, and L be the channel length and W the channel width.

We have

$$R_{ON} = R_N \cdot \frac{L}{W} \quad (\text{review P6})$$

→ the resistance of the channel

The S model neglects  $R_{ON}$ . A more realistic model takes  $R_{ON}$  into account, and we call it the SR model:



$$V_{GS} \geq V_T \Rightarrow \text{ON state}$$

$i_{DS}$



$$i_{DS} = \frac{V_{DS}}{R_{ON}}$$

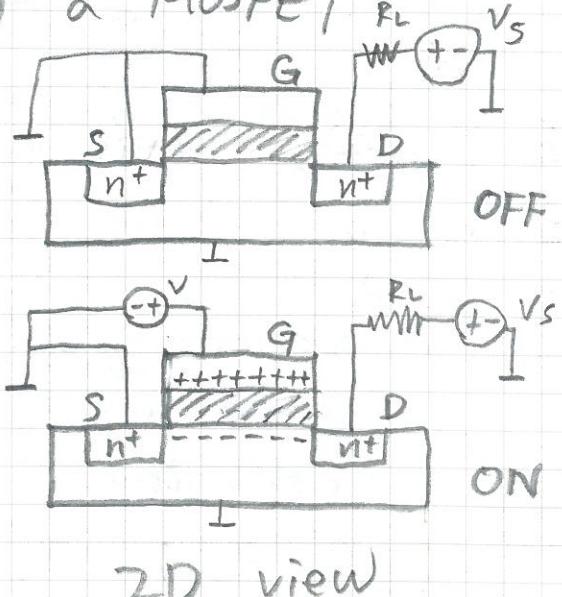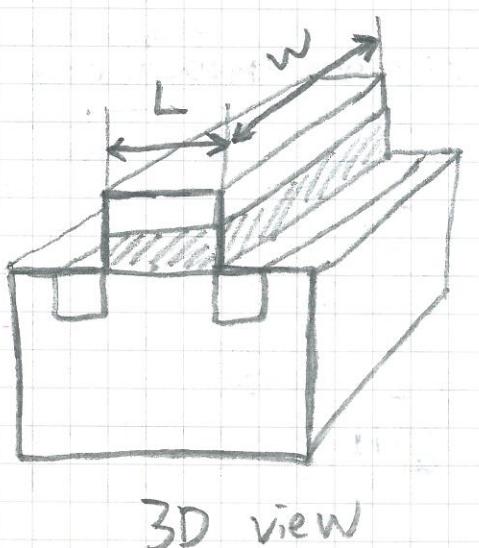
(the OFF state is same as that in the S model)


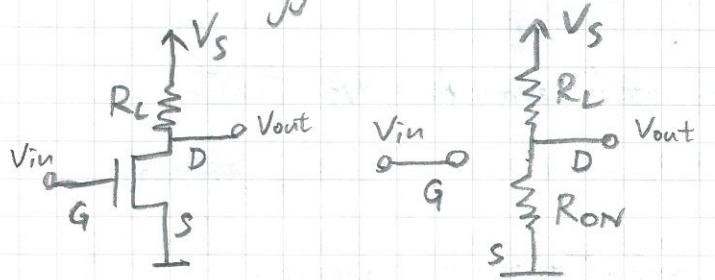
## P60 \* Analyzing a MOSFET circuit using the SR model

Taking into account the impact from  $R_{ON}$ , the analysis may seem complicated, but it is still based on what we've learned so far.

Let's analyze an inverter to illustrate this:




Because now we consider  $R_{ON}$ , the output voltage  $V_{out}$  will not be zero when  $V_{GS} \geq V_T$  ;

instead,

$$V_{out} = V_s \times \frac{R_{on}}{R_L + R_{on}}$$

following the voltage-divider relationship.

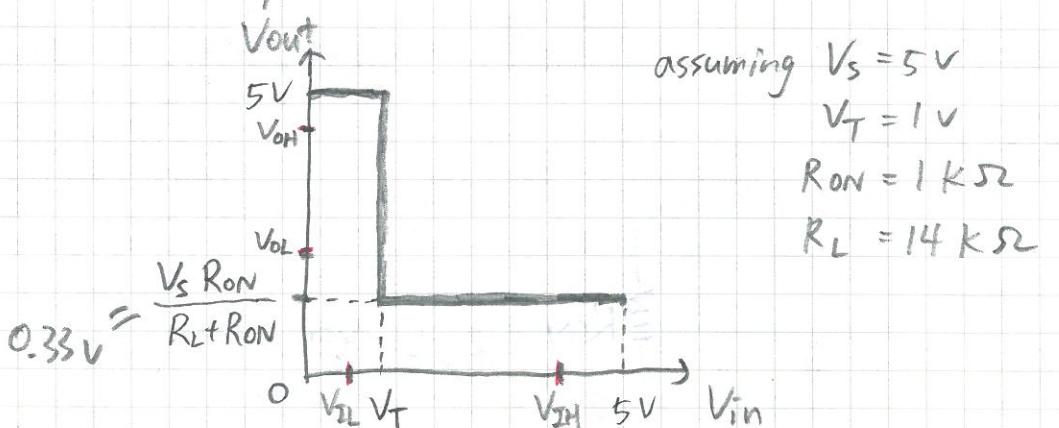And thus the transfer characteristic will become as follows (compare to one on P51):



This change of  $V_{out}$  value has at least two impacts:


P61

in ON state  
① To meet the static discipline,  $V_{out}$  needs to be lower than  $V_{OL}$ ; otherwise, we may observe that even though the magnitude of noise is within the specified margin, the value of  $V_{in}$  still exceeds  $V_{IL}$ .

→ solution A: redesign to reduce  $V_{out}$ .  
(from the manufacturer's viewpoint)

→ solution B: replace by a compatible device.  
(from the consumer's viewpoint)

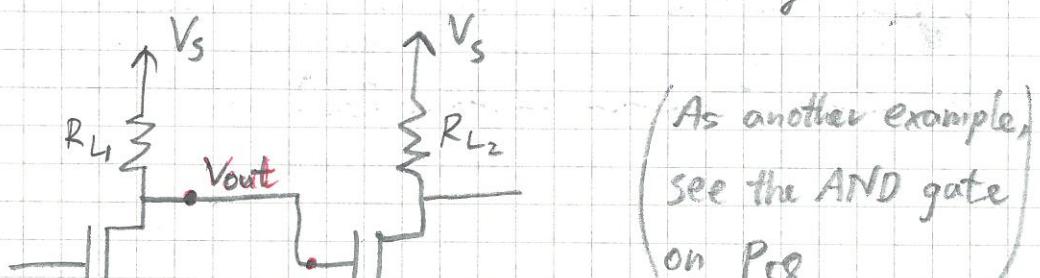② To drive another MOSFET,  $V_{out}$  in ON state needs to be lower than  $V_T$ , since  $V_{out}$  in OFF state equals  $V_s \geq V_T$ .  
usually



the driving MOSFET

the MOSFET whose ON/OFF state is driven by the preceding MOSFET.

P62

study Examples 6.5 and 6.6 in the textbook.

In general, since  $V_{out} = V_s \times \frac{R_{on}}{R_L + R_{on}}$ ,  
on state

to change  $V_{out}$ , we may  
 { ① change  $V_s$   
 ② change  $R_L$   
 ③ change  $R_{on}$

①  $\Rightarrow$  as a side-effect, it will also  
change  $V_{out}$  in OFF state!


②  $\Rightarrow$  { larger resistance is hard to achieve in VLSI;  
larger resistance would cause nontrivial  
voltage drop in the presence of leakage current;

③  $\Rightarrow$  may be achieved by changing the W/L ratio  
of the MOSFET.

$\Rightarrow$  An engineer's job often involves in finding  
the best solution among "multiple" options !!


\* Signal restoration, gain, and nonlinearity P63  
(Section 6.9 in the textbook)

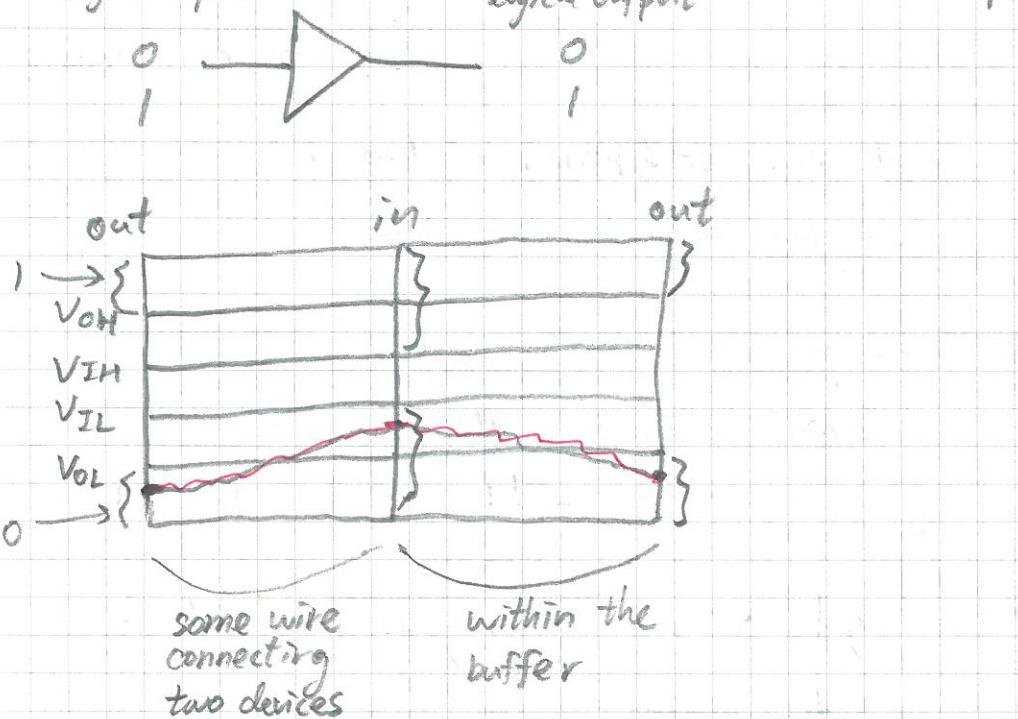We may use a device called "buffer" to  
restore a distorted signal (distorted by noise,  
logical input logical output for example):




As long as the system follows the static discipline, the output of a buffer will be closer to the output of the device that precedes it.

A rough implementation  
of a buffer:

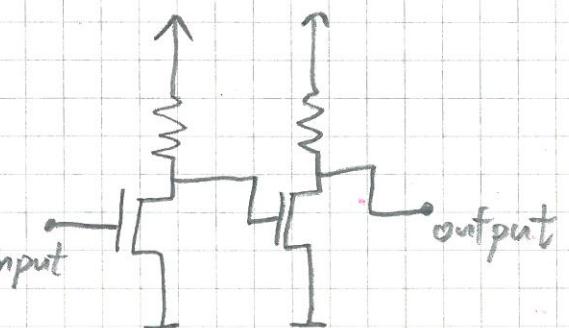

P64

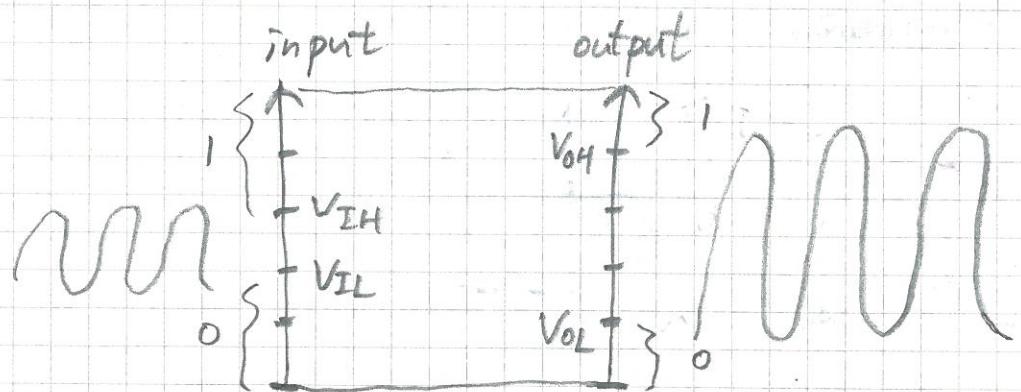In order for an electronic device to satisfies the system's specification of the static discipline, it turns out that such a device must be capable of amplifying an input signal. Why? Because a signal may fluctuate between logic 0 and logic 1:




Definition:

$$\text{Gain} = \frac{V_{OH} - V_{OL}}{V_{IH} - V_{IL}} \quad \text{for } V_{IL} \rightarrow V_{IH} \text{ transition}$$


for example, if  $V_{OH}=4$ ,  $V_{IH}=3$ ,  $V_{IL}=2$ ,  $V_{OL}=1$   
then the gain is 3.

P65

The transfer characteristic of a buffer:

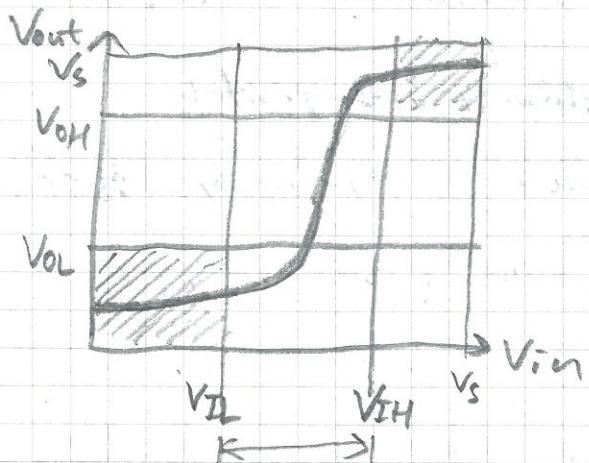

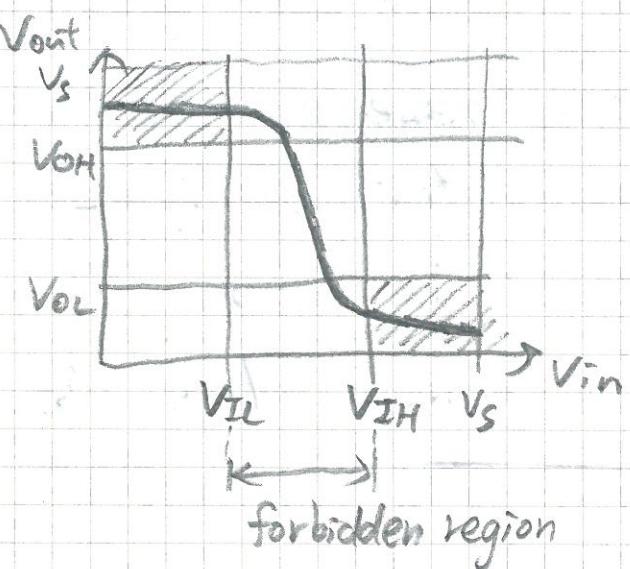The transfer characteristic of an inverter:



In both cases, the shaded region represents the valid region for the transfer curve.



Note that since  $V_{OL} < V_{IL}$  and  $V_s - V_{OH} < V_s - V_{IH}$ , the magnitude of the slope of the curve in the valid region is smaller than 1.

P66

So far, our discussion of MOSFET include its behavior as a switch (S model) as well as its linear  $V_{DS} - i_{DS}$  relation in its ON state (SR model, with resistor  $R_{ON}$ ).

In science and engineering, we are often curious about how a system would behave should we increase/decrease the value of a certain parameter. We have seen that a MOSFET will go from OFF state to ON state as we increase voltage  $V_{GS}$ .

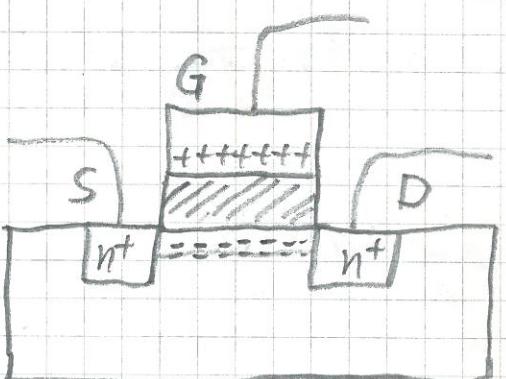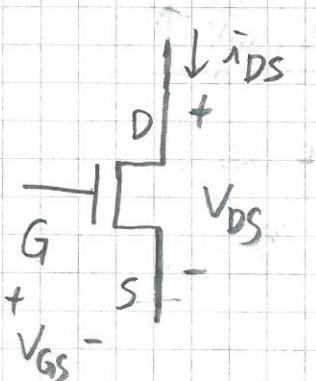
Now, let's consider what will happen if we gradually increase  $V_{DS}$ .




As we increase  $V_{DS}$ , the difference in electrical potentials between G and D decreases. 電位差

P67

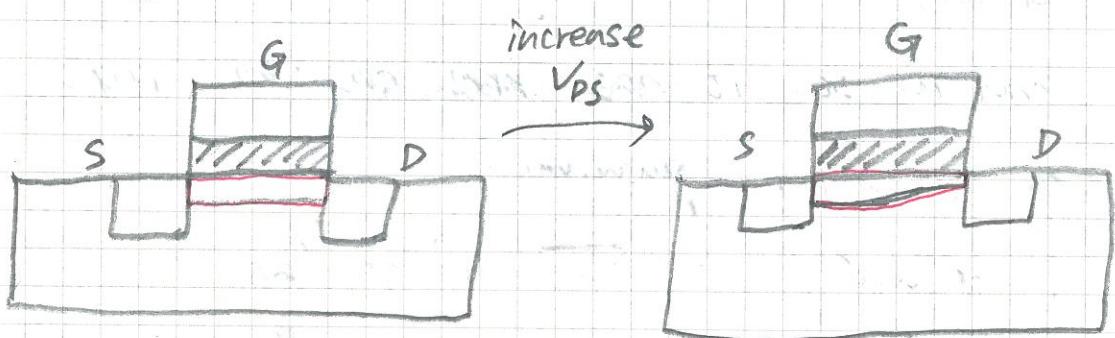This in turn will reduce the amount of free electrons near D, essentially shrinking the thickness of the conductible channel near D:



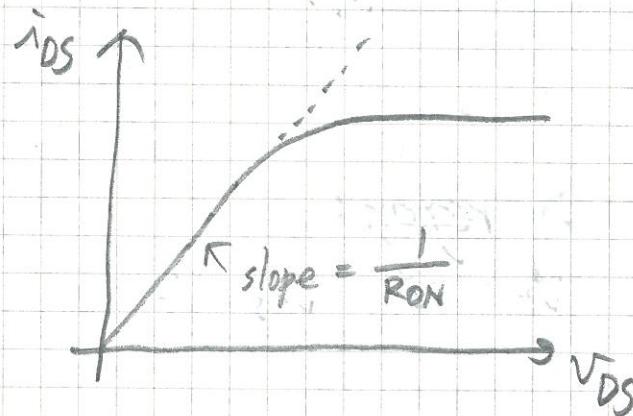Therefore we will see a bending of the curve on the  $i_{DS} - V_{DS}$  plot:




電阻截面積  $\downarrow$   
 $\Rightarrow$  電阻值  $\uparrow$   
 $\Rightarrow$  slope  $\downarrow$
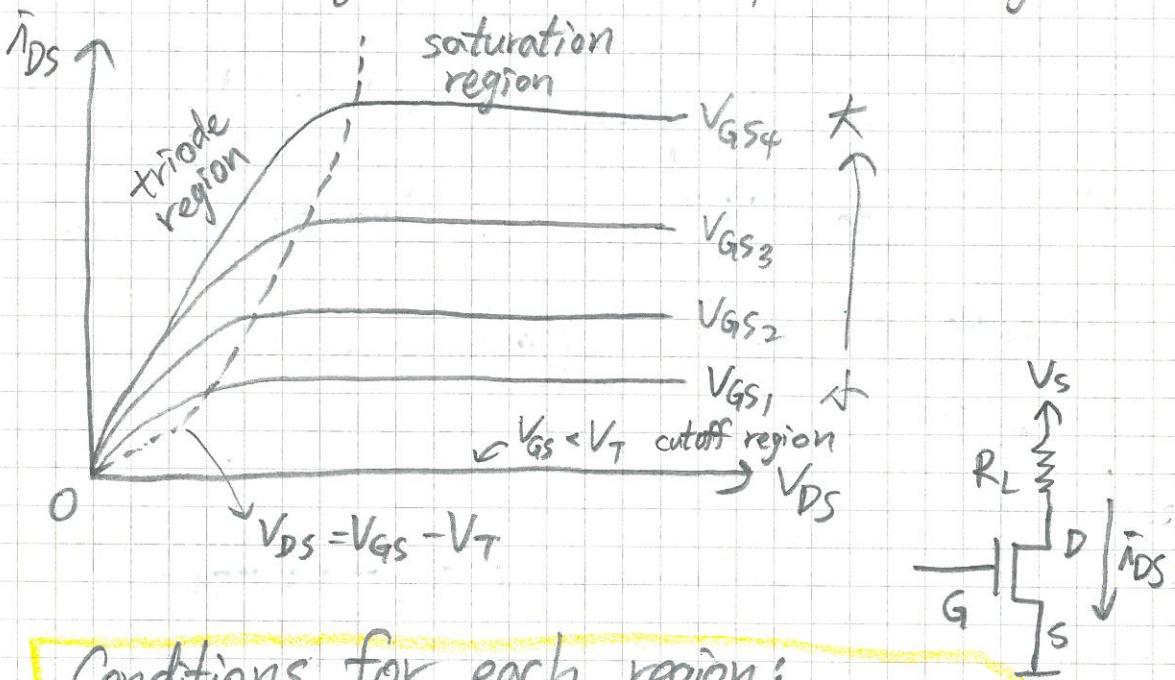
## P68 \* The SCS model of a MOSFET switch-current source

Compared to the S model and the SR model, the SCS model is a more accurate MOSFET model (closer to the real physical characteristic).

In the SCS model, a MOSFET can operate with three very different behaviors, and we say it has three "operational regions".




Conditions for each region:

$$\text{cutoff: } V_{GS} < V_T, \text{ i.e., } V_{GS} - V_T < 0$$

$$\text{saturation: } 0 \leq V_{GS} - V_T \leq V_{DS}$$

$$\text{triode: } V_{DS} < V_{GS} - V_T$$

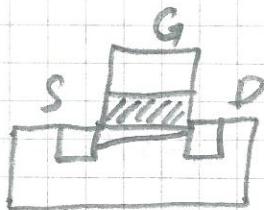In the saturation region, current  $i_{DS}$  would stay the same as we keep increasing  $V_{DS}$ , because the channel between source and drain has become stable :






(review P58, P66-67)

Therefore, we may consider such a behavior as if there is a "current source" (P13)

But  $i_{DS}$  would depend on voltage  $V_{GS}$ , and thus we say it is like a "voltage-controlled current source".

symbol:

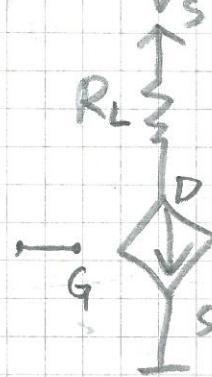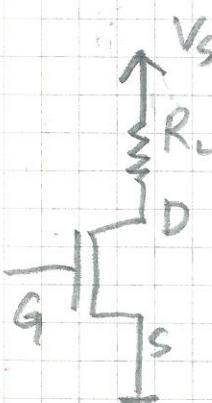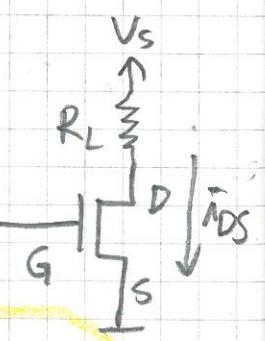

$$i_{DS} = f(V_{GS})$$

$$= \frac{K(V_{GS} - V_T)^2}{2}$$

(according to physics)


Note that  $K$  is a coefficient;

unit:  $\text{mA/V}^2$

if  $0 \leq V_{GS} - V_T \leq V_{DS}$   
→ in saturation region

P70

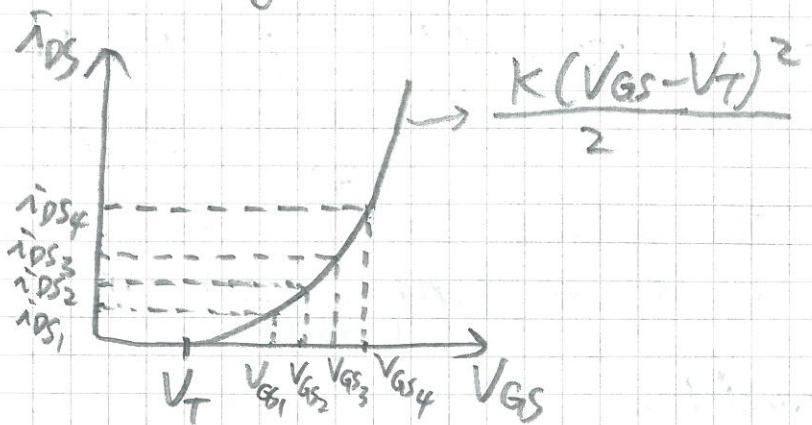
Plotting the  $i_{DS}$  -  $V_{GS}$  relation, we see:



$$\begin{aligned} \text{Therefore, if } |V_{GS_1} - V_{GS_2}| &= |V_{GS_2} - V_{GS_3}| \\ &= |V_{GS_3} - V_{GS_4}| \end{aligned}$$

we will have


$$|i_{DS_1} - i_{DS_2}| < |i_{DS_2} - i_{DS_3}| < |i_{DS_3} - i_{DS_4}|$$

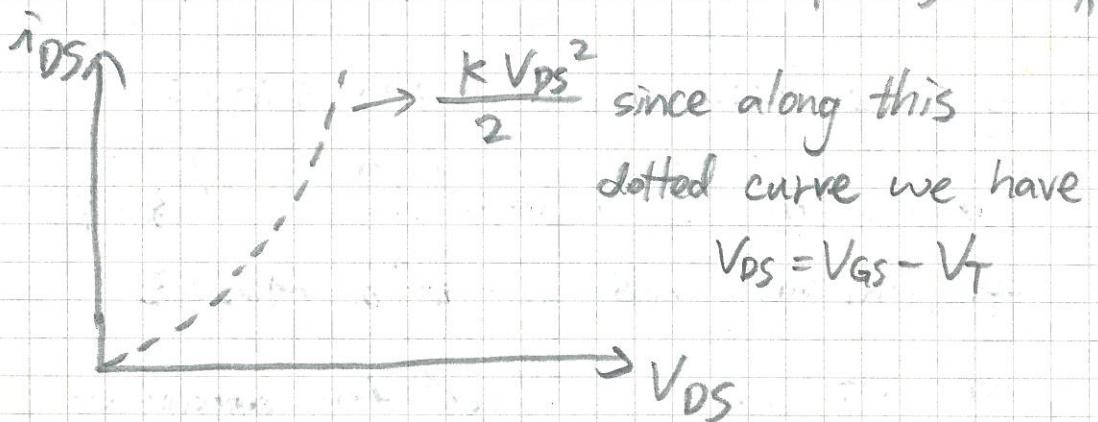

$$\Rightarrow i_{DS} = \begin{cases} 0 & \text{for } V_{GS} < V_T \\ \frac{K(V_{GS} - V_T)^2}{2} & \text{for } 0 \leq V_{GS} - V_T \leq V_{DS} \end{cases}$$

P71

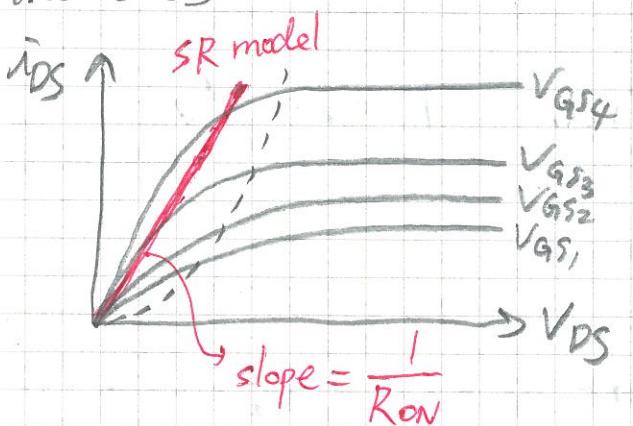From the aspect of the SCS model, the  $R_{ON}$  in the SR model can be thought of as a piecewise approximation of the  $i_{DS}$  -  $V_{DS}$  relation in the triode region in the SCS model:



We may summarize in this way:


The S model is good for analyzing the ON/OFF behavior of a MOSFET.

The SR model is good for approximating the MOSFET's behavior in the triode region.

P72 Let's work on two examples to

get ourselves familiar with the SCS model  
and its analysis:

Example 1.

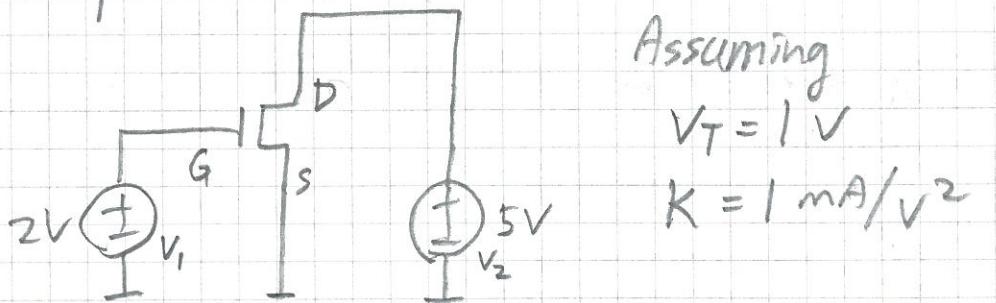

①  $i_{DS} = ?$  since  $V_{GS} = 2 \text{ V} > V_T$

and  $V_{DS} = 5 \text{ V} > V_{GS} - V_T = 1$ ,

we see the MOSFET is operating in the saturation region  $\Rightarrow i_{DS} = \frac{k(V_{GS}-V_T)^2}{2} = 0.5 \text{ mA}$

② If we keep  $V_1$  and decrease  $V_2$ , at what condition of  $V_2$  will the MOSFET enter the triode region?

$\rightarrow$  As long as  $V_{DS} \geq V_{GS} - V_T$  the MOSFET will stay in the saturation region

$\rightarrow$  if  $V_2 = V_{DS} < V_{GS} - V_T = 1 \text{ V}$ , the MOSFET will enter the triode region.


P73  
③ If we keep  $V_2$ , what would be the range of  $V_1$  for the MOSFET to stay in the saturation region?

$$\rightarrow V_{DS} \geq V_{GS} - V_T$$

$$\rightarrow 5 \geq V_{GS} - 1 \rightarrow V_{GS} \leq 6$$

$$\rightarrow V_1 = V_{GS} \leq 6 *$$

Example 2.

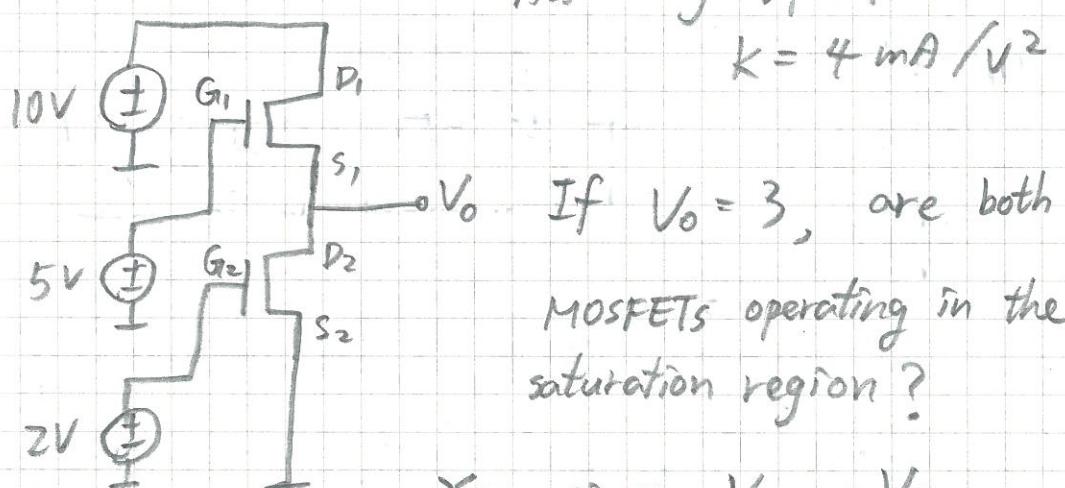

If  $V_0 = 3$ , are both MOSFETs operating in the saturation region?

Yes, since  $V_{G1S1} - V_T = (5-3) - 1 = 1 > 0$

and  $\underline{V_{G1S1} - V_T} \leq \underline{V_{RS1}} = 10 - 3 = 7$

And  $V_{G2S2} - V_T = 2 - 1 = 1 > 0$

and  $\underline{V_{G2S2} - V_T} \leq \underline{V_{RS2}} = 2 - 1 = 1$


And  $V_{G1S1} = V_{G2S2}$  correctly implies  $i_{D1S1} = i_{D2S2} *$

P74 (Note on 2020/6/1 3PM:

I apologize for the confusion regarding whether  $V_o=2$  in Example 2 makes sense or not.

After some more thoughts, I think what I said this morning is wrong.

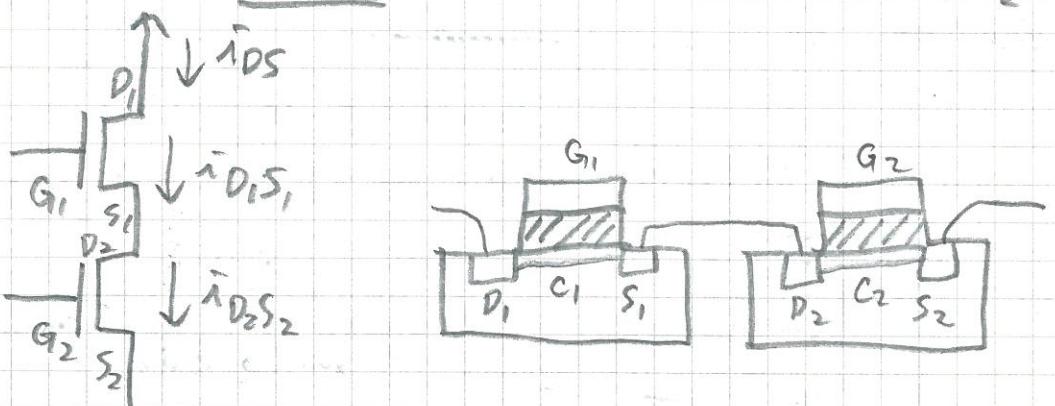It is wrong that  $\bar{i}_{DS} = \bar{i}_{D_1S_1} + \bar{i}_{D_2S_2}$



In physics,  $\bar{i}_{D_1S_1}$  is constrained by channel  $C_1$ , and  $\bar{i}_{D_2S_2}$  is constrained by channel  $C_2$ . It should be that

$$\bar{i}_{DS} = \bar{i}_{D_1S_1} = \bar{i}_{D_2S_2}.$$


And therefore  $V_o=2$  does NOT make sense.)

Now let's see how we may leverage P75

a MOSFET operating in the saturation region for some useful purposes.

It turns out that in the saturation region a MOSFET may be used to amplify a signal.

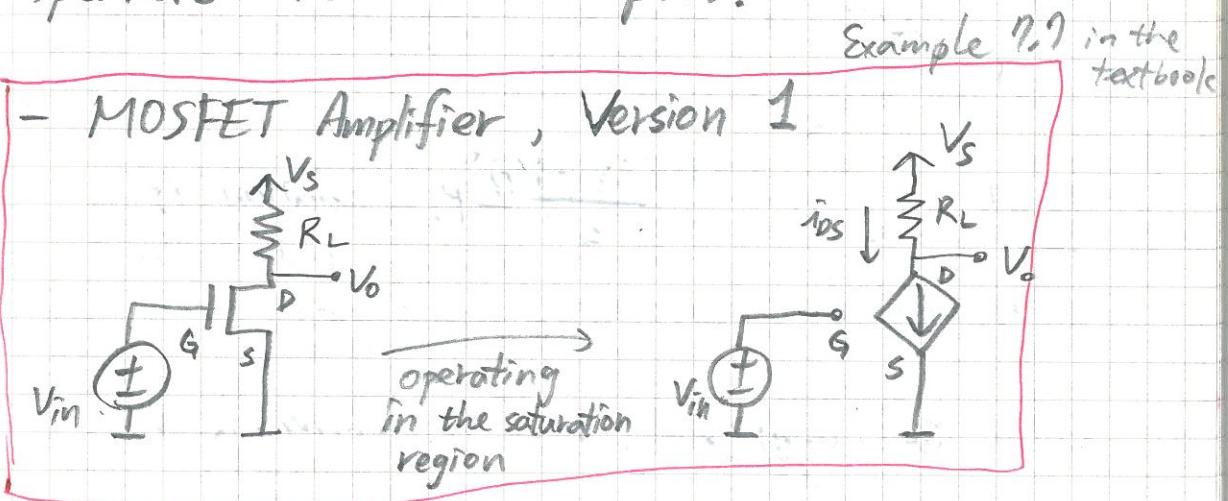Amplifiers are used in many real-world applications and systems. Headphones and speakers are two examples.



The voltage-controlled current source gives


$$\bar{i}_{DS} = \frac{K(V_{GS} - V_T)^2}{2} \quad (\text{see P69})$$

and in addition, by Ohm's law  $\bar{i}_{DS} = \frac{V_s - V_o}{R_L}$

$$\Rightarrow \left\{ \frac{K(V_{GS} - V_T)^2}{2} = \frac{V_s - V_o}{R_L} \right\} \Rightarrow V_o = V_s - K \cdot \frac{(V_{in} - V_T)^2}{2} \cdot R_L$$

(and that  $V_{GS} = V_{in}$ )

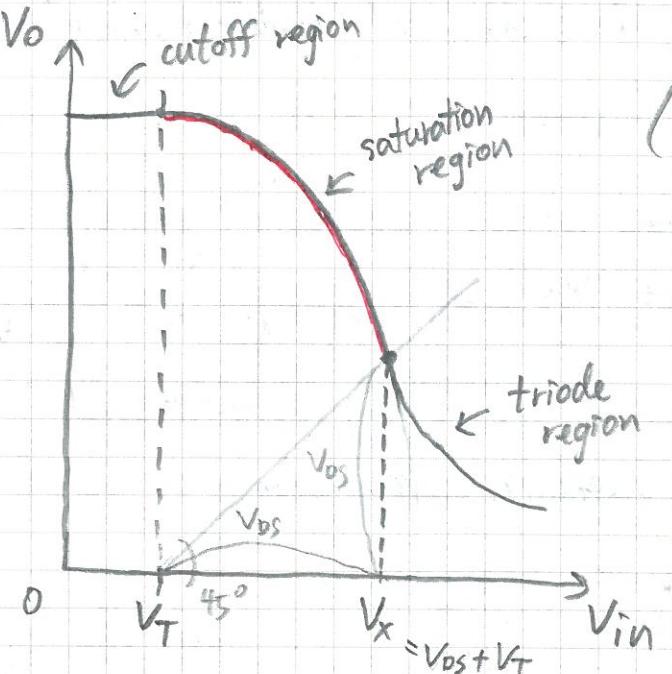P76 following the equation on P75, we have



( compare this to the plots on P57 and P65 )

The  $V_o = V_s - \frac{K(V_{in}-V_T)^2}{2} R_L$  relation is only valid when  $V_T \leq V_{in} \leq V_x$ .

Later we will study how to determine  $V_x$ .  
(P81)

The slope  $\frac{V_o}{V_{in}}$  is also the ratio between  $V_{in}$  and  $V_o$ .

We see that in some part of the saturation region the magnitude of the slope is greater than one. Therefore we may amplify  $V_{in}$  by  $\frac{V_o}{V_{in}}$  times and output the result as  $V_o$ .

The "gain" of the amplifier is defined to be  $\frac{V_o}{V_{in}}$ .

Using this MOSFET amplifier, however,

the output will be inverted, which might not be what we want:

$$\begin{cases} V_{in} \downarrow \Rightarrow V_o \uparrow \\ V_{in} \uparrow \Rightarrow V_o \downarrow \end{cases}$$

( can be verified by the sign of the slope in the  $V_o - V_{in}$  plot. )



Let's study an alternative design

example 7.12  
in the textbook

### - MOSFET Amplifier, Version 2

In this configuration, we use one voltage source to provide voltages to the gate and the drain.

This is equivalent to :

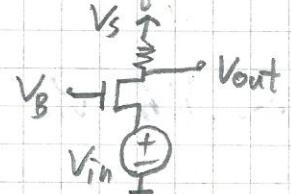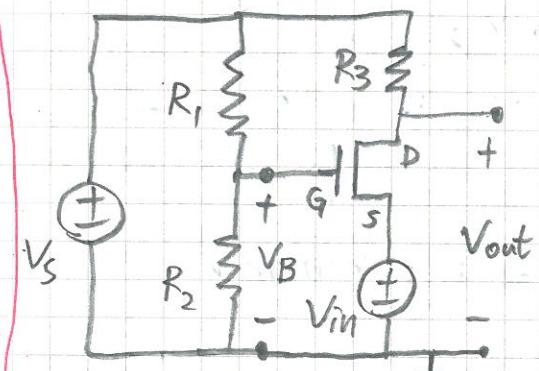

$$V_{GS} = V_B - V_{in}$$

$$= \left( V_s \times \frac{R_2}{R_1 + R_2} \right) - V_{in}$$

Therefore, we have  

$$\frac{K(V_{GS}-V_T)^2}{2} = \frac{V_s - V_{out}}{R_3}$$

In saturation region, we have

$$I_{DS} = \frac{K(V_{GS}-V_T)^2}{2}$$

and by Ohm's law


$$I_{DS} = \frac{V_s - V_{out}}{R_3}$$

$$\Rightarrow \frac{K(V_s \times \frac{R_2}{R_1 + R_2} - V_{in} - V_T)^2}{2} = \frac{V_s - V_{out}}{R_3}$$

P78 following the equation on P77, suppose

that  $\begin{cases} V_S = 10 \text{ V} \\ R_1 = 84 \text{ k}\Omega, R_2 = 16 \text{ k}\Omega, R_3 = 20 \text{ k}\Omega \\ V_T = 1 \text{ V}, K = 1 \text{ mA/V}^2 \end{cases}$

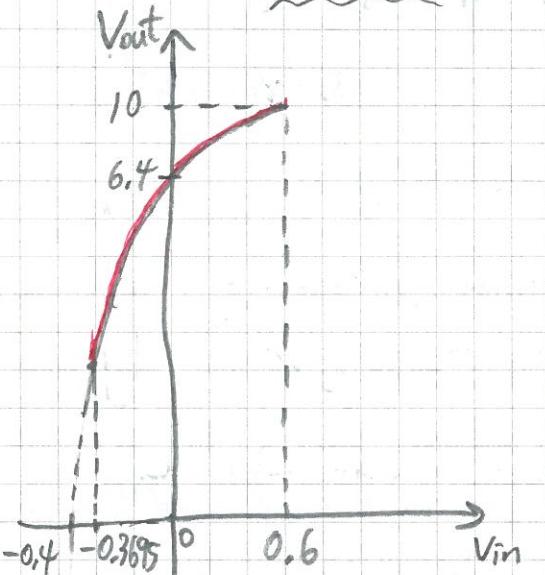then  $V_B = 1.6$  and  $V_{out} = 10 - 10(0.6 - V_{in})^2$



To operate in the saturation region, both of the following conditions must be satisfied:

$$\begin{cases} V_{GS} \geq V_T \quad \text{--- (1)} \\ V_{GS} - V_T \leq V_{DS} \quad \text{--- (2)} \end{cases}$$

from (1),  $1.6 - V_{in} \geq 1 \Rightarrow V_{in} \leq 0.6 \text{ V}$

from (2),  $(1.6 - V_{in}) - 1 \leq V_{out} - V_{in}$

$$\Rightarrow V_{out} \geq 0.6 \text{ V}$$

$$\Rightarrow 10 - 10(0.6 - V_{in})^2 \geq 0.6$$

$$\Rightarrow -0.3695 \text{ V} \leq V_{in} \leq 1.5695 \text{ V}$$

$$-0.3695 \text{ V} \leq V_{in} \leq 0.6 \text{ V}$$

Thus we see that

it is an amplifier ( $\frac{V_{out}}{V_{in}} > 1$ )

and  $\begin{cases} V_{in} \uparrow \Rightarrow V_{out} \uparrow \\ V_{in} \downarrow \Rightarrow V_{out} \downarrow \end{cases}$

\*  $\downarrow$

P79  
For the purpose of signal amplification, and for the SCS model in general, we would want to make sure that the MOSFET operates in the saturation region. Given the circuit's parameters, in order to determine whether the MOSFET will operate in the saturation region (or to determine the valid range of values of parameters), we may use the conditions listed on P68 or use graphical analysis.

For example, for the MOSFET amplifier on P75, suppose  $V_S = 5 \text{ V}$ ,  $R_L = 1 \text{ k}\Omega$ ,  $V_T = 0.8 \text{ V}$ ,  $V_{in} = 2.5 \text{ V}$ ,  $K = 0.5 \text{ mA/V}^2$   
is the MOSFET in the saturation region?

Answer:  $V_{GS} = V_{in} = 2.5 \text{ V}$

$$V_{DS} = V_o = V_S - K \frac{(V_{in} - V_T)^2}{2} R_L = 4.28 \text{ V}$$

and we see that both  $\begin{cases} V_{GS} \geq V_T \\ V_{DS} \geq V_{GS} - V_T \end{cases}$

Therefore, it is indeed in the saturation region. #