

☆ Signals, Systems, and Computing

P1

- In computing systems, information (and energy) is stored and transferred in terms of signals, which are currents or voltages as a function of time.


A circuit (or a system of circuits), as we study in this course, is used to

- ① carry signals
- ② transform signals from one to another


Computing is also a transformation of signals; though the signals are digital and the transformation is described at a higher layer of the abstraction (Figure 1.1 in the textbook).

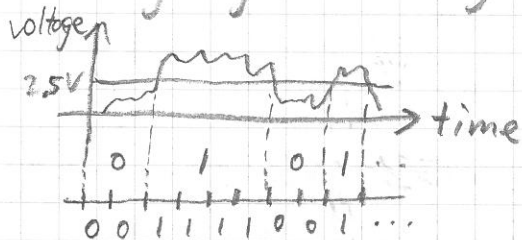Example: We use a smart phone to record this lecture (voice signal \rightarrow currents and voltages), and the recording is stored in the phone, transferred via USB to your laptop, uploaded to a cloud drive, downloaded by your friend who cannot make it to the class, and finally played by your friend's speakers/headphone (currents and voltages \rightarrow voice signals).

- Analog signal to digital signal via discretization:



P₂ - The lumped circuit abstraction

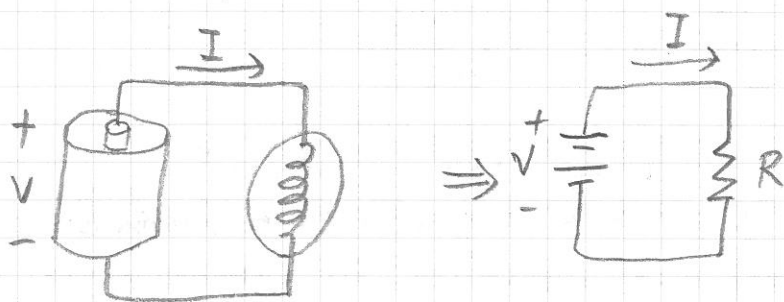

for now, let's just consider elements having two terminals, e.g.,



battery,
lightbulb

We may ignore the internal structure of an element and consider it as a "lump", where we may completely describe relevant properties (such as voltage and current) by only observing its terminals.

For example, if a resistor with resistance R obeys Ohm's law, then we may compute the current flowing through the resistor by the voltage across its terminals: $I = V/R$.

The lumped circuit abstraction works only under certain constraints, which we call the lumped matter discipline (LMD).


From Physics to Electronic Circuit:

★ The lumped matter discipline (LMD) → a set of rules that control an activity or situation.


- simplify the analysis of electronic circuit
- modularize a complex circuit into analyzable elements

Derivation of LMD:

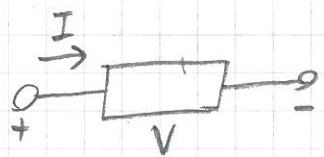goal #1:
able to describe a unique voltage across the terminals x and y



example element
燈絲, U型, 長度為 l

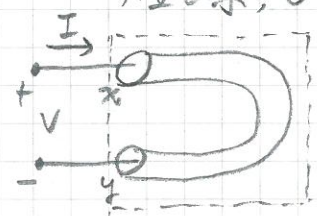

definition of voltage:

$$V_{yx} = - \int_x^y \mathbf{E} \cdot d\mathbf{l}$$

where \mathbf{E} is the electrical field (a vector)
 $d\mathbf{l}$ is a tiny portion of l

and Faraday's law of induction:

$$\oint \mathbf{E} \cdot d\mathbf{l} = - \frac{\partial \Phi_B}{\partial t}$$

where Φ_B is the magnetic flux.

\oint represents a closed path integral

a sufficient condition
充分條件


Thus, we see that if there's no time-varying magnetic flux,

$$\oint \mathbf{E} \cdot d\mathbf{l} = 0 \Rightarrow \int_x^y \mathbf{E} \cdot d\mathbf{l} + \int_y^x \mathbf{E} \cdot d\mathbf{l} = 0$$

along path 1 path 2

$$\Rightarrow \int_x^y \mathbf{E} \cdot d\mathbf{l} = \int_x^y \mathbf{E} \cdot d\mathbf{l}$$

path 1 path 2

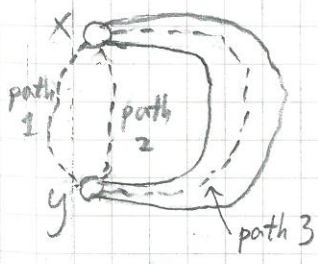

Think about it.
Why is this important?

也就是說 $\int_x^y \mathbf{E} \cdot d\mathbf{l}$ 的值和路徑無關! $(= \int_x^y \mathbf{E} \cdot d\mathbf{l})$

P4

Therefore, the constraint for goal #1 is

$$\frac{\partial \phi_B}{\partial t} = 0,$$

and we assumed that holds for all time.

(To make sure this constraint holds, we may need to revise the model and introduce an element called "inductor".)

goal #2:

able to define a unique current through the terminals x and y

First of all, the definition of current:

$$I = \int_{S_z} \mathbf{J} \cdot d\mathbf{S}$$




where \mathbf{J} is the current density at a given point within a filament and S_z is the cross-sectional surface of the filament at point z .

Due to the conservation of charge, we have

$$\oint \mathbf{J} \cdot d\mathbf{S} = - \frac{\partial q}{\partial t} \quad \text{for a closed surface}$$

~~~~~  
流出的电量      减少的电量

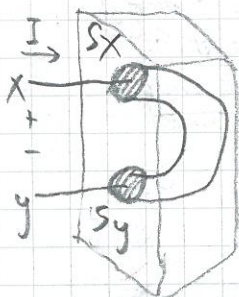

假設  $S_x$  為唯一入口  
 $S_y$  為唯一出口。

Thus, if there's no time-varying charge within the closed surface, we have

$$\oint \mathbf{J} \cdot d\mathbf{S} = 0 \Rightarrow - \int_{S_x} \mathbf{J} \cdot d\mathbf{S} + \int_{S_y} \mathbf{J} \cdot d\mathbf{S} = 0$$

$$\Rightarrow \int_{S_y} \mathbf{J} \cdot d\mathbf{S} = \int_{S_x} \mathbf{J} \cdot d\mathbf{S}$$



$$I_{in} = I_{out}$$

Therefore, the constraint for goal # 2 is

P5

$$\frac{\partial g}{\partial t} = 0,$$

and we assume that holds for all time.


(To make sure this constraint holds, we may need to revise the model and introduce an element called "capacitor".)

Besides goals #1 and #2, we also need to assume that the signal timescale must be much larger <sup>→ rate of change, i.e., frequency</sup> than the propagation delay of electromagnetic waves across the lumped elements. (Otherwise, ... see textbook pages 11, 12)

... 0110100... for example

⇒ the size of our lumped elements must be much smaller than the wavelength associated with the V and I signals, and such a condition may be challenging to hold as we reduce the element size and increase the operating frequency (e.g., a 2GHz CPU).

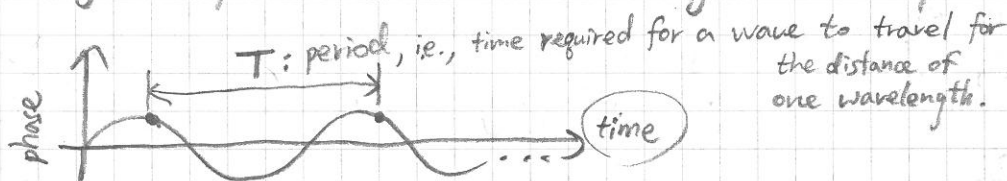definition of wavelength<sup>(λ)</sup>: the distance between two adjacent points in the wave having the same phase.



$$\lambda = v \cdot T = v \cdot \frac{1}{f} \Rightarrow f \uparrow \text{ then } \lambda \downarrow$$

↑ wavelength    ↑ wave speed    ↑ period    ↑ frequency



For example, electromagnetic waves travel at about  $15 \times 10^4$  km/s, or  $15 \times 10^9$  cm/s, within a microprocessor (to be specific, through silicon dioxide).

Now, suppose that the microprocessor operates at a clock rate of 2 GHz. This translates to the wavelength equal to  $\lambda = 15 \times 10^9 / 2 \times 10^9 = 7.5$  cm,

which means that LMD may not hold if the microprocessor chip is larger than 7.5 cm on a side.

Think about it: what if ① clock rate  $\uparrow$  ?  
② wave speed  $\uparrow$  ?

In general, in computer engineering, people are often working to meet various constraints (such as this) so that they may apply a previously established model (such as LMD) and make use of known results/properties that depend on the given model. This is like "Standing on the shoulders of giants."


- Basic lumped element 1: batteries

Two key properties { energy 能量 (unit: joule or ampere-hours)  
power 功率 (unit: watt or watt-hours)

能量轉換或使用的速率

$$P = V \cdot I$$
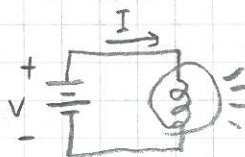
$$1 \text{ watt} = 1 \text{ volt} \cdot 1 \text{ ampere}$$



erties

55

tain  
(LMD)

P7 Let  $\mathcal{E}$  be the amount of energy supplied to an element over an interval  $T$ , then we have  $\mathcal{E} = P \cdot T$ . In general, the amount of energy supplied is the time integral of the power.

$$1 \text{ joule} = 1 \text{ watt-second}$$

Example: Suppose a Raspberry Pi consumes 2W of power and its energy is supplied by a 3.7V, 2600 mA-h battery. For how long can the battery power the Raspberry Pi?

$$P = V \cdot I = 3.7 \times 2600 \times 10^{-3} \text{ W-h} \\ = 9.62 \text{ W-h}$$

$$\frac{9.62 \text{ W-h}}{2 \text{ W}} = 4.81 \text{ hours}^*$$

## - Basic lumped element 2: resistors (linear)

Ohm's law: the voltage measured across the terminals of a resistor is linearly proportional to the current flowing through the resistor.


That is,  $\boxed{\frac{V}{I} = R}$

we call it the resistance of a resistor.

Further,  $\boxed{R = \rho \frac{l}{a}}$


(see Appendix A.3 in the textbook)

resistivity

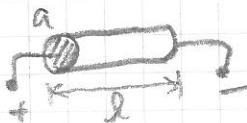




also,  $R = \rho \frac{l}{wh}$

for a cube

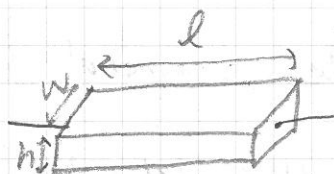

P8

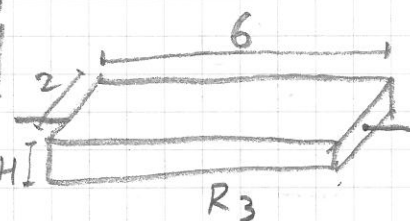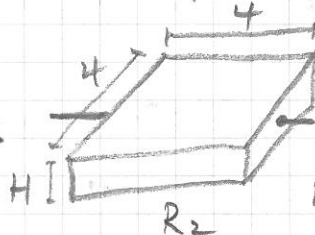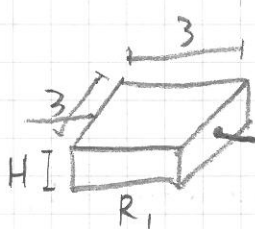Example: Consider three planar resistors as follows



Let  $R_0 = \rho_0 \frac{1}{1 \cdot H} = 2 \text{ k}\Omega$  and assume  $\rho_0 = \rho_1 = \rho_2 = \rho_3$

Then  $R_1 = \rho_1 \frac{3}{3 \cdot H} = R_0 = 2 \text{ k}\Omega$

$$\frac{R_1}{R_2} = \frac{\rho_1 \frac{3}{3H}}{\rho_2 \frac{4}{4H}} = 1 \text{ and } R_2 = R_1 = 2 \text{ k}\Omega$$

$$\frac{R_2}{R_3} = \frac{\rho_2 \frac{4}{4H}}{\rho_3 \frac{6}{2H}} = \frac{1}{3} \Rightarrow R_3 = 6 \text{ k}\Omega$$

exercise: you can verify that  $\frac{R_1}{R_3} = \frac{R_2}{R_3}$ .

⇒ 等比例縮小長及寬，則相對電阻值 \_\_\_\_\_ ?

⇒ 縮小晶片的大小不會改變相對電阻值

A. ↓ B. ↑ C. 不變

⇒ Often, signal values are derived as a function of resistance ratios. Therefore, by such a process shrink, the chip may continue to function as before!

example: a "voltage divider," which we will study soon this semester.