

Solution

## CSU0007 Basic Electronics, Homework 4


- Three questions in total. Submit your work via Moodle before 9PM, Dec 4th, 2020.
- Clearly state your reasoning to earn full score.
- Textbook coverage: Section 6.1 to Section 6.8 (before Section 6.8.1).
- The assignment for self-study: Section 6.8.1 in the textbook (no need to submit this assignment).

1. (30 points) Consider the S model. In the following circuit, suppose the input {A, B, C} corresponds to logical {0, 1, 0}. What would be the logical value output at D?

$$D \equiv \overline{AB+C} = AB + \overline{C}$$

$$\{A, B, C\} = \{0, 1, 0\}$$

$$\Rightarrow D \equiv 0$$

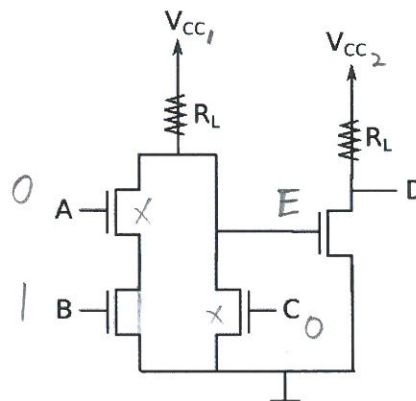

Typically, in this configuration we'll get E as logical 1, and therefore D is logical 0. In an unusual case where  $V_{CC1} < V_{IL}$ , then E will be always logical 0; similarly, if  $V_{CC2} < V_{OH}$ , then there's no way to make D equal to logical 1.

2. (40 points) Now, consider the SR model. Explain in your own words that under the static discipline,


1. (20 points) why we must have  $V_{IL} < V_T$ ?
2. (20 points) why we must have  $V_{OL} > V_{CC} \frac{R_{ON}}{R_{ON} + R_L}$ ?

3. (30 points) Consider the SR model and the following specification: The noise margin is 0.5V for logical 0 and 1V for logical 1. The forbidden region is from 1V to 1.5V.  $V_T = 1.2V$ ,  $V_{CC} = 3.3V$ , and  $R_N = 5k\Omega$ . Now, to build a MOSFET to meet this specification, what would be the maximum feasible value of ratio  $\frac{L}{W}$ ? Assuming that  $R_L = 8k\Omega$ .

2.1 otherwise, we might have two outcomes for logical 0 input  $\left\{ \begin{array}{l} \text{outcome A for } V_T < V_{in} < V_{IL} \\ \text{outcome B for } V_{in} < V_T \end{array} \right.$

2.2 otherwise, we may never be able to output logical 0, since  $V_{CC} \times \frac{R_{ON}}{R_{ON} + R_L}$  is the minimum value of the output voltage.

3

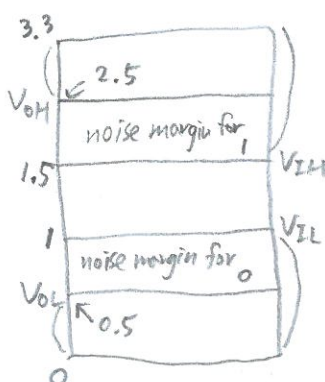

To meet the static discipline, we must have  $V_{IL} < V_T$  and  $V_{OL} > V_{CC} \times \frac{R_{ON}}{R_{ON} + R_L}$

$$\Rightarrow 0.5 > 3.3 \times \frac{R_{ON}}{R_{ON} + 8}$$

$$\Rightarrow R_{ON} < \frac{4}{2.8}$$

$$\Rightarrow 5 \times \frac{L}{W} < \frac{4}{2.8} \Rightarrow \frac{L}{W} < \frac{2}{7}$$