



When calculating the input/output resistance, it is important that we suppose all "independent" voltage sources and current sources are turned off:



are turned off;

Why? Because those voltage/current sources theoretically have i-v characteristics that

resemble zero/ $\infty$  resistance :

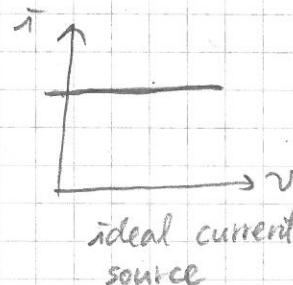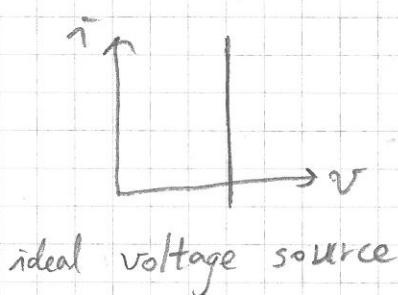

(resistance is the inverse of the slope of the curve.)


For "dependent" voltage sources and current sources, however, we do not always <sup>suppose</sup> they are turned off, because their values depend on others.

Finally, for small-signal  $r_i$  and  $r_o$ , we will still consider the corresponding DC biases because it is their existence that determines the structure of the small-signal circuit.

# \* Difference Amplifier

The physical environment in which an electronic system operates often introduces noises to


the system :

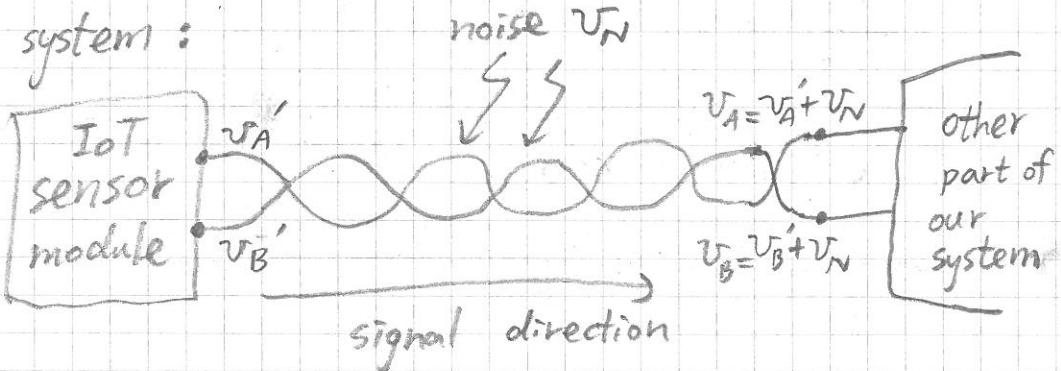

It would be good if we can <sup>①</sup>reduce the noise and <sup>②</sup>amplify the original signal.

Difference amplifiers are designed for this purpose.

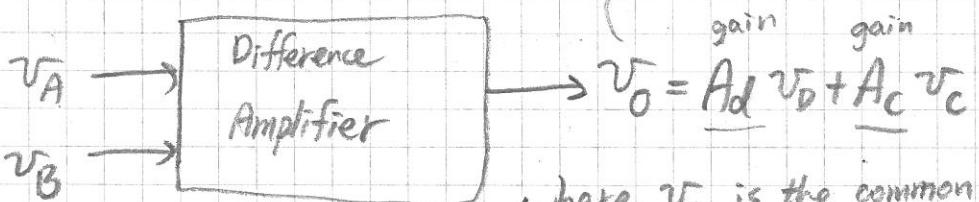( Note that the two wires are twisted together so that the same amount of noise infects both signals, which then can be reduced by having the amplifier reduce <sup>the magnitude of</sup> the common component of the signals. )




where  $V_C$  is the common component shared by  $V_A$ ,  $V_B$  and  $V_D$  is the difference between  $V_A$ ,  $V_B$

think about it as  $V_O = f(V_D, V_C)$

gain gain

$$V_O = Ad V_D + Ac V_C$$

We can visualize the setup this way:

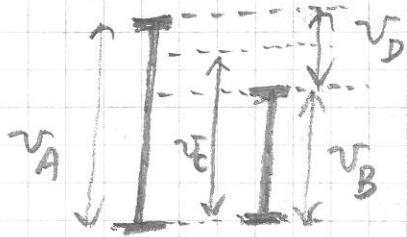

$$V_D = V_A - V_B$$

is called the difference-mode component signal.

$V_C = (V_A + V_B)/2$  is called the common-mode component signal.

Therefore, we may represent  $V_A$  and  $V_B$  in terms of  $V_C$  and  $V_D$ :

$$\begin{cases} V_A = V_C + \frac{1}{2}V_D \\ V_B = V_C - \frac{1}{2}V_D \end{cases}$$

A reason to choose  $V_C = (V_A + V_B)/2$  is just for convenience; as long as the quantity  $V_A - V_B$  is represented by some variable ( $V_D$  here), we may choose other linear combination of  $\{V_A, V_B\}$  for  $V_C$ .

It is convenient if we choose  $V_C$  such that  $V_A \leq V_C \leq V_B$ . Otherwise, for example, letting

$V_C = V_B - \Delta V$ , then we'll have

$$\begin{cases} V_A = V_C + \Delta V + V_D \\ V_B = V_C - \Delta V \end{cases} \quad \text{which is ugly.}$$

Going back to equation  $V_o = A_D V_d + A_c V_c$ ,

$A_D$  is called the difference-mode gain, and

$A_c$  is called the common-mode gain.

Our goal is to design a circuit so that

$A_D$  is large and  $A_c$  is small (relatively),  
to reduce noise.

In particular, people use  $\frac{A_D}{A_c}$  to quantify  
the ability of the circuit to reject noise.

$\frac{A_D}{A_c}$  is called Common-Mode Rejection Ratio.  
(CMRR)

We are in particular interested in the small-signal behavior of a difference amplifier. To be specific, represent the small-signal output

as  $V_o = \tilde{A}_D \tilde{V}_d + \tilde{A}_c \tilde{V}_c$ , and we want a large  $\tilde{A}_D$  and a small  $\tilde{A}_c$ .


Represent the small-signal inputs as

$$\left\{ \begin{array}{l} \tilde{V}_a = \tilde{V}_c + \frac{1}{2} \tilde{V}_d \\ \tilde{V}_b = \tilde{V}_c - \frac{1}{2} \tilde{V}_d \end{array} \right.$$

Conventionally, people use superposition to consider each mode separately. We'll do this in the following pages.


P98

First of all, the overall structure:

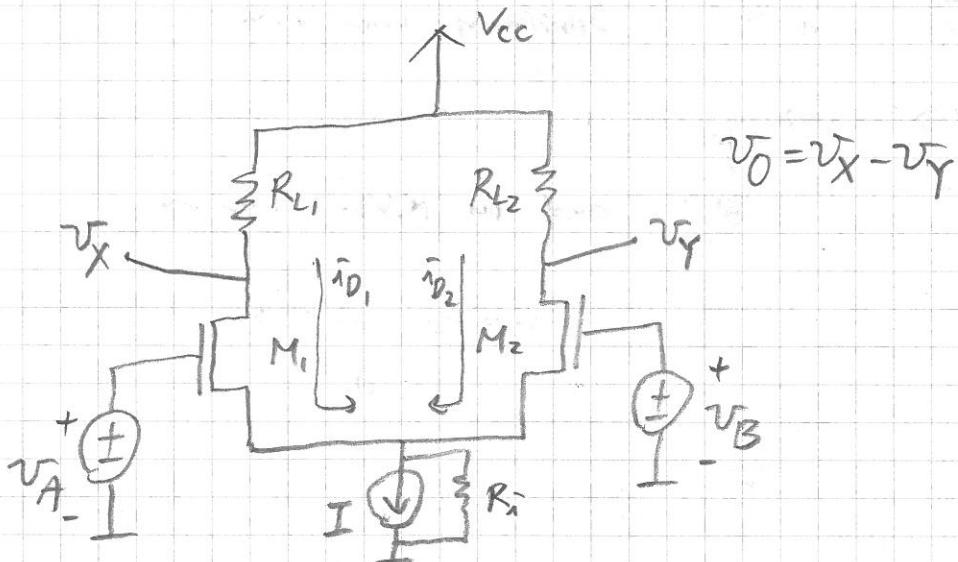

Assuming symmetry, that is,  $R_{L1} = R_{L2}$  and MOSFETs  $M_1 = M_2$ . And assume  $R_i$  is very large. Also, assume that both  $M_1$  and  $M_2$  operates under the saturation discipline.

Difference Mode (small signal):

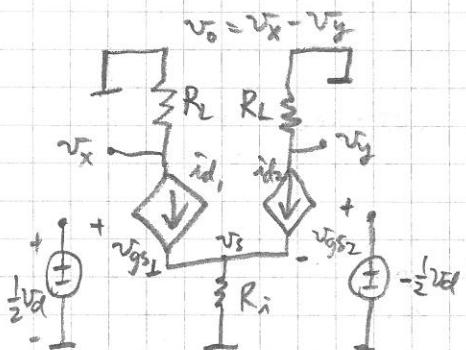

$$\begin{cases} \bar{i}_{d1} = g_m \cdot v_{gs1}, \\ \bar{i}_{d2} = g_m \cdot v_{gs2} \end{cases}$$


$$\begin{aligned} \text{from KVL, we may replace } v_{gs1}, v_{gs2} \\ \Rightarrow \begin{cases} \bar{i}_{d1} = g_m \left( \frac{1}{2}v_d - v_s \right) \\ \bar{i}_{d2} = g_m \left( -\frac{1}{2}v_d - v_s \right) \end{cases} \end{aligned}$$

$$v_o = v_x - v_y = -\bar{i}_{d1} R_{L1} + \bar{i}_{d2} R_{L2}$$

$$= -g_m \bar{v}_d \cdot R_L$$

$$\Rightarrow A_d = \frac{v_o}{v_d} = -g_m \cdot R_L$$

## Common Mode (small signal):

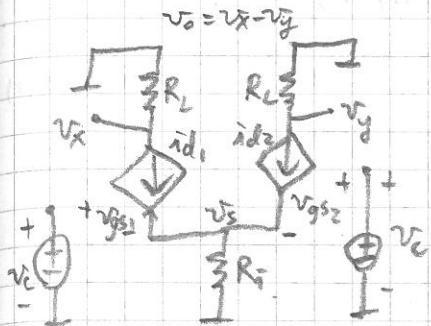

Similarly, we have

$$\begin{cases} id_1 = g_m \cdot v_{gs1} \\ id_2 = g_m \cdot v_{gs2} \end{cases}$$

and by KVL, we get

$$\begin{cases} id_1 = g_m (v_c - v_s) \\ id_2 = g_m (v_c - v_s) \end{cases}$$

$$v_o = v_x - v_y = -id_1 R_L - (-id_2 R_L) = 0$$

$$\Rightarrow A_c = \frac{v_o}{v_c} = 0$$

Therefore, with  $A_d = -g_m R_L$  and  $A_c = 0$ , we see

$$v_o = A_d v_d + A_c v_c = -g_m R_L v_d$$

which means that, from small-signal viewpoint, the output of the difference amplifier is effectively the amplified version of the signal difference between input  $v_a$  and  $v_b$ , and with no component from the common component among  $v_a$  and  $v_b$ !

Next, let's analyze the <sup>small-signal</sup> output resistance of this difference amplifier (the input resistance is  $\infty$ , since

To do so, we in the follow page use

Thévenin's Theorem to transform the circuit in each mode, and then use superposition to jointly calculate the output resistance.


Note that this is a good strategy because  $\rightarrow$

-15  
insulation


P100

often Thévenin's Theorem simplifies the circuit, and, more importantly, Thévenin's Theorem will yield the same structure of the circuit, which makes it trivial to apply superposition.


Difference Mode (small signal):

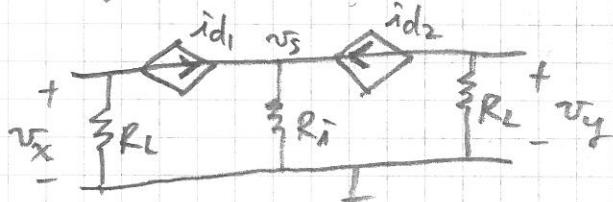

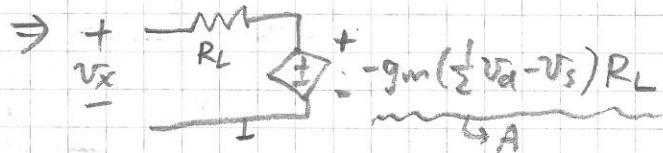Seen from  $v_x$   $\Rightarrow$  setting  $v_d = 0$ , we have  
 $v_{gs1} = v_{gs2} = 0 - v_s = -v_s$ ,  
which implies  $i_{d1} = i_{d2} = 0$   
 $\Rightarrow R_{TH} = R_L$   
 $\Rightarrow V_{TH} = -i_{d1} \cdot R_L = -g_m \left( \frac{1}{2} v_d - v_s \right) R_L$




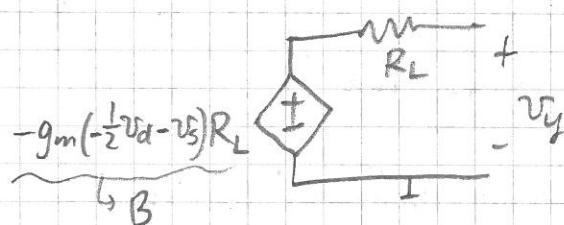Seen from  $v_y$ , using similar derivation, we have


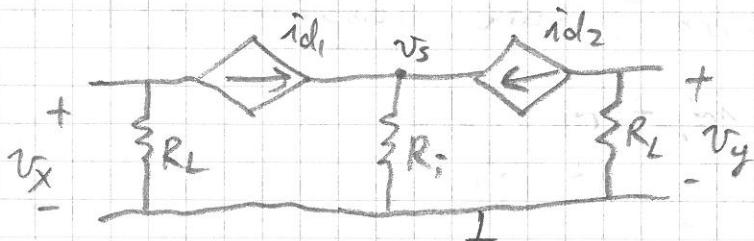
# Common Mode (Small signal):

the following derivation will be very similar to what we did for the difference mode, since the only difference in the circuit structure is the different input voltage source:




Seen from  $v_x \Rightarrow$  setting  $v_c = 0$ , we have


$$v_{gs1} = v_{gs2} = -v_s, \text{ which again implies } id_1 = id_2 = 0$$

$$\Rightarrow R_{TH} = R_L$$

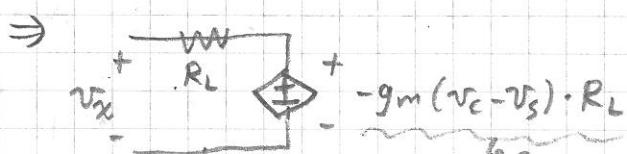
$$\Rightarrow V_{TH} = -id_1 \cdot R_L = -g_m(v_c - v_s) \cdot R_L$$



Seen from  $v_y$ , by symmetry, we have

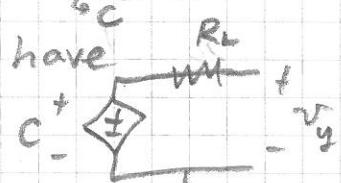

Combining the two modes, we have

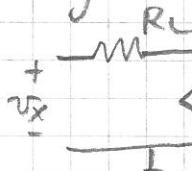

$A_{TC}$  seen from  $v_x$ , and thus output resistance  $r_o = R_L$



$B_{TC}$  seen from  $v_y$ , and thus output resistance  $r_o = R_L$

\*\*

You might notice that in the previous, the resulting voltage source we got is a bit different from that on P435 in the textbook.

Here is some explanation :

- In the common mode, applying KCL

$$\text{we have } id_1 + id_2 = \frac{v_s}{R_i}$$

$$\Rightarrow 2gm(v_c - v_s) = \frac{v_s}{R_i} \text{ and since both inputs are } v_c$$

$$\text{therefore, we can say } id_1 = id_2 = \frac{v_s}{2R_i}.$$

Further, because of the biasing current source, I, we can say that  $v_s \neq 0$ .

- In the difference mode, apply KCL

$$\text{we have } id_1 + id_2 = \frac{v_s}{R_i}$$

$$\Rightarrow -2gm \cdot v_s = \frac{v_s}{R_i} \text{ and the textbook said}$$

that since  $gm$  and  $R_i$  are independent  $\Rightarrow v_s = 0$

So, what we've got in the previous page is equivalent to that in the textbook.

Interestingly, in the difference mode  $v_s$  does not necessarily equal zero; it equals zero <sup>only</sup> because the inputs happened to be  $\frac{1}{2}v_d$  and  $-\frac{1}{2}v_d$ .

To see this, let's consider the two inputs are  $v_d$  and 0 instead :

in this case we will have, from KCL,

$$g_m(v_d - v_s) + g_m(0 - v_s) = \frac{v_s}{R_i}$$

$$\Rightarrow g_m v_d - 2 g_m v_s = \frac{v_s}{R_i}$$

/ which does not necessarily imply  $v_s = 0$


$$\Rightarrow g_m v_d = \left(2 g_m + \frac{1}{R_i}\right) v_s$$

$$\Rightarrow v_s = \frac{g_m}{2 g_m + \frac{1}{R_i}} \cdot v_d$$

if  $R_i \gg 1$ , this implies  $v_s = \frac{1}{2} v_d$  and thus

$$\frac{\frac{1}{2} g_m v_d}{R_i} \parallel \frac{\frac{1}{2} g_m v_d}{R_i}$$


on the whole circuit it means :

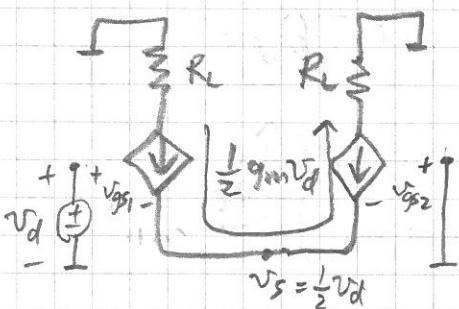

notice that now  $v_{gs1} = \frac{1}{2} v_d$   
and  $v_{gs2} = -\frac{1}{2} v_d$

Now, it is very interesting to ponder  
this from the aspect of "total signal" ]

P104 ↳ If we think about the case where  $V_A$  and  $V_B$  differs only by a tiny amount, say,  $\Delta V$ . Then we have  $V_D = V_A - V_B = \Delta V$  and  $v_d = \Delta V$ ,  $V_D = 0$ . The fact that a tiny amount of current,  $\frac{1}{2}g_m v_d$ , flowing through MOSFETs  $M_1$  and  $M_2$  is equivalent as both a small amount of increase of total current flowing through  $M_1$  and a small amount of decrease of total current flowing through  $M_2$ :

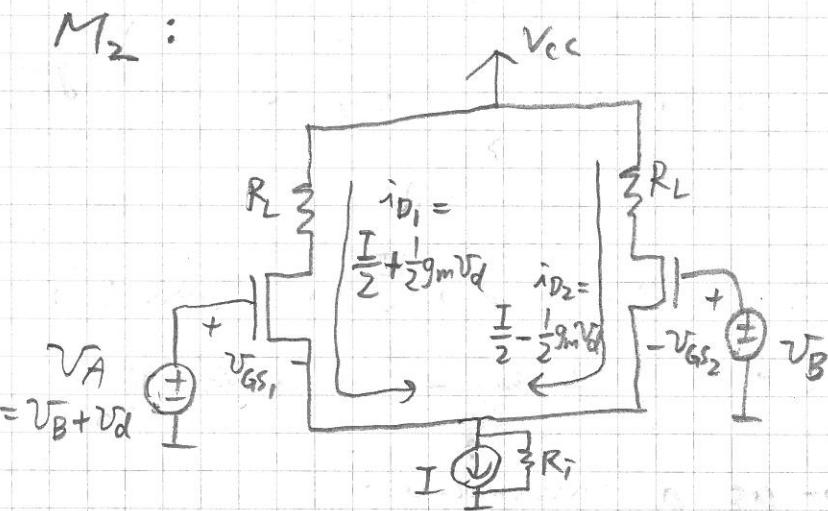

which makes sense, because we see that  $v_{GS_1}$ , being slightly larger than  $v_{GS_2}$ , will cause  $i_{D1}$ , being slightly larger than  $i_{D2}$ .

We may double check this by observing

that  $V_{GS_1} = V_{GS_2} + V_d$ , and thus

$$\bar{I}_{D_1} = \frac{1}{2} IK(V_{GS_2} + V_d - V_T)^2$$

$$\bar{I}_{D_2} = \frac{1}{2} IK(V_{GS_2} - V_T)^2$$

$$\bar{I}_{D_1} - \bar{I}_{D_2} = \frac{1}{2} IK((V_{GS_2} - V_T + V_d)^2 - (V_{GS_2} - V_T)^2)$$

$$= \frac{1}{2} IK(2V_{GS_2} - 2V_T + V_d) \cdot V_d \quad (\frac{a^2 - b^2}{= (a+b)(a-b)})$$

$$\approx \frac{1}{2} IK(2V_{GS_2} - 2V_T) \cdot V_d \quad (\because V_d \ll V_{GS_2})$$

$$= IK(V_{GS_2} - V_T) \cdot V_d$$

$$= g_m \cdot V_d$$

which is equal to

$$\bar{I}_{D_1} - \bar{I}_{D_2} = \left(\frac{I}{2} + \frac{1}{2} g_m V_d\right) - \left(\frac{I}{2} - \frac{1}{2} g_m V_d\right) = g_m \cdot V_d$$

Amazing.

- Now, back to P98 and P101 we saw that

$$A_d = -g_m R_L \text{ and the output resistance is } R_L.$$

This gives us a dilemma:

If we want to have a larger voltage gain we will have a larger output resistance should we choose to increase  $R_L$ ; and if we want to have a smaller output resistance we will have to decrease the voltage gain.

P106

Facing trade-offs is common to engineers. Often, a good system design involves finding a good balance that suits a particular application requirement.

Fortunately, in our case here we may have a way to increase the voltage gain while not sacrificing the output resistance.

In Homework 7, Question 2, we see that

$$A_{dI} = -R_L \sqrt{IK} \sqrt{I}$$


This means that we may increase the voltage gain by increasing  $I$  :)

(Perhaps that's also a reason why we use such a biasing current source)

To conclude our discussion of MOSFET, we look at two interesting applications :

① MOSFET as a small-signal resistor  
(see Example 8.1 in the textbook)

② MOSFET as a current source (next page)

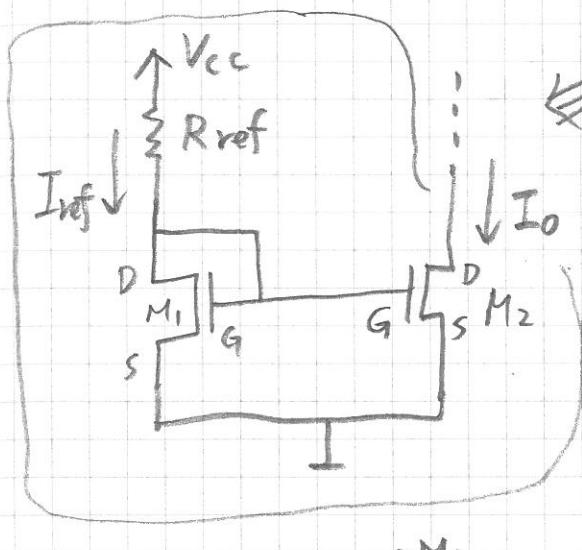

In this configuration, we'll have  $I_o = I_{ref}$  if both MOSFETs are ① identical, and ② operating under the saturation discipline.

The left MOSFET is in saturation because

$$V_{GS} = V_{DS} \quad (\text{i.e., } V_{GS} - V_T < V_{DS})$$

$$\text{Then } I_{ref} = \frac{1}{2} K_1 (V_{GS_1} - V_T)^2$$

$$I_o = \frac{1}{2} K_2 (V_{GS_2} - V_T)^2$$

Since  $M_1, M_2$  have both gates and sources short-circuited,

$$V_{GS_1} = V_{GS_2} \quad \text{and}$$

$$\boxed{\frac{I_o}{I_{ref}} = \frac{K_2}{K_1}}$$

$$\text{Considering that } \begin{cases} K_2 = K' \sqrt{\frac{W_2}{L_2}} \\ K_1 = K' \sqrt{\frac{W_1}{L_1}} \end{cases}$$

$\Rightarrow$  We may change the ratio between  $I_o$  and  $I_{ref}$  by changing the geometric structure of the MOSFET :)

Finally, observe that  $I_{ref}$  can be determined by

$$\begin{cases} I_{ref} = \frac{1}{2} K_1 (V_{GS_1} - V_T)^2 \\ V_{DS_1} = I_{ref} \cdot R_L \end{cases}$$

$$V_{DS_1} = V_{GS_1} \quad *$$