

Solution

National Taiwan Normal University
Department of Computer Science and Information Engineering
CSU0007 - Basic Electronics

Homework 2

Seven questions. 100 points total. Due on 10PM, Tuesday, 3/31/2020. Submit your answer via Moodle
Clearly state each step of your calculation to receive full score.

1. (20 points) Find the node voltages e_1 and e_2 and the branch voltages v_1 and v_2 . 5 points each.

Using KVL we see that $v_1 = v_2$, and it must be, since the two circuits are the same (grounding point is just an artificial way to aid our analysis).

$$\text{KVL: } 0.5 - 6 + 5 - v_1 = 0 \Rightarrow v_1 = -0.5 \text{ V} \quad v_2 = v_1$$

$$e_1 = 0 - v_1 = 0.5 \text{ V}$$



Via either node A or node B we may see $e_2 = 5.5 \text{ V}$. For example, node voltage at A is $0 + 6 = 6 \text{ V}$, thus $e_2 = 6 - 0.5 = 5.5$ *

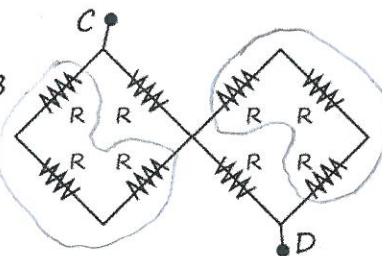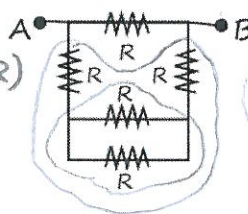2. (10 points) Find the equivalent resistance from the viewpoint of A-B and from that of C-D. 5 points each.



$$\begin{aligned} R_{AB} &= R \parallel (R + (R \parallel R) + R) \\ &= R \parallel \left(\frac{5}{2}R\right) \\ &= \left(\frac{1 \times \frac{5}{2}}{1 + \frac{5}{2}}\right)R = \frac{5}{7}R \end{aligned}$$

$$\begin{aligned} R_{CD} &= R \parallel (3R) + R \parallel (3R) \\ &= 2 \cdot \left(\frac{1 \times 3}{1 + 3}\right)R \\ &= \frac{3}{2}R \end{aligned}$$



3. (10 points) Find the current i_3 .

Way ① current divider:

$$i_3 = 2 \times \frac{R_2}{R_2 + R_3} = \frac{2R_2}{R_2 + R_3} \text{ A}$$

since 2A flows through R_1


Way ② node method:

$$\text{KCL at node A} \Rightarrow i_1 = 2 \text{ A}$$

KCL at node B

$$\Rightarrow i_1 = i_2 + i_3$$
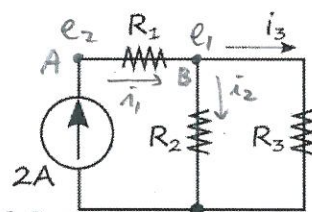
$$\Rightarrow 2 = \frac{e_1 - 0}{R_2} + \frac{e_1 - 0}{R_3} \Rightarrow e_1 = \frac{2R_2R_3}{R_2 + R_3} \Rightarrow i_3 = \frac{e_1}{R_3} = \frac{2R_2}{R_2 + R_3} \text{ A} *$$




4. (10 points) Find the voltage v_0 .

Use superposition. $v_0 = v_{01} + v_{02} + v_{03} + v_{04}$



We see $v_{01} = v_{02}$ if $V_1 = V_2$, and $v_{03} = v_{04}$ if $V_3 = V_4$

For v_{04} and v_{03} :

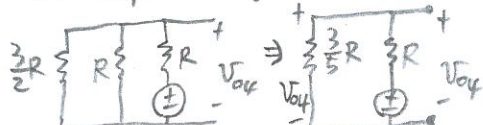

$$\frac{\frac{3}{2} \times 1}{\frac{3}{2} + 1} = \frac{3}{5}$$

Using voltage divider,

$$v_{04} = V_4 \times \frac{\frac{3}{5}}{\frac{3}{5} + 1} = \frac{3}{8} V_4 \Rightarrow v_{03} = \frac{3}{8} V_3$$

For v_{01} and v_{02} :




apply voltage divider twice

$$v_{01} = \left(V_1 \times \frac{1 \times \frac{3}{5}}{1 + \frac{3}{5}}\right) \times \frac{1 \times \frac{1}{2}}{1 + \frac{1}{2}} = \frac{1}{8} V_1$$

$$\Rightarrow v_{02} = \frac{1}{8} V_2$$
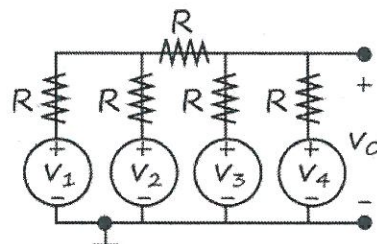
$$\Rightarrow v_0 = \frac{1}{8} (V_1 + V_2) + \frac{3}{8} (V_3 + V_4) *$$



5. (15 points) Find node voltage e_1 and e_2 , and then find the current i . 5 points each.

Way ① node method:

$$\text{KCL at A: } 2 + \frac{e_1 - 0}{1} + \frac{e_1 - e_2}{2} = 0$$


$$\text{KCL at B: } \frac{e_1 - e_2}{2} + \frac{0 - e_2}{3} + 4 = 0$$

$$\Rightarrow \begin{cases} 4 + 2e_1 + e_1 - e_2 = 0 \\ 3e_1 - 3e_2 - 2e_2 + 24 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} 3e_1 - e_2 = -4 \\ 3e_1 - 5e_2 = -24 \end{cases}$$


$$\Rightarrow \begin{cases} e_2 = 5 \\ e_1 = \frac{1}{3} \end{cases}$$
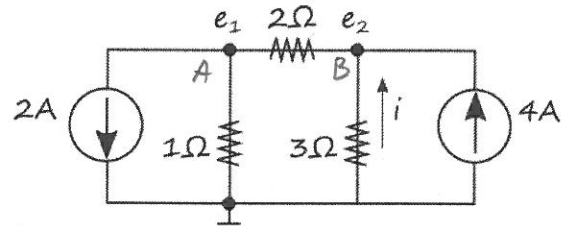
$$\bar{i} = \frac{0 - e_2}{3} = -\frac{5}{3} \text{ A}$$




Way ② supposition:

$$\bar{i} = \bar{i}_1 + \bar{i}_2$$

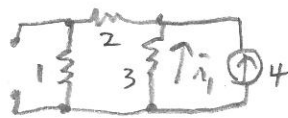

for \bar{i}_1 , using current divider
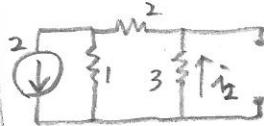
$$\bar{i}_1 = -4 \times \frac{(1+2)}{(1+2)+3} = -2$$



for \bar{i}_2 , using current divider




$$\bar{i}_2 = 2 \times \frac{1}{1+(2+3)} = \frac{1}{3}$$

$$\text{then } \bar{i} = \bar{i}_1 + \bar{i}_2 = -2 + \frac{1}{3} = -\frac{5}{3} \text{ A}$$

6. (10 points) Find the current i .

Let's use superposition in a bit fancy way:


$$\bar{i} = \bar{i}_1 + \bar{i}_2$$

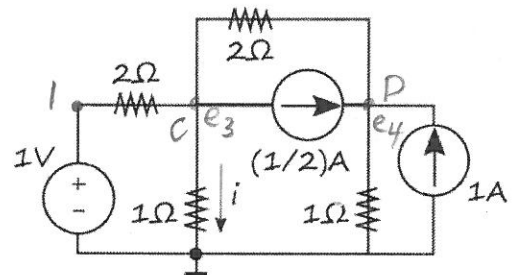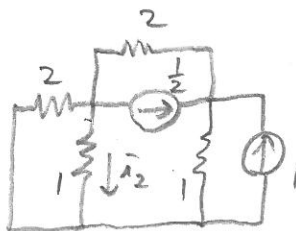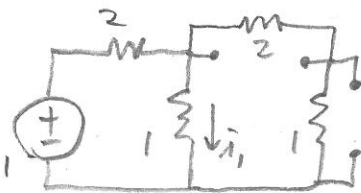

using voltage divider and element law

$$\bar{i}_1 = \left(1 \times \frac{\frac{1 \times 3}{1+3}}{2 + \frac{1 \times 3}{1+3}} \right) \times 1 = \frac{3}{11}$$

use node method here then

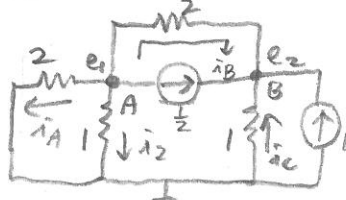

$$\text{KCL at A: } \frac{e_1 - 0}{2} + \frac{e_1 - 0}{1} + \frac{1}{2} + \frac{e_1 - e_2}{2} = 0$$

$$\text{KCL at B: } \frac{1}{2} + \frac{e_1 - e_2}{2} + \frac{0 - e_2}{1} + 1 = 0$$

$$\Rightarrow \begin{cases} 4e_1 - e_2 = -1 \\ e_1 - 3e_2 = -3 \end{cases} \Rightarrow \begin{cases} 12e_1 - 3e_2 = -3 \\ e_1 - 3e_2 = -3 \end{cases}$$

$$\Rightarrow e_1 = 0 \Rightarrow \bar{i}_2 = \frac{e_1 - 0}{1} = 0$$

$$\Rightarrow \bar{i} = \bar{i}_1 + \bar{i}_2 = \frac{3}{11} \text{ A}$$

Alternatively, we can directly use the node method

$$\text{KCL at } e_3: \frac{1 - e_3}{2} + \frac{0 - e_3}{1} + \frac{e_4 - e_3}{2} + \frac{1}{2} = 0$$

$$\text{KCL at } e_4: \frac{e_3 - e_4}{2} + \frac{1}{2} + \frac{0 - e_4}{1} + 1 = 0$$

$$\Rightarrow \begin{cases} -4e_3 + e_4 = 0 \\ e_3 - 3e_4 = -3 \end{cases}$$


$$\Rightarrow \begin{cases} -12e_3 + 3e_4 = 0 \\ e_3 - 3e_4 = -3 \end{cases}$$

$$\Rightarrow e_3 = \frac{3}{11}$$


$$\Rightarrow \bar{i} = \frac{e_3 - 0}{1} = \frac{3}{11} \text{ A}$$

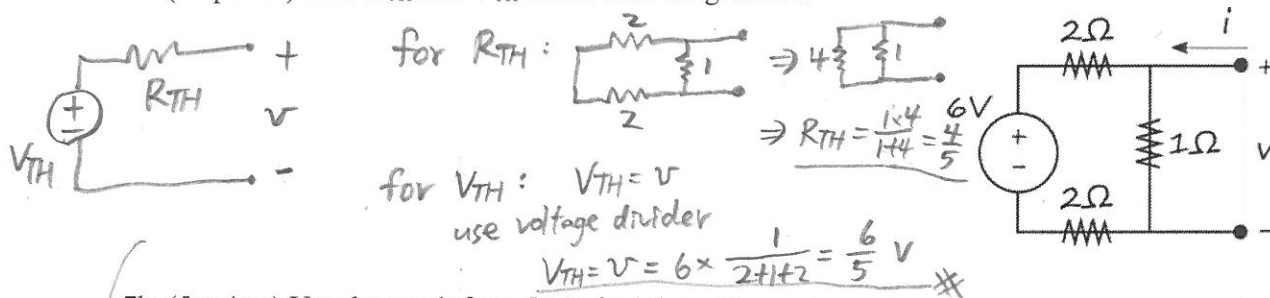7. (25 points) Thévenin's Theorem and its application:

7a. (10 points) Find R_{TH} and V_{TH} of the following circuit:




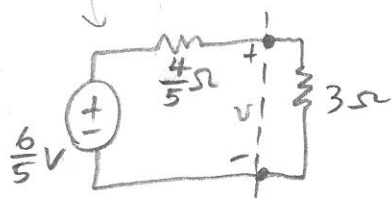7b. (5 points) Use the result from 7a to find the voltage v here.






voltage divider
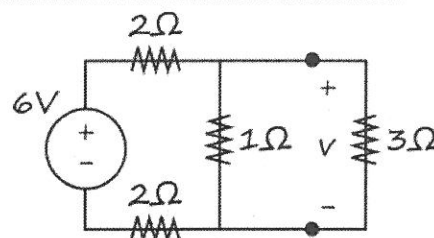
$$v = \frac{6}{5} \times \frac{3}{\frac{4}{5} + 3} = \frac{6}{5} \times \frac{15}{19} = \frac{18}{19} V$$



7c. (10 points) In the following circuit, find the current i . (Hint: study Example 3.22 in the textbook)

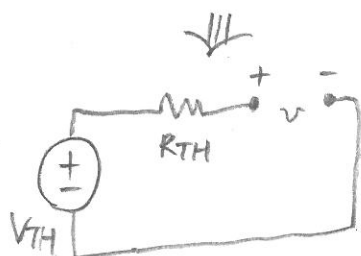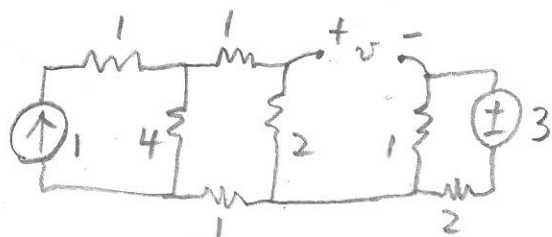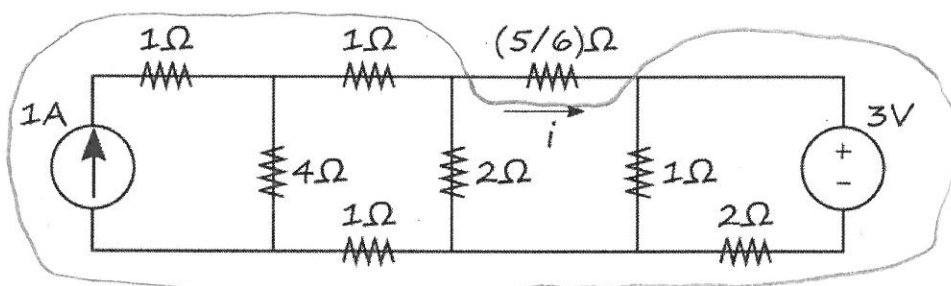Besides textbooks method,
we may consider one
single equivalent circuit:




for R_{TH} :

$$R_{TH} = \left[(1 + (1 \parallel 4) + 1) \parallel 2 \right] + 1$$

$$= \left[\frac{14}{5} \parallel 2 \right] + 1$$

$$= \frac{\frac{14}{5} \times 2}{\frac{14}{5} + 2} + 1 = \frac{28}{24} + 1 = \frac{13}{6}$$

for V_{TH} , we may use superposition

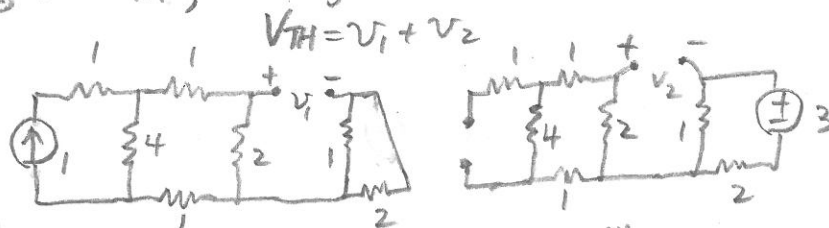

use current divider
and element law

$$V_1 = \left[1 \times \frac{4}{4 + (1+2+1)} \right] \times 2 = 1$$

use voltage divider

$$V_2 = -3 \times \frac{1}{1+2} = -1$$

Therefore $V_{TH} = V_1 + V_2 = 0$

