

National Taiwan Normal University
Department of Computer Science and Information Engineering
CSU0007 - Basic Electronics
Final Exam (June. 15, 2020)


Clearly state each step of your answer.

In the following questions, consider the circuit in Figure 1 (drawn on the blackboard).

$$K = 1 \text{ mA/V}^2$$


1. (10 points) Consider the S model of the MOSFET. $V_{S1}=V_{S2}=5\text{V}$. $R_{L1}=R_{L2}=10\text{ k}\Omega$. $V_T=1\text{V}$. Suppose that $v_{IN}=0\text{V}$. $v_{OUT}=?$
2. (10 points) Consider the SR model. We want to design a circuit such that if $v_{IN}=\text{logic 0}$, v_{OUT} will be logic 0, and that if $v_{IN}=\text{logic 1}$, v_{OUT} will be logic 1. Suppose $V_T=1\text{V}$, $V_{S1}=V_{S2}=5\text{V}$, $R_{ON}=1\text{ k}\Omega$, $R_{L1}=9\text{ k}\Omega$, $R_{L2}=19\text{ k}\Omega$. And we want to have a noise margin of 0.5V for logic 0 and a noise margin of 1V for logic 1. Give a valid set of thresholds V_{OL} , V_{OH} , V_{IL} , and V_{IH} .
3. (10 points) Following Question 2, suppose that now $V_{OL}=0.5\text{V}$, $V_{OH}=4\text{V}$, $V_{IL}=0.9\text{V}$, and $V_{IH}=3\text{V}$, and $R_{ON}=2\text{ k}\Omega$, $R_{L1}=8\text{ k}\Omega$, $V_{S1}=5\text{V}$, $V_T=1\text{V}$. What are the valid value ranges for R_{L1} and V_{S2} ?
4. (10 points) Again, consider the SR model. Suppose that we $V_{S1}=V_{S2}=5\text{V}$. $R_{L1}=10\text{ k}\Omega$. $R_{ON}=2\text{ k}\Omega$. $V_T=1\text{V}$. If we want $|v_{OUT}/v_{IN}|=0.5$, given $v_{IN}=0.5\text{V}$. What should be the value of resistance R_{L2} ?
5. (10 points) Following Question 4, but now consider the SCS model. If we still want $|v_{OUT}/v_{IN}|=0.5$, given $v_{IN}=0.5\text{V}$. Explain why in this case the right MOSFET will not operate in the saturation region.
6. (10 points) Following Question 5, but now consider the SCS model. If $v_{IN}=1.8\text{V}$, find $v_{OUT}=?$
7. (10 points) Following Question 5, but now consider the SCS model. If $R_{L1}=8\text{ k}\Omega$ and $R_{L2}=1.5\text{ k}\Omega$. Find the maximum valid v_{IN} range for both MOSFETs to operate in the saturation region.
8. (10 points) Using graphical analysis to show that for a SCS model, if we increase R_{L2} and keep the same v_{IN} as before, then for the same v_{OUT} we will need to produce a smaller value of v' .
9. (10 points) Draw the small-signal model of the circuit in Figure 1.
10. (10 points) Following Question 9, suppose that we want to have the magnitude of the small-signal gain $|v_{out}/v_{in}|=0.5$, what should be the DC bias V_{IN1} ?

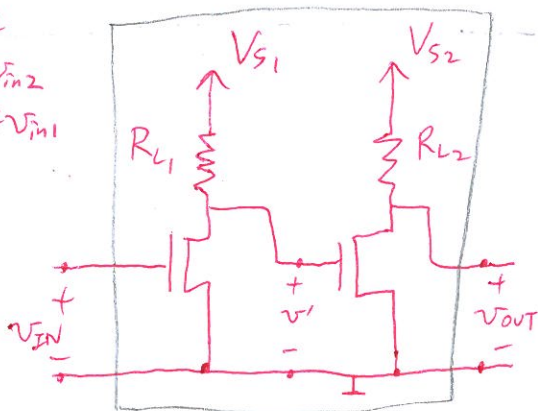↓ in this case
 $v' = V_{IN2} + v'_{in2}$
 $v_{IN} = V_{IN1} + v'_{in1}$



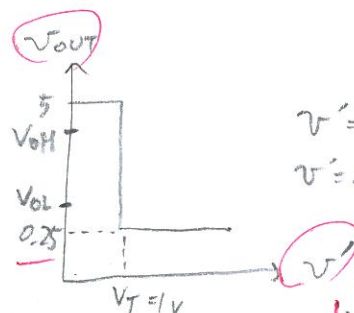
(2) $v_{OUT} = \text{logic 1} \Rightarrow v_{OUT} = V_{S2} = 5\text{V}$

$$v_{OUT} = \text{logic 0} \Rightarrow v_{OUT} = 5 \times \frac{1}{19+1} = 0.25\text{V}$$



$$v' = \text{logic 1} \Rightarrow v' = V_{S1} = 5$$
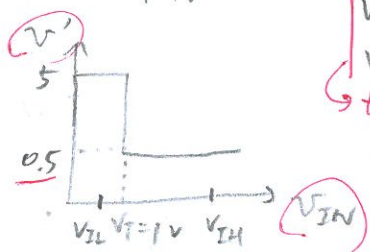
$$v' = \text{logic 0} \Rightarrow v' = 5 \times \frac{1}{9+1} = 0.5\text{V}$$



$$V_{IL} - V_{OL} = 0.5$$

$$V_{OH} - V_{IH} = 1$$

the definition of noise margin


$$\Rightarrow \begin{cases} V_{IL} = 0.8 \\ V_{OL} = 0.3 \\ V_{IH} = 3 \\ V_{OH} = 4 \end{cases}$$

(1) $v_{IN} = 0 < V_T$ the MOSFET is OFF

$$\Rightarrow v' = V_{S1} \Rightarrow v' \geq V_T$$

\Rightarrow the right MOSFET is ON

$$\Rightarrow v_{OUT} = 0\text{V}$$

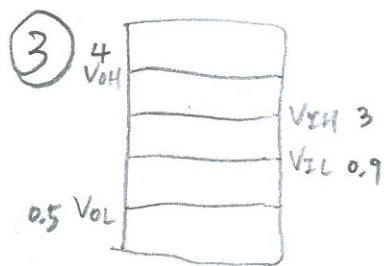

left MOSFET ON \rightarrow right MOSFET OFF

$$\Rightarrow V' = V_{S1} \times \frac{2}{R_{L1} + 2} < V_T \Rightarrow \underline{R_{L1} > 8 \text{ k}\Omega}$$

right MOSFET ON $\Rightarrow V_{OUT} \leq 0.5 \text{ V}$

$$\Rightarrow V_{S2} \times \frac{2}{R_{L2} + 2} < 0.5 \Rightarrow V_{S2} \leq 5 \text{ V}$$

right MOSFET OFF $\Rightarrow V_{S2} \geq 4 \Rightarrow 4 \leq V_{S2} \leq 5$

(Note that if $R_{L2} = 8 \text{ k}\Omega$, we'll have $V_{S2} \times \frac{2}{8+2} < 0.5 \Rightarrow V_{S2} < 2.5$, which conflicts to $V_{S2} \geq 4$)

If you think of the left MOSFET inverter and the right MOSFET inverter as two components, you may write

$$V' = V_{S1} \times \frac{2}{R_{L1} + 2} < V_{OL}, \text{ which gives } \underline{R_{L1} > 18 \text{ k}\Omega}$$

④ $5 \times \frac{2}{R_{L2} + 2} = \overset{V_{OUT}}{0.25} \Rightarrow \underline{R_{L2} = 38 \text{ k}\Omega}$ #

⑤ $\left| \frac{V_{OUT}}{V_{IN}} \right| = 0.5$ and $V_{IN} = 0.5 \text{ V}$ means we need $V_{OUT} = 0.25 \text{ V}$

This suggests that the V_{DS} of the right MOSFET is 0.25 V .

But $V_{IN} = 0.5 \text{ V}$ implies that V_{GS} of the right MOSFET is 5 V .

Thus we have $V_{GS} - V_T > V_{DS}$ and $V_{GS} > V_T$, which means that the right MOSFET is operating in the triode region.

⑥ $V_{IN} > V_T$ suppose in saturation, then $V' = V_{S1} - \frac{K(V_{IN} - V_T)^2}{2} \cdot R_{L1} = 5 - \frac{10^{-3} \times 0.64}{2} \times 10 \times 10^3$
 $\Rightarrow V' = 1.8 \text{ V}$

verify $V_{IN} - V_T < 1.8 \text{ V}$, so indeed it operates in the saturation region.

To compute V_{OUT} , apply the same procedure for the right MOSFET.

Since I did not give the value of R_{L2} in this question, it's fine to

just write $V_{OUT} = V_{S2} - \frac{K(V' - V_T)^2}{2} R_{L2} = 5 - 0.32 \times 10^{-3} R_{L2}$ #

① A First, for the right MOSFET to operate in the saturation region, the maximum input voltage range is

$$V_T \rightarrow \frac{-1 + \sqrt{1 + 2V_{S1} R_{L2} K}}{R_{L2} \cdot K} + V_T \quad (\text{see Pages 358~359 in the textbook})$$

$$\Rightarrow 1 \rightarrow \frac{-1 + \sqrt{1 + 2 \times 5 \times 1.5 \times 10^3 \times 10^{-3}}}{1.5 \times 10^3 \times 10^{-3}} + 1$$

≈ 2

$\Rightarrow 1 \sim 3 \text{ V}$ for v' this range dominates.

B Then, for the left MOSFET, the maximum output range for the saturation region is


$$V_{S1} \rightarrow \frac{-1 + \sqrt{1 + 2V_{S1} \cdot R_{L1} \cdot K}}{R_{L1} \cdot K} \quad (\text{again, see pages 358~359})$$

$$\Rightarrow 5 \rightarrow \frac{-1 + \sqrt{1 + 2 \times 5 \times 8 \times 10^3 \times 10^{-3}}}{8 \times 10^3 \times 10^{-3}}$$

$\Rightarrow 5 \sim 1 \text{ V}$ for v'

C Similarly, the maximum input range for the left MOSFET to operate in the saturation region is $V_T \rightarrow \frac{-1 + \sqrt{1 + 2V_{S1} \cdot R_{L1} \cdot K}}{R_{L1} \cdot K} + V_T$
 $\Rightarrow 1 \sim 2 \text{ V}$ for v_{IN}

Combining A, B, C:

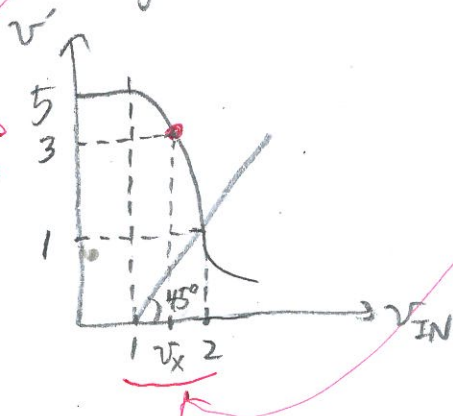

The maximum valid v_{IN} range is

$$v_x \sim 2 \text{ V}$$

$$\text{where } 3 = 5 - \frac{K(v_x - V_T)^2}{2} \cdot R_{L1}$$

$$3 = 5 - 4(v_x - 1)^2$$

$$v_x = 1 + \sqrt{0.5}$$

$$\Rightarrow 1 + \sqrt{0.5} \text{ V} \leq v_{IN} \leq 2 \text{ V}$$


#

Name: _____

Solution

Student ID: _____



8

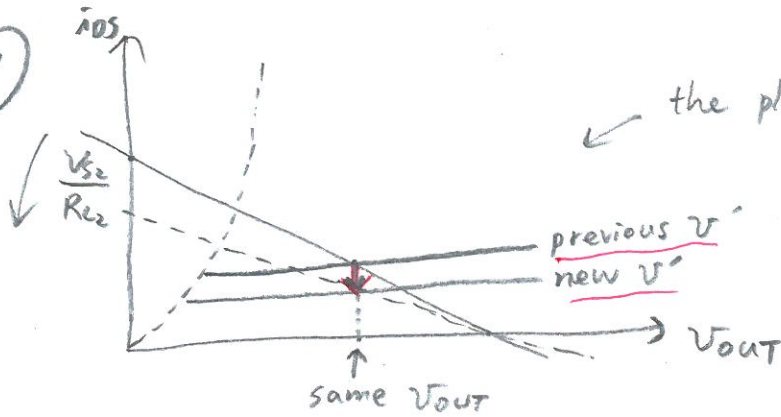

(the phrase "keep the same V_{IN} " is unnecessary.)

for further study, that means we will need a larger value of R_{L1} , and beware that R_{L1} must not be too large to cause the left MOSFET to enter the triode region.

9

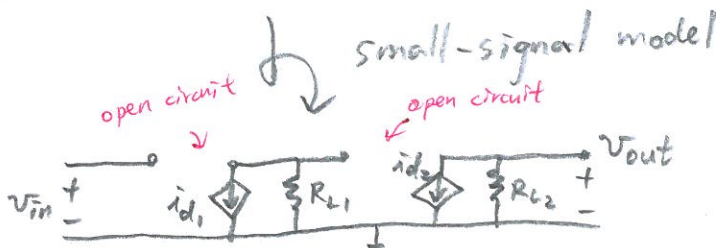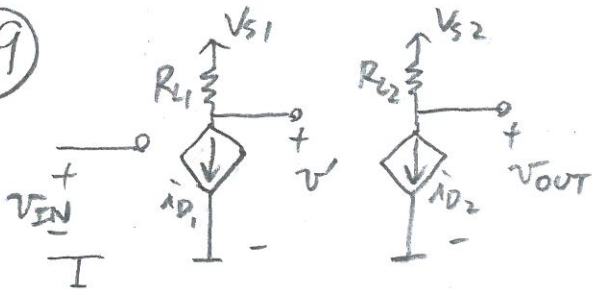

10

$$\begin{cases} 0.5 = \left| \frac{V_{out}}{V_{in2}} \right| = K(V_{IN2} - V_T)R_{L2} \\ V_{IN2} = V_{S1} - \frac{K(V_{IN1} - V_T)^2}{2} \cdot R_{L1} \end{cases}$$

$$\Rightarrow \begin{cases} V_{IN2} = \frac{0.5}{K R_{L2}} + V_T \\ V_{S1} - V_{IN2} = \frac{K R_{L1} (V_{IN1} - V_T)^2}{2} \end{cases}$$

$$\Rightarrow V_{IN1} = V_T + \sqrt{(V_{S1} - V_{IN2}) \cdot \frac{2}{K R_{L1}}}$$

$$= V_T + \sqrt{\frac{2(V_{S1} - V_{IN2})}{K R_{L1}}}$$

$$= V_T + \sqrt{\frac{2(V_{S1} - \frac{0.5}{K R_{L2}} - V_T)}{K R_{L1}}}$$

(note that $V' = V_{IN2} + V_{in2}$
 $V_{IN} = \underbrace{V_{IN1}}_{\text{our target}} + \underbrace{V_{in1}}_{\text{I mistakenly circled this one on the blackboard...}}$)